


## DoctorD's Solution to Practice problem 8.4 of the text

Note that the battery is 50v here, not 100v – this changes the coefficient of sine in the answer.
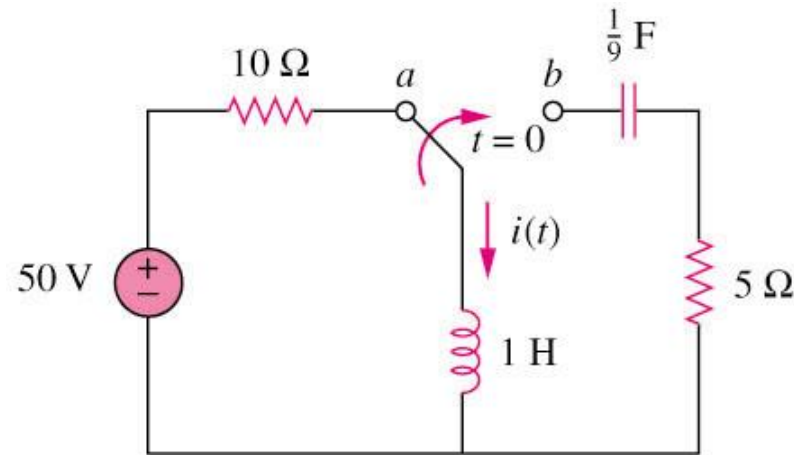
### Example 2

The circuit shown below has reached steady state at  $t = 0^-$ .

If the make-before-break switch moves to position b at  $t = 0$ , calculate  $i(t)$  for  $t > 0$ .



The Author is assuming that the voltage on the capacitor is 0 at  $t = 0^-$

Please refer to lecture or textbook for more detail elaboration.

Answer:  $i(t) = e^{-2.5t} [5\cos 1.6583t - 7.538\sin 1.6583t] \text{ A}$

1. Find the initial current in the inductor

$$i(0^-) = 50/10 = 5 \text{ amps (down)}$$

2. Determine the differential equation after the switch is thrown

Use a loop equation: (I assume the loop current flows counter clockwise)

$$V_R + V_C + V_L = 0$$

$$Ri + \frac{1}{C} \int i dt + L \frac{di}{dt} = 0$$

or, after taking the derivative of the equation,

$$R \frac{di}{dt} + \frac{1}{C} i + L \frac{d^2i}{dt^2} = 0$$
$$5 \frac{di}{dt} + 9i + \frac{d^2i}{dt^2} = 0$$

3. Let  $i = A\varepsilon^{st}$  and we get the characteristic equation  $s^2 + 5s + 9 = 0$

4. Complete the square

$$(s + 2.5)^2 + 2.75 = 0$$

$$(s + 2.5)^2 = -2.75$$

$$s + 2.5 = \pm 1.6583j$$

$s = -2.5 \pm 1.6583j$  We have an underdamped system so the answer is:

$$i(t) = A_1 \varepsilon^{-(2.5+1.6583j)t} + A_2 \varepsilon^{-(2.5-1.6583j)t}$$

5. Find  $A_1$  and  $A_2$

$$i(0) = 5 = A_1 + A_2, \text{ or } A_2 = 5 - A_1$$

but we need another equation so take the derivative of the solution

$$\frac{di}{dt} = -(2.5 + 1.6583j)A_1 \varepsilon^{-(2.5+1.6583j)t} - (2.5 - 1.94j)A_2 \varepsilon^{-(2.5-1.6583j)t}$$

but the initial voltage on the inductor is -25 volts (resistor current) and  $V_L = L * di/dt$

$$25 = (2.5 + 1.6583j)A_1 + (2.5 - 1.96583j)A_2$$

or

$$5 = (0.5 + .3317j)A_1 + (0.5 - .3317j)A_2$$

Substituting

$$5 = (0.5 + .3317j)A_1 + (0.5 - .3317j) * (5 - A_1)$$

$$5 = (0.5 + .3317j)A_1 + (2.5 - 1.6583j) - (0.5 - .3317j) * A_1$$

$$2.5 + 1.6583j = [(0.5 + .3317j) - (0.5 - .3317j)] * A_1$$

$$2.5 + 1.6583j = [(.3317j) + (.3317j)] * A_1$$

$$A_1 = \frac{2.5+1.6538j}{0.6633j} = 2.5 - 3.75j \text{ and } A_2 = 2.5 + 3.75j$$

So the answer is (in exponential form) is

$$i(t) = (2.5 - 3.75j)\varepsilon^{-(2.5+1.6583j)t} + (2.5 + 3.75j)\varepsilon^{-(2.5-1.6583j)t}$$

6. To get the sine-cosine form we need to do some complex (this doesn't mean hard, but it can be tedious) algebra.

Collecting terms:

$$i(t) = \varepsilon^{-2.5t}[(2.5 - 3.75j)\varepsilon^{-1.6583jt} + (2.5 + 3.75j)\varepsilon^{+1.6583jt}]$$

$$i(t) = \varepsilon^{-2.5t}[2.5\varepsilon^{-1.6583jt} + 2.5\varepsilon^{+1.6583jt} + (-3.75j)\varepsilon^{-1.6583jt} + (3.75j)\varepsilon^{+1.6583jt}]$$

or

$$i(t) = \varepsilon^{-2.5t} \left[ \frac{5\varepsilon^{1.6583jt} + 5\varepsilon^{-1.6583jt}}{2} - \frac{7.5\varepsilon^{1.6583jt} - 7.5\varepsilon^{-1.6583jt}}{2j} \right]$$

or

$$i(t) = \varepsilon^{-2.5t}[5\cos(1.6583t) - 7.5\sin(1.6583t)] \text{ amps}$$