

## LAB 2.4

# Instrumentation Amplifier

[See Section 2.4.2, p. 76 of Sedra/Smith]

### OBJECTIVES:

To study an instrumentation amplifier circuit by:

- Completing the analysis of the circuit and selecting resistors that satisfy design specifications.
- Simulating the circuit to compare the results with the paper analysis.
- Implementing the circuit in an experimental setting, taking measurements, and comparing its performance with theoretical and simulated results.

### MATERIALS:

- Laboratory setup, including breadboard
- Three 741-type operational amplifiers
- Several wires and resistors of varying sizes

### PART 1: DESIGN AND ANALYSIS

Consider the circuit shown in Figure L2.4:

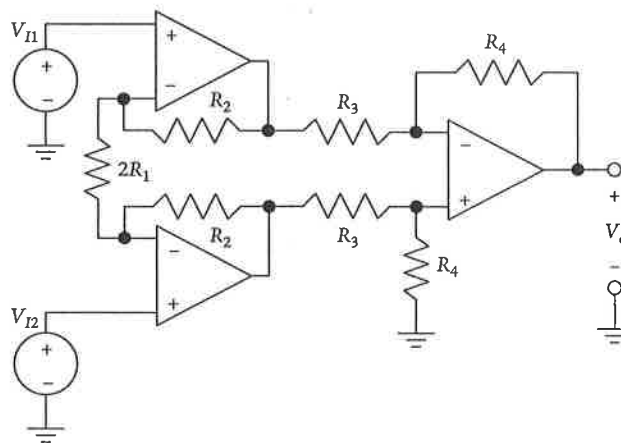


FIGURE L2.4:  
Instrumentation amplifier.  
Based on Fig. 2.20(c),  
p. 77 S&S.

Design the circuit in Figure L2.4 such that  $A_d = 110$  V/V. Select resistor values such that the first stage provides a gain of 11 V/V (magnitude) and  $R_1 = 1$  k $\Omega$  and the second stage provides a gain of  $-10$  V/V. Use supplies of  $V_+ = -V_- = 15$  V.

#### Hand calculations

- Sketch the circuit in your lab book, clearly labeling the op-amp terminals.
- What values of  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$  do you need to use to meet the gain and input resistance specifications? Is the problem completely specified?

#### Simulation

- Use a 50-mV<sub>pk-pk</sub> 1-kHz input sine wave applied to  $v_{I1}$  and another 50-mV<sub>pk-pk</sub> 1-kHz input sine wave applied to  $v_{I2}$  that is 180° out of phase with  $v_{I1}$ . In your simulation, assume your input voltage sources have an output resistance of 50  $\Omega$ . What are  $V_{Id}$  and  $V_{Icm}$ ? What are  $V_{Od}$  and  $V_{Ocm}$ ?
- Plot the input and output waveforms for all simulations.
- For all simulations, report the DC voltage at the inverting terminal and output of each op-amp.
- What are the simulated values of differential and common-mode gain?

### PART 2: PROTOTYPING AND MEASUREMENT

- Assemble the circuit onto a breadboard. Do not include the 50- $\Omega$  output resistance of your signal sources.
- While leaving  $v_{I2}$  grounded, provide a DC input to  $v_{I1}$  in increments of 0.01 V, from  $-0.1$  V to  $+0.1$  V. Record the values of  $v_O$  and plot your results.
- While leaving  $v_{I1}$  grounded, provide a DC input to  $v_{I2}$  in increments of 0.01 V, from  $-0.1$  V to  $+0.1$  V. Record the values of  $v_O$  and plot your results.
- Using a function generator, provide a 1-kHz 50-mV<sub>pk-pk</sub> sine wave to input  $v_{I1}$  and ground input  $v_{I2}$ . Using an oscilloscope, capture the output voltage waveform.
- Using a function generator, provide a 1-kHz 50-mV<sub>pk-pk</sub> sine wave to input  $v_{I2}$  and ground input  $v_{I1}$ . Using an oscilloscope, capture the output voltage waveform.
- Using a digital multimeter, measure all resistors to three significant digits.

### PART 3: POST-MEASUREMENT EXERCISE

- Calculate the values of  $A_d$  and  $A_{cm}$  obtained in your measurement. What is the common-mode rejection ratio (CMRR) of the circuit? Express the CMRR in units of decibels. Explain any discrepancies between the experiments, simulations, and hand analysis.

- Recalculate the theoretical gains of the circuit, using the measured resistor values. Are the recalculated values closer to your measured gains?

#### **PART 4 [OPTIONAL]: EXTRA EXPLORATION**

- In your measurement setup, replace  $R_4$  with a resistor that is 10% smaller in value and remeasure  $A_d$  and  $A_{cm}$ . How do their values change? What do you conclude?