

## LAB 5.1

# NMOS I-V Characteristics

[See Sections 5.1–5.2, p. 238 of Sedra/Smith]

### OBJECTIVES:

To study NMOS transistor I-V curves by:

- Simulating a transistor to investigate the drain current vs. gate-to-source voltage and drain-to-source voltage.
- Implementing a circuit and taking measurements of the  $I_D$  vs.  $V_{GS}$  and  $I_D$  vs.  $V_{DS}$  curves.
- Extracting values of  $k_n$ ,  $V_{tn}$ , and  $\lambda_n$ .

### MATERIALS:

- Laboratory setup, including breadboard
- 1 enhancement-type NMOS transistor (e.g., MC14007)
- Several wires

### PART 1: SIMULATION

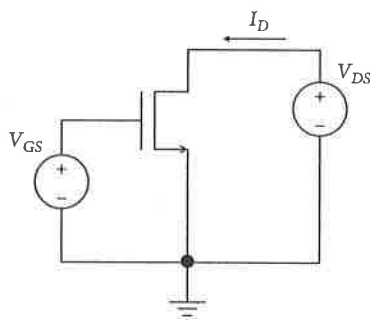


FIGURE L5.1: Transistor measurement circuit.

Consider the circuit in Figure L5.1. Enter the circuit into your simulator's schematic editor, applying DC voltage supplies to the gate and drain of the transistor.

**$I_D$  vs.  $V_{GS}$**

While setting  $V_{DS}$  to a constant value of 5 V, sweep the gate voltage from 0 V to 5 V in increments of 0.1 V. Plot a curve of  $I_D$  vs.  $V_{GS}$ . At what value of  $V_{GS}$  does the current turn on?

**$I_D$  vs.  $V_{DS}$**

For three values of  $V_{GS}$  (2.5 V, 3.0 V, and 3.5 V), sweep the drain voltage from 0 V to 5 V in increments of 0.1 V. Plot the curves for  $I_D$  vs.  $V_{DS}$  onto a single graph, clearly indicating the value of  $V_{GS}$  next to each curve.

**PART 2: MEASUREMENTS**

Assemble the circuit from Figure L5.1, using a power supply to generate the DC voltages.

**$I_D$  vs.  $V_{GS}$**

While setting  $V_{DS}$  to a constant value of 5 V, sweep the gate voltage from 1.0 V to 3.5 V in increments of 0.25 V (note, we have reduced the number of data points with respect to the simulations), and measure the drain current using the power supply. (Note: Not all power supplies allow you to measure current accurately; if this is the case for your lab setup, you may place a small resistor in series with the drain and measure the voltage drop across the resistor.) Plot a curve of  $I_D$  vs.  $V_{GS}$ . At what value of  $V_{GS}$  does the NMOS turn on?

**$I_D$  vs.  $V_{DS}$**

For three values of  $V_{GS}$  (2.5 V, 3.0 V, and 3.5 V), sweep the drain voltage from 0 V to 3.5 V in increments of 0.5 V, and measure the drain current using the power supply. Plot the curves for  $I_D$  vs.  $V_{DS}$  onto a single graph, clearly indicating the value of  $V_{GS}$  next to each curve.

**PART 3: POST-MEASUREMENT EXERCISE**

**Simulation vs. measurement**

What are the main differences between your simulated and measured curves? Can you explain the differences?

**Parameter extraction**

**[1] Threshold voltage,  $V_{tn}$**

From the measured  $I_D$  vs.  $V_{GS}$  curve, at what value of  $V_{GS}$  does the NMOS turn on? Set this as the threshold voltage  $V_{tn}$  of your transistor.

**[2] MOSFET transconductance parameter,  $k_n$**

Based on the value of drain current  $I_D$  at  $V_{GS} = 3.0$  V, and using the saturation model for the transistor, i.e.,  $I_D = (1/2)k_n(V_{GS} - V_{tn})^2$ , extract the value of  $k_n = \mu_n C_{ox}(W/L)$ . Using your extracted values of  $V_{tn}$  and  $k_n$ , plot a curve of  $I_D$  vs.  $V_{GS}$ .

using the saturation model, and compare with your simulated and measured curves. Are there any differences? Can you explain the differences?

**(3) Early voltage,  $V_A$**

Based on your measured  $I_D$  vs.  $V_{DS}$  curves for a saturated transistor, extract the Early voltage  $V_A$ . Does  $V_A$  change significantly for each value of  $V_{GS}$ ? What is the average value of  $V_A$ ? Based on your average value of  $V_A$ , calculate  $\lambda_n = 1/V_A$ .

Repeat Steps 1 to 3 for your measured results.

Summarize your results in the following table.

MEASURED
$V_{tn}$ [V]
$k_n$ [mA/V <sup>2</sup> ]
$\lambda_n$ [V <sup>-1</sup> ]

**PART 4 [OPTIONAL]: EXTRA EXPLORATION**

If you have access to a semiconductor parameter analyzer, generate the  $I_D$  vs.  $V_{DS}$  curves using the analyzer. How do they compare to the curves you generated in Part 3? Re-extract values of  $V_{tn}$ ,  $k_n$ , and  $\lambda_n$ .