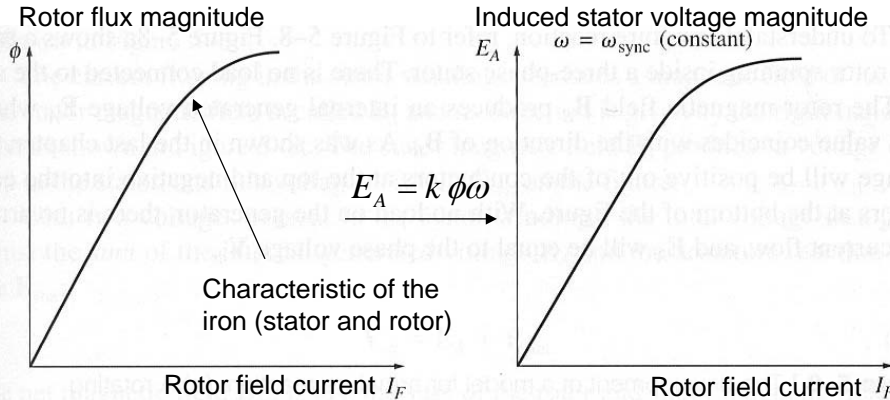



## SM No-Load Characteristic



**Effect of saturation:** for large field currents the no-load armature voltage magnitude scales sub-proportionally with  $I_F$  and the voltage waveform becomes non sinusoidal (distorted).

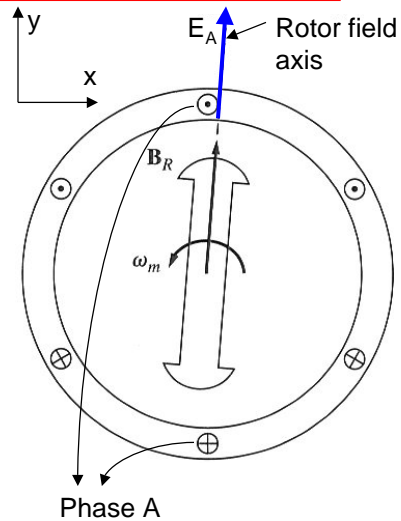
## SM Armature Reaction I

- Unloaded generator at arbitrary rotor position
- Phase-A induced voltage can be represented by a space vector  $E_A$  which aligns with rotor field vector  $B_R$ 
  - ◆ The time evolution of phase-A voltage and current is the projection of the respective space vector onto the y-axis



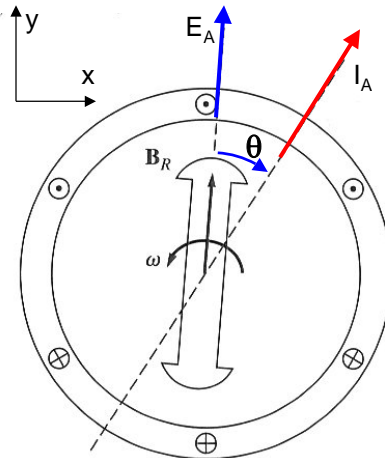
## SM Armature Reaction II

- Generator with lagging load current (balanced)
- Phase-A current space vector  $I_A$  is rotated (in space) out of the rotor  $B_R$  axis by the load phase angle  $\theta$ 
  - ◆ It will require the time  $\theta/\omega$  for the  $I_A$  space vector to reach the rotor axis
  - ◆ The phase-A current produces a magnetic excitation in the x-axis only


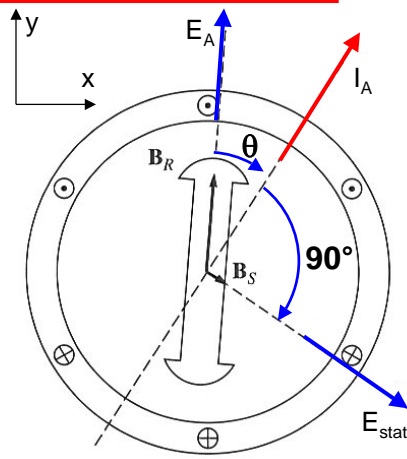
## SM Armature Reaction II

- The balanced 3-phase stator current system generates a rotating magnetic field  $B_S$  which is another  $90^\circ$  "behind" the phase-A current space vector
  - ◆ Reasoning:  $B_S$  points in x-direction when  $i_A(t)$  is at its peak, i.e. when  $I_A$  reaches the y-direction
- $B_S$  itself induces voltages  $E_{stat}$  in the stator



## SM Armature Reaction II

- The resulting terminal voltage of the machine is

$$\vec{V}_\phi = \vec{E}_A + \vec{E}_{stat}$$


- Which aligns with the resulting (net) magnetic field

$$\vec{B}_{net} = \vec{B}_R + \vec{B}_S$$

- Since  $E_{stat}$  is proportional to  $I_A$  the relationship in phasor quantities becomes

$$V_\phi = E_A - jXI_A$$

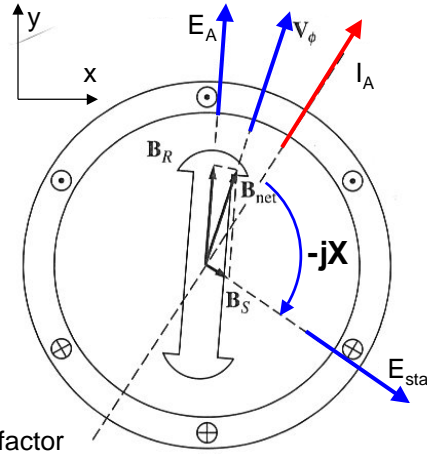$\swarrow$  X is a factor  
 $\searrow$  -j accounts for the  $-90^\circ$  rotation




## SM Single-Phase Equivalent Circuit Model

Armature reaction  $\rightarrow$  Armature (self) reactance

$$V_\phi = E_A - (jX + jX_A + R_A)I_A$$

$$V_\phi = E_A - (jX_S + R_A)I_A$$

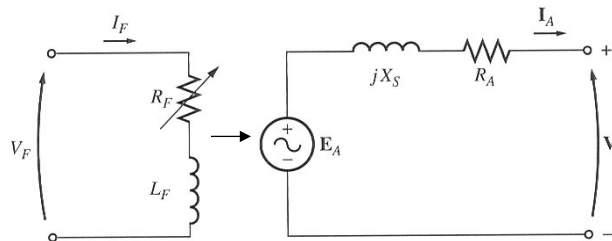Synchronous reactance  $\uparrow$  Armature resistance




$$E_A = kI_F$$


(below saturation)

## SM 3-Phase Equivalent Circuit Model

**Y-connection**

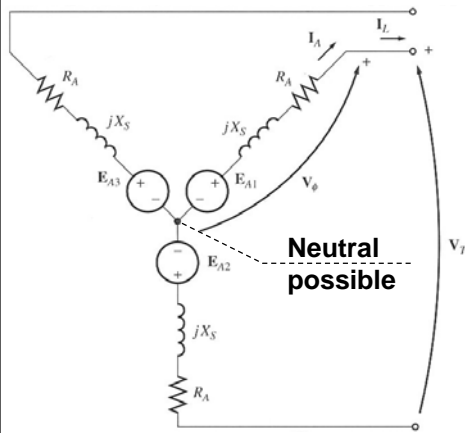


**Δ-connection**

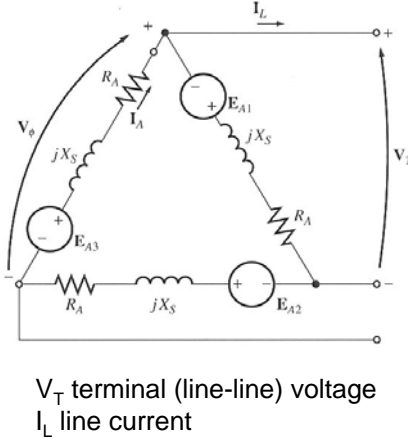
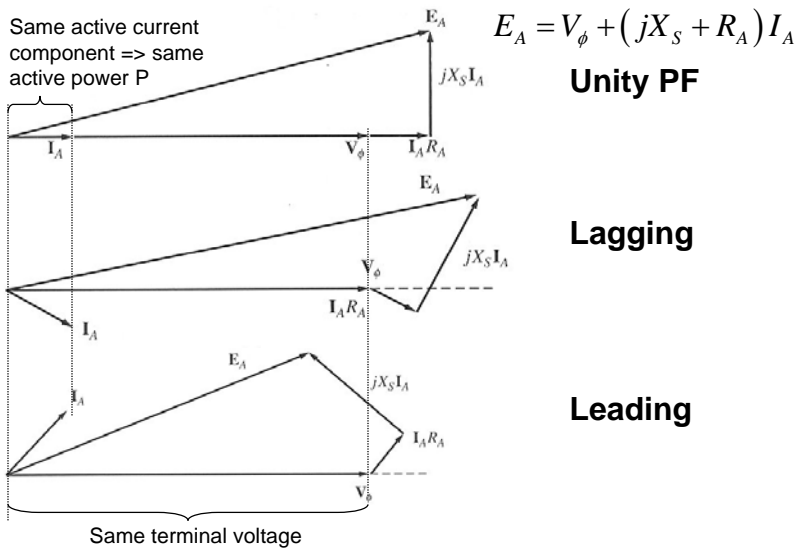
## SM Phasor Diagrams (incl. $R_A$ ), Generator

Same active current component  $\Rightarrow$  same active power P




## Measuring Machine Parameters

---


- Parameters required for machine model
  - ◆  $E_A = f(I_F)$
  - ◆  $X_S$
  - ◆  $R_A$
  - ◆ Losses (other than  $I^2R_A$ )

## Open Circuit Test

---

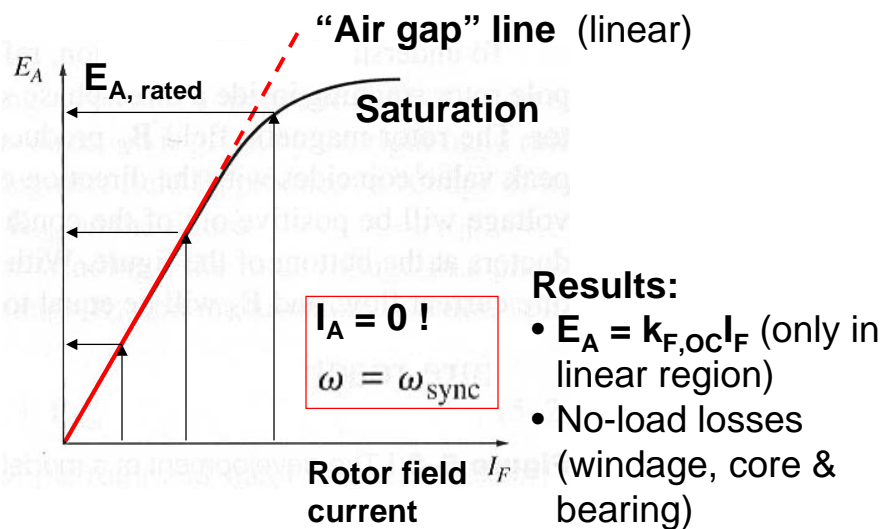

## Short Circuit Test

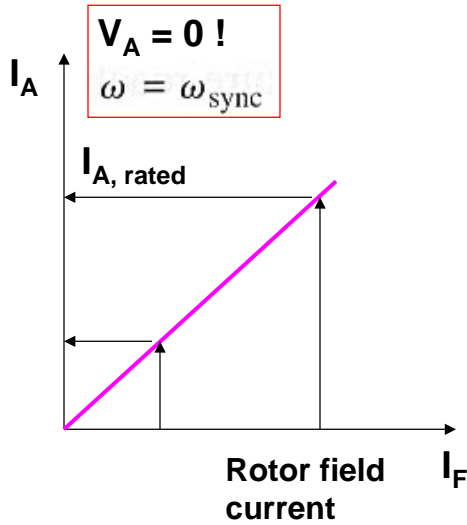

### Results:

- $I_A = k_{F, \text{sc}} I_F$
- Load losses (windage, **copper** & bearing)

$$\frac{E_A(I_F)}{I_A(I_F)} = jX_S + R_A$$

$$X_S \gg R_A$$

$$X_S \cong \frac{E_A}{I_A}$$