

# Electron Flow and Resistance: Kirchoff, Thevenin, & Norton Review: The Water Model

Session 1e of Basic Electricity  
A Fairfield University E-Course  
Powered by LearnLinc

# Basic Electricity

## Two Sections

- Electron Flow and Resistance
  - 5 on-line sessions
  - Lab
- Inductance and Capacitance
  - 5 on-line sessions
  - Lab

## *Mastery Test, Part 1*

# Basic Electricity (Continued)

- **Text:** “Electricity One-Seven,” Harry Mileaf, Prentice-Hall, 1996, ISBN 0-13-889585-6 (Covers several Modules and more)
- **References:**
  - “Digital Mini Test: Principles of Electricity Lessons One and Two,” SNET Home Study Coordinator, (203) 771-5400
  - [Electronics Tutorial](#) (Thanks to Alex Pounds at [alex\\_tb@hotmail.com](mailto:alex_tb@hotmail.com) )
  - [Electronics Tutorial](#) (Thanks to Mark Sokos at [sokos@desupernet.net](mailto:sokos@desupernet.net) )

# Section 1:

## Electron Flow and Resistance

- **OBJECTIVES:** This section introduces five basic electrical concepts as well as the underlying atomic structure of electrical materials.
  - Conductance( $G$ ),
  - Resistance ( $R$ ),
  - Current ( $I$ ),
  - Power ( $P$ ), and
  - Electromotive force ( $E$ ) or voltage ( $V$ ).


# Section 1 Schedule:

Session a – 03/04 <i>03/06 &amp; 03/08 were Math Tutorials</i>	Atoms, Charge and Current Conductivity (G), Electric Fields and Electromotive Force (EMF)	Text 1.1 – 1.39 Text 1.40 – 1.68
Session b – 03/11	Resistance (R), Conductance (G), Ohms Law ( $\Omega$ ) & Power (Watts)	Text 2.1 – 2.52
Session c – 03/13 (lab - 03/16, sat.)	Resistors in Series and Parallel and Working with Equations	Text 2.53 – 2.98
Session d – 03/18	Series / Parallel Simplification Voltage and Current Dividers	2.99 – 2.115
<b>Session e – 03/20</b>	<b>Kirchoff, Thevenin &amp; Norton Review: The Water Model</b>	<b>2.116 – 2.133 1.42, 1.63, 2.5, 2.129 Sokos</b>

# Kirchoff's Voltage Law


- The sum of all the voltages around a “loop” is zero
- Be careful to take signs into account
- Starting at the top left corner and going clockwise:

$$20 - 75 + 10 + 60 = 0$$

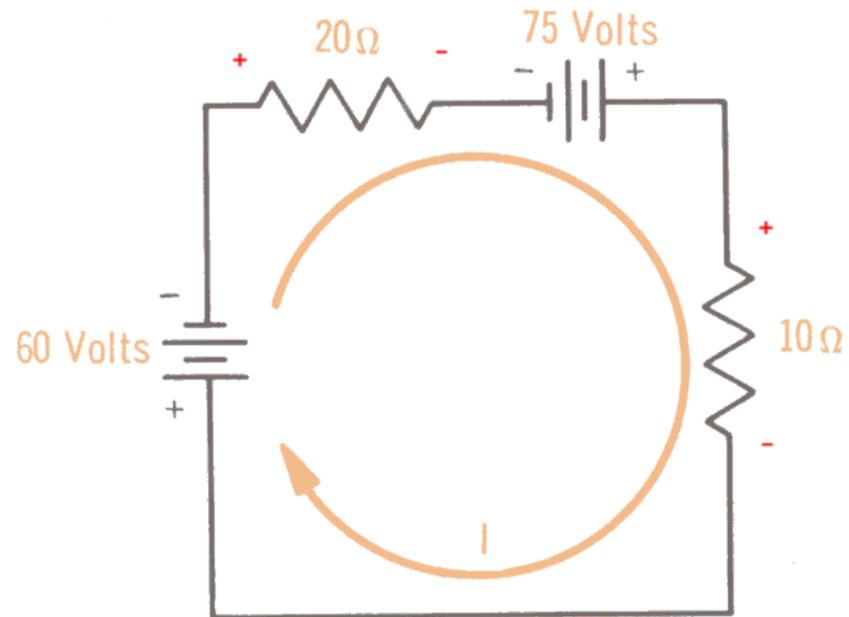

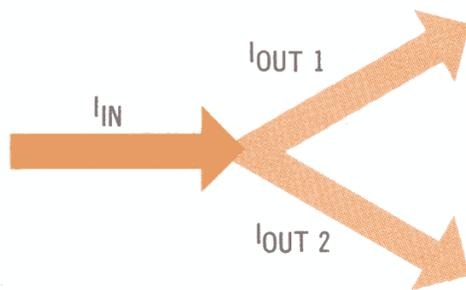
# Kirchoff's Current Law

- The sum of all currents into a node equals zero.
- Again watch out for signs (direction of current flow)




$$I_{IN} = I_{OUT 1} + I_{OUT 2}$$

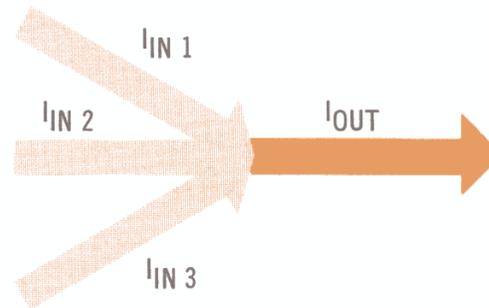

$$I_{IN 1} + I_{IN 2} + I_{IN 3} = I_{OUT}$$

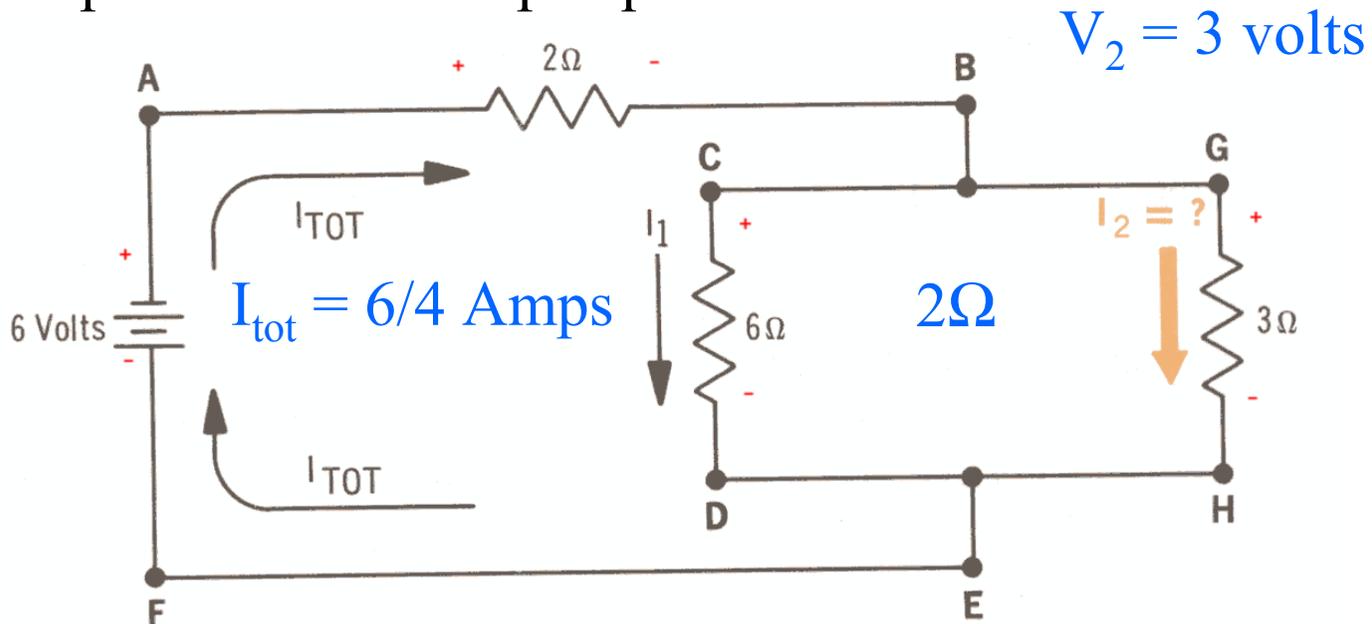
# Using Kirchoff

- Use voltage divider or,
- Kirchoff's Voltage Law and a current divider, or
- Set up and solve "Loop Equations"



# Kirchoff: Example 2

## Using Loop Equations

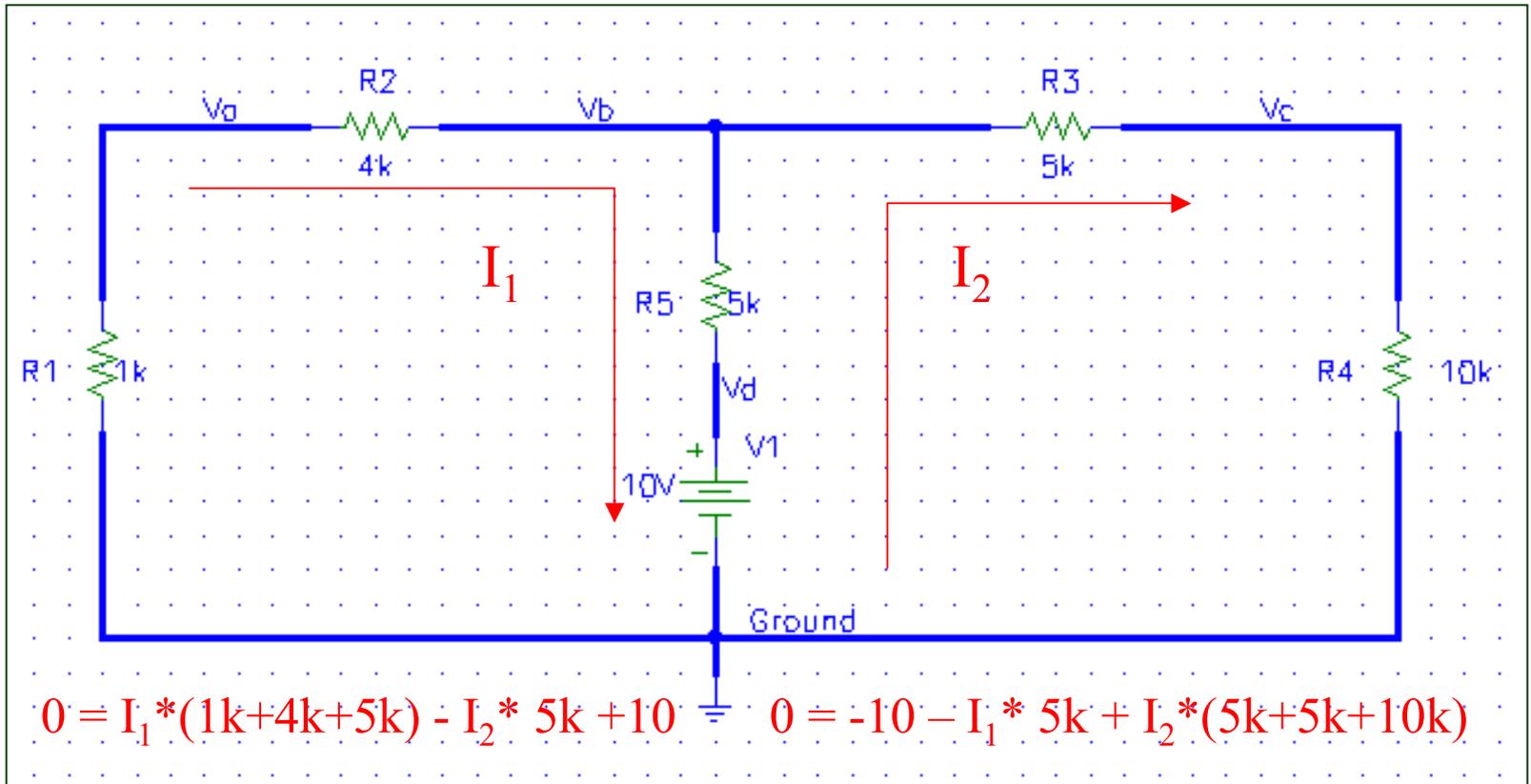

# Solving Loop Equations

$$0 = I_1*(1k+4k+5k) - I_2*5k + 10 \text{ or}$$

$$-10 = 10k * I_1 - 5k * I_2$$

$$0 = -10 - I_1* 5k + I_2*(5k+5k+10k) \text{ or}$$

$$10 = -5k * I_1 + 20k * I_2 \text{ or}$$

$$20 = -10k * I_1 + 40k * I_2$$

Adding the bottom two simplified equations

$$10 = 0 * I_1 + 35k * I_2 \text{ or}$$

$I_2 = 10/35 = 2/7$  mA and by substituting into one of the above

$$-10 = 10 * I_1 - 5 * 2/7$$


$$10 * I_1 = -10 + 5 * 2/7 = -70/7 + 10/7 = -60/7$$

$$I_1 = -6/7 \text{ mA}$$




The minus sign just says that  $I_1$  goes in the other direction
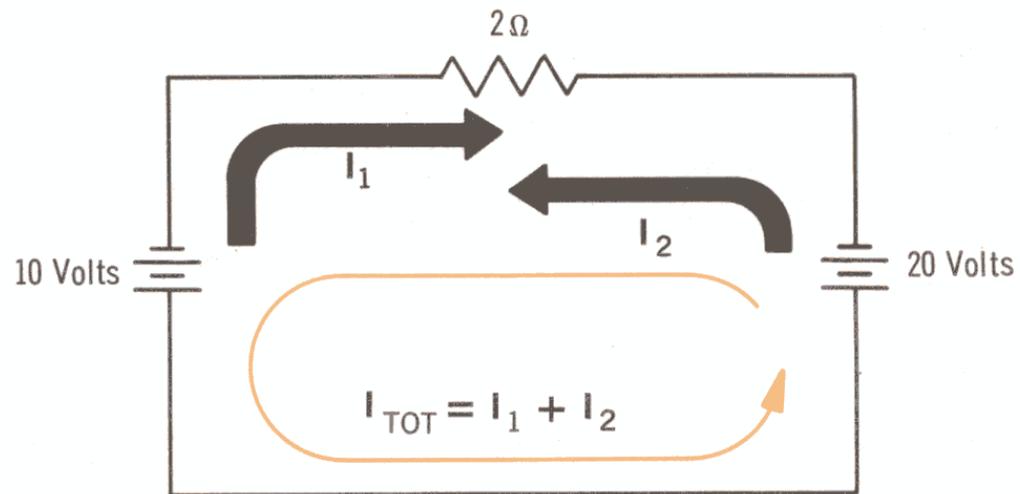
# Superposition

- Linear systems (R, L and C circuits are linear)
  - You can deal separately with each power source and then add the resulting currents (or voltages) to get the total result.



# Thevenin Equivalent Circuits

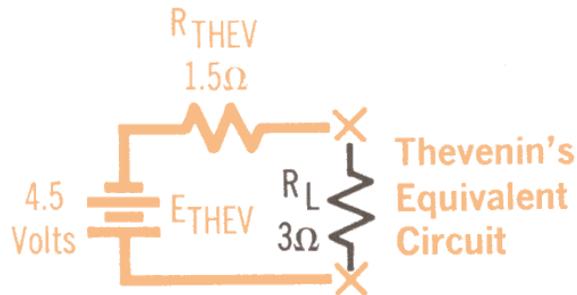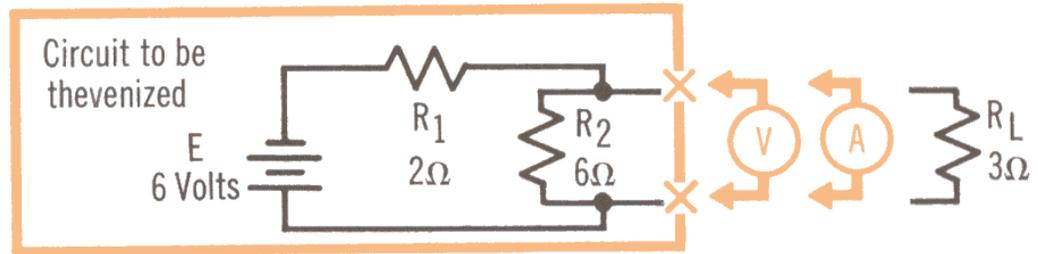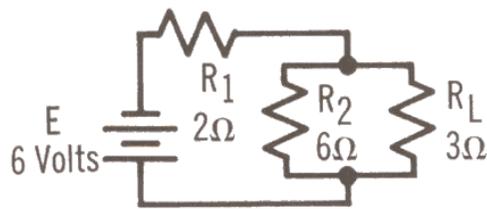


$$\text{Voltmeter reading} = E \left( \frac{R_2}{R_1 + R_2} \right) = 4.5 \text{ Volts} = E_{\text{THEV}}$$

$$\text{Ammeter reading} = E/R_1 = 6/2 = 3 \text{ Amperes} = I_{\text{THEV}}$$

$$E_{\text{THEV}}/I_{\text{THEV}} = 4.5/3 = 1.5 = R_{\text{THEV}}$$


$$I_L = \frac{E_{\text{THEV}}}{R_{\text{THEV}} + R_L} = \frac{4.5}{1.5 + 3} = 1 \text{ Ampere}$$

# Thevenin (Continued)

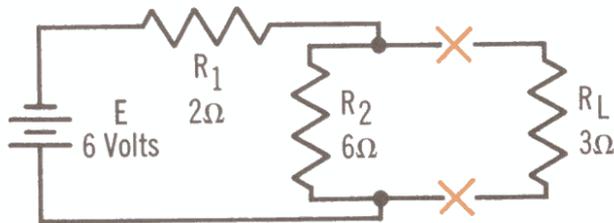


$E_{THEV}$  is the voltage drop across  $R_2$
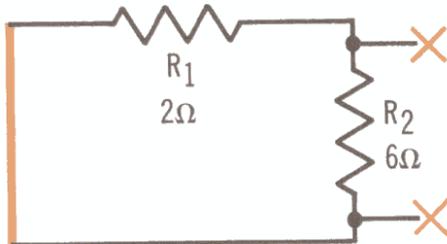
$$E_{THEV} = E \left( \frac{R_2}{R_1 + R_2} \right) = 6 \left( \frac{6}{8} \right) = 4.5 \text{ Volts}$$



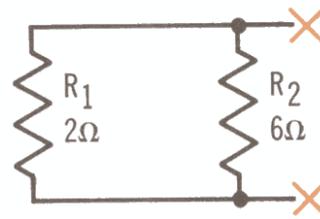
When the source voltage is shorted, this circuit becomes



this circuit




and reduces to  $R_{THEV}$

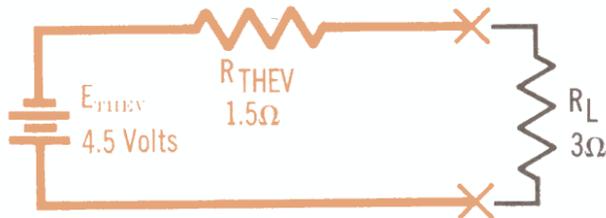


$E_{THEV}$  and  $R_{THEV}$  are connected in series with  $R_L$  to produce Thevenin's equivalent circuit

# Norton Equivalent Circuits

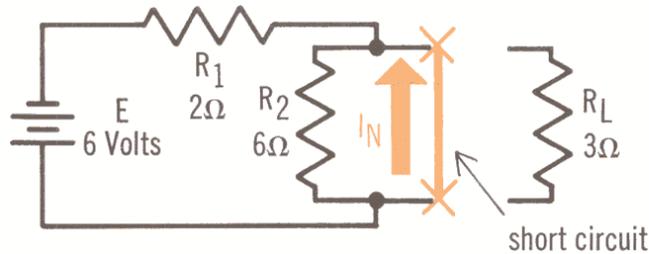

$I_{NORTON}$  is the current through a short across the output terminals
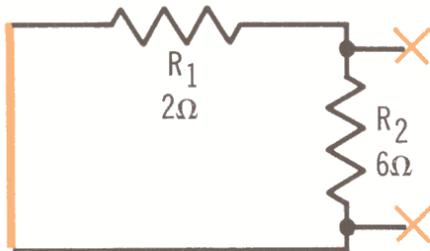
$$I_N = E/R_1 = 6/2 = 3 \text{ Amperes}$$



When the voltage source is shorted, this circuit becomes



this circuit



and reduces to  $R_{NORTON}$



The constant current source,  $I_N$  feeds  $R_N$  and  $R_L$  in parallel to produce Norton's equivalent circuit

# Next Class

- Review of all topics in chapters 1 and 2 of the text
- Quiz (via email to see how we're doing)