

Parallel Resonance

Session 4c for Basic Electricity
A Fairfield University E-Course
Powered by LearnLinc

Module: Basic Electronics

(AC Circuits and Impedance: two parts)

- Text: “Electricity One-Seven,” Harry Mileaf, Prentice-Hall, 1996, ISBN 0-13-889585-6 (Covers much more material than this section)
- References:
 - “Digital Mini Test: Principles of Electricity Lessons One and Two,” SNET Home Study Coordinator, (203) 771-5400
 - [Electronics Tutorial](#) (Thanks to Alex Pounds)
 - [Electronics Tutorial](#) (Thanks to Mark Sokos)
 - [Basic Math Tutorial](#) (Thanks to George Mason University)
 - [Vector Math Tutorial](#) (Thanks to California Polytec at atom.physics.calpoly.edu)
- Alternating Current and Impedance
 - 5 on-line sessions plus one lab
- Resonance and Filters
 - 5 on-line sessions plus one lab

Section 4:

AC, Inductors and Capacitors

- **OBJECTIVES:** This section discusses AC voltage / current and their effects on parallel circuit components (resistors, inductors, transformers and capacitors). The concept of resonance and its use to produce filters is also described.

Section 4 Schedule:


Session 4a	– 07/08	Parallel L-C Circuits	Text 4.114 – 4.122
Session 4b	– 07/10	Parallel R-L-C Circuits	Text 4.123 – 4.132
(break for a week)		(no class on 07/15 or 07/17)	
Session 4c	– 07/22	Parallel Resonance	Text 4.133 – 4.146
Session 4d	– 07/24	Tuning and Filters	Text 4.147 – 4.153
(lab - Postponed)			
Session 4e	– 07/29	Transformers and Impedance	Text 4.154 – 4.160
(Quiz 4 due 08/12)		Matching	
Session 4f	– 08/12	Review (Discuss Quiz 4)	
	08/14	MT2 Review	
	08/17	MT2 – AC Circuits	

(Parallel R-L-C) Review

- Capacitive reactance $X_C = 1/2\pi fC$ at -90°
- Inductive reactance $X_L = 2\pi fL$ at 90°
- Impedances in parallel add as inverses
- Break the problem down into two simple problems
 - First combine the Inductive and Capacitive branches
 - Here the vectors are in opposite directions; they just subtract.
 - Inductive reactance points up (90°); the inverse points down
 - Capacitive reactance points down (-90°); the inverse points up
 - The larger of the two inverses dominates
 - Now add in the inverse of the resistive branch
 - Find the magnitude (lengths) by using the square root of the sum of squares
 - Find the phases as the angle whose tangent is the vertical / horizontal
- Now just invert again to get the total parallel impedance


Resonance

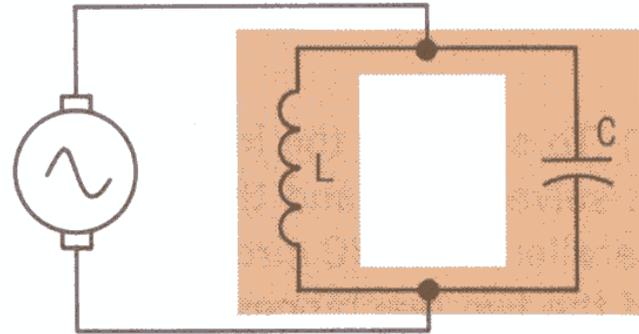- X_L and X_C cancel
- Parallel Resonance
 - High Impedance
 - Low line current
(high current in the LC loop!)
- Series Resonance
 - Low impedance
 - High line current
- Resonant frequency
$$2\pi fL = 1/2\pi fC$$
$$f = 1/2\pi(LC)^{1/2}$$




The Tank Circuit


- A “tank” circuit “rings” like a bell

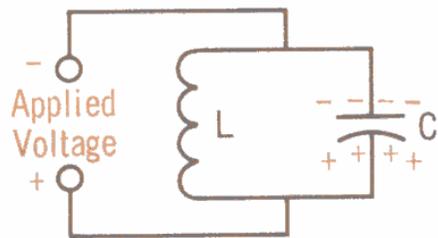


(A) C is charged by applied voltage

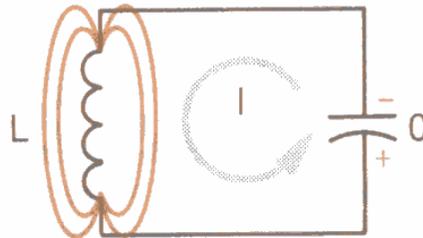

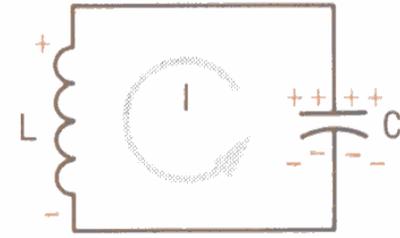
(B) C discharges and builds up field around L




(C) Field around L collapses, charging C

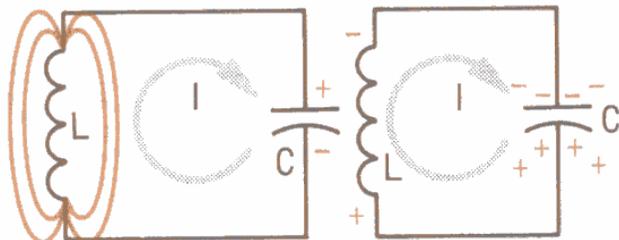

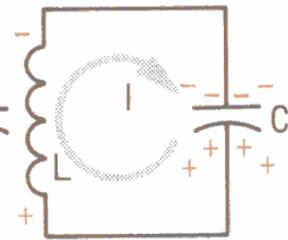(D) C discharges and builds up field around L




(E) Field around L collapses, charging C

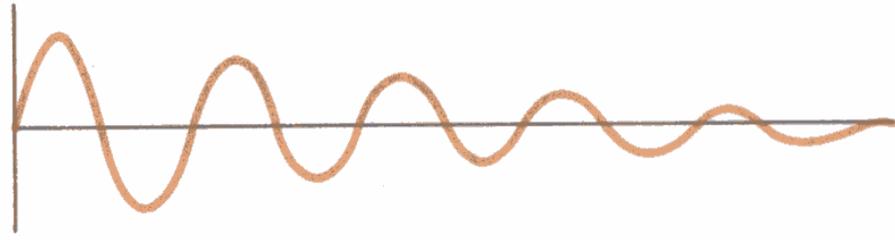

Because of resistance in the circuit, the circulating action diminishes, and a damped series of sine waves is produced

Current at Resonance




- At Resonance (for an Ideal parallel RC)
 - $|I_L| = |I_C|$ but they are in opposition
 - $I_{Line} = I_L + I_C = 0$

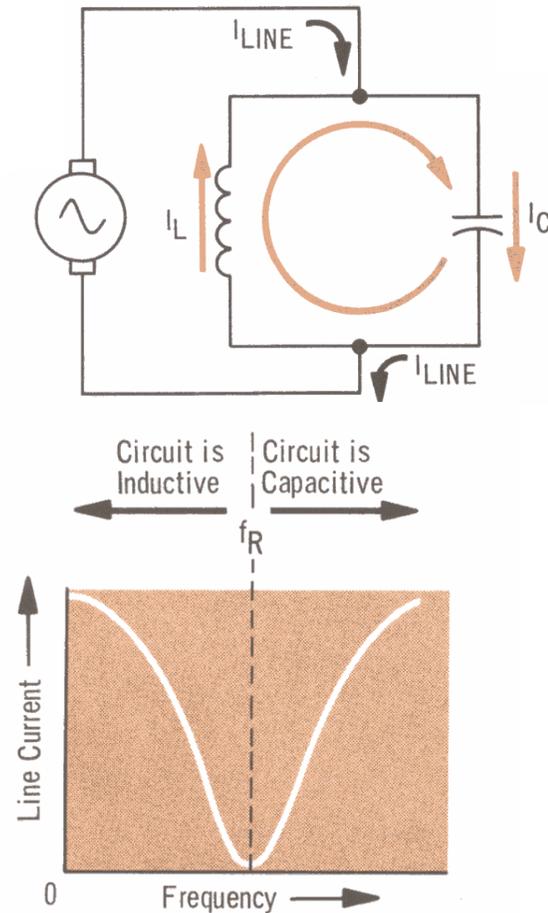

Impedance at Resonance



- At Resonance (for an Ideal parallel RC)
 - $|X_L| = |X_C|$ but they are in opposition
 - $1/Z = 1/X_L + 1/X_C = 1/\infty$

Z is very large near resonance!

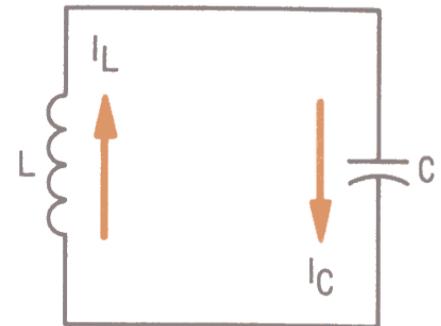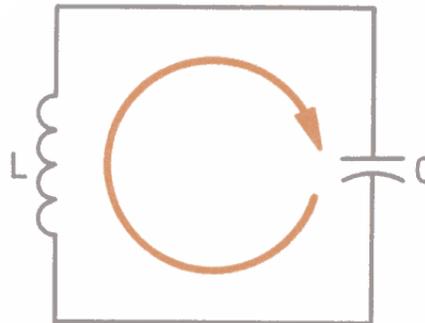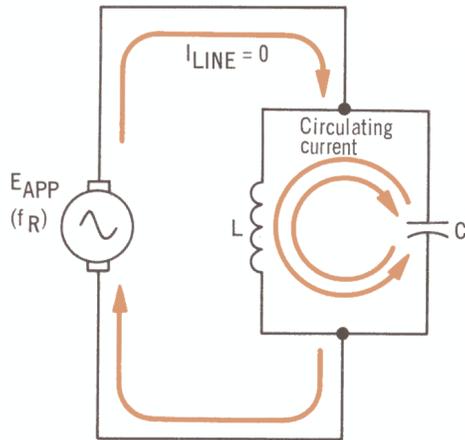


Line Current off Resonance

- If $|I_L| < |I_C|$ the line current is capacitive
- If $|I_L| > |I_C|$ the line current is inductive

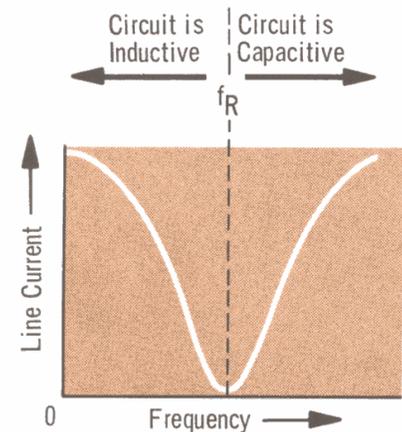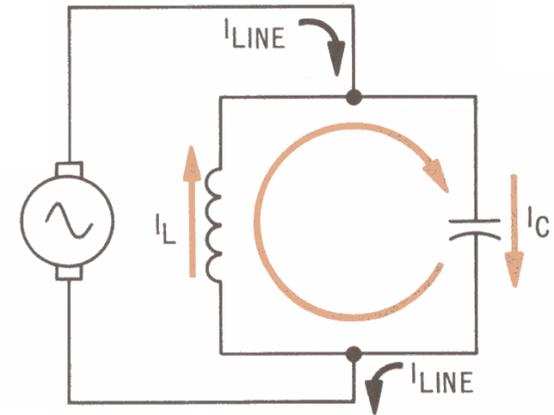


Impedance off Resonance

- If $|X_L| > |X_C|$ the impedance is capacitive
- If $|X_L| < |X_C|$ the impedance is inductive
- Line Impedance
 - $1/Z = 1/X_L + 1/X_C$

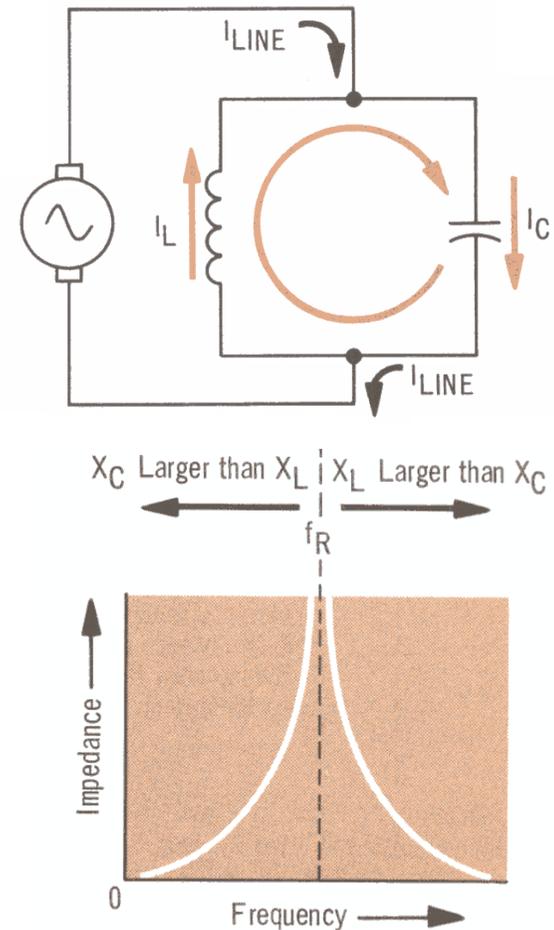

Real Tank Circuits

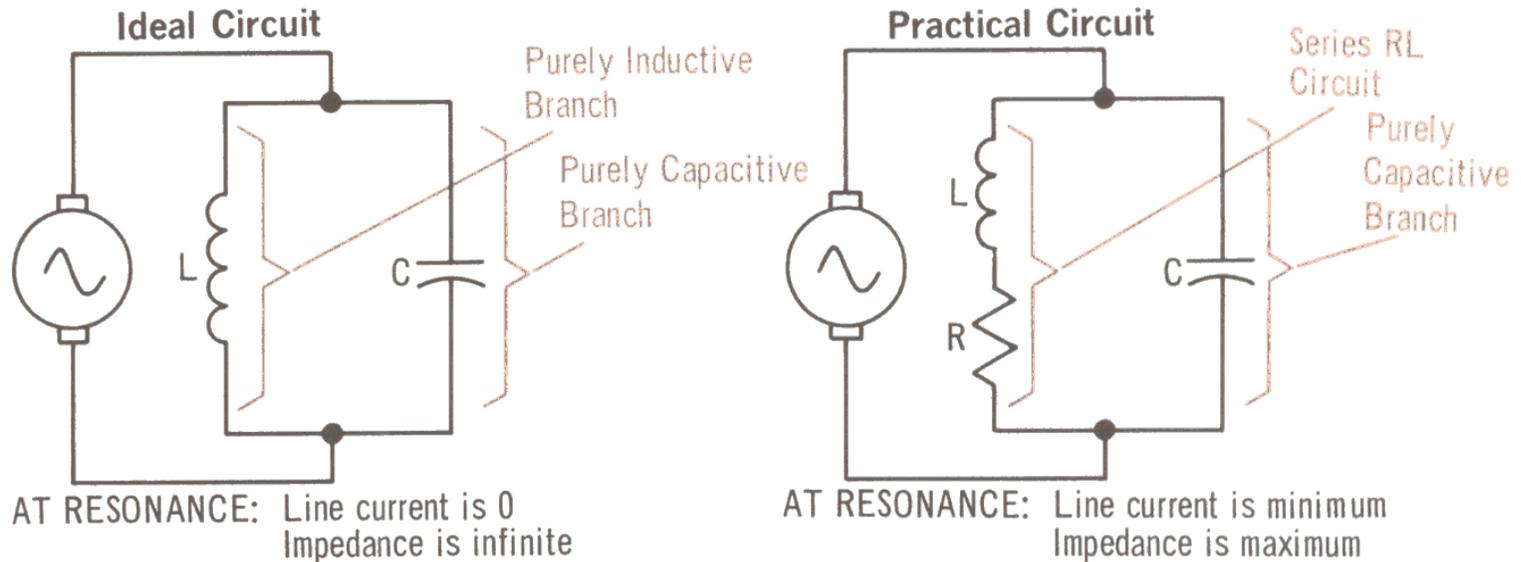- Inductors have a series resistance; not a parallel one



A Parallel RLC Example

- First invert the series RL


$$\begin{aligned}
 1/Z_1 &= 1/(50\angle 0^\circ + 200\angle 90^\circ) \\
 &= 1/[(50^2 + 200^2)^{1/2} \angle \arctan(200/50)] \\
 &= 1/[(50^2 + 200^2)^{1/2} \angle \arctan(200/50)] \\
 &= 1/(206.2\angle 76^\circ) \\
 &= 0.00485\angle -76^\circ
 \end{aligned}$$

$$1/Z_2 = 1/(200\angle -90^\circ)$$

$$1/Z_t = 0.00485\angle -76^\circ + 0.005\angle 90^\circ$$


$$= .00485 * \cos(76)\angle 0^\circ + .00485 * \sin(-76)\angle 90^\circ + .005\angle 90^\circ$$
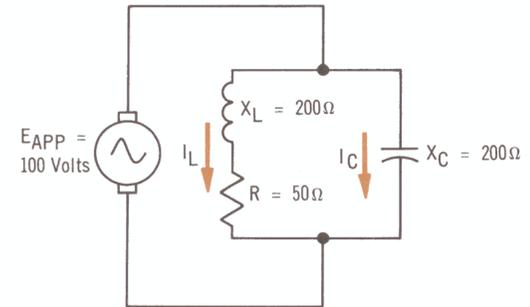
$$= 0.00117\angle 0^\circ + 0.0003\angle 90^\circ = 0.0012\angle 14.4^\circ$$



The Resonance Band


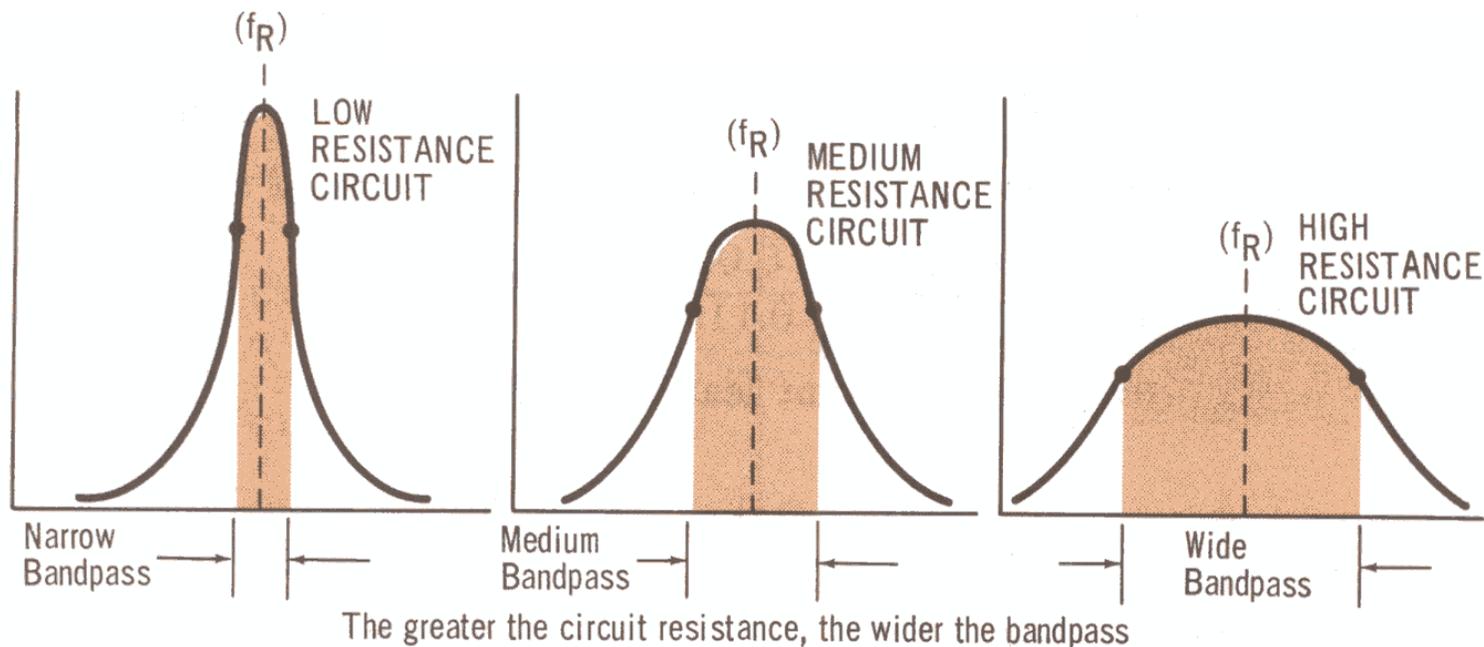
- Changing the Inductor's series resistance changes the "Bandwidth"



“Q”

- $Q = X_L / R = X_C / R$ at resonance

A High Q Means a Narrow Bandpass

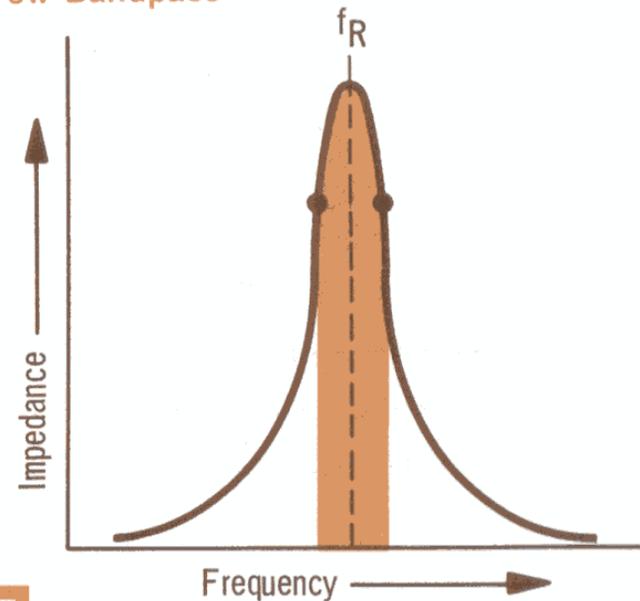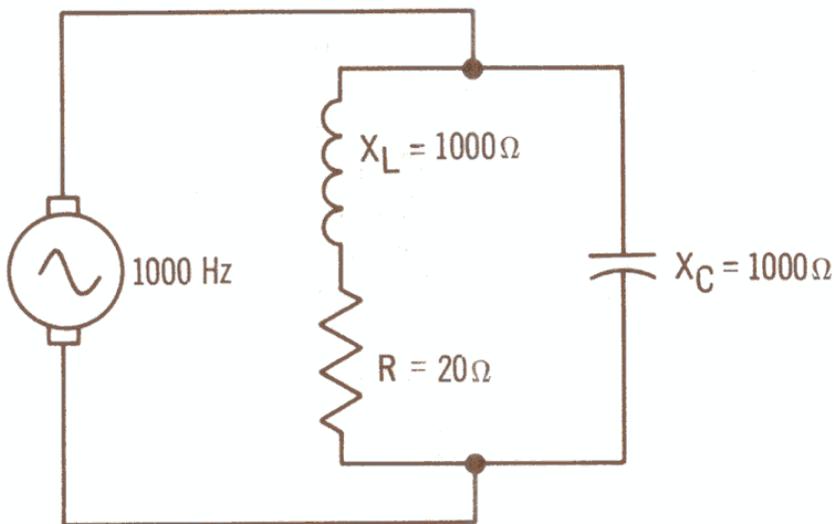

$$Q = 50$$

Changing Q

- Adding a parallel (shunt) resistor lowers Q
- More resistance in tank loop lowers Q

Section 4 Schedule:

Session 4a	– 07/08	Parallel L-C Circuits	Text 4.114 – 4.122
Session 4b	– 07/10	Parallel L-R-C Circuits	Text 4.123 – 4.132
(break for a week)		(no class on 07/15 or 07/17)	
Session 4c	– 07/22	Parallel Resonance	Text 4.132 – 4.146
Session 4d	– 07/24	Tuning and Filters	Text 4.147 – 4.153
(lab - Postponed)			
Session 4e	– 07/29	Transformers and Impedance	Text 4.154 – 4.160
(Quiz 4 due 08/12)		Matching	
Session 9 starts	– 08/05	Business Writing	
Session 4f	– ??	Review (Discuss Quiz 4)	
	??	MT2 Review	
7/23/2002	??	MT2 – AC Basic Circuits	