

Transistor Amplifiers

Session 5e for Electronics and
Telecommunications
A Fairfield University E-Course
Powered by LearnLinc

Module: Semiconductor Electronics

(in two parts)

- Text: “Electronics,” Harry Kybett, Wiley, 1986, ISBN 0-471-00916-4
- References:
 - [Electronics Tutorial](#) (Thanks to Alex Pounds)
 - [Electronics Tutorial](#) (Thanks to Mark Sokos)
- Semiconductors, Diodes and Bipolar Transistors
 - 5 on-line sessions plus one lab
- FETs, SCRs, Other Devices and Amplifiers
 - 5 on-line sessions plus one lab
- Mastery Test part 3 follows this Module

Section 5: Semiconductors, Diodes and Bipolar Transistors

- **OBJECTIVES:** This section reviews semiconductors, doping and junctions. The characteristics and application of Diodes and Bipolar Transistors are then studied.

Section 5 Schedule:

Session 5a	– 09/18	Semiconductors and Doping	Elect 1-7 1.23 – 1.39
MT2 Results	– 09/23	We'll discuss MT2	
Session 5b	– 09/25	Diodes	Kybett Chapter 2
Session 5c	– 09/30	Diode Applications	Kybett Chapter 11
Session 5d	– 10/02	Bipolar Transistors	Kybett pp 51 - 70
(lab - 10/05, Sat.)			
Session 5e	– 10/07	Transistor Amplifiers	Kybett pp 173 - 201
(Quiz 4 due 10/12)			
Session 5f	– 10/16	Review (Discuss Quiz 4)	
(Oct 14 is a holiday)			

Break to introduce
Learnlinc version 6.1

About 2 weeks to set up the
computers and retrain us

Transistor Review

- Transistors have three leads: base, emitter and collector
- Testing via ohm meter
 - Two diodes back to back: test each separately for impedance ratio
 - Check collector to emitter for high impedance (leakage)
- Beta (β): Current gain $\beta = I_C/I_B$, as long as no “saturation” ($V_{CE} > 0.2\text{v}$)
 - Transistor “action”
 - Carriers injected into “depletion region” (very thin base region)
- NPN and PNP: currents and voltages reversed
- Analyze Base current (I_B) flow as a diode
- Collector current: $I_C = I_B * \beta$
- Collector voltage: $V_C = V_{\text{batt}} - I_C * R_C$




Today's Topics

- Transistor Biasing
 - Setting the “Quiescent Point”
 - Stability
- Amplifier characteristics
 - Gain
 - Impedances (input and output)
- Amplifier Configurations
 - Common Emitter
 - Common Collector
 - Common Base


Transistor Biasing

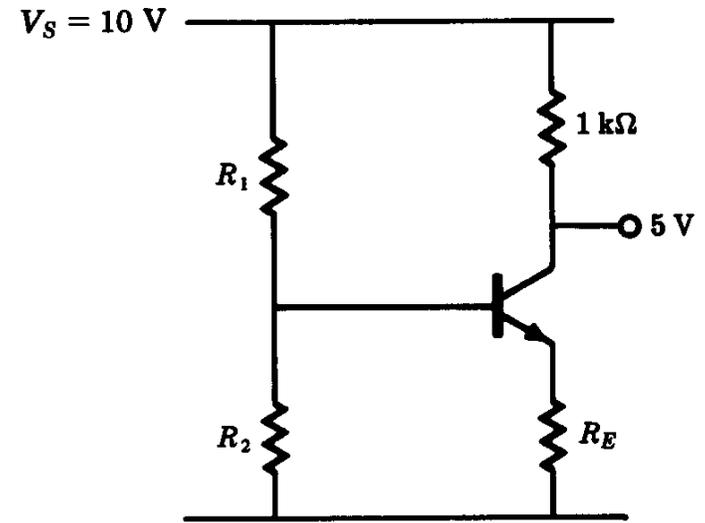1. Set $V_B = 0.7\text{V} + \text{desired } V_E$
2. R_1 & R_2 form a voltage divider
 $V_B = V_S * R_2 / (R_1 + R_2)$
3. Determine $R_E = V_E / I_E$
($I_E = I_C + I_B$)
4. DC gain is approx. R_C / R_E
5. Input Impedance is approx. $\beta * R_E$
(in parallel with R_1 and R_2
so keep them reasonably large)




Biasing (continued)

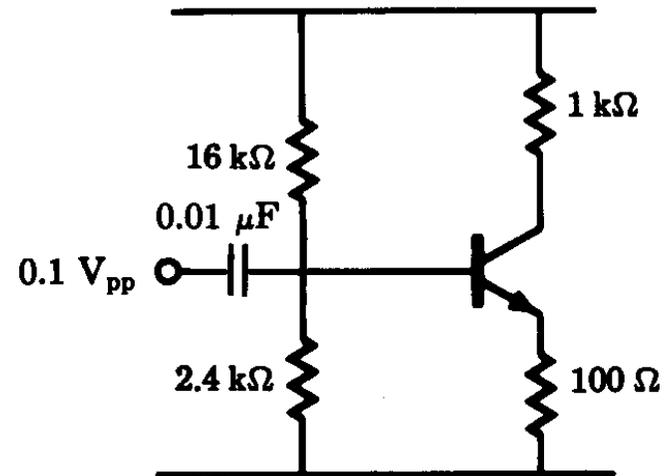- $V_{bb} = 10 \text{ v}$; $V_C = 5 \text{ v}$
 $I_C = 5 \text{ mA} \sim I_E$ ($I_B = I_C/\beta$)
- Set $V_E = 0.5 \text{ v}$; $R_E = 100 \Omega$
- $V_B = 0.5 + 0.7 = 1.2 \text{ v}$
- $R_2 / (R_1 + R_2) = 1.2/10$
(Use resistors at least 10
times those in the output)
 $R_2 = 2.2 \text{ k}\Omega$; $R_1 = 16 \text{ k}\Omega$




Amplifier characteristics

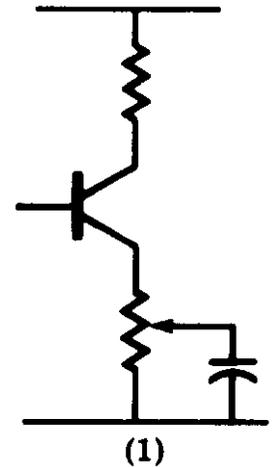- Gain (AC and DC can be different)
 - Voltage (V_{out} / V_{in})
 - Power (P_{out} / P_{in})
- Impedance
 - Input: loads the source reducing the input
 - Output: A low output impedance makes the output voltage independent of the load impedance.



Common Emitter

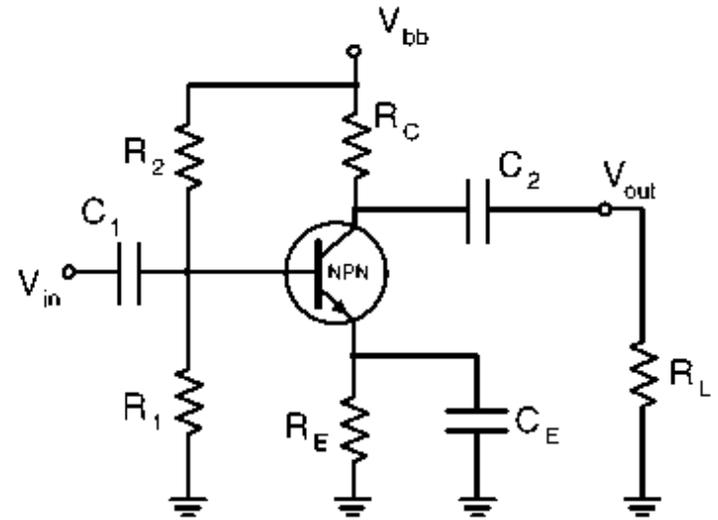
- High input impedance
 - $R_1 \parallel R_2 \parallel (R_{in} + \beta * R_E) \dots R_{in} = h_{ie} \sim 1 \text{ k}\Omega$
- High voltage gain
 - $\beta * R_C / (R_{in} + \beta * R_E)$ (general case)
 - $\sim R_C / R_E$ (no bypass capacitor)
 - $\sim \beta * R_C / R_{in}$ (fully bypassed)
- Medium output impedance



Common Collector (Emitter Follower)


- The common collector junction transistor amplifier is commonly called an emitter follower. The voltage gain of an emitter follower is just a little less than one since the emitter voltage is constrained at the diode drop of about 0.7 volts below the base. Its function is not voltage gain but current or power gain and impedance matching.
- It's input impedance is much higher than its output impedance. The low output impedance of the emitter follower matches a low impedance load and buffers the signal source from that low impedance.

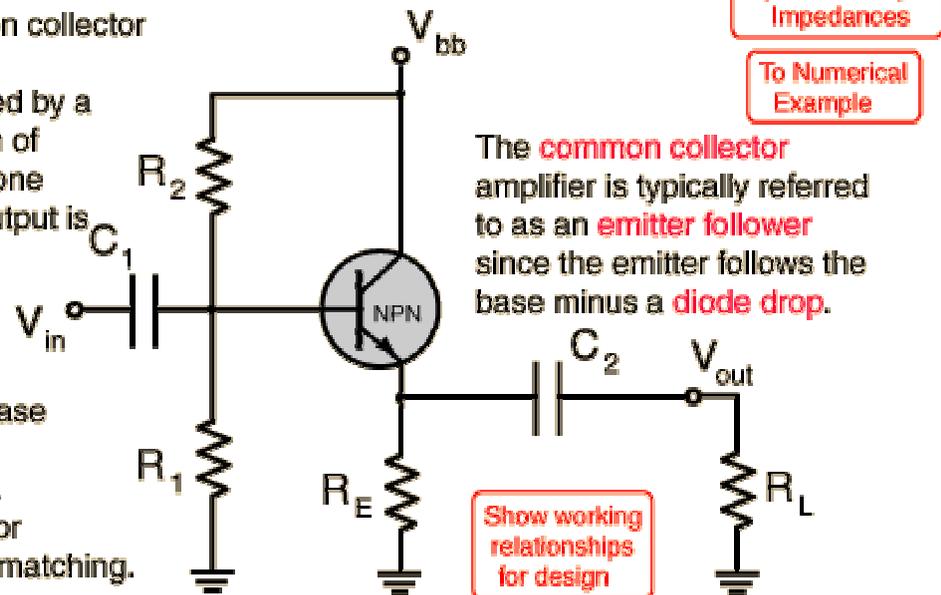The common collector amplifier is characterized by a voltage gain of essentially one since the output is **constrained** at a voltage about 0.6 volts below the base which is the signal input. It is useful for impedance matching.



Common Base

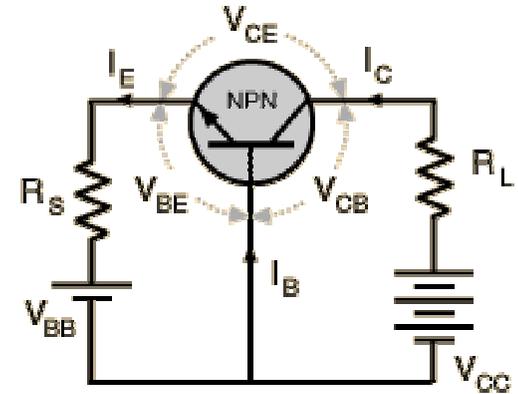- This configuration is sometimes used for high frequency applications because the base separates the input and output, minimizing oscillations at high frequency. It has a high voltage gain, relatively low input impedance and high output impedance compared to the common collector.



Summary

- Transistor Biasing
 - Setting the “Quiescent Point”
 - DC Stability
- Amplifier characteristics
 - Gain
 - Impedances (input and output)
- Amplifier Configurations
 - Common Emitter (voltage gain)
 - Common Collector (buffer, low output impedance)
 - Common Base
(only used in some high frequency applications)

Section 5 Schedule:

Session 5a	– 09/18	Semiconductors and Doping	Elect 1-7 1.23 – 1.39
MT2 Results	– 09/23	We'll discuss MT2	
Session 5b	– 09/25	Diodes	Text Chapter 2
Session 5c	– 09/30	Diode Applications	Text Chapter 11
Session 5d	– 10/02	Bipolar Transistors	Text pp 51 - 70
(lab - 10/05, Sat.)			
Session 5e	– 10/07	Transistor Amplifiers	Text pp 173 - 201
(Quiz 4 due 10/12)			
Session 5f	– 10/16	Review (Discuss Quiz 4)	
(the 14th is a Holiday)			

Break to introduce
Learnline version 6.1

About 2 weeks to set up the
computers and retrain us