

Review: Quiz 5

Session 5e for Electronics and
Telecommunications
A Fairfield University E-Course
Powered by LearnLinc

Module: Semiconductor Electronics

(in two parts)

- Text: “Electronics,” Harry Kybett, Wiley, 1986, ISBN 0-471-00916-4
- References:
 - [Electronics Tutorial](#) (Thanks to Alex Pounds)
 - [Electronics Tutorial](#) (Thanks to Mark Sokos)
- Semiconductors, Diodes and Bipolar Transistors
 - 5 on-line sessions plus one lab
- FETs, SCRs, Other Devices and Amplifiers
 - 5 on-line sessions plus one lab
- Mastery Test part 3 follows this Module

Section 5: Semiconductors, Diodes and Bipolar Transistors

- **OBJECTIVES:** This section reviews semiconductors, doping and junctions. The characteristics and application of Diodes and Bipolar Transistors are then studied.

Section 5 Schedule:


Session 5a	– 09/18	Semiconductors and Doping	Elect 1-7 1.23 – 1.39
MT2 Results	– 09/23	We'll discuss MT2	
Session 5b	– 09/25	Diodes	Kybett Chapter 2
Session 5c	– 09/30	Diode Applications	Kybett Chapter 11
Session 5d	– 10/02	Bipolar Transistors	Kybett pp 51 - 70
(lab - 10/05, Sat.)			
Session 5e	– 10/07	Transistor Amplifiers	Kybett pp 173 - 201
(Quiz 4 due 10/12)			
Session 5f	– 10/16	Review (Discuss Quiz 4)	
(Oct 14 is a holiday)			

Break to introduce
Learnline version 6.1

About 2 weeks to set up the
computers and retrain us

Quiz_5 Results

- Those that turned in their Quiz 5 so far– Nice Job.

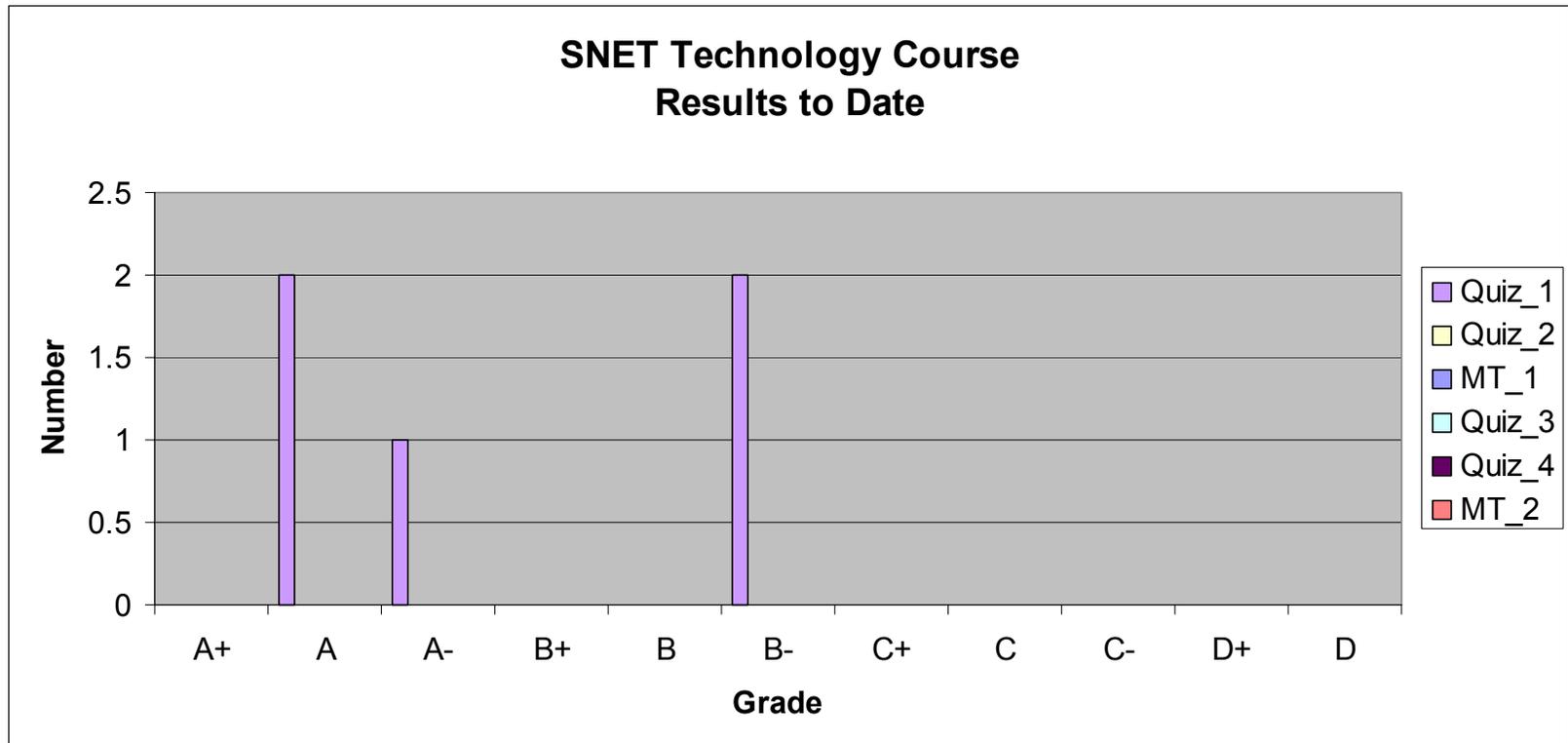


Quiz 5

- We'll use Appshare and Word to go over the T/F and Multiple Choice parts of Quiz_5
- The circuit will take a little longer.
My error made it a difficult problem


Common Emitter Amplifier

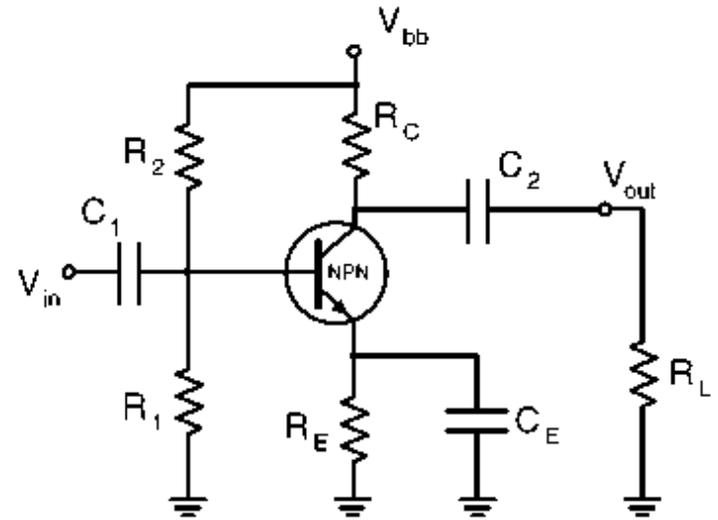- High input impedance
 - $R_1 \parallel R_2 \parallel (R_{in} + \beta * R_E) \dots R_{in} = h_{ie} \sim 1 \text{ k}\Omega$
- High voltage gain
 - $\beta * R_C / (R_{in} + \beta * R_E)$ (general case)
 - $\sim R_C / R_E$ (no bypass capacitor)
 - $\sim \beta * R_C / R_{in}$ (fully bypassed)



- All this is true **ONLY** if the transistor is biased properly
 - $V_{be} \sim 0.7 \text{ volts}$ $V_{ce} \sim V_{bb}/2$
- In our Quiz: C_1 , C_2 and C_E have large values
 - $V_{bb} = 10 \text{ volts}$ $R_1 = 2 \text{ k}\Omega$ $R_2 = 8 \text{ k}\Omega$
 - $R_E = 100 \Omega$ $R_C = 1 \text{ k}\Omega$ $\beta = 200$


Biasing

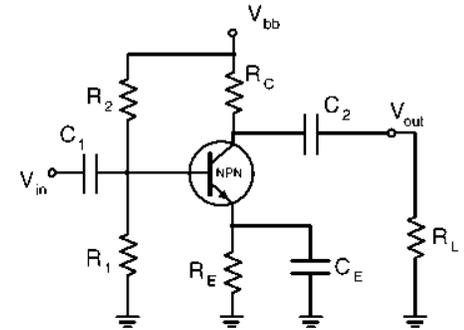

- To find V_b :
We have a voltage divider formed by R_1 (2k) and R_2 (8k)
 - If there is no base current: $V_b = 10\text{v} * 2\text{k} / (2\text{k} + 8\text{k}) = 2$ volts
 - The Thevenin resistance of this bias voltage is $R_1 \parallel R_2$ or $1/R = 1/2 + 1/8 = 5/8 = 1/1.6$ so $R_{th} = 1.6$ kohms
this can be used to determine the voltage drop if I_b is not zero
- Assuming I_b is small:
 - $V_e = V_b - 0.7 = 1.3$ volts
- $I_e = 1.3$ volts / 100 ohms = 13 mA
- $V_c = V_{bb} - I_c * R_c = 10 - 0.013 * 1000 = -3$ volts ... oops
- The transistor is “Saturated”
 $V_{ce} \sim 0.2$ volts - We have to start over and it’s not easy
note: This is good stuff, but NOT required for the MTs

Saturated Transistor

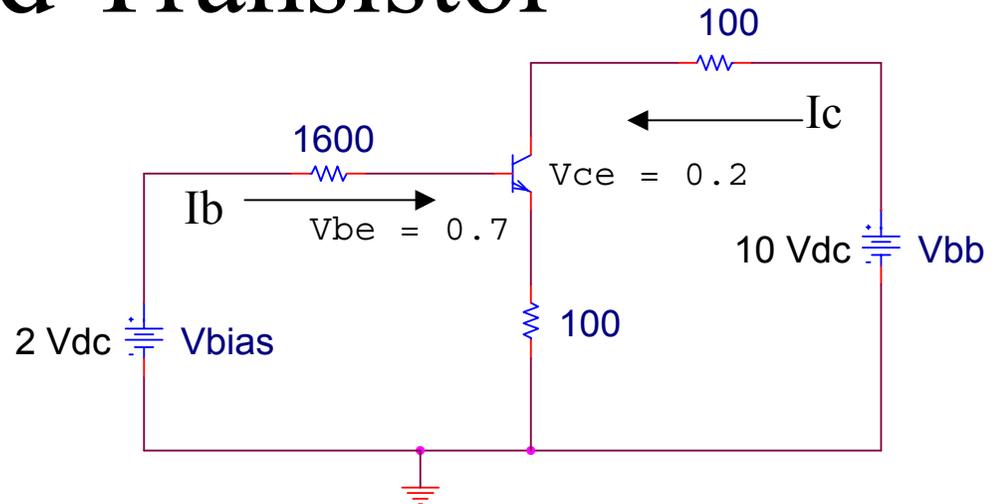- There are two loops!
- Use Kirchoff twice



- In the Base loop
$$2\text{v} = 1600 * I_b + 0.7 + 100 * (I_b + I_c) \text{ or}$$
$$1.3\text{v} = 1700 * I_b + 100 * I_c$$
- In the Collector loop
$$10\text{v} = 1000 * I_c + 0.2 + 100 * (I_b + I_c) \text{ or}$$
$$9.8\text{v} = 100 * I_b + 1100 * I_c$$

Two Equations in Two Unknowns

- Our Equations:

$$1.3\text{v} = 1700 * I_b + 100 * I_c$$

$$9.8\text{v} = 100 * I_b + 1100 * I_c$$

- Several ways to find a solution

- Solve one for I_b and substitute into the other to get I_c
- I used a tool called MatLab


- $I_c = 8.89 \text{ mA}$ and $I_b = 0.24 \text{ mA}$

- $V_c = 10 - 8.89 = 1.1 \text{ v}$

- $V_e = 0.091 * 100 = 0.9 \text{ v}$ and

- $V_b = 2 - 0.00024 * 1600$ (using Thevenin)
 $= 2 - 0.384 = 1.62\text{v}$

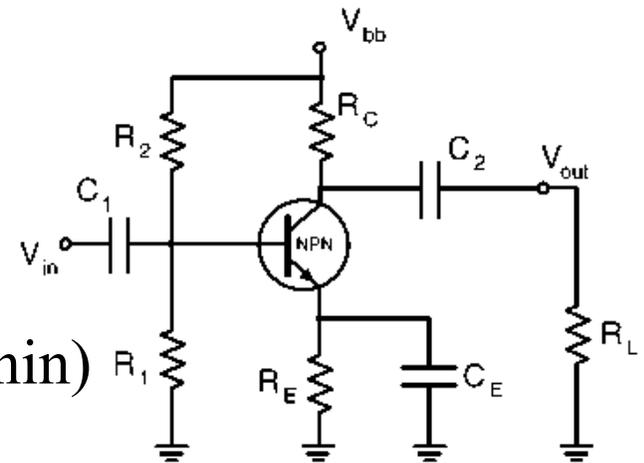- $\beta = I_c / I_b = 8.89 / 0.24 = 37$ **It has dropped in saturation**



Section 5 Schedule:

Session 5a	– 09/18	Semiconductors and Doping	Elect 1-7 1.23 – 1.39
MT2 Results	– 09/23	We'll discuss MT2	
Session 5b	– 09/25	Diodes	Text Chapter 2
Session 5c	– 09/30	Diode Applications	Text Chapter 11
Session 5d	– 10/02	Bipolar Transistors	Text pp 51 - 70
(lab - 10/05, Sat.)			
Session 5e	– 10/07	Transistor Amplifiers	Text pp 173 - 201
(Quiz 4 due 10/12)			
Session 5f	– 10/16	Review (Discuss Quiz 4)	
(the 14 th is a Holiday)			

**Break to introduce
Learnline version 6.1**

**About 2 weeks to set up the
computers and retrain us**