

Semiconductor Electronics Q & A

Session 6e for Electronics and
Telecommunications
A Fairfield University E-Course
Powered by LearnLinc

Module: Semiconductor Electronics

(in two parts)

- Text: “Electronics,” Harry Kybett, Wiley, 1986, ISBN 0-471-00916-4
- References:
 - [Electronics Tutorial](#) (Thanks to Alex Pounds)
 - [Electronics Tutorial](#) (Thanks to Mark Sokos)
- 5 - Semiconductors, Diodes and Bipolar Transistors
 - 5 on-line sessions plus one lab
- 6 - FETs, SCRs, Other Devices and Amplifiers
 - 5 on-line sessions plus one lab
- Mastery Test part 3 follows this Module

Section 6: FETs, SCRs, Other Devices and Operational Amplifiers

- **OBJECTIVES:** This section reviews additional important semiconductor devices and their applications. The Operational Amplifier is also studied.

Section 6 Schedule:

Session 6a	01/15	Field Effect Transistors	Kybett pp 70 – 77, pp 201-209
Session 6b	01/20	Transistors as a switch	Kybett pp 78 –107
Session 6c	01/22	SCR's, Triacs and UJT's	Notes
Session 6d	01/27	Class A, B, and C Amplifiers	Notes
Session 6e (no class Monday)	01/29	Q & A	
Session 6e (Lab - 02/08, Sat.)	02/05	Operational Amplifiers	Kybett pp 209-215
Session 6f (Quiz 6 due 02/23)	02/10	Review for Quiz 6 (no class 2/17 or 2/19)	
Session 6g	02/24	Discuss Quiz 6	
Session 6h	02/26	Review for MT3	
MT3	03/01	MT3 Exam	
Session 6i	03/10	Discuss MT3	

Topics

- Semiconductors and Doping
- Diodes and Applications
- Bipolar Transistors
- Transistor Amplifiers
- Field Effect Transistors
- Transistors as a switch
- Other Devices
- Class A, B, and C amplifiers
- Operational Amplifiers (next time)

Diodes

- Diodes are electronic one-way valves
 - Current can flow from anode to cathode
 - Current is blocked in the reverse direction

- Forward voltage drop



Current flows from A to B
but not from B to A.

- Silicon $V_f = 0.7$ volts
 - Germanium $V_f = 0.3$ volts
 - Schottky $V_f = 0.1$ volts
 - GaAs $V_f = 2$ volts
- Peak Inverse Voltage (PIV, PRV, Zener)
- These are non-linear devices (no superposition)

Diode Analysis Review

- First determine if the diode is:
 - Forward biased: conducting with a small voltage drop
 - Reverse biased: an open switch
 - In reverse breakdown (PIV): conducting with a large voltage drop (The Zener voltage)
- Replace the diode with a simple equivalent and then analyze the circuit (Ohm and Kirchoff)
- Check power dissipation in each component to avoid overheating

Transistor Review

- Transistors have three leads: base, emitter and collector
- Testing via ohm meter
 - Two diodes back to back: test each separately for impedance ratio
 - Check collector to emitter for high impedance (leakage)
- Beta (β): Current gain $\beta = I_C/I_B$, as long as no “saturation” ($V_{CE} > 0.2\text{v}$)
 - Transistor “action”
 - Carriers injected into “depletion region” (very thin base region)
- NPN and PNP: currents and voltages reversed
- Analyze Base current (I_B) flow as a diode
- Collector current: $I_C = I_B * \beta$
- Collector voltage: $V_C = V_{\text{batt}} - I_C * R_C$



Transistor Review (2)



- Amplifier Configurations
 - Common Emitter (voltage gain)
 - Common Collector (buffer, low output impedance)
 - Common Base
(only used in some high frequency applications)
- Non-Linear Operation
 - Saturation: Transistor is fully on ($V_{ce} = 0.2$, low β)
 - Cutoff: Transistor is off ($V_{be} < 0.5$, $I_c = 0$)

FET Summary

- A voltage-controlled resistor
- Channel material
 - N-channel FET
 - P-channel FET
- FET types
 - Junction FET (JFET)
 - Metal Oxide Gate FET (MOSFET)
 - Complementary Symmetry MOSFET (CMOS)
- Simple high input impedance amplifiers
- Very effective as switches



Transistor Switch Summary

- Can be either Bipolar or FET
 - They operate fully in saturation or cutoff
 - Bipolar: Current controlled switch
 - NPN: +0.7 volt base-emitter ON
 - PNP: -0.7 volt base-emitter ON
 - FET: Voltage controlled switch
 - N-Ch JFET: -5 volt gate-source OFF, 0 volt ON
 - P-Ch JFET: +5 volt gate-source OFF, 0 volt ON
 - MOSFET: 0 volt gate-source Off,
5 volt gate-source ON
- Positive for N-Ch, Negative for P-Ch

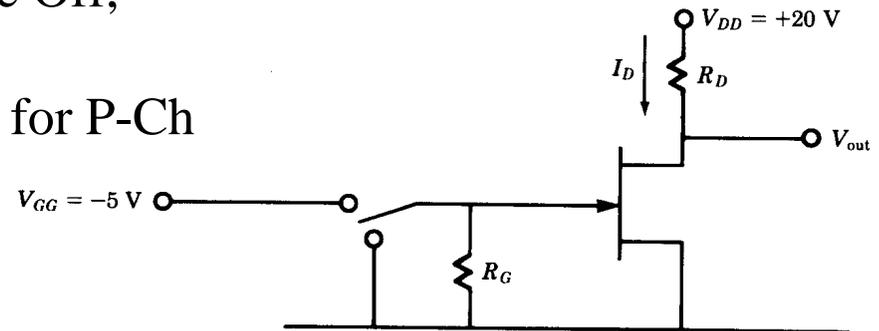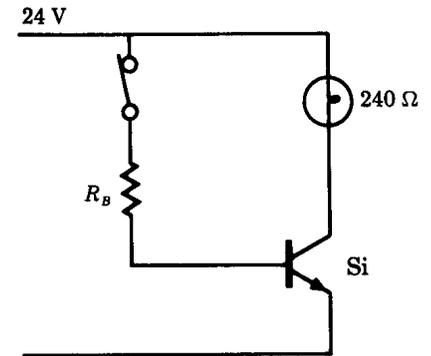


Other Devices

- SCR: Half wave current controlled triggered switch
 - 4 layers, normally off, triggered on
 - Reverse bias turns it off
- Triac: Full wave triggered switch
 - Effectively two SCR's in parallel (reverse polarity)
- Diac (and neon bulb): 2-terminal Avalanche device
 - Normally high impedance,
 - Low impedance triggered by threshold voltage
 - Reverse bias turns it off
- UJT: 3-terminal voltage controlled avalanche/recovery

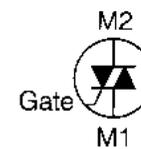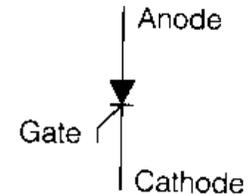

Triac

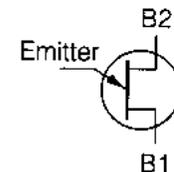

UJT



Neon tube

Amplifier Summary

Class	Duty Cycle	Efficiency	Application
A	100%	Low	Linear small signal
B (AB)	50%	~ 50%	Linear power
C	< 50%	~ 80%	RF Power
D	High speed switching	~ 85%	DC power supplies and Low frequency linear power

Section 6 Schedule:

Session 6a	01/15	Field Effect Transistors	Kybett pp 70 – 77, pp 201-209
Session 6b	01/20	Transistors as a switch	Kybett pp 78 –107
Session 6c	01/22	SCR's, Triacs and UJT's	Notes
Session 6d	01/27	Class A, B, and C Amplifiers	Notes
Session 6e (no class Monday)	01/29	Q & A	
Session 6e (Lab - 02/08, Sat.)	02/05	Operational Amplifiers	Kybett pp 209-215
Session 6f (Quiz 6 due 02/23)	02/10	Review for Quiz 6 (no class 2/17 or 2/19)	
Session 6g	02/24	Discuss Quiz 6	
Session 6h	02/26	Review for MT3	
MT3	03/01	MT3 Exam	
Session 6i	03/10	Discuss MT3	