

Digital Electronics 1

Part 7a of
“Electronics and Telecommunications”
A Fairfield University E-Course
Powered by LearnLinc

Module: Digital Electronics

(in two parts)

- Text: “[Digital Logic Tutorial](http://www.play-hookey.com/digital/),” [Ken Bigelow](#),
<http://www.play-hookey.com/digital/>
- References:
 - “[Electronics Tutorial](#)”, part 10 (Thanks to Alex Pounds)
http://doctord.dyndns.org:8000/courses/Topics/Electronics/Alex_Pounds/Index.htm
- Contents:
 - 7 – Digital Electronics 1
 - 5 on-line sessions plus one lab and a quiz
 - 8 – Digital Electronics 2
 - 5 on-line sessions plus one lab and a quiz
- Mastery Test part 4 follows this Module

Section 7: Digital Electronics 1

- Logic gates and Boolean algebra
- Truth Tables
- Binary numbers
- Memory
- Flip-Flops

Section 8: Digital Electronics 2

- Clocks and Counters
- Shift Registers
- Decoders
- Multiplexers & Demultiplexers
- Sampling

- **MT4**

Section 7 Schedule

Session 7a	03/05	Introduction: Binary, Logic Gates and Boolean	Alex Pounds: Part 10 “Ken B”: Home, Basic Gates, & Boolean Algebra
Session 7b	03/10	Logic Gates and Truth Tables	Alex Pounds: Part 10 “Ken B”: Derived Gates, Xor
Session 7c	03/12	Binary numbers	“Keb B”: Binary Addition
Session 7d	03/17	Memory: Registers, RAM & ROM	“Ken B”: RS Nand Latch, Clocked RS Latch, D Latch
Session 7e (Lab - 03/22, Sat.)	03/19	Pulses, Clocks and Flip-Flops	“Ken B”: RS Flip-Flop, JK Flip-Flop, D Flip-Flop, Flip-Flop Symbols
Session 7f (Quiz 7 due 03/30)	03/24	Review for Quiz 7	
Session 7g	03/31	Quiz Results	

Introduction to Logic

- In this Digital world a value is either:
 - 1, “True”, “On”, “High” (5 volts in electronics)
 - 0, “False”, “Off”, “Low” (0 volts in electronics)
- The equivalent Mathematics is Boolean Algebra
George Boole (1854)
- A “Variable” (A, B, X, ...) is either true or false
- An “Expression” ($X = A + B$) is evaluated using the rules of Boolean Algebra
(see Boolean at play-hookey.com)

Logic Continued


- We represent a logical operation using “Gate” symbols
- Each “Gate” corresponds to an electrical circuit that performs the Boolean equivalent operation on its input values.

Truth Tables

- A “Truth Table” enumerates all of the possible input conditions to a Gate and shows the resulting output values.


Basic Logic Gates

- AND

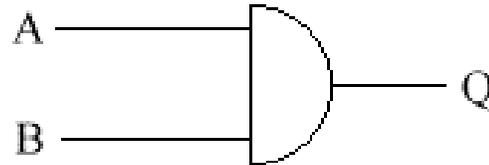

- Q is True when both A AND B are True
- $Q = A * B$

- OR

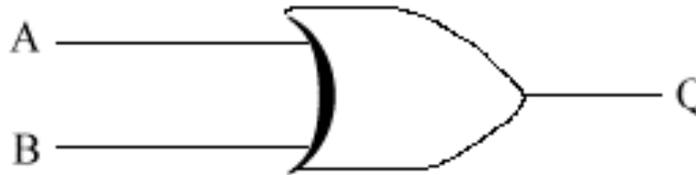

- Q is True when either A or B is True
- $Q = A + B$

- NOT



- Q is true when A is false and false when A is true
- $Q = A$ (or A')

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

A	Q
0	1
1	0

Simulation

- We'll go to www.play-hookey.com/digital to see these gates in action

Section 7 Schedule

Session 7a	03/05	Introduction: Binary, Logic Gates and Boolean	“Hookey”: Home, Basic Gates, & Boolean Algebra Alex Pounds: Part 10
Session 7b	03/10	Logic Gates and Truth Tables	“Hookey”:
Session 7c	03/12	Binary numbers	“Hookey”:
Session 7d	03/17	Memory: Registers, RAM & ROM	“Hookey”:
Session 7e (Lab - 03/22, Sat.)	03/19	Pulses, Clocks and Flip-Flops	“Hookey”:
Session 7f (Quiz 7 due 03/30)	03/24	Review for Quiz 7	
Session 7g	03/31	Quiz Results	