

Derived Logic Gates and Truth Tables

Part 7b of
“Electronics and Telecommunications”
A Fairfield University E-Course
Powered by LearnLinc

Module: Digital Electronics

(in two parts)

- Text: “[Digital Logic Tutorial](http://www.play-hookey.com/digital/),” [Ken Bigelow](#),
<http://www.play-hookey.com/digital/>
- References:
 - “[Electronics Tutorial](#)”, part 10 (Thanks to Alex Pounds)
http://doctord.dyndns.org:8000/courses/Topics/Electronics/Alex_Pounds/Index.htm
- Contents:
 - 7 – Digital Electronics 1
 - 5 on-line sessions plus one lab and a quiz
 - 8 – Digital Electronics 2
 - 5 on-line sessions plus one lab and a quiz
- Mastery Test part 4 follows this Module

Section 7: Digital Electronics 1

- Logic gates and Boolean algebra
- Truth Tables
- Binary numbers
- Memory
- Flip-Flops

Section 8: Digital Electronics 2

- Clocks and Counters
- Shift Registers
- Decoders
- Multiplexers & Demultiplexers
- Sampling

- **MT4**

Section 7 Schedule


Session 7a	03/05	Introduction: Binary, Logic Gates and Boolean	Alex Pounds: Part 10 “Ken B”: Home, Basic Gates, & Boolean Algebra
Session 7b	03/10	Logic Gates and Truth Tables	Alex Pounds: Part 10 “Ken B”: Derived Gates, Xor
Session 7c	03/12	Binary numbers	“Keb B”: Binary Addition
Session 7d	03/17	Memory: Registers, RAM & ROM	“Ken B”: RS Nand Latch, Clocked RS Latch, D Latch
Session 7e (Lab - 03/22, Sat.)	03/19	Pulses, Clocks and Flip-Flops	“Ken B”: RS Flip-Flop, JK Flip-Flop, D Flip-Flop, Flip-Flop Symbols
Session 7f (Quiz 7 due 03/30)	03/24	Review for Quiz 7	
Session 7g	03/31	Quiz Results	

Review

- Binary
 - 1, “True”, “On”, “High” (5 volts in electronics)
 - 0, “False”, “Off”, “Low” (0 volts in electronics)
- Basic Logic Gates
 - AND, OR, NOT
- Truth Tables:
 - Enumerate outputs for all input combinations
- Boolean Algebra
 - Named Variables: True or False
 - Expressions: Equations describing relationships


Basic Logic Gates

- **AND**

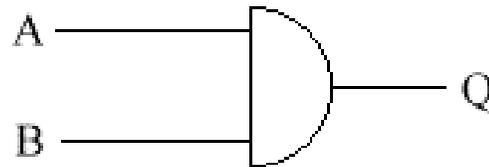

- Q is True when both A AND B are True
- $Q = A * B$

- **OR**

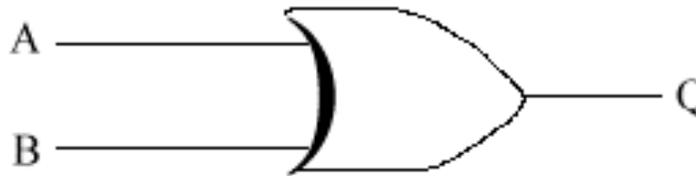

- Q is True when either A or B is True
- $Q = A + B$

- **NOT**



- Q is true when A is false and false when A is true
- $Q = A$ (or A')

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

A	Q
0	1
1	0

Boolean operators

- Complement: $X\bar{c}$ (opposite of X)
 - AND: $X \times Y$
 - OR: $X + Y$
- binary operators, described functionally by truth table.

X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

X	NOT X
0	1
1	0

Theorems

(T1)	$X + 0 = X$	(T1')	$X \cdot 1 = X$	(Identities)
(T2)	$X + 1 = 1$	(T2')	$X \cdot 0 = 0$	(Null elements)
(T3)	$X + X = X$	(T3')	$X \cdot X = X$	(Idempotency)
(T4)	$(X')' = X$			(Involution)
(T5)	$X + X' = 1$	(T5')	$X \cdot X' = 0$	(Complements)

More Theorems

(T6)	$X + Y = Y + X$	(T6')	$X \cdot Y = Y \cdot X$	(Commutativity)
(T7)	$(X + Y) + Z = X + (Y + Z)$	(T7')	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	(Associativity)
(T8)	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$	(T8')	$(X + Y) \cdot (X + Z) = X + Y \cdot Z$	(Distributivity)
(T9)	$X + X \cdot Y = X$	(T9')	$X \cdot (X + Y) = X$	(Covering)
(T10)	$X \cdot Y + X \cdot Y' = X$	(T10')	$(X + Y) \cdot (X + Y') = X$	(Combining)
(T11)	$X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$			(Consensus)
(T11')	$(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$			


Derived Logic Gates

- Derived gates are those made out of simple combinations of the basic gates.
- Common derived functions
 - NAND: inverted AND
 - NOR: inverted OR
 - XOR: the exclusive or A or B but not A and B
- These derived gates are the ones seen most often.

NAND Gate

- Q is False when both A AND B are True and True otherwise
 - $Q = \overline{(A*B)} = (A*B)'$
 - It can have any number of inputs
 - Note that this is an AND followed by a NOT


A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

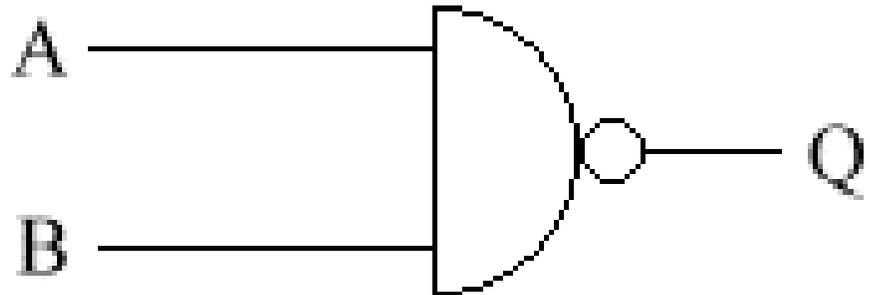

NOR Gate

- Q is False when either A or B is True
 - $Q = \overline{(A+B)} = (A+B)'$
 - It can have any number of inputs
 - Note that this is an OR followed by a NOT

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0



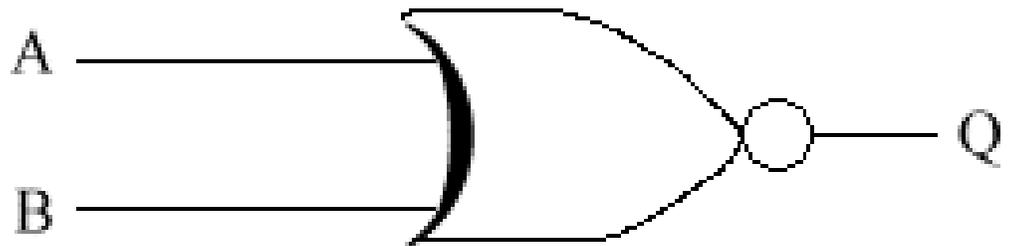


XOR: The Exclusive OR

- Q is True when either A OR B is True, but not when both A AND B are True

$$- Q = \bar{A} * B + A * \bar{B} = A \oplus B$$

A	B	X	Y	Z	Q
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	0

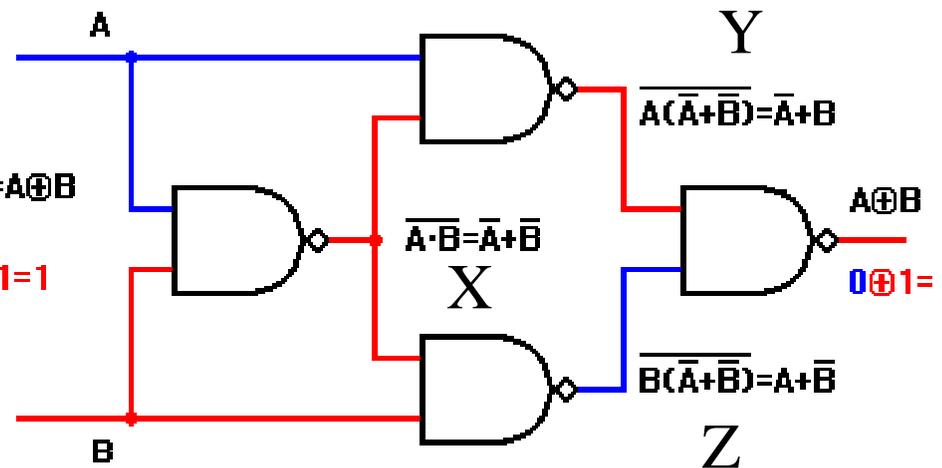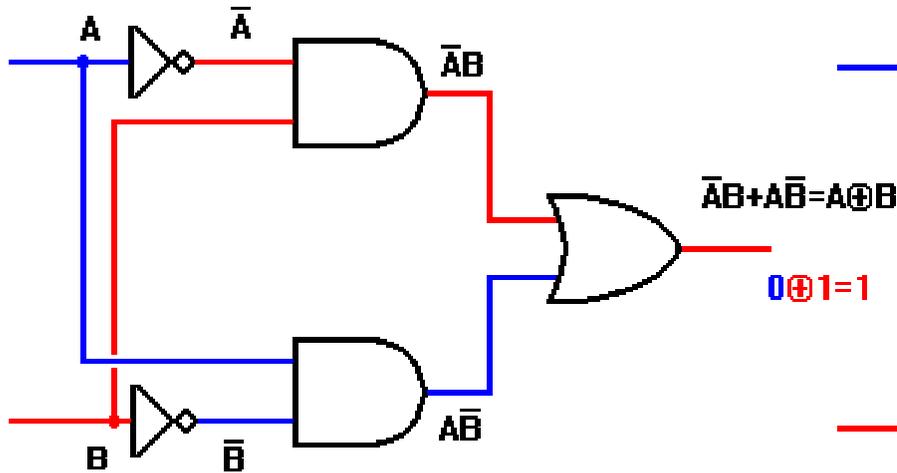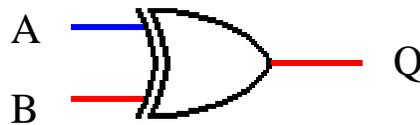

Simulation

- We'll again go to www.play-hookey.com/digital to see these gates in action

Section 7 Schedule

Session 7a	03/05	Introduction: Binary, Logic Gates and Boolean	“Hookey”: Home, Basic Gates, & Boolean Algebra Alex Pounds: Part 10
Session 7b	03/10	Logic Gates and Truth Tables	“Hookey”: Derived Gates, Xor
Session 7c	03/12	Binary numbers	“Hookey”: Binary Addition
Session 7d	03/17	Memory: Registers, RAM & ROM	“Hookey”: RS Nand Latch, Clocked RS Latch, D Latch, Notes
Session 7e (Lab - 03/22, Sat.)	03/19	Pulses, Clocks and Flip-Flops	“Hookey”: RS Flip-Flop, JK Flip-Flop, D Flip-Flop, Flip-Flop Symbols,
Session 7f (Quiz 7 due 03/30)	03/24	Review for Quiz 7	
Session 7g	03/31	Quiz Results	