

Memory: The Latch, Registers, RAM & ROM

Part 7d of
“Electronics and Telecommunications”
A Fairfield University E-Course
Powered by LearnLinc

Module: Digital Electronics

(in two parts)

- Text: “[Digital Logic Tutorial](http://www.play-hookey.com/digital/),” [Ken Bigelow](#),
<http://www.play-hookey.com/digital/>
- References:
 - “[Electronics Tutorial](#)”, part 10 (Thanks to Alex Pounds)
http://doctord.dyndns.org:8000/courses/Topics/Electronics/Alex_Pounds/Index.htm
- Contents:
 - 7 – Digital Electronics 1
 - 5 on-line sessions plus one lab and a quiz
 - 8 – Digital Electronics 2
 - 5 on-line sessions plus one lab and a quiz
- Mastery Test part 4 follows this Module

Section 7: Digital Electronics 1

- Logic gates and Boolean algebra
- Truth Tables
- Binary numbers
- Memory
- Flip-Flops

Section 8: Digital Electronics 2

- Clocks and Counters
- Shift Registers
- Decoders
- Multiplexers & Demultiplexers
- Sampling

- **MT4**

Section 7 Schedule



Session 7a	03/05	Introduction: Binary, Logic Gates and Boolean	Alex Pounds: Part 10 "Ken B": Home, Basic Gates, & Boolean Algebra
Session 7b	03/10	Logic Gates and Truth Tables	Alex Pounds: Part 10 "Ken B": Derived Gates, Xor
Session 7c	03/12	Binary numbers	"Keb B": Binary Addition "Vinay ": Binary Numbers
Session 7d	03/17	Memory: The Latch, Registers, RAM & ROM	"Ken B": RS Nand Latch, Clocked RS Latch, D Latch
Session 7e (Lab - 03/22, Sat.)	03/19	Pulses, Clocks and Flip-Flops	"Ken B": RS Flip-Flop, JK Flip-Flop, D Flip-Flop, Flip-Flop Symbols
Session 7f (Quiz 7 due 03/30)	03/24	Review for Quiz 7	
Session 7g	03/31	Quiz Results	

Review

- Binary: 1, 0; True, False; On, Off; High, Low; 5 volts, 0 volts
- Basic Logic Gates: AND, OR, NOT
- Derived Logic Gates: NAND, NOR, XOR
- Truth Tables: Enumerate outputs for all input combinations
- Boolean Algebra: Named Variables, Expressions, Equations, Rules
- Binary Numbers:
 - Based on powers of 2
 - k bits can count up to $2^k - 1$ (2^k values including zero)
 - 8-bits \Rightarrow 256 values, 16-bits \Rightarrow 65536 values (64k binary)
 - 10-bits \Rightarrow 1024 values (1k binary)
 - 20-bits \Rightarrow 1,048,576 values (1 meg binary)
 - Bits, Nibbles, Bytes, and Words
 - Negative Numbers: Two's complement
 - Binary Adders: half and full



The RS Latch

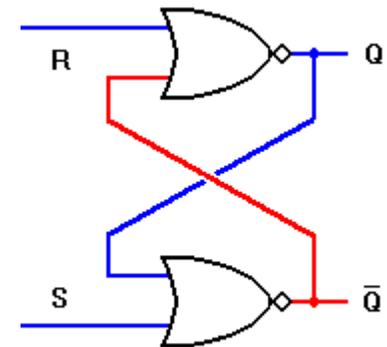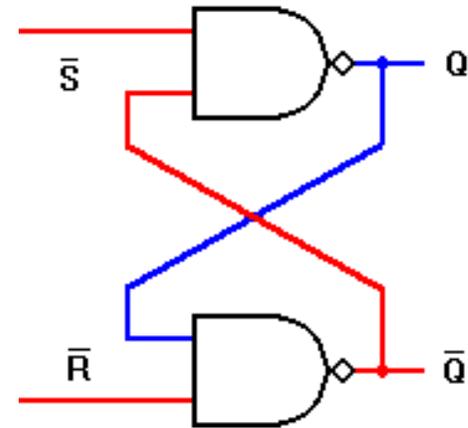- Two NAND (or NOR) gates;
 - One bit of Storage
- Two stable states
 - If on gate is on; the other must be off
- Bringing S' low (or S high) turns the top gate on
 - the “SET” state; $Q = 1, Q' = 0$
- Bringing R' low (or R high) turns the bottom gate on;
 - the “RESET” state; $Q = 0, Q' = 1$



The RS Latch

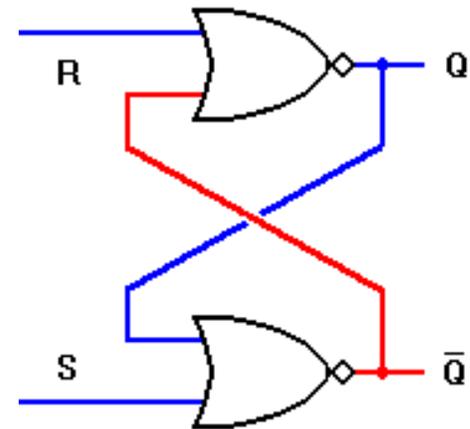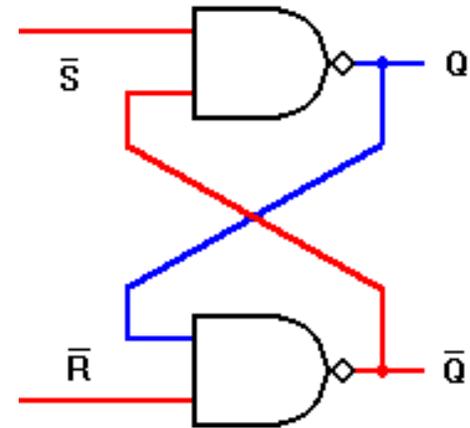- Two NAND (or NOR) gates;
 - One bit of storage
- Two stable states
 - If on gate is on; the other must be off
- Bringing S' low (or S high) turns the top gate on
 - the “SET” state; $Q = 1, Q' = 0$
- Bringing R' low (or R high) turns the bottom gate on;
 - the “RESET” state; $Q = 0, Q' = 1$



Simulation


- We'll again go to www.play-hookey.com/digital to see Latches in action

Parallel Register

- Use k latches to store a k -bit word
- Stores a k -bit binary number
 - 0 to $(2^k - 1)$: an “unsigned integer” or
 - $- [2^{(k-1)} - 1]$ to $[2^{(k-1)} - 1]$: a “signed” integer or
 - A k -bit “Floating Point” number
(not yet covered)

RAM Memory Unit

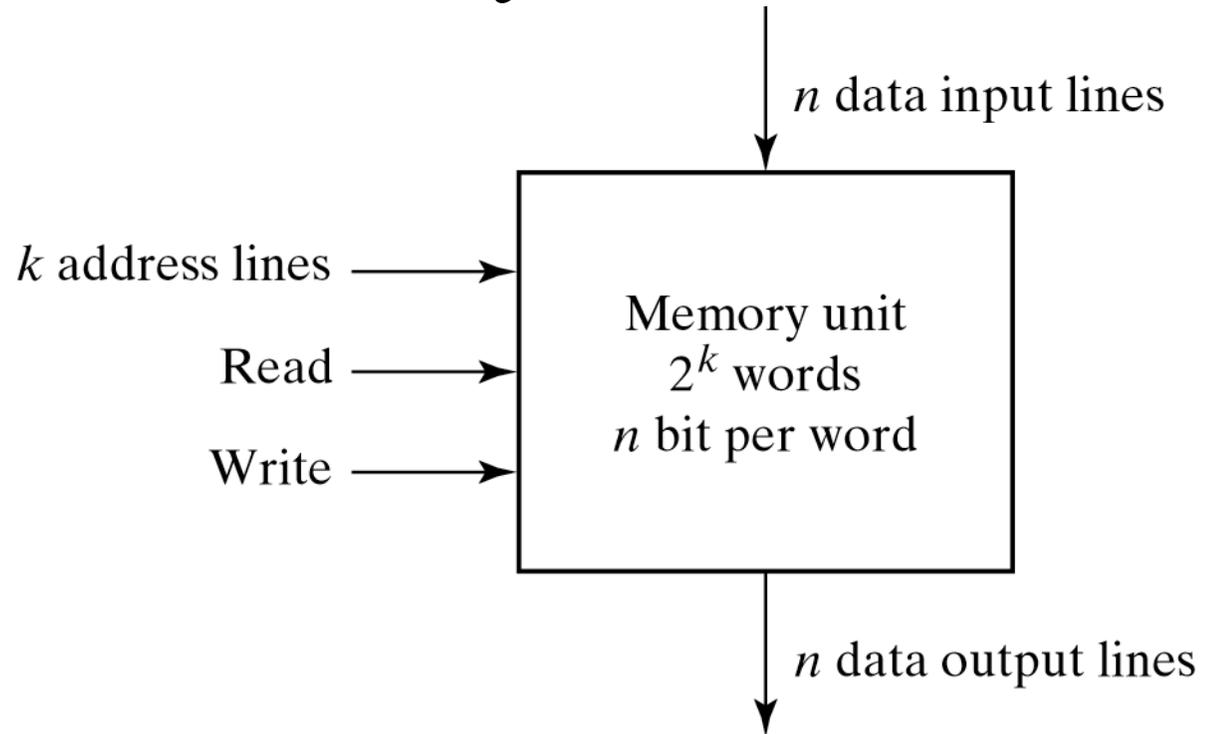- “Address”
Selects a word
- “Write”
Sets or resets bits
- “Read”
“strokes” the selected word into an output register



Read-Only Memory (ROM)

- Same as RAM, but simpler
- Data is established when manufactured and cannot be altered

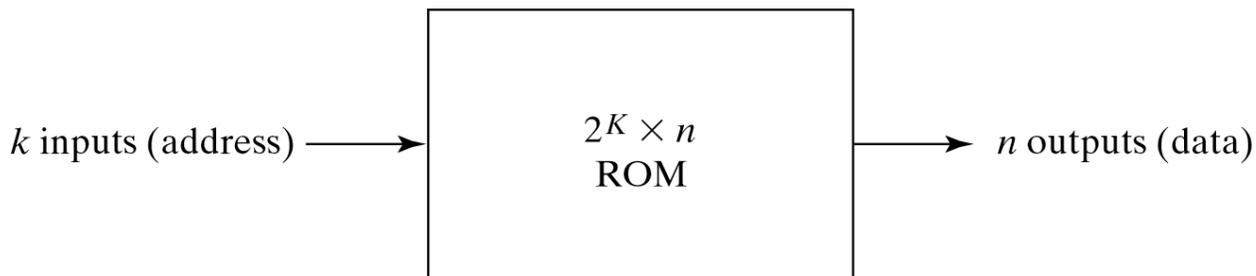


Fig. 7-9 ROM Block Diagram

Other Semiconductor Memories

- PROM: Data “burned” in after manufacture
- EPROM: PROMS that are “erasable”
(usually by exposure to UV light)
(note that x-rays can also change them as in airport security)
- Flash or EEROM: Electrically erasable. Can be fully erased and rewritten in place using higher voltages than used to read data.

Section 7 Schedule

Session 7a	03/05	Introduction: Binary, Logic Gates and Boolean	“Hookey”: Home, Basic Gates, & Boolean Algebra Alex Pounds: Part 10
Session 7b	03/10	Logic Gates and Truth Tables	“Hookey”: Derived Gates, Xor
Session 7c	03/12	Binary numbers	“Hookey”: Binary Addition “Vinay “: Binary Numbers
Session 7d	03/17	Memory: The Latch, Registers, RAM & ROM	“Hookey”: RS Nand Latch, Clocked RS Latch, D Latch, Notes
Session 7e (Lab - 03/22, Sat.)	03/19	Pulses, Clocks and Flip-Flops	“Hookey”: RS Flip-Flop, JK Flip-Flop, D Flip-Flop, Flip-Flop Symbols,
Session 7f (Quiz 7 due 03/30)	03/24	Review for Quiz 7	
Session 7g	03/31	Quiz Results	