

# Review for Quiz 7

Part 7f of  
“Electronics and Telecommunications”  
A Fairfield University E-Course  
Powered by LearnLinc

# Module: Digital Electronics

## (in two parts)

- Text: “[Digital Logic Tutorial](http://www.play-hookey.com/digital/),” [Ken Bigelow](#),  
<http://www.play-hookey.com/digital/>
- References:
  - “[Electronics Tutorial](#)”, part 10 (Thanks to Alex Pounds)  
[http://doctord.dyndns.org:8000/courses/Topics/Electronics/Alex\\_Pounds/Index.htm](http://doctord.dyndns.org:8000/courses/Topics/Electronics/Alex_Pounds/Index.htm)
- Contents:
  - 7 – Digital Electronics 1
    - 5 on-line sessions plus one lab and a quiz
  - 8 – Digital Electronics 2
    - 5 on-line sessions plus one lab and a quiz
- Mastery Test part 4 follows this Module

# Section 7: Digital Electronics 1

- Logic gates and Boolean algebra
- Truth Tables
- Binary numbers
- Memory
- Flip-Flops

# Section 8: Digital Electronics 2


- Clocks and Counters
- Shift Registers
- Decoders
- Multiplexers & Demultiplexers
- Sampling
  
- **MT4**

# Section 7 Schedule

Session 7a	03/05	Introduction: Binary, Logic Gates and Boolean	Alex Pounds: Part 10 “Ken B”: Home, Basic Gates, & Boolean Algebra
Session 7b	03/10	Logic Gates and Truth Tables	Alex Pounds: Part 10 “Ken B”: Derived Gates, Xor
Session 7c	03/12	Binary numbers	“Keb B”: Binary Addition “Vinay “: Binary Numbers
Session 7d	03/17	Memory: The Latch, Registers, RAM & ROM	“Ken B”: RS Nand Latch, Clocked RS Latch, D Latch
Session 7e (Lab - 03/22, Sat.)	03/19	Pulses, Clocks and Flip-Flops	“Ken B”: RS Flip-Flop, JK Flip-Flop, D Flip-Flop, Flip-Flop Symbols
<b>Session 7f (Quiz 7 due 03/30)</b>	<b>03/24</b>	<b>Review for Quiz 7</b>	
Session 7g	03/31	Quiz Results	
 
# Basics

- Binary: 1, 0; True, False; On, Off; High, Low; 5 volts, 0 volts
- Basic Logic Gates:
  - AND:  $Q = A * B * C$   
( Q is only true if all inputs are true )
  - OR:  $Q = A + B + C$   
( Q is only false if all inputs are false )
  - NOT:  $Z = X'$   
( Q is true if A is false, Q is false if A is true )
- Derived Logic Gates:
  - NAND  
( Q is only false if all inputs are true )
  - NOR  
( Q is only true if all inputs are false )
  - XOR  
( Q is true if one of A or B is true but not both )



# Truth Tables

- Truth Tables: Enumerate outputs for all input combinations
  - Example: 5 people are voting for one of two candidates  
Let 0 represent Candidate A and 1 represent candidate B

Voter1	Voter2	Voter3	Winner
0	0	0	A
0	0	1	A
0	1	0	A
0	1	1	B
1	0	0	A
1	0	1	B
1	1	0	B
1	1	1	B

# Boolean Algebra

- Named Variables

---

(T1)	$X + 0 = X$	(T1')	$X \cdot 1 = X$	(Identities)
------	-------------	-------	-----------------	--------------

- Operators

(T2)	$X + 1 = 1$	(T2')	$X \cdot 0 = 0$	(Null elements)
------	-------------	-------	-----------------	-----------------

- Expressions

(T3)	$X + X = X$	(T3')	$X \cdot X = X$	(Idempotency)
------	-------------	-------	-----------------	---------------

(T4)	$(X')' = X$			(Involution)
------	-------------	--	--	--------------

(T5)	$X + X' = 1$	(T5')	$X \cdot X' = 0$	(Complements)
------	--------------	-------	------------------	---------------

---

- Equations

---

(T6)	$X + Y = Y + X$	(T6')	$X \cdot Y = Y \cdot X$	(Commutativity)
------	-----------------	-------	-------------------------	-----------------

- Rules

(T7)	$(X + Y) + Z = X + (Y + Z)$	(T7')	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	(Associativity)
------	-----------------------------	-------	---	-----------------

(T8)	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$	(T8')	$(X + Y) \cdot (X + Z) = X + Y \cdot Z$	(Distributivity)
------	---	-------	---	------------------

(T9)	$X + X \cdot Y = X$	(T9')	$X \cdot (X + Y) = X$	(Covering)
------	---------------------	-------	-----------------------	------------

(T10)	$X \cdot Y + X \cdot Y' = X$	(T10')	$(X + Y) \cdot (X + Y') = X$	(Combining)
-------	------------------------------	--------	------------------------------	-------------

(T11)	$X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$			(Consensus)
-------	---	--	--	-------------

(T11')	$(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$			
--------	---	--	--	--

---

# Binary Numbers:

– Based on powers of 2

$$\begin{array}{cccccccc} 0 & 1 & 1 & 0 & 1 & 1 & 0 & 1 \\ 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1 \end{array} = 64 + 32 + 8 + 4 + 1 = 109$$


– k bits can count up to  $2^k - 1$  ( $2^k$  values including zero)

- 8-bits  $\Rightarrow$  256 values, 16-bits  $\Rightarrow$  65536 values (64k binary)
- 10-bits  $\Rightarrow$  1024 values (1k binary)
- 20-bits  $\Rightarrow$  1,048,576 values (1 meg binary)
- Bits, Nibbles (4), Bytes (8), and Words
- Negative Numbers: Two's complement
- Binary Adders: half and full

$$\begin{array}{r} 01101101 = 109 \\ +00001011 = \underline{11} \\ \hline 01111000 = 120 \end{array}$$
 
# Storage


- The RS Latch (a “bit” of storage)
  - Set = 1:  $Q=1$
  - Reset = 1:  $Q=0$
- Register (n-bits of storage)
  - n latches (or flip-flops)
  - Stores a word (or byte) of data
- RAM (addressable words of memory)
  - Read / write
  - Volatile (data lost if power lost)
- ROMs, PROMs, EPROMs and EEROMS
  - Non-volatile memories


 
# Pulses and Clocks


- Single Pulse

- Signal normally low then high for a short time and goes back to low



- Clock

 
- Signal alternates high-low at a regular rate



Positive going edge
 
# Clocked Logic


- Clock signal “enables Set and Reset pins
- Synchronous Logic
  - Slower than “ripple” logic
    - Gates have input to output “delay”
    - Delays build up as signals propagate through the logic
  - Predictable timing
    - Clocked (synchronous) logic prevents the build up of delays


 
# The JK Flip-Flop

- Edge Triggered  
Generic Flip-Flop

- the triangle symbol
  - triangle: rising edge triggers change
  - Not then triangle: falling edge triggers change



- Truth Table

- J and K determines state change


J	K	Q(t+1)
0	0	Q(t) – No change
0	1	0 – Reset
1	0	1 – Set
1	1	Q'(t) – Complement

# The T Flip-Flop

- State toggles (flips) on each positive going clock edge


Triangle: edge triggered

T	$Q(t+1)$
0	$Q(t)$ – No change
1	$Q'(t)$ - Complement

 
 
# The D Flip-Flop

- Simple triggered storage Flip-Flop
  - Note the half circle
  - It is controlled by clock level, not an edge



D	Q(t+1)
0	0 - Reset
1	1 - Set

# Section 7 Schedule

Session 7a	03/05	Introduction: Binary, Logic Gates and Boolean	“Hookey”: Home, Basic Gates, & Boolean Algebra Alex Pounds: Part 10
Session 7b	03/10	Logic Gates and Truth Tables	“Hookey”: Derived Gates, Xor
Session 7c	03/12	Binary numbers	“Hookey”: Binary Addition “Vinay “: Binary Numbers
Session 7d	03/17	Memory: The Latch, Registers, RAM & ROM	“Hookey”: RS Nand Latch, Clocked RS Latch, D Latch, Notes
Session 7e <b>(Lab - 03/22, Sat.)</b>	03/19	Pulses, Clocks and Flip-Flops	“Hookey”: RS Flip-Flop, JK Flip-Flop, D Flip-Flop, Flip-Flop Symbols,
Session 7f <b>(Quiz 7 due 03/30)</b>	03/24	Review for Quiz 7	
<b>Session 7g</b>	<b>03/31</b>	<b>Quiz Results</b>	