

# Review for Quiz 8

Part 8f of  
“Electronics and Telecommunications”  
A Fairfield University E-Course  
Powered by LearnLinc

# Module: Digital Electronics

## (in two parts)

- Text: “[Digital Logic Tutorial](http://www.play-hookey.com/digital/),” [Ken Bigelow](#),  
<http://www.play-hookey.com/digital/>
- References:
  - “[Electronics Tutorial](#)”, part 10 (Thanks to Alex Pounds)  
[http://doctord.dyndns.org:8000/courses/Topics/Electronics/Alex\\_Pounds/Index.htm](http://doctord.dyndns.org:8000/courses/Topics/Electronics/Alex_Pounds/Index.htm)
- Contents:
  - 7 – Digital Electronics 1
    - 5 on-line sessions plus one lab and a quiz
  - 8 – Digital Electronics 2
    - 5 on-line sessions plus one lab and a quiz
- Mastery Test part 4 follows this Module

# Section 7: Digital Electronics 1

- Logic gates and Boolean algebra
- Truth Tables
- Binary numbers
- Memory
- Flip-Flops

# Section 8: Digital Electronics 2


- Clocks and Counters
- Shift Registers
- Decoders
- Multiplexers & Demultiplexers
- Sampling
  
- **MT4**

# Section 8 Schedule

Session 8a	04/02	Clocks and Counters	“Hookey”: “Counter” pages Alex Pounds: Part 27
Session 8b	04/09	Shift Registers	“Hookey”: “Register” pages
Session 8c	04/14	Decoders	“Hookey”: Decoders and Demultiplexers
Session 8d	04/16	Multiplexers and Demultiplexers	“Hookey”: Multiplexers, Decoders and Demultiplexers
Session 8e	04/21	Sampling (A/D & D/A)	Notes
<b>Session 8f (Quiz 8 due 04/27)</b>	<b>04/23</b>	<b>Review for Quiz 8</b>	
Session 8g	04/28	Quiz Results	
Session 8h (Lab - 05/03, Sat.)	04/30	MT4 Q&A	
MT4 (Sat, Cheshire)	05/10		
MT4 Results	05/12		

 
# Counter Review

- **Clock:** Sets system speed
- **Bit Storage:** Latch or Flip-Flop
- **Register** (n-bits of storage)
- **Counters**
  - Ripple Counter
  - Synchronous Counter
- **Frequency Divider:**  
Counter Divides clock rate by an integer





 
# Shift Register Review

- Cascade chain of Flip-Flops
- Data marches down the line at the beat of the clock
- Parallel or serial load, Parallel or serial read
- Applications:
  - Parallel to serial (serial transfer of data)
  - Serial to parallel (serial reception of data)
  - Feedback shift registers


   
# Decoder Review


- A small number of input bits; treated as a binary number
- A larger set of output bits (up to  $2^n$ )
- The output bit values are “decoded” from the combination of the input bits
- Examples:
  - 1 of N decoding
    - Line Decoder
    - Address Decoder
  - Seven segment display decoder
  - BCD to Decimal line decoder



# Mux and Demux Review
 
## 4.4 Multiplexer

- Multiplexer - A **data selector** that selects one of many inputs to appear on a single output line
- Demultiplexer - A **data distributor** that takes a single input line and routes it to one of several output lines




National Central University

[www.ee.ncu.edu.tw/~ccsu](http://www.ee.ncu.edu.tw/~ccsu)

Introduction to Digital Systems


Chapter 4 P.25

# Analog to Digital Conversion

 

- **Analog Signal:** A continuous electrical signal
- **Aliasing:** Confusion of high and low frequencies if sampling is too slow (filter ensures Nyquist criterion; Nyquist rate  $f_s > 2 f_{\max}$  to avoid aliasing)
- **Sampling:** The process of approximating an analog signal by a sequence of narrow pulses
- **A/D:** Representing the “strength” of a pulse by a binary number (introduces an error due to word length)


# Digital to Analog Conversion

 


- **Digital Signal:** A sequence of binary numbers representing an analog signal (approximate – digital “noise”)
- **PAM:** Pulse Amplitude Modulation - A sequence of pulses with strengths corresponding to the analog signal
- **Reconstruction Filter:** Averaging out the pulse sequence to reproduce the original analog signal (almost identical to the “anti-aliasing filter”)
 
# Analog to Digital Conversion

- Flash (or parallel) A/D
  - Very fast
  - Either low resolution (8-bits) or very expensive
- Successive approximation A/D
  - Determines the MSB first
  - Repeatedly refines the representation
  - Accurate (high resolution) but slow
- Counting A/D: Uses a ramp signal and a high speed counter to determine the time that the ramp exceeds the signal value
- Over-Sampled (Sigma-Delta) A/D
  - Flash encodes a low-resolution value at high speeds
  - Uses a digital filter (anti-alias) to lower the bandwidth
    - Allows reduction of the sampling rate
    - Improves the resolution (number of bits)



# Digital to Analog Conversion

 

- Reverses the A/D sequence
- D/A: generates a PAM pulse sequence where each pulse magnitude corresponds to the value of the corresponding digital number
- Reconstruction filter: Almost identical to the Anti-Aliasing filter used in A/D. Smooths out the pulse sequence to reproduce the original signal.

# Applications

- North American Telephony (64 kbits/sec)
  - Sampling rate = 8 kHz (3 dB: 3.3 kHz ,  $f_{\max}$ : 3.8 kHz)
  - $\mu$ 255 (logarithmic), 8-bit words (256 levels)
- CD Audio
  - Sampling rate = 44.1 kHz per channel (3 dB: 20 kHz,  $f_{\max}$ : 21 kHz)  
(note: DAT = 48 kHz - Prof Audio = 96 kHz, 24 bit)
  - Linear 16-bit words
- PC sound card:
  - Sampling rate = 8, 16, 11.025, 22.05, 44.1 kHz
  - 8 or 16 bit word size

# Section 8 Schedule

Session 8a	04/02	Clocks and Counters	“Hookey”: “Counter” pages Alex Pounds: Part 27
Session 8b	04/09	Shift Registers	“Hookey”: “Register” pages
Session 8c	04/14	Decoders	“Hookey”: Decoders and Demultiplexers
Session 8d	04/16	Multiplexers and Demultiplexers	“Hookey”: Multiplexers, Decoders and Demultiplexers
Session 8e	04/21	Sampling (A/D & D/A)	Notes
Session 8f <b>(Quiz 8 due 04/27)</b>	04/23	Review for Quiz 8	
<b>Session 8g</b>	<b>04/28</b>	<b>Quiz Results</b>	
Session 8h (Lab - 05/03, Sat.)	04/30	MT4 Q&A	
MT4 (Sat, Cheshire)	05/10		
MT4 Results	05/12		