

Digital Design

Lecture 14

ROMs and RAMs

Mano, 7.6-7.8

PLD Configurations

 
 
 


Fig. 7-13 Basic Configuration of Three PLDs

An Example PLA

- Buffers provide true and complement of inputs
- XORs provide programmable complementors on outputs
- Similar to PROM
 - Partial variable decoding
 - Only some minterms

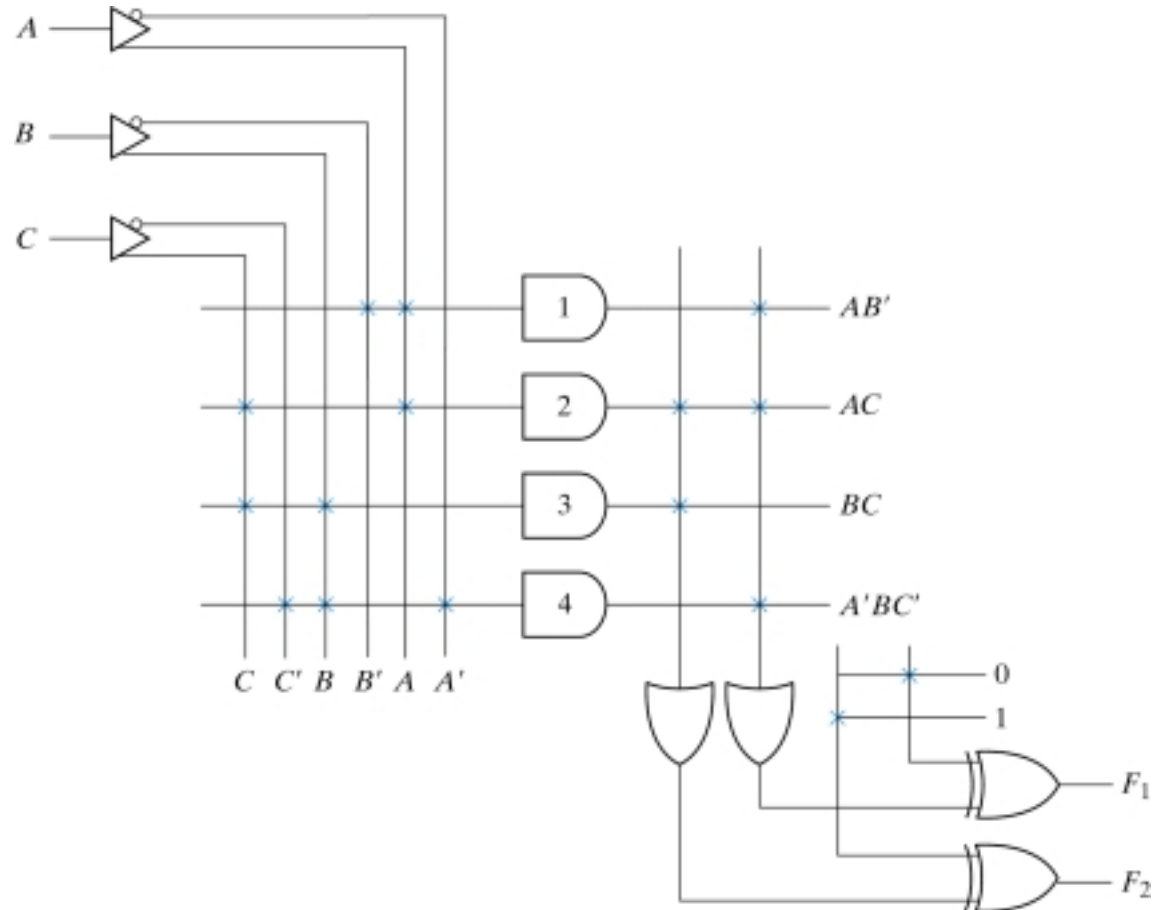


Fig. 7-14 PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

PLA Programming Table

		Inputs			Outputs	
Product Term		A	B	C	(T) F ₁	(C) F ₂
AB'	1	1	0	-	1	-
AC	2	1	-	1	1	1
BC	3	-	1	1	-	1
A'BC'	4	0	1	0	1	-

Table 7-5

Solution to Example 7-2

Implement

$$F_1(A,B,C) = \Sigma(0,1,2,4)$$

$$F_2(A,B,C) = \Sigma(0,5,6,7)$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	1	0	1
	1	1	0	0	0
		<i>C</i>			

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	0	0	0
	1	0	1	1	1
		<i>C</i>			

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C)'$$

PLA programming table

	Outputs					
	Product term	Inputs			(C)	(T)
		<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i> ₁	<i>F</i> ₂
<i>AB</i>	1	1	1	-	1	1
<i>AC</i>	2	1	-	1	1	1
<i>BC</i>	3	-	1	1	1	-
<i>A'B'C'</i>	4	0	0	0	-	1

Fig. 7-15 Solution to Example 7-2

Programmable Array Logic

- Fixed OR array
- Programmable AND array

 


Fig. 7-16 PAL with Four Inputs, Four Outputs, and Three-Wide AND-OR Structure

PAL Fuse Map

PAL Programming Table

Product Term	AND Inputs					Outputs
	A	B	C	D	E	
1	1	1	0	-	-	$w = ABC' + A'B'CD'$
2	0	0	1	0	-	
3	-	-	-	-	-	$x = A + BCD$
4	1	-	-	-	-	
5	-	1	1	1	-	$y = A'B + CD + B'D$
6	-	-	-	-	-	
7	0	1	-	-	-	$z = w + A'C'D' + A'B'CD$
8	-	-	1	1	-	
9	-	0	-	0	-	
10	-	-	-	-	1	
11	1	-	0	0	-	
12	0	0	0	1	-	

Table 7-6

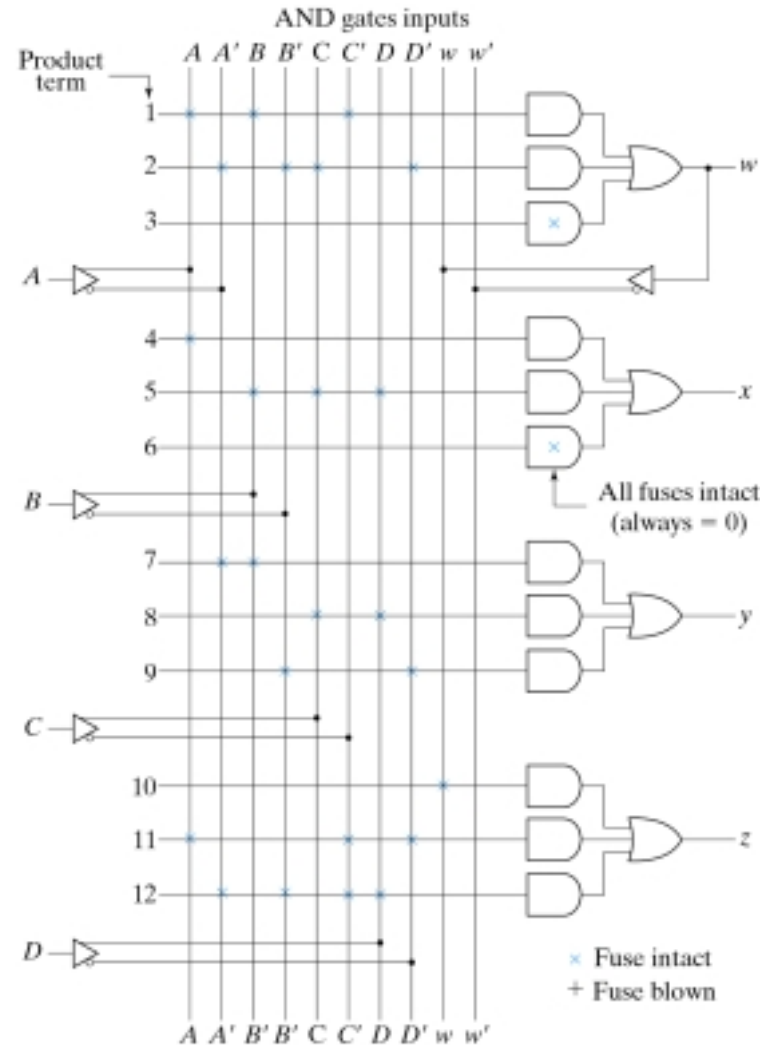


Fig. 7-17 Fuse Map for PAL as Specified in Table 7-6

Sequential PLDs

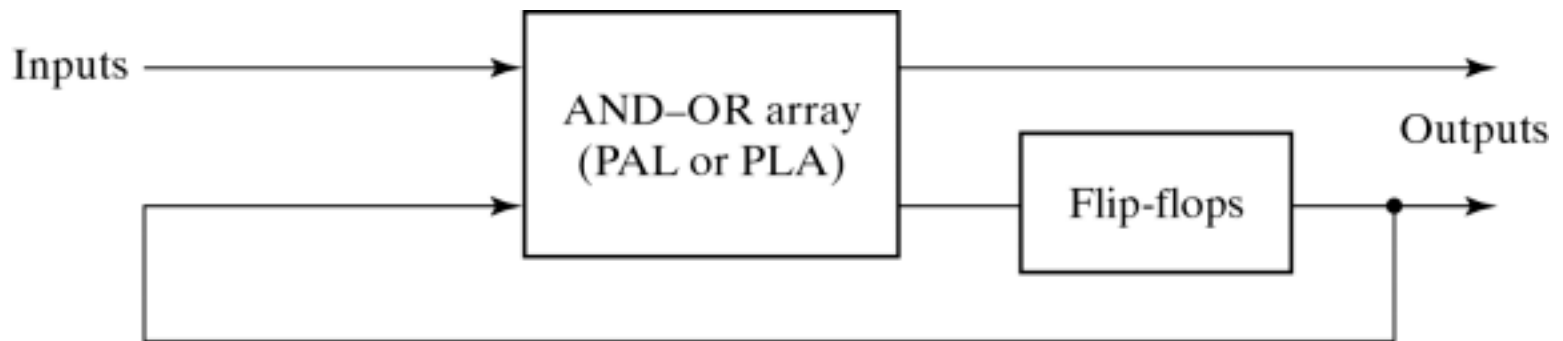


Fig. 7-18 Sequential Programmable Logic Device

Sequential Programmable Devices

- Sequential (simple) programmable Logic device (SPLD)
 - Field-programmable logic sequence (FPLS, defunct – too hard to use)
 - Registered PAL / macrocell structure
- Complex programmable logic device (CPLD)
 - Collection of SPLDs on a chip
- Field programmable gate array (FPLA)
 - Logic blocks (look-up tables, multiplexers, gates, flip-flops)
 - Programmable input/output blocks
 - Programmable interconnections
- Microprocessor (using PROM)

Macrocell Logic

 


Fig. 7-19 Basic Macrocell Logic

CPLD

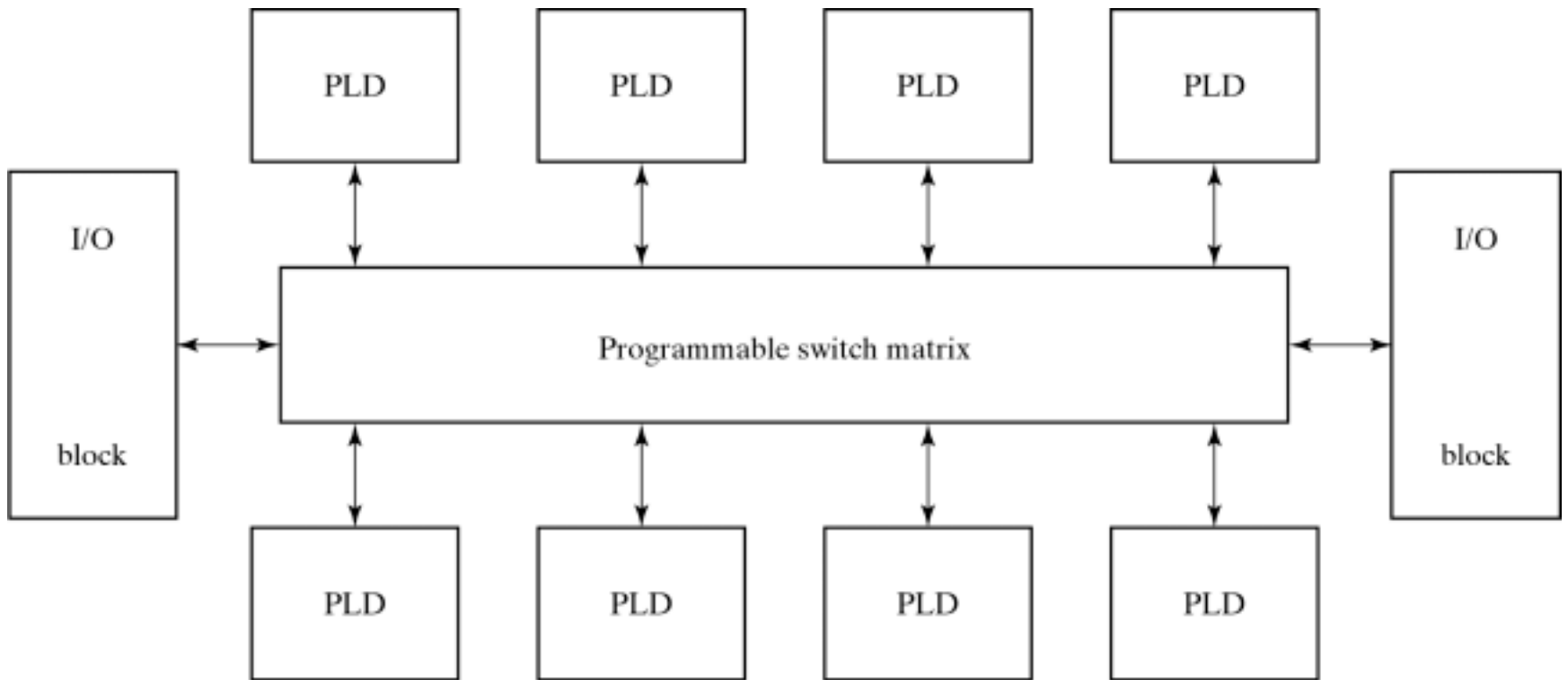


Fig. 7-20 General CPLD Configuration