


19.1 Introduction (1)

What is a port?

It is a pair of terminals through which a **current** may enter or leave a network.


3

19.1 Introduction (2)

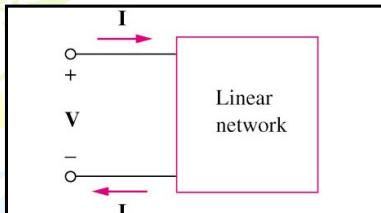

(a)

One port or two terminal circuit

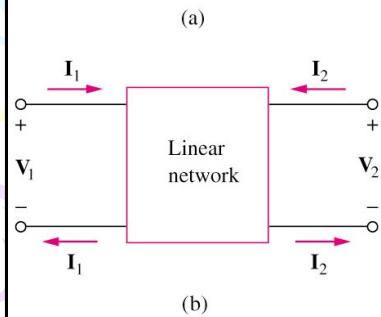

(b)


Two port or four terminal circuit

It is an electrical network with two separate ports for input and output.

No independent sources.

4

19.2 Impedance parameters (1)

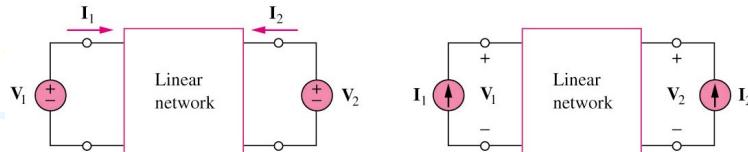


Assume no independent source in the network

$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned} \rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

where the **z** terms are called the impedance parameters, or simply **z** parameters, and have units of ohms.

5

19.2 Impedance parameters (2)

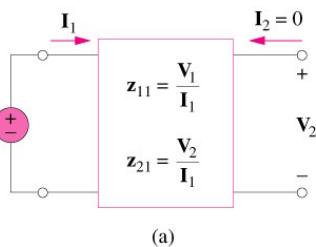


(a)

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

z_{11} = Open-circuit input impedance

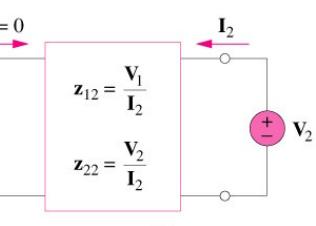z_{21} = Open-circuit transfer impedance from port 1 to port 2



(b)


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

z_{12} = Open-circuit transfer impedance from port 2 to port 1

z_{22} = Open-circuit output impedance


6

19.2 Impedance parameters (2a)

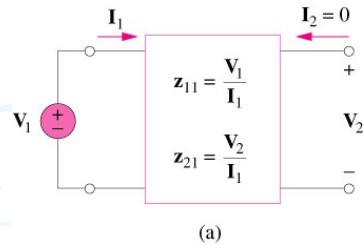

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

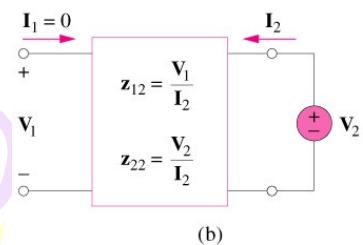

When $z_{11} = z_{22}$, the two-port network is said to be **symmetrical**.


When the two-port network is **linear** and has **no dependent sources**, the transfer impedances are equal ($z_{12} = z_{21}$), and the two-port is said to be **reciprocal**.

7

19.2 Impedance parameters (3)

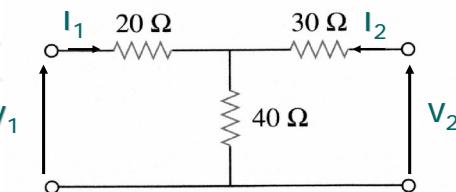Example 1

Determine the Z-parameters of the following circuit.



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{and} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{and} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$


Answer: $z = \begin{bmatrix} 60 & 40 \\ 40 & 70 \end{bmatrix} \Omega$

\downarrow

$$Z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \Omega$$

8

19.3 Admittance parameters (1)

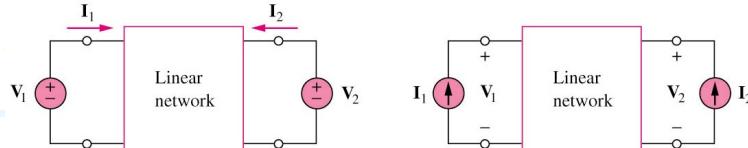


Assume no independent source in the network

$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned} \rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where the **y** terms are called the admittance parameters, or simply **y** parameters, and they have units of Siemens.

9

19.3 Admittance parameters (2)

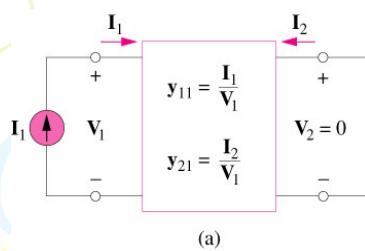


(a)

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

y_{11} = Short-circuit input admittance

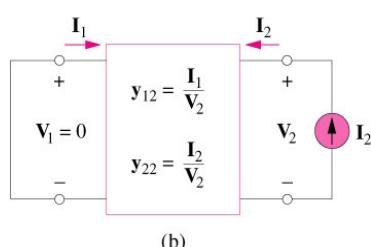y_{21} = Short-circuit transfer admittance from port 1 to port 2



(b)

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

y_{12} = Short-circuit transfer admittance from port 2 to port 1


y_{22} = Short-circuit output admittance

10

19.3 Admittance parameters (3)

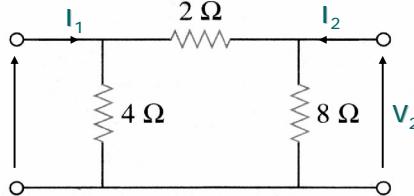Example 2

Determine the y-parameters of the following circuit.



$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad \text{and} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad \text{and} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

Answer: $y = \begin{bmatrix} 0.75 & -0.5 \\ -0.5 & 0.625 \end{bmatrix} S$


$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} S$$

11

19.3 Admittance parameters (4)

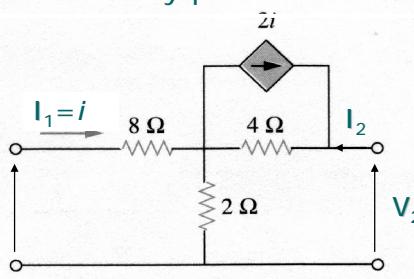Example 3

Determine the y-parameters of the following circuit.



$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned}$$

Apply KVL


$$\begin{aligned} V_1 &= 8I_1 + 2(I_1 + I_2) \\ V_2 &= 4(2i + I_2) + 2(I_1 + I_2) \end{aligned}$$

Answer: $y = \begin{bmatrix} 0.15 & -0.05 \\ -0.25 & 0.25 \end{bmatrix} S$

$$\begin{aligned} I_1 &= 0.15V_1 - 0.05V_2 \\ I_2 &= -0.25V_1 + 0.25V_2 \end{aligned}$$

12

19.4 Hybrid parameters (1)

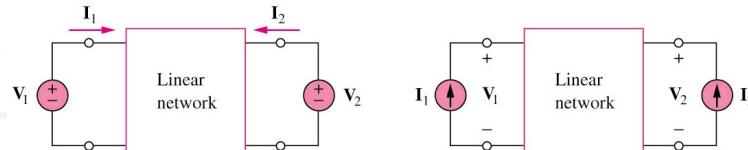


Assume no independent source in the network

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned} \quad \rightarrow \quad \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where the **h** terms are called the impedance parameters, or simply **h** parameters, and each parameter has different units, refer above.

13

19.4 Hybrid parameters (2)

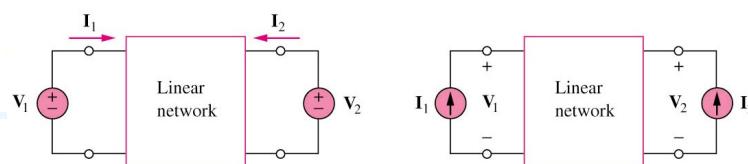

Assume no independent source in the network

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

h_{11} = short-circuit input impedance (Ω)

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

H_2 = short-circuit forward current gain

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

H_{12} = open-circuit reverse voltage-gain

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$


H_{22} = open-circuit output admittance (S)

14

19.4 Hybrid parameters (3)

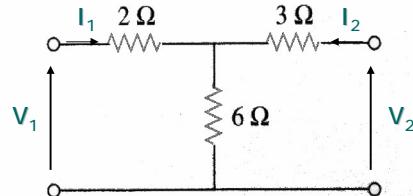Example 4

Determine the h-parameters of the following circuit.



$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{and} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$


$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

Answer: $h = \begin{bmatrix} 4\Omega & -\frac{2}{3} \\ \frac{2}{3} & \frac{1}{9}\text{S} \end{bmatrix}$

$$h = \begin{bmatrix} h_{11}\Omega & h_{12} \\ h_{21} & h_{22}\text{S} \end{bmatrix}$$

15

19.5 Transmission parameters (1)

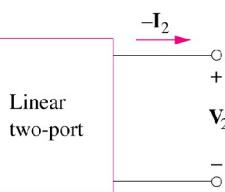

Assume no independent source in the network

$$V_1 = AV_2 - BI_2$$


$$I_1 = CV_2 - DI_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = [T] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

where the T terms are called the transmission parameters, or simply T or ABCD parameters, and each parameter has different units.

16

19.5 Transmission parameters (2)

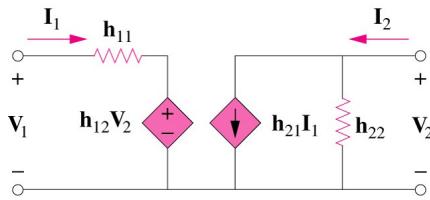

$$A = \left| \frac{V_1}{V_2} \right|_{I_2=0}$$

A=open-circuit voltage ratio

$$C = \left| \frac{I_1}{V_2} \right|_{I_2=0}$$

C=open-circuit transfer admittance (S)

$$B = -\left| \frac{V_1}{I_2} \right|_{V_2=0}$$

$$D = -\left| \frac{I_1}{I_2} \right|_{V_2=0}$$

B=negative short-circuit transfer impedance (Ω)


D=negative short-circuit current ratio

17

19.5 Transmission parameters (3)

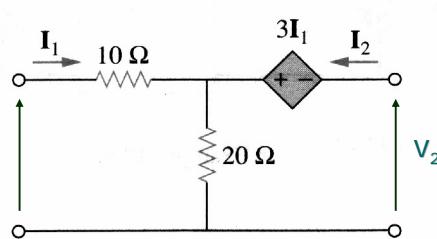Example 5

Determine the T-parameters of the following circuit.



$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

Apply KVL

$$\begin{aligned} V_1 &= 10I_1 + 20(I_1 + I_2) \\ V_2 &= -3I_1 + 20(I_1 + I_2) \end{aligned}$$

Answer:

$$T = \begin{bmatrix} 1.765 & 15.294\Omega \\ 0.059S & 1.176 \end{bmatrix}$$

$$\begin{aligned} V_1 &= \frac{30}{17}V_2 - \frac{260}{17}I_2 \\ I_1 &= \frac{1}{17}V_2 - \frac{20}{17}I_2 \end{aligned}$$

18


19.5 Transmission parameters (4)

Example 6

The ABCD parameters of the two-port network below are

$$T = \begin{bmatrix} 4 & 20 \Omega \\ 0.1S & 2 \end{bmatrix}$$

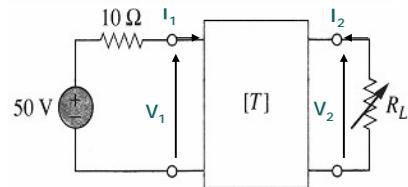The output port is connected to a variable load for maximum power transfer. Find R_L and the maximum power transferred.



Answer: $V_{TH} = 10V$; $R_L = 8\Omega$; $P_m = 3.125W$.

19

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.