

MICROELECTRONIC CIRCUIT DESIGN

Third Edition

Richard C. Jaeger and Travis N. Blalock

Answers to Selected Problems – Updated 1/25/08

Chapter 1

- 1.3 1.52 years, 5.06 years
- 1.5 1.95 years, 6.46 years
- 1.8 113 MW, 511 kA
- 1.10 2.50 mV, 5.12 V, 5.885 V
- 1.12 19.53 mV/bit, 10001110₂
- 1.16 0.002 A, 0.002 cos (1000t) A
- 1.19 $v_{DS} = [5 + 2 \sin (2500t) + 4 \sin (1000t)]$ V
- 1.21 15.7 V, 2.31 V, 70.0 μ A, 210 μ A
- 1.23 120 μ A, 125 μ A, 10.3 V
- 1.25 39.6 Ω , 0.0253 v_s
- 1.27 56 k Ω , 1.33 x 10⁻³ v_s
- 1.29 1.00 M Ω , 2.50 x 10⁸ i_s
- 1.33 5/-45°, 100/-12°
- 1.35 -90.1 sin 750 π t mV, 11.0 sin 750 π t μ A
- 1.37 1 + R₂/R₁
- 1.39 -1.875 V, -2.500 V
- 1.41 Band-pass amplifier
- 1.43 50.0 sin (2000 π t) + 30.0 cos (8000 π t) V
- 1.45 0 V
- 1.47 [2970 Ω , 3030 Ω], [2850 Ω , 3150 Ω], [2700 Ω , 3300 Ω]
- 1.52 6200 Ω , 800 ppm/ $^{\circ}$ C
- 1.58 3.29, 0.995, -6.16; 3.295, 0.9952, -6.155

Chapter 2

- 2.4 For Ge: $35.9/\text{cm}^3$, $2.27 \times 10^{13}/\text{cm}^3$, $8.04 \times 10^{15}/\text{cm}^3$
- 2.7 $-1.75 \times 10^6 \text{ cm/s}$, $+6.25 \times 10^5 \text{ cm/s}$, $2.80 \times 10^4 \text{ A/cm}^2$, $1.00 \times 10^{-10} \text{ A/cm}^2$
- 2.8 305.2 K
- 2.10 4 MA/cm²
- 2.13 $1.60 \times 10^7 \text{ A/cm}^2$, 4.00 A
- 2.15 316.6 K
- 2.19 Donor, acceptor
- 2.20 200 V/cm
- 2.22 5×10^3 atoms
- 2.24 $4 \times 10^{16}/\text{cm}^3$, $2.50 \times 10^5/\text{cm}^3$
- 2.28 $6 \times 10^{18}/\text{cm}^3$, $16.7/\text{cm}^3$, $5 \times 10^9/\text{cm}^3$, $8.80 \times 10^{-10}/\text{cm}^3$
- 2.30 $3 \times 10^{17}/\text{cm}^3$, $333/\text{cm}^3$
- 2.32 $100/\text{cm}^3$, $10^{18}/\text{cm}^3$, $375 \text{ cm}^2/\text{s}$, $100 \text{ cm}^2/\text{s}$, p-type, $62.4 \text{ m}\Omega\text{-cm}$
- 2.34 $10^{16}/\text{cm}^3$, $10^4/\text{cm}^3$, $800 \text{ cm}^2/\text{s}$, $1230 \text{ cm}^2/\text{s}$, n-type, $0.781 \text{ }\Omega\text{-cm}$
- 2.38 $3.06 \times 10^{18}/\text{cm}^3$
- 2.40 Yes—add equal amounts of donor and acceptor impurities. Then $n = n_i = p$, but the mobilities are reduced. See Prob. 2.37.
- 2.42 $2.00/\Omega\text{-cm}$, $3.1 \times 10^{19}/\text{cm}^3$,
- 2.44 75K: 6.64 mV, 150K: 12.9 mV, 300K: 25.8 mV, 400K: 34.5 mV
- 2.46 $-1.20 \times 10^5 \exp(-5000 \text{ x/cm}) \text{ A/cm}^2$; 12.0 mA
- 2.48 The width in the figure should be 2 μm : For $x = 0$, -535 A/cm^2
- 2.50 1.108 μm

Chapter 3

- 3.1 0.0373 μm , 0.0339 μm , $3.39 \times 10^{-3} \mu\text{m}$, 0.979 V, $5.24 \times 10^5 \text{ V/cm}$
- 3.3 $10^{18}/\text{cm}^3$, $10^2/\text{cm}^3$, $10^{18}/\text{cm}^3$, $10^2/\text{cm}^3$, 0.921 V, 0.0488 μm
- 3.6 2.55 V, 1.05 μm
- 3.10 6400 A/cm²
- 3.13 $1.00 \times 10^{21}/\text{cm}^4$
- 3.17 290 K
- 3.20 312K
- 3.21 1.39, 3.17 pA
- 3.22 0.837 V; 0.768 V; 0 A; 9.43×10^{-19} A, -1.00×10^{-18} A
- 3.25 1.34 V; 1.38 V
- 3.28 0.518 V; 0.633 V
- 3.31 0.757 V; 0.721 V
- 3.34 -1.96 mV/K
- 3.37 0.633 V, 0.949 μm , 3.89 μm , 12.0 μm
- 3.39 374 V
- 3.41 4 V, 0 Ω
- 3.43 9.80 nF/cm²; 188 pF
- 3.45 400 fF, 10 fC; 100 pF, 0.5 pC
- 3.49 9.97 MHz; 15.7 MHz
- 3.51 0.495 V, 0.668 V
- 3.53 0.708 V, 0.718 V
- 3.56 (a) Load line: (450 μA , 0.500 V); SPICE: (443 μA , 0.575 V)
(b) Load line: (-667 μA , -4 V);
(c) Load line: (0 μA , -3 V);
- 3.59 (0.600 mA, -4 V) , (0.950 mA, 0.5 V) , (-2.00 mA, -4 V)
- 3.65 Load line: (50 μA , 0.5 V); Mathematical model: (49.9 μA , 0.501 V); Ideal diode model: (100 μA , 0 V); CVD model: (40.0 μA , 0.6 V)
- 3.69 (a) 0.625 mA, 3 V; 0.625 mA, -5 V; 0 A, -5 V; 0 A, 7 V
- 3.71 (a) (409 μA , 0 V), (270 μA , 0 V); (c) (0 A -3.92 V), (230 μA , 0 V)
- 3.73 (a) (0.990 mA, 0 V) (0 mA, -1.73 V) (1.09 mA, 0)
(d) (0 A, -0.452 V) (0 A, -0.948 V) (1.16 mA, 0.600 V)
- 3.76 (1.50 mA, 0 V) (0 A, -5.00 V) (1.00 mA, 0)
- 3.78 (I_z , V_z) = (792 μA , 4.00 V)
- 3.81 10.8 mW
- 3.83 2.25 W, 4.50 W
- 3.88 17.6 V
- 3.91 -7.91 V; 1.05 F; 17.8 V; 3530 A; 841 A ($\Delta T = 0.628$ ms)

- 3.94** -7.91V, 0.158 F, 17.8 V, 3540 A, 839 A
3.97 6.06 F; 8.6 V; 3.04 V; 1920 A; 9280 A
3.100 -20.2 V; 1.35 F; 42.4 V; 10800 A; 1650 A
3.103 3.03 F, 8.6 V, 3.04 V, 962 A, 4910 A
3.107 278 μ F; 3000 V; 2120 V; 44.4 A; 314 A
3.115 5 mA, 4.4 mA, 3.6 mA, 5.59 ns
3.119 (0.969 A, 0.777 V); 0.753 W; 1 A, 0.864 V
3.121 1.11 μ m, 0.875 μ m; far infrared, near infrared

Chapter 4

- 4.3 $10.5 \times 10^{-9} \text{ F/cm}^2$
- 4.4 $34.5 \mu\text{A/V}^2, 86.3 \mu\text{A/V}^2, 173 \mu\text{A/V}^2, 345 \mu\text{A/V}^2$
- 4.9 (a) 4.00 mA/V^2 (b) $4.00 \text{ mA/V}^2, 8.00 \text{ mA/V}^2$
- 4.11 $840 \mu\text{A}; -880 \mu\text{A}$
- 4.15 $23.0 \Omega; 35.7 \Omega$
- 4.18 $125 \mu\text{A/V}^2; 1.5 \text{ V};$ enhancement mode; 1.25/1
- 4.20 $0 \text{ A}, 0 \text{ A}, 1.88 \text{ mA}, 7.50 \text{ mA}, 3.75 \text{ mA/V}^2$
- 4.22 (a) $460 \mu\text{A}$, triode region; 1.56 mA , saturation region; 0 A , cutoff
- 4.23 saturation; cutoff; saturation; triode; triode; saturation
- 4.27 $6.50 \text{ mS}, 13.0 \text{ mS}$
- 4.30 $2.48 \text{ mA}; 2.25 \text{ mA}$
- 4.33 $9.03 \text{ mA}, 18.1 \text{ mA}, 10.8 \text{ mA}$
- 4.37 Triode region
- 4.38 $1.13 \text{ mA}; 1.29 \text{ mA}$
- 4.39 $99.5 \mu\text{A}; 199 \mu\text{A}; 99.5 \mu\text{A}; 99.5 \mu\text{A}$
- 4.43 $202 \mu\text{A}; 184 \mu\text{A}$
- 4.44 5.17 V
- 4.49 $40.0 \mu\text{A}; 72.0 \mu\text{A}; 4.41 \mu\text{A}; 32.8 \mu\text{A}$
- 4.50 $5810/1; 2330/1$
- 4.54 $235 \Omega; 235 \Omega$
- 4.55 0.629 A/V^2
- 4.57 $400 \mu\text{A}$
- 4.64 $14\lambda \times 18\lambda; 7.9\%$
- 4.71 $3.45 \times 10^{-8} \text{ F/cm}^2; 17.3 \text{ fF}$
- 4.81 ($350 \mu\text{A}, 1.7 \text{ V}$); triode region
- 4.84 ($390 \mu\text{A}, 4.1 \text{ V}$); saturation region
- 4.86 ($778 \mu\text{A}, 9.20 \text{ V}$)
- 4.94 ($134 \mu\text{A}, 4.64 \text{ V}$) ; ($116 \mu\text{A}, 5.36 \text{ V}$)
- 4.97 $510 \text{ k}\Omega, 470 \text{ k}\Omega, 12 \text{ k}\Omega, 12 \text{ k}\Omega, 5/1$
- 4.100 ($124 \mu\text{A}, 2.36 \text{ V}$)
- 4.103 (a) ($33.3 \mu\text{A}, 1.01 \text{ V}$)
- 4.106 ($23.5 \mu\text{A}, 0.967 \text{ V}$)
- 4.109 ($73.1 \mu\text{A}, 9.37 \text{ V}$)
- 4.116 $2.25 \text{ mA}; 16.0 \text{ mA}; 1.61 \text{ mA}$
- 4.119 $18.1 \text{ mA}; 45.2 \text{ mA}; 13.0 \text{ mA}$
- 4.122 $1/3.57$
- 4.123 ($153 \mu\text{A}, -3.53 \text{ V}$) ; ($195 \mu\text{A}, -0.347 \text{ V}$)

- 4.125** 4.04 V, 10.8 mA, 43.2 mA
- 4.126** 14.4 mA; 27.1 mA; 10.4 mA
- 4.129** (59.8 μA , -5.47 V) , $\leq 130 \text{ k}\Omega$
- 4.131** (55.3 μA , -7.09 V) , $\leq 164 \text{ k}\Omega$
- 4.134** 40.1 $\text{k}\Omega \rightarrow$ (138 μA , -5 V)
- 4.138** One possible design: 220 $\text{k}\Omega$, 200 $\text{k}\Omega$, 5.1 $\text{k}\Omega$, 4.7 $\text{k}\Omega$
- 4.141** (260 μA , -12.4 V)
- 4.144** (36.1 μA , 80.6 mV); (32.4 μA , -1.32 V); (28.8 μA , -2.49 V)
- 4.146** 34.5 fF, 17.3 fF
- 4.148** 6.37 GHz, 2.55 GHz; 637 GHz, 255 GHz
- 4.149** 690 μA , 86.3 μA
- 4.150** 10^{-22} A , 10^{-15} A

Chapter 5

- 5.4 0.0167, 0.667, 3.00, 0.909, 49.0, 0.9950, 0.9990, 5000
- 5.5 2 fA; 1.01 fA, -0.115 V
- 5.6 0.374 μ A, -149.6 μ A, +150 μ A, 0.591 V
- 5.9 2.02 fA
- 5.11 5.34 mA; -5.34 mA
- 5.14 25 μ A, -100 μ A, +75 μ A, 65.7, 1/3, 0, 0.599 V
- 5.17 1.77 μ A, -33.2 μ A, +35 μ A, 0.623 V
- 5.20 723 μ A
- 5.24 0.990, 0.333, 2.02 fA, 6.00 fA
- 5.26 83.3, 87.5, 100
- 5.33 39.6 mV/dec, 49.5 mV/dec, 59.4 mV/dec, 69.3 mV/dec
- 5.34 6 V, 50 V, 6 V
- 5.35 2.31 mA; 388 μ A; 0
- 5.36 65.7 V
- 5.40 Cutoff
- 5.42 saturation, forward-active region, reverse-active region, cutoff
- 5.46 13.3 aA, 0.263 fA, 0.25 fA
- 5.47 $I_C = 16.3$ pA, $I_E = 17.1$ pA, $I_B = 0.857$ pA, forward-active region; although I_C , I_E , I_B are all very small, the Transport model still yields $I_C \cong \beta_F I_B$
- 5.48 65.7, 6.81 fA
- 5.49 62.5, 1.73 fA
- 5.50 55.3 μ A, 0.683 μ A, 54.6 μ A
- 5.51 6.67 MHz
- 5.53 0.875, 24.2 aA
- 5.55 -19.9 μ A, 26.5 μ A, -46.4 μ A
- 5.58 17.3 mV, 0.251 mV
- 5.60 1.81 A, 10.1 A
- 5.62 0.803 V, 0.714 V, 27.5 mV
- 5.65 23.2 μ A
- 5.66 4.0 fF; 0.4 pF; 40 pF
- 5.68 750 MHz, 3.75 MHz
- 5.71 0.147 μ m
- 5.72 71.7, 43.1 V
- 5.74 72.9, 37.6 V
- 5.75 100 μ A, 4.52 μ A, 95.5 μ A, 0.589 V, 0.593
- 5.77 (c) 38.7 mS
- 5.78 0.388 pF at 1 mA

- 5.82** (80.9 μA , 3.80 V) ; (405 μA , 3.80 V)
5.86 (42.2 μA , 4.39 V)
5.92 (7.5 mA, 4.3 V)
5.94 (5.0 mA, 1.3 V)
5.96 30 k Ω , 620 k Ω ; 24.2 μA , 0.770 V
5.98 5.28 V
5.100 3.21 Ω
5.103 616 μA , 867 μA , 3.90 V, 5.83 V
5.107 4.4 percent; 70 percent
5.109 The minimum I_C case, (109 μA , 7.36 V). For the maximum I_C case, the transistor is saturated.

Chapter 6

- 6.1 10 $\mu\text{W}/\text{gate}$, 4 $\mu\text{A}/\text{gate}$
- 6.3 2.5 V, 0 V, 0 W, 62.5 μW ; 3.3 V, 0 V, 0 V, 109 μW
- 6.5 $V_{OL} = 0$ V, $V_{OH} = 3.3$ V, $V_{REF} = 1.1$ V; $Z = A$
- 6.7 3 V, 0 V, 2 V, 1 V, -3
- 6.9 2 V, 0 V, 2 V, 5 V, 3 V, 2 V
- 6.11 3.3 V, 0 V, 3.0 V, 0.25 V, 1.8 V, 1.5 V, 1.2 V, 1.25 V
- 6.13 -0.80 V, -1.35 V
- 6.15 1 ns
- 6.17 1 $\mu\text{W}/\text{gate}$, 0.40 $\mu\text{A}/\text{gate}$, 1 fJ
- 6.19 2.20 RC; 2.20 RC
- 6.21 -0.78 V, -1.36 V, 1 ns, 1 ns, 9.5 ns, 9.5 ns, 4 ns, 4 ns, 4 ns
- 6.24 $Z = 0\ 0\ 0\ 1\ 0\ 0\ 1\ 1$
- 6.26 $Z = 0\ 1\ 0\ 1\ 0\ 1\ 0\ 1$
- 6.29 2 ; 1
- 6.31 84.5 A
- 6.32 0.583 pF
- 6.35 1 $\mu\text{W}/\text{gate}$, 0.556 $\mu\text{A}/\text{gate}$
- 6.37 155 k Ω , 1/1.08
- 6.39 (b) 2.5 V, 0.0329 V, 30.8 μW
- 6.40 (a) 0.412 V, 1.49 V
- 6.44 40.9 k Ω ; 1.52/1; 1.49 V, 0.267 V
- 6.47 417 Ω ; 1000 Ω ; a resistive channel exists connecting the source and drain; 20/1
- 6.50 1.44 V
- 6.53 1.29 V, 0.06 V
- 6.56 1.40/1, 6.67/1
- 6.59 0.106 V
- 6.61 ratioed logic so $V_H = 1.55$ V, $V_L = 0.20$ V; $P = 0.24$ mW
- 6.65 3.79 V
- 6.69 1.014
- 6.71 1.16/1, 1.36/1
- 6.72 1.46/1, 1/2.48
- 6.74 1.80/1, 0.610 V, 0.475 V
- 6.77 (a) 88.8 μA , 0.224 V (b) 0.700 V, 0.449 V
- 6.80 1.65/1, 1/1.80, 0.821 V, 0.440 V
- 6.84 2.22/1, 1.81/1
- 6.87 6.66/1, 1.11/1, 0.203 V, 6.43/1, 6.74/1, 7.09/1

- 6.90 $Y = \overline{(A + B)(C + D)(E + F)}$, 6.66/1, 1.81/1
- 6.94 $Y = \overline{ACE + ACDF + BF + BDE}$, 3.33/1, 26.6/1, 17.8/1
- 6.97 1/1.80, 3.33/1
- 6.100 $Y = (C + E)[A(B + D) + G] + F$; 3.62/1, 13.3/1, 4.44/1, 6.67/1
- 6.103 3.45/1, 6.43/1, 7.09/1, 6.74/1
- 6.105 7.09/1, 6.43/1, 6.74/1
- 6.108 7.24/1, 26.6/1, 8.88/1, 13.3/1
- 6.110 (a) 5.43/1, 9.99/1, 20.0/1
- 6.113 $I'_{DS} = 2I_{DS}$, $P'_D = 2P_D$
- 6.114 80 mW, 139 mW
- 6.116 1 ns
- 6.118 60.2 ns, a potentially stable state exists with no oscillation
- 6.119 31.7 ns, 4.39 ns, 5.86 ns
- 6.123 114 ns, 5.94 ns, 15.3 ns
- 6.126 78.7 ns, 10.2 ns, 9.00 ns
- 6.128 3.52/1, 27.8/1, 12.8 ns, 0.924 ns
- 6.130 (a) 1/1.68 (d) 1/5.89 (f) 1/1.60
- 6.132 -1.90 V, -0.156 V
- 6.133 1/3.30, 1.75/1
- 6.134 2.30 V, 1.07 V
- 6.136 $Y = \overline{A + B}$

Chapter 7

- 7.1 $173 \mu\text{A}/\text{V}^2$; $6.1 \mu\text{A}/\text{V}^2$
- 7.3 250 pA; 450 pA; 450 pA
- 7.6 2.5 V, 0 V
- 7.8 cutoff, triode, triode, cutoff, saturation, saturation
- 7.11 1.25 V, 42.3 μA ; 1.104 V, 25.4 μA
- 7.13 0.90 V, 16.0 μA ; 0.810 V, 96.2 μA
- 7.15 (b) 2.5 V, 0.0928 V
- 7.17 0.9836 V, 2.77 mA
- 7.18 1.16 V, 0.728 V
- 7.22 2.36 ns, 2.36 ns, 0.788 ns
- 7.23 11.9 ns, 4.74 ns, 2.77 ns
- 7.26 2.11/1, 5.26/1
- 7.28 6.00/1, 15.0/1
- 7.30 1.7 ns, 2.3 ns, 1.1 ns, 0.9 ns, $\langle C \rangle = 138 \text{ fF}$
- 7.33 2.5 $\mu\text{W}/\text{gate}$, 45.9 fF, 80.0 fF
- 7.35 1.00 W; 1.74 W
- 7.37 90.3 μA ; 25.0 μA
- 7.41 0.290 pJ, 283 MHz, 616 μW
- 7.44 $\alpha\Delta T$, $\alpha^2 P$, $\alpha^3 \text{PDP}$
- 7.48 2/1, 20/1; 6/1, 60/1
- 7.53 1.25/1
- 7.59 3.95 ns, 3.95 ns, 11.8 ns
- 7.60 (a) 5 transistors (b) The CMOS design requires 47% less area.
- 7.62 $Y = \overline{(A + B)(C + D)E} = \overline{ACE + ADE + BDE + BCE}$, 18/1, 30/1, 15/1
- 7.64 $Y = \overline{(\overline{A + B})(\overline{C + D})(\overline{E + F})} = \overline{AB + CD + EF}$, 4/1, 15/1
- 7.67 2/1, 4/1, 6/1, 20/1
- 7.69 (a) Path through NMOS A-D-E (d) Paths through PMOS A-C and B-E
- 7.71 4/1, 6/1, 10/1
- 7.72 20/1, 24/1, 40/1
- 7.78 5.37 ns, 2.21 ns
- 7.82 9.47 ns, 23.7 ns
- 7.84 5.8 ns, 3.7 ns
- 7.91 $V_{DD} \rightarrow \frac{2}{3} V_{DD} \rightarrow \frac{1}{2} V_{DD}$; $R \geq \frac{2V_{IH}}{V_{DD} - V_{IH}} = \frac{2V_{IH}}{NM_H}$, $C_1 \geq 83.1C_2$
- 7.97 $N = 8$, $A = 22.6 \text{ A}_0$

- 7.101** 263 Ω , 658 Ω
- 7.103** 240/1, 96.2/1
- 7.104** 1.4 V, 2.5 V
- 7.106** Latchup does not occur.

Chapter 8

- 8.1** 268,435,456 bits, 1,073,741,824 bits; 2048 blocks
- 8.2** 3.73 pA/cell , 233 fA/cell
- 8.5** 3 V, 0.667 μ V
- 8.9** 1.55 V, 0 V, 3.59 V
- 8.10** “1” level is discharged by junction leakage current
- 8.11** 1.47 V, 1.43 V
- 8.12** -19.8 mV; 2.48 V
- 8.15** 0 V, 1.90; Junction leakage will destroy the “1” level
- 8.16** 5.00 V, 1.60 V; -1.83 V
- 8.18** 33.6 mW
- 8.21** 402 μ A, 1.36 W
- 8.23** For $C_{BL} = 500$ fF, 0.266 V
- 8.24** 0.945 V, (The sense amplifier provides a gain of 10.5.)
- 8.30** 0 V, 1.43 V, 3.00 V
- 8.31** 53,296
- 8.35** $V_{DD} \rightarrow \frac{2}{3}V_{DD} \rightarrow \frac{1}{2}V_{DD}$; $R \geq \frac{2V_{IH}}{V_{DD} - V_{IH}} = \frac{2V_{IH}}{NM_H}$; $C_1 \geq 2.88C_2$
- 8.37** $W_1 = 01000110_2$, $W_3 = 00101011_2$
- 8.41** 1.16/1

Chapter 9

- 9.1 0 V, -1.70 V
- 9.2 -1.38 V, -1.12
- 9.3 -1.75 V, 0 V
- 9.6 0 V, -0.4 V; 3.39 k Ω ; Saturation, cutoff; Cutoff, saturation
- 9.8 -0.700 V, -1.70 V, -1.20 V, 1.00 V
- 9.11 -0.700 V, -1.50 V, -1.10 V, 2.67 k Ω ; 0.289 V, -0.100 V, +0.300 V
- 9.13 267 Ω , -1.90 V, -2.30 V, -2.10 V
- 9.15 14.8 k Ω , 16.0 k Ω , 93.6 k Ω , 336 k Ω
- 9.17 -1.10 V, -1.50 V, -1.30 V, 0.400 V, 0.107 V, 1.10 mW
- 9.18 0.383 V
- 9.21 0.430 V
- 9.23 50.0 μ A, -2.30 V
- 9.24 Standard values: 11 k Ω , 150 k Ω , 136 k Ω
- 9.28 +0.300 V, -0.540 V, 336 Ω
- 9.31 5.15 mA
- 9.34 0.13 mA
- 9.38 500 Ω , 60.0 mA
- 9.40 (c) 0 V, -0.7 V, 3.93 mA (d) -3.7 V, 0.982 mA (e) 2920 Ω
- 9.43 $Y = A + \bar{B}$
- 9.45 359 ns
- 9.47 -0.850 V; 3.59 pJ
- 9.48 0 V, -0.600 V, 5.67 mW; $Y = A + B + C$, 5 vs. 6
- 9.51 5.00 k Ω , 5.40 k Ω , 31.6 k Ω , 113 k Ω
- 9.52 1 k Ω , 1 k Ω , 1.30 mW
- 9.54 2.23 k Ω , 4.84 k Ω , 60.1 k Ω
- 9.56 2.98 pA, 74.5 fA
- 9.58 160; 0.976; 5; 0.773 V
- 9.59 0.691 V, 0.710 V
- 9.64 40.2 mV, 0.617 mV
- 9.66 3 V, 0.15 V, 0.66 V, 0.80 V, 33
- 9.68 68.2 mV, 2.47 mA
- 9.72 44.8 k Ω , 22.4 k Ω
- 9.74 5 V, 0.15 V, 0, -1.06 mA, 31; -1.06 mA vs. -1.01 mA, 0 mA vs. 0.2 mA
- 9.82 8
- 9.84 234 mA, 34.9 mA

- 9.88** (I_B, I_C): (a) ($135 \mu\text{A}, -169 \mu\text{A}$); ($515 \mu\text{A}, 0$); ($169 \mu\text{A}, 506 \mu\text{A}$); ($0, 0$) (b) all 0 except $I_{B1} = I_{E1} = 203 \mu\text{A}$
- 9.94** $1.85 \text{ V}, 0.15 \text{ V}; 62.5 \mu\text{A}, -650 \mu\text{A}; 13$
- 9.96** $Y = \overline{ABC}; 1.9 \text{ V}; 0.15 \text{ V}; 0, -408 \mu\text{A}$
- 9.98** $1.5 \text{ V}, 0.25 \text{ V}; 0, -1.00 \text{ mA}; 16$
- 9.99** $0.7 \text{ V}, 191 \mu\text{A}, 59 \mu\text{A}, 1.18 \text{ mA}$
- 9.100** $1.13 \text{ mA}, 0, 4.28 \text{ mA}, 0, 129 \mu\text{A}, 1.00 \text{ mA}; 0, 0, 0, 0, 1.23 \text{ mA}, 0$
- 9.102** $Y = A + B + C; 0 \text{ V}, -1.0 \text{ V}; -0.90 \text{ V}$
- 9.103** $Y = A + B + C; 0 \text{ V}, -0.80 \text{ V}; -0.40 \text{ V}$
- 9.104** $1.05 \text{ mA}, 26.9 \mu\text{A}$
- 9.105** $2 \text{ fJ}; 10 \text{ fJ}$
- 9.107** $1.67 \text{ ns}; 0.5 \text{ mW}$

Chapter 10

10.2 (a) 41.6 dB, 35.6 dB, 94.0 dB, 100 dB, -0.915 dB

10.3 Using MATLAB:

```
t = linspace(0,.004);
```

```
vs = sin(1000*pi*t)+0.333*sin(3000*pi*t)+0.200*sin(5000*pi*t);
```

```
vo = 2*sin(1000*pi*t+pi/6)+sin(3000*pi*t+pi/6)+sin(5000*pi*t+pi/6); plot(t,vs,t,vo)par
```

500 Hz: 1 0°, 1500 Hz: 0.333 0°, 2500 Hz: 0.200 0°; 2 30°, 1 30°, 1 30° 2 30°, 3 30°, 5 30° yes

10.5 35.0 dB, 111 dB, 73.2 dB

10.8 25.1 dB, 93.0 dB, 59.0 dB; $V_o = 17.9$ V, recommend ± 20 -V supplies

10.13 -10 (20 dB), 0.1 V; 0, 0 V

10.14 $v_o = [8 - 4 \sin(1000t)]$ volts; there are only two components; dc: 8 V, 159 Hz: -4 V

10.17 24.1 dB, 11.2%

10.20 4.12×10^{-8} S, -9.90×10^{-3} , 1.00, 99.0 Ω

10.22 0.286 mS, -0.286, -1710, 1.78 M Ω

10.23 1.00 mS, -1.00, 2001, 20.0 k Ω

10.25 53.7 dB, 150 dB, 102 dB; 11.7 mV; 31.3 mW

10.26 45.3 mV, 1.00 W

10.30 -7800

10.33 0, ∞ , 125 mW, ∞

10.37 -4.44 dB, 26.5 kHz

10.39 10 k Ω , 0.015 μ F

10.41 -1.05 dB, 181 Hz

10.43 60 dB, 10 kHz, 10 Hz, 9.99 kHz, band-pass amplifier

10.44 80 dB, ∞ , 100 Hz, ∞ , high-pass amplifier

10.48 60 dB, 100 kHz, 28.3 Hz, 100 kHz

10.56 $0.030 \sin(2\pi t + 89.4^\circ)$ V, $1.34 \sin(100\pi t + 63.4^\circ)$ V, $3.00 \sin(10^4\pi t + 1.15^\circ)$ V

10.59 $0.956 \sin(3.18 \times 10^5 \pi t + 101^\circ)$ V, $5.00 \sin(10^5 \pi t + 180^\circ)$ V, $5.00 \sin(4 \times 10^5 \pi t - 179^\circ)$ V

10.61 $\frac{2 \times 10^8 \pi}{s + 10^7 \pi} \quad \Bigg| \quad - \frac{2 \times 10^8 \pi}{s + 10^7 \pi}$

10.63 60 dB, 16.1 kHz, -40 dB/decade

10.64 66 dB, 12.8 kHz, -60 dB/decade

10.65 $10 \sin(1000\pi t + 10^\circ) + 3.33 \sin(3000\pi t + 30^\circ) + 3.00 \sin(5000\pi t + 50^\circ)$ V; Using MATLAB:

```
t = linspace(0,.004);
```

```
A=10^(10/20);
```

```
vs = sin(1000*pi*t)+0.333*sin(3000*pi*t)+0.200*sin(5000*pi*t);
```

```
vo = A*sin(1000*pi*t+pi/18)+3.33*sin(3000*pi*t+3*pi/18)+2.00*sin(5000*pi*t+5*pi/18);
```

```
plot(t, A*vs, t, vo)
```

Chapter 11

- 11.1 59.9 dB, 120 dB, 89.9 dB; 5.05 mV
- 11.3 $R_{id} \geq 4.95 \text{ M}\Omega$
- 11.5 0.100 mV, 140 dB
- 11.7 (a) -46.8, 4.7 k Ω , 0, 33.4 dB
- 11.10 (d) $(-1.10 + 0.75 \sin 2500\pi t) \text{ V}$
- 11.13 30.1 k Ω , 1.00 M Ω + 576 k Ω , $A_v = -20.1$, $R_{in} = 30.1 \text{ k}\Omega$
- 11.15 92.5, ∞ , 0, 83.9 dB
- 11.18 (d) $(1.98 - 1.08 \sin 3250\pi t) \text{ V}$
- 11.21 20.0 k Ω , 1.05 k Ω , $A_v = 20.0$
- 11.24 $(0.510 \sin 3770t - 1.02 \sin 10000t) \text{ V}$, 0
- 11.25 $-0.3750 \sin 4000\pi t \text{ V}$; $-0.6875 \sin 4000\pi t \text{ V}$; 0 to -0.9375 V in - 62.5-mV steps
- 11.26 455/1, 50/1
- 11.27 -10, 110 k Ω , 10 k Ω , $(-30 + 15\cos 8300\pi t) \text{ V}$, $(-30 + 30\cos 8300\pi t) \text{ V}$
- 11.28 3.2 V, 3.1 V, 2.82 V, 2.82 V, -1.00 V; 3.80 μA ; 3.80 μA , 2.80 μA
- 11.30 -12, $(-6.00 + 1.20 \sin 4000\pi t) \text{ V}$
- 11.34 (a) 10 k Ω , 100 k Ω , 79.6 pF (b) 10 k Ω , 100 k Ω , 82 pF, 19.4 kHz
- 11.35 $T(s) = -sRC$
- 11.38 -6.00, 20.0 k Ω , 0; +9.00, 75.0 k Ω , 0; 0, 160 k Ω , 0
- 11.39 -70.0, 10 k Ω , 0
- 11.40 1 A, 2.83 V, $> 10 \text{ W}$ (choose 15 W)
- 11.41 0.484 A; 0.730 V; 0.730 V; $\geq 7.03 \text{ W}$ (choose 10 W), 7.27 W
- 11.44 $\frac{V_1 - V_2}{R}$, ∞ ; If the voltage gain were finite with value A , $R_{out} = R(1 + A)$
- 11.46 3.99 V, 3.99 V, 1.99 V, 1.99 V, 3.99 V, 200 μA ; -5 M Ω !
- 11.48 4.96 k Ω , ∞
- 11.50 -1.00 k Ω
- 11.51 11 resistors, 1024:1
- 11.53 -0.3125 V, -0.6250 V, -1.250 V, -2.500 V
- 11.54 $3.415469 \text{ V} \leq V_x \leq 3.415781 \text{ V}$
- 11.55 1.90735 μV , 11010000101000111101₂, 01111111100111011101₂
- 11.56 19.1 ns
- 11.58 A and B taken together, B and C taken together
- 11.61 48.0, ∞ , 0
- 11.64 -1080, 3.9 k Ω , 0
- 11.65 8.62 k Ω , 8.62 k Ω
- 11.66 -1500, 47 k Ω , 0, 0.010 V, 0V, -0.100 V, 0 V, +1.00 V, 0 V, -15.0 V, 0V (ground node)
- 11.70 2744, 2434, 3094, 1 M Ω , 1.02 M Ω , 980 k Ω

11.73 (b) 0.005 μF , 0.0025 μF , 1.13 $\text{k}\Omega$

$$\mathbf{11.77} \quad \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{K}{s^2 R_1 R_2 C_1 C_2 + s [R_1 C_1 (1 - K) + C_2 (R_1 + R_2)] + 1} \quad | \quad S_K^Q = \frac{K}{3 - K}$$

11.79 -1

11.81 270 pF, 270 pF, 23.2 $\text{k}\Omega$

11.82 (a) 51.2 kHz, 7.07, 7.23 kHz

11.85 (a) 1 rad/s, 4.65, 0.215 rad/s

11.87 5.48 kHz, 4.09, 1.34 kHz

11.89 10 $\text{k}\Omega$, 100 $\text{k}\Omega$, 20 $\text{k}\Omega$, 0.0133 μF

11.92 0.759 V

11.93 2.4 Hz

11.98 $V_o = -V_1 V_2 / 10^4 I_s$

11.99 2.62 V, 2.38 V, 0.24 V

11.101 0.487 V, -0.487 V, 0.974 V

11.103 9.86 kHz

11.104 $f = 0$. $V_o = 0$ is a stable state. The circuit does not oscillate.

11.106 0, 0.298 V, 69.0 mV

11.107 13 $\text{k}\Omega$, 30 $\text{k}\Omega$, 51 $\text{k}\Omega$, 150 pF

Chapter 12

- 12.1 (a) 13.49, 9.11×10^{-3} , 0.0675%
- 12.3 (a) -9.997, 2.76×10^{-3} , 0.0276%
- 12.5 106 dB
- 12.10 100 μA , 100 μA , -48.0 pA
- 12.11 (a) 13.5, 371 M Ω , 169 m Ω
- 12.13 (a) -8.39, 5.60 k Ω , 37.5 m Ω
- 12.15 785 M Ω , 785 M Ω , 3.75 m Ω
- 12.17 If the gain specification is met, the input and output specifications cannot be met.
- 12.21 $\leq 0.374\%$
- 12.23 0.869 V, 1.00 V, 13.1%
- 12.26 114 dB
- 12.27 60 dB
- 12.29 4.500 V, 4.99 V, 5.01 V, 5.500 V, 2.7473 V, 2.7473 V, 0.991 V, -75.4 μA , -375 μA , +175 μA
- 12.31 -0.026 V, -26 mV, 90.9 k Ω
- 12.33 +7500, 0.667 mV
- 12.36 The nearest 5% values are 1 M Ω and 10 k Ω
- 12.40 -5.00 V, 0 V; -12.0 V, 0.182 V
- 12.42 10 V, 0 V; 15 V, 0.125 V
- 12.45 220 Ω and 22 k Ω represent the smallest acceptable resistor pair.
- 12.47 39.2 Ω
- 12.49 +50.0, 24.0 k Ω , 6.00 m Ω
- 12.51 -42.0, 3.57 G Ω , 14.0 m Ω
- 12.53 3

$$12.54 \quad A_v(s) = \frac{V_o}{V_s} = \left(1 + \frac{R_2}{R_1}\right) \frac{SC(R_1 \parallel R_2) + 1}{SCR_2 + 1}$$

12.55 -33.0, -40.3, -27.0; 4.83 kHz, 3.65 kHz, 10.7 kHz

12.56 3 stages, 270 pF, 15.0 k Ω , 1.5 k Ω

12.57

$$Z_{out} = \frac{R_o}{(1 + A_o\beta)} \frac{1 + \frac{s}{\omega_B}}{1 + \frac{s}{\omega_B(1 + A_o\beta)}} \cong \frac{R_o}{(1 + A_o\beta)} \frac{1 + \frac{s}{\omega_B}}{1 + \frac{s}{\beta\omega_T}}$$

12.59

$$Z_{in} = R_1 + \left(R_{id} \parallel \frac{R_2}{(1 + A_o)} \right) \frac{\left(1 + \frac{s}{\omega_B} \right)}{1 + \frac{s}{\omega_B(1 + A_o)} \frac{R_{id} + R_2}{R_{id} + \frac{R_2}{(1 + A_o)}}}$$

12.62

$$(a) A_v(s) = \frac{V_o(s)}{V_s(s)} = -\frac{1}{sRC}$$

$$(b) A_v(s) = -\frac{\frac{\omega_T}{RC}}{s^2 + s\left(\omega_B + \omega_T + \frac{1}{RC}\right) + \frac{\omega_B}{RC}} \cong -\frac{\frac{\omega_T}{RC}}{(s + \omega_T)\left(s + \frac{1}{A_o RC}\right)}$$

12.64 -20, 143 kHz; -8000, 72.9 kHz

12.67 Two stages

12.69 (a) In a simulation of 5000 cases, 33.5% of the amplifiers failed to meet one of the specifications.
(b) 1.5% tolerance.

12.71 6.91, 7.53, 6.35; 145 kHz, 157 kHz, 133 kHz

12.73 1.89 V/ μ s

12.75 10.0 V/ μ s

12.82 $10^{10} \Omega$, 7.96 pF, 4×10^6 , R_o not specified

12.84 -1500, 47.0 k Ω , 40.0 m Ω , 79.9 kHz; 50.0 mV, 5.00 μ V, -500 mV, -50.0 μ V, +5.00 V, +3.56 V, -18.0 V, +18.0 V, -18.0 V, 0 V

12.88 2740, 3070, 2460; 1 M Ω , 1.02 M Ω , 980 k Ω ; 21.0 m Ω , 21.8 m Ω , 20.2 k Ω ; 357 kHz, 371 kHz, 344 kHz

12.89 -2380, 613 M Ω , 98.0 m Ω , 29.6 kHz; 0 V, 10.0 mV, 49.0 mV, 389 μ V, -3.89 V, -3.06 V, -15.0 V, +15.0 V, -15.0 V, 0 V

Chapter 13

- 13.1** $0.700 + 0.005 \sin 2000\pi t$ V; $-1.03 \sin 2000\pi t$ V; $5.00 - 1.03 \sin 2000\pi t$ V; 2.82 mA
- 13.3** (a) C_1 is a coupling capacitor that couples the ac component of v_1 into the amplifier. C_2 is a coupling capacitor that couples the ac component of the signal at the collector to the output v_o . C_3 is a bypass capacitor. (b) The signal voltage at the top of resistor R_4 will be zero.
- 13.5** (a) C_1 is a coupling capacitor that couples the ac component of v_1 into the amplifier. C_2 is a bypass capacitor. C_3 is a coupling capacitor that couples the ac component of the signal at the collector to output v_o . (b) The signal voltage at the emitter will be $v_e = 0$.
- 13.7** (a) C_1 is a coupling capacitor that couples the ac component of v_1 into the amplifier. C_2 is a coupling capacitor that couples the ac component of the signal at the drain to output v_o .
- 13.11** (a) C_1 is a coupling capacitor that couples the ac component of v_1 into the amplifier. C_2 is a bypass capacitor. C_3 is a coupling capacitor that couples the ac component of the signal at the drain to the output v_o . (b) The signal voltage at the top of R_4 will be zero.
- 13.15** (22.5 μ A, 6.71 V)
- 13.17** (1.78 mA, 6.08 V)
- 13.19** (98.4 μ A, 4.96 V)
- 13.23** (82.2 μ A, 6.04 V)
- 13.27** (307 μ A, 3.88 V)
- 13.31** (338 μ A, 5.41 V)
- 13.33** (1.25 mA, 10.6 V)
- 13.45** Thévenin equivalent source resistance, gate-bias voltage divider, gate-bias voltage divider, source-bias resistor—sets source current, drain-bias resistor—sets drain-source voltage, load resistor
- 13.46** 94.4 Ω , 2.5 T Ω , ≤ -0.150 V
- 13.47** 17.3 Ω for $T = 200$ K
- 13.48** Errors: +10.7%, -9.37%; +23.0%, - 17.5%
- 13.49** (c) 1.25 μ A
- 13.51** (188 μ A, $V_{CE} \geq 0.7$ V), 7.50 mS, 533 k Ω
- 13.55** (b) +16.7%, -13.6%
- 13.56** 90, 120; 95, 75
- 13.61** [-95.0, -94.1]
- 13.63** -40.0
- 13.65** 3
- 13.67** -120
- 13.69** Yes, using $I_C R_C = (V_{CC} + V_{CE})/2$
- 13.71** 2.5 mA; 30.7 V
- 13.72** 0.500 V
- 13.73** No, there will be significant distortion
- 13.74** (b) -314

- 13.76 50/1, 0.160 V
- 13.77 1.25 A
- 13.79 10%, 20%
- 13.82 (156 μ A, 9 V)
- 13.83 Virtually any desired Q-point
- 13.84 $400 = 133,000i_P + v_{PK}$; (1.4 mA, 215 V); 1.6 mS, 55.6 k Ω , 89.0; -62.7
- 13.85 BJT
- 13.86 FET
- 13.87 111 μ A, 1400
- 13.88 2000, 200, 8.00 mS, 0.800 mS
- 13.91 21.6 dB
- 13.93 0.300 V
- 13.94 (125 μ A, 7.5 V)
- 13.95 0.5 V, 28 V
- 13.97 3
- 13.99 -10.9
- 13.102 -7.34
- 13.107 33.3 k Ω , 94.4 k Ω
- 13.109 833 k Ω , 1.46 M Ω
- 13.111 243 k Ω , 40.1 k Ω
- 13.113 6.8 M Ω , 45.8 k Ω , independent of K_n
- 13.115 1 M Ω , 3.53 k Ω
- 13.117 -336 v_i , 3.62 k Ω
- 13.119 -23.6 v_i , 508 k Ω
- 13.116 (b) 1 M Ω , 0, -7.45 M Ω , 3.53 M Ω
- 13.121 -31.8, 1.42 k Ω , 982 Ω
- 13.123 -27.0, 142 k Ω , 98.2 k Ω
- 13.127 1.38 μ W, 0.581 mW, 0.960 mW, 0.887 mW, 2.43 mW
- 13.131 0.497 mW, 0.554 mW, 0.182 mW, 16.4 μ W, 44.3 μ W, 1.29 mW
- 13.134 $V_{CC}/15$
- 13.135 3.38 V, 13.6 V
- 13.136 $(V_{CC})^2/8R_L$, $(V_{CC})^2/2R_L$, 25%
- 13.137 0.854 V
- 13.139 2.80 V
- 13.141 2.80 V
- 13.139 1.76 V
- 13.153 2.5 V, 8.5 V

Chapter 14

- 14.1 (a) C-C or emitter-follower (b) not useful, signal is being injected into the drain (c) C-E (h) C-B (k) C-G (o) C-D or source-follower
- 14.8 -3.64 , $2\text{ M}\Omega$, $26.5\text{ k}\Omega$, -3770 ; -8.03 , $2\text{ M}\Omega$, $10.0\text{ k}\Omega$, -10000
- 14.9 -32.2 , $9.58\text{ k}\Omega$, $596\text{ k}\Omega$, -27.1 ; -17.0 , $11.6\text{ k}\Omega$, $1060\text{ k}\Omega$, -17.1
- 14.10 (a) -6.91 (e) -240
- 14.11 $3.3\text{ k}\Omega$, $33\text{ k}\Omega$
- 14.14 -182 , -7.10 , $19.0\text{ k}\Omega$, $39\text{ k}\Omega$, 5.13 mV
- 14.15 -75.9 , -4.23 , $3.86\text{ k}\Omega$, $8.20\text{ k}\Omega$, 6.30 mV , -90
- 14.16 -12.9 , -10.1 , $368\text{ k}\Omega$, $75\text{ k}\Omega$, 160 mV , -18.8
- 14.18 -3.43 , -952 , $10\text{ M}\Omega$, $1,80\text{ k}\Omega$, 1.00 V
- 14.19 -3560 , -6.41 , $1.55\text{ k}\Omega$, $95.1\text{ k}\Omega$, 5.81 mV
- 14.20 0.747 , $29.8\text{ k}\Omega$, $104\ \Omega$, 9.7
- 14.21 0.907 , $2\text{ M}\Omega$, $100\ \Omega$, $20,000$
- 14.22 0.874 , $7.94\text{ M}\Omega$, $247\ \Omega$, ∞
- 14.23 0.984 , $45.2\text{ k}\Omega$, $27.8\ \Omega$, 0.784 V
- 14.24 0.960 , $1\text{ M}\Omega$, $507\ \Omega$, 6.19 V
- 14.25 0.992 , $12.6\text{ M}\Omega$, $1.34\text{ k}\Omega$, 0.601 V
- 14.26 $v_i \leq (0.005 + 0.2 V_{RE})\text{ V}$
- 14.28 0.999 , 25.0 V
- 14.30 48.7 , $1.94\text{ k}\Omega$, $4.92\text{ M}\Omega$, 0.990 ; 23.6 , $1.94\text{ k}\Omega$, $10.1\text{ M}\Omega$, 0.969
- 14.31 28.8 , $1.20\text{ k}\Omega$, ∞ , 0.600 ; 5.81 , $1.43\text{ k}\Omega$, ∞ , 0.714
- 14.33 40.7 , $185\ \Omega$, $39.0\text{ k}\Omega$, 18.5 mV
- 14.35 4.12 , $1.32\text{ k}\Omega$, $20\text{ k}\Omega$, 354 mV
- 14.37 5.01 , $3.02\text{ k}\Omega$, $24\text{ k}\Omega$, 352 mV
- 14.39 $44.5\ \Omega$
- 14.40 $633\ \Omega$
- 14.42 $(\beta_o + 1)r_o = 154\text{ M}\Omega$
- 14.43 Low R_{in} , high gain: Either a common-base amplifier operating at a current of $71.4\ \mu\text{A}$ or a common-emitter amplifier operating at a current of approximately 7.14 mA can meet the specifications with $V_{CC} \approx 14\text{ V}$.
- 14.45 Large R_{in} , moderate gain: Common-source amplifier.
- 14.47 Low R_{in} , high gain: Common-emitter amplifier with $5\text{-}\Omega$ input "swamping" resistor.
- 14.49 Common-drain amplifier.
- 14.51 Cannot be achieved with what we know at this stage in the text.
- 14.53 $1.66\ \Omega$
- 14.55

| v_i | 1 kHz | 2 kHz | 3 kHz | THD |
|-------|---------|-----------------|------------------|-------|
| 5 mV | 5.8 mV | 0.335 mV (5.7%) | 0.043 mV (0.74%) | 5.9% |
| 10 mV | 12.4 mV | 1.54 mV (12.5%) | 0.258 mV (2.1%) | 12.8% |
| 15 mV | 20.6 mV | 4.32 mV (21%) | 1.18 mV (5.4%) | 22% |

- 14.57 $479v_i$, 384 k Ω
- 14.59 v_i , 297 Ω
- 14.61 0.947, 0
- 14.63 41.7, -0.167
- 14.65 -9.75, 0
- 14.67 -0.984, 0.993, 0.703 V
- 14.69 SPICE: (116 μ A, 7.53 V), -150, 19.6 k Ω , 37.0 k Ω
- 14.71 SPICE: (115 μ A, 6.30 V), -20.5, 368 k Ω , 65.1 k Ω
- 14.73 SPICE: (12.7 μ A, 5.68 V), 0.986, 10.7 M Ω , 2.00 k Ω
- 14.75 SPICE: (66.7 μ A, 4.47 V), -16.8, 1.10 M Ω , 81.0 k Ω
- 14.77 SPICE: (5.59 mA, -5.93 V), -3.27, 10.0 M Ω , 1.52 k Ω
- 14.79 SPICE: (6.20 mA, 12.0 V), 0.953, 2.00 M Ω , 388 Ω
- 14.81 0.01 μ F, 270 μ F, 0.15 μ F; 2.7 μ F
- 14.83 0.20 μ F, 270 μ F; 100 μ F, 0.15 μ F
- 14.85 1.80 μ F, 0.033 μ F
- 14.87 8200 pF, 820 pF; 0.042 μ F, 1800 pf, 0.015 μ F
- 14.89 33.3 mA
- 14.91 $R_1 = 120$ k Ω , $R_2 = 110$ k Ω
- 14.93 The second MOSFET
- 14.95 $45.1 \leq A_v \leq 55.3$ - Only slightly beyond the limits in the Monte Carlo results.
- 14.99 Voltage is not sufficient - transistor will be saturated.
- 14.101 4.08, 1.00 M Ω , 64.3 Ω
- 14.104 2.17, 1.00 M Ω , 64.3 Ω
- 14.109 468, 73.6 k Ω , 18.8 k Ω
- 14.110 0.670, 107 k Ω , 20.0 k Ω
- 14.112 7920, 10.0 k Ω , 18.8 k Ω
- 14.113 140, 94.7 Ω , 113 Ω
- 14.115 Use $C_3 = 2.2$ μ F, 19.2 Hz, 18.0 Hz
- 14.117 1.56 Hz, 1.22 Hz
- 14.119 6.40 Hz, 5.72 Hz
- 14.121 0.497 Hz, 0.427 Hz
- 14.122 Use 1 μ F for all capacitors; 1.42 kHz, 1.68 kHz

Chapter 15

- 15.1 (20.7 μA , 5.87 V); -273, 243 k Ω , 660 k Ω ; -0.604, 47.1 dB, 27.3 M Ω
- 15.2 (5.25 μA , 1.68 V); -21.0, -0.636, 24.4 dB, 572 k Ω , 4.72 M Ω , 200 k Ω , 50.0 k Ω
- 15.4 (182 μA , 0.92 V); -728, -1.05, 50.8 dB, 27.4 k Ω , 4.75 M Ω , 200 k Ω , 50.0 k Ω
- 15.7 $R_{EE} = 1.1 \text{ M}\Omega$, $R_C = 1.0 \text{ M}\Omega$
- 15.8 (a) (198 μA , 4.98 V); differential output: -309, 0, ∞ (b) single-ended output: -155, -0.0965, 64.1 dB; 25.2 k Ω , 20.2 M Ω , 78.0 k Ω , 19.5 k Ω
- 15.9 2.593 V, 5.663 V, -3.078 V, 3.94 V
- 15.11 $V_O = 0.991 \text{ V}$, $v_o = 0$; $V_O = 0.991 \text{ V}$; $v_o = 1.36 \text{ V}$, $V_O = 0.991 \text{ V}$, $v_o = 0.360 \text{ V}$; 5.48 mV
- 15.14 (47.4 μA , 6.22 V); Differential output: -380, 0, ∞ ; single-ended output: -190, -0.661, 49.2 dB; 158 k Ω , 22.7 M Ω
- 15.15 -5.850 V, -3.450 V, -2.40 V
- 15.17 (4.94 μA , 1.77 V); differential output: -77.2, 0, ∞ ; single-ended output: -38.6, -0.661, 25.4 dB; 808 k Ω , 405 M Ω , 1.60 V
- 15.19 -283, -.00494, 95.2 dB
- 15.19 -300, -.00499, 95.6 dB
- 15.23 (107 μA , 10.1 V); differential output: -18.2, 0, ∞ ; single-ended output: -9.1, -0.487, 25.4 dB; ∞ , ∞
- 15.25 2.4 k Ω , 5.6 k Ω
- 15.29 (20 μA , 4.32 V); differential output: -38.0, 0, ∞ ; single-ended output: -19.0, -0.120, 44.0 dB; ∞ , ∞
- 15.31 (20 μA , 5.71 V); differential output: -38.1, 0, ∞ ; single-ended output: -19.0, -0.120, 44.0 dB; ∞ , ∞
- 15.33 312 μA , 27 k Ω
- 15.35 -21.6, -0.783, 13.8, ∞ , ∞
- 15.37 -3.80 V, -2.64 V, 48.3 mV
- 15.39 -79.9, -0.494, 751 k Ω
- 15.40 (99.0 μA , 10.8 V); -30.1, -0.165, 554 k Ω
- 15.42 (49.5 μA , 3.29 V), (49.5 μA , 8.70 V); -149, -0.0619, 101 k Ω
- 15.43 (100 μA , 1.63 V), (100 μA , 3.16 V); -13.4, 0, ∞
- 15.45 (24.8 μA , 12.0 V), (500 μA , 12.0 V), 893, 202 k Ω , 20.6 k Ω , 147 M Ω , v_2
- 15.46 [-10.6 V, 11.3 V]
- 15.49 (24.8 μA , 11.3 V), (4.95 μA , 11.3 V), (495 μA , 12.0 V), 9180, 202 k Ω , 19.2 k Ω , 145 M Ω , v_2
- 15.50 (98.8 μA , 14.3 V), (300 μA , 14.3 V); 551, 40.5 k Ω ; 34.6 M Ω ; v_2
- 15.51 [-13.6 V, 13.6 V]
- 15.55 (98.8 μA , 14.3 V), (300 μA , 14.3 V); 27800, 40.5 k Ω ; 2.51 M Ω
- 15.59 (250 μA , 15.6 V), (500 μA , 15.0 V); 4300, ∞ ; 165 k Ω
- 15.61 5770

- 15.63 (250 μA , 4.92 V), (6.10 μA , 4.30 V), (494 μA , 5.00 V); 4230, ∞ ; 97.5 k Ω
- 15.67 (49.5 μA , 15.0 V), (360 μA , 14.3 V), (990 μA , 15.0 V); 12100, 101 k Ω ; 1.80 k Ω ; 66.3 M Ω ; v_2
- 15.69 (250 μA , 10.9 V), (2.00 mA, 9.84 V), (5.00 mA, 12.0 V); 868, ∞ ; 127 Ω
- 15.71 (300 μA , 5.10 V), (500 μA , 2.89 V), (2.00 mA, 5.00 V), 528, ∞ , 341 Ω
- 15.73 (300 μA , 5.55 V), (500 μA , 2.89 V), (2.00 mA, 5.00 V), 2810, ∞ , 341 Ω
- 15.75 (99.0 μA , 4.96 V), (500 μA , 3.41V), (2.00 mA, 5.00 V), 11400, 50.5 k Ω , 224 Ω
- 15.77 (49.5 μA , 13.0 V), (98.0 μA , 13.7 V), (735 μA , 18.0 V); 2700, 101 k Ω , 3.37 k Ω ; [undefined, 12.3 V]; 0.689 mV
- 15.79 No, R_{id} must be reduce or R_{out} must be increased.
- 15.81 (24.8 μA , 17.3 V), (24.8 μA , 17.3 V), (9.62 μA , 15.9 V), (490 μA , 16.6 V), (49.0 μA , 17.3 V), (4.95 mA, 18.0 V), 88.5 dB, 202 k Ω , 18.1 Ω
- 15.83 36.8 μA
- 15.85 196 μA
- 15.89 22.8 μA
- 15.91 5 mA, 0 mA, 10 mA, 12.5 percent
- 15.93 66.7 percent
- 15.95 70.0 mA, 19.6 V
- 15.97 23.5 μA
- 15.98 6.98 mA, 0 mA
- 15.99 25.0 m Ω
- 15.101 (a) 22.8 μA , 43.9 M Ω
- 15.103 (a) 144 μA , 7.83 M Ω
- 15.105 Two of many: 75 k Ω , 62 k Ω , 150 Ω ; 68 k Ω , 12 k Ω , 1 k Ω
- 15.107 0, ∞
- 15.109 88.6 μA , 18.6 M Ω
- 15.111 94.6 μA , 13.1 M Ω
- 15.113 17.0 μA , 131 M Ω
- 15.115 430 k Ω , 200 k Ω , 33 k Ω
- 15.117 97.2 μA , 27.4 M Ω , 201 μA , 11.0 M Ω , 391 μA , 4.30 M Ω
- 15.119 44.1 μA , 22.1 M Ω , 10.1 μA , 209 M Ω
- 15.122 100 μA , 6.57×10^{11} Ω
- 15.123 (4.62 μA , .62 V), (9.34 μA , 9.03 V); 40.9 dB, 96.5 dB
- 15.125 $\beta_{ol}\mu_{f1}/2$, For typical numbers: 20(100)(70) =140,000 or 103 dB
- 15.127 3σ limits: $I_O = 199 \mu\text{A} \pm 32.5 \mu\text{A}$, $R_{OUT} = 11.8 \text{ M}\Omega \pm 2.6 \text{ M}\Omega$
 3σ limits: $I_O = 201 \mu\text{A} \pm 34.7 \mu\text{A}$, $R_{OUT} = 21.7 \text{ M}\Omega \pm 3.6 \text{ M}\Omega$
- 15.129 2.50 mV; 5.02 mV; 2%
- 15.131 7.7%, 0.813 μA , 0.855 μA , ($I_{OS} = -42.0 \text{ nA}$)

- 15.133 25.0 mV, 1.2%, 0.4%
- 15.135 84.3 μA , 164 μA , 346 μA , 909 k Ω , 455 k Ω , 227 k Ω
- 15.137 75.0 μA , 150 μA , 300 μA , 0.124 Lsb 0.187 LSB,).613 LSB
- 15.139 274 μA , 383 k Ω , 574 μA , 192 k Ω
- 15.143 (a) 631 μA , 103 k Ω , 1.02 mA, 61.8 k Ω
- 15.145 507 k Ω , 93.1 μA ; 599 k Ω , 93.2 μA
- 15.147 185 μA , 299 μA
- 15.149 472 μA , 759 μA ; 479 μA , 759 μA ; 430 μA , 692 μA
- 15.151 63.8 k Ω , 11.8 μA , 123 μA
- 15.153 10
- 15.155 63.8 k Ω , 0.667
- 15.157 15.7 μA , 5.10 M Ω
- 15.159 5.35 k Ω
- 15.161 115 k Ω , 17.0 k Ω , 0.297
- 15.163 22.7 μA , 18.3 M Ω ; 45.5 μA , 9.17 M Ω
- 15.165 49.6 μA , 55.8 M Ω ; 146 μA , 19.0 M Ω ; 2770; 1.40 V
- 15.169 21.8 μA , 80/1
- 15.171 $2/g_{m3}$
- 15.173 3.80/1
- 15.175 17.5 μA , 1.16 G Ω ; 20.3 kV; 2.11 V
- 15.177 18.4 μA , 3.89 nA
- 15.179 (b) 50 μA , 240 M Ω ; 12.0 kV; 3.07 V
- 15.181 16.9 μA , 163 M Ω , 2750 V; $2V_{BE} = 1.40$ V
- 15.183 2.86 k Ω
- 15.185 (a) 64.0 μA , 3.59 M Ω
- 15.187 8.22 k Ω
- 15.189 318 μA , 295 μA , 66.5 μA
- 15.193 14.5 k Ω , 225 k Ω
- 15.195 11.4 k Ω , 210 k Ω
- 15.197 $I_{C1} = 140$ μA , $I_{C2} = 47.8$ μA
 $S_{V_{CC}}^{I_{C1}} = 2.92 \times 10^{-2}$ $S_{V_{CC}}^{I_{C2}} = 9.92 \times 10^{-3}$
- 15.199 $n > 1/3$
- 15.201 26.4 μA
- 15.203 (b) $I_{D1} = 8.19$ μA $I_{D2} = 7.24$ μA $S_{V_{DD}}^{I_{D1}} = 7.75 \times 10^{-2}$ $S_{V_{DD}}^{I_{D2}} = 6.31 \times 10^{-2}$
 The currents differ considerably from the hand calculations. The currents are quite sensitive to the value of λ . The hand calculations used $\lambda = 0$. If the simulations are run with $\lambda = 0$, then the results are identical to the hand calculations.
- 15.205 5.23 μA , 6.00 μA , 3.45 μA

- 15.207** $I_{C2} = 15.2 \mu\text{A}$ $I_{C1} = 28.5 \mu\text{A}$ - Similar to hand calculations.
 $S_{V_{CC}}^{I_{C1}} = 1.81 \times 10^{-3}$ $S_{V_{CC}}^{I_{C2}} = 7.07 \times 10^{-4}$
- 15.209** 462 μA , 308 μA
- 15.211** 107 μA
- 15.212** 79.1, 6.28×10^{-5} , 122 dB
- 15.214** 47.2, 6.97×10^{-5} , 117 dB
- 15.216** 1200, 4×10^{-3} , 110 dB, $\pm 2.9 \text{ V}$
- 15.220** (100 μA , 8.70 V), (100 μA , 7.45 V), (100 μA , -2.50 V), (100 μA , -1.25 V), 323, 152
- 15.222** (125 μA , 1.54 V), (125 μA , -2.79 V), (125 μA , 2.50 V), (125 μA , 1.25 V); 19600
- 15.225** 171 μA
- 15.226** (b) 100 μA
- 15.227** (250 μA , 5.00 V), (250 μA , 5.00 V), (250 μA , -1.75 V), (250 μA , -1.75 V), (500 μA , -3.21 V), (135 μA , 5.00 V), (135 μA , -5.00 V), (250 μA , 2.16 V), (500 μA , 3.25 V), (500 μA , 3.21 V), (500 μA , 3.58 V); 4130; 2065
- 15.229** 12,600
- 15.231** (250 μA , 7.50 V), (250 μA , 7.50 V), (250 μA , -1.75 V), (1000 μA , -5.13 V), (330 μA , 7.50 V), (330 μA , -7.50 V), (1000 μA , 4.75 V), (250 μA , 2.16 V), (500 μA , 5.75 V), (1000 μA , 5.13 V), 3180
- 15.233** (b) 42.9/1 (c) 14800
- 15.237** 7.78, 574 Ω , 3.03×10^5 , 60.0 k Ω
- 15.239** $\pm 1.4 \text{ V}$, $\pm 2.4 \text{ V}$
- 15.240** (a) 9.72 μA , 138 μA , 46.0 μA
- 15.241** 271 k Ω , 255 Ω
- 15.243** $V_{EE} \geq 2.8 \text{ V}$, $V_{CC} \geq 1.4 \text{ V}$; 3.8 V, 2.4 V
- 15.245** 2.84 M Ω , 356 k Ω . 6.11×10^5
- 15.248** (100 μA , 15.7 V), (100 μA , 15.7 V), (50 μA , -12.9 V), (50 μA , -0.700 V), (50 μA , -0.700 V), (50 μA , -12.9 V), (50 μA , 1.40 V), (50 μA , 1.40 V), (1.00 μA , 29.3 V), (100 μA , 0.700 V), (100 μA , 13.6 V); 1.00 mS, 752 k Ω
- 15.248** (50 μA , 15.7 V), (50 μA , 15.7 V), (50 μA , 12.9 V), (50 μA , 12.9 V), (50 μA , 1.40 V), (50 μA , 1.40 V), (1.00 μA , 29.3 V), (100 μA , 1.40 V), (1 μA , 0.700 V), (1 μA , 13.6 V); 1.00 mS, 864 k Ω

Chapter 16

16.1 $A_{mid} = 50$, $F_L(s) = \frac{s^2}{(s+2)(s+30)}$, yes, $A_v(s) \approx 50 \frac{s}{(s+30)}$, 4.77 Hz, 4.80 Hz

16.4 300, $\frac{1}{\left(1 + \frac{s}{10^4}\right)\left(1 + \frac{s}{10^5}\right)}$, yes, 1.58 kHz, 1.58 kHz

16.7 300, $\frac{s^2}{(s+1)(s+2)}$, $\frac{1}{\left(1 + \frac{s}{500}\right)\left(1 + \frac{s}{1000}\right)}$, 0.356 Hz, 142 Hz; 0.380 Hz, 133 Hz

16.9 (b) -16.5, 7.58 Hz

16.10 (b) -14.1 (23.0 dB), 11.5 Hz

16.11 1.52 μF ; 1.50 μF , 49.3 Hz

16.13 (b) 0.33 μF ; 1770 Hz

16.14

$$A_v(s) = A_{mid} \frac{s^2}{(s + \omega_1)(s + \omega_2)} \mid \omega_1 = \frac{1}{C_1 \left(R_S + R_E \parallel \frac{1}{g_m} \right)} \mid \omega_2 = \frac{1}{C_2 (R_C + R_3)} \mid 2 \text{ zeros at } \omega = 0$$

19.4 dB, 151 Hz; -5.0 V, 7.9 V

16.16 123 Hz; 91 Hz

16.18 -131, 50.0 Hz, 12.0 V

16.19 45.5 Hz

16.21 7.24 dB, 19.2 Hz

16.23 0.739, 15.5 Hz, 12.0 V

16.24 0.15 μF

16.25 0.56 μF

16.27 Cannot reach 1 Hz; $f_L = 13.1$ Hz for $C_1 = \infty$, limited by C_3

16.29 0.39 μF

16.31 308 ps

16.33 (a) 22.5 GHz

16.34 -117; -113

16.35 0.977; 0.978

16.37 -5100, -98.0, -5000, -100, 2% error; -350, -42.9, -300, -50, 18% error

16.39 Real roots: -100, -20, -15, -5

16.41 -90.0, 1.96 MHz, 176 MHz

16.43 -15.7, 849 kHz

16.45 -12.0, 2.75 MHz, 33 MHz

- 16.49 61.0 pF, 303 MHz
- 16.51 $1/10^5 RC$; $1/10^6 RC$; $1/sRC$
- 16.53 39.2 dB, 5.53 MHz
- 16.55 -114, 1.12 MHz, 128 MHz, 531 MHz
- 16.57 865Ω , -31.9, 160 MHz
- 16.59 -29.3, 7.41 MHz
- 16.61 300Ω , 1 k Ω
- 16.62 -1300; -92.3; -100, -1200
- 16.63 13.1, 64.4 MHz
- 16.65 9.14, 40.9 MHz
- 16.68 2.30, 10.9 MHz
- 16.69 3.19, 11.3 MHz, 20.6Hz
- 16.71 0.964, 114 MHz
- 16.73 -1.46 dB, 75.4 MHz
- 16.75 $C_{GD} + C_{GS}/(1 + g_m R_L)$ for $\omega \ll \omega_T$
- 16.77 Using a factor of 2 margin: 8 GHz, 19.9 ps
- 16.79 672 mA - not a realistic design. A different FET is needed.
- 16.81 8.33 MHz
- 16.82 393 kHz, 640 kHz
- 16.85 294 kHz
- 16.87 48.2 kHz
- 16.89 66.2 KHz
- 16.91 568 kHz
- 16.93 2.01 MHz
- 16.95 54.3 dB, 833 Hz, 526 kHz
- 16.96 22.5 MHz, -41.1, 2.90
- 16.97 20.1 pF, 12.6, $n = 2.81$, 21.9 pF
- 16.98 15.2 MHz; 27.5 MHz
- 16.99 13.4 MHz, 7.98, $112/\underline{-90^\circ}$; 4.74 MHz, 5.21, $46.1/\underline{-90^\circ}$
- 16.100 10.1 MHz, 3.96, -35.4; 10.9 MHz, 16.4, -75.1
- 16.103 65 pF; 240, -4.41×10^4 , 25.1 kHz
- 16.105 67.3 pF; 40

Chapter 17

- 17.1 (b) 2000, 5.00, 0.05%
- 17.3 1/101, 99.0, -99.0
- 17.5 80 dB
- 17.7 100 dB
- 17.8 $1/(1+A\beta)$; 9.99×10^{-3} percent
- 17.9 (b) shunt-series feedback (d) series-shunt feedback
- 17.13 8.00×10^5 , 20 S
- 17.15 9.96, 6.58 M Ω , 3.18 Ω
- 17.17 8.27, 1.51 M Ω , 3.60 Ω
- 17.18 0.999, 43.9 M Ω , 2.49 Ω , 98.9 μ S
- 17.21 -36.0 k Ω ; 11.1 Ω ; 0.790 Ω
- 17.23 82.2 Ω ; 46.2 Ω ; -32.4 k Ω ; -32.4
- 17.25 -446 k Ω , 50.2 k Ω , 2.45 k Ω
- 17.27 0.973, 973 Ω
- 17.28 1.00, 36.0 Ω
- 17.31 1/10.5 k Ω , 2.82 k Ω , -1/11, 4000; -11.0, 35.2 Ω , 3.57 M Ω
- 17.33 -1.00, 36.5 M Ω , 14.9 M Ω
- 17.37 $\beta_o/(\beta_o + 1)$, $2/g_m$, $(\beta_o + 1)r_o$
- 17.39 $\mu_{f4}(1 + \mu_{f3})r_{o2}$, 21.9 G Ω
- 17.41 58.9 dB
- 17.43 8.95
- 17.45 $(s/R_2C_2)/[s^2 + s(1/R_2C_2 + 1/(R_1||R_2)C_1) + 1/R_1R_2C_1C_2]$
- 17.47 816
- 17.49 18.5
- 17.53 41.2 Ω , 21.3 Ω
- 17.55 38.0 M Ω , 2.48 Ω
- 17.57 $\mu_{f4}r_{o2}(1 + \mu_{f3})$, $1/g_{m3}$
- 17.59 80 dB, 1 kHz, 1 MHz; 101 MHz, 9.90 Hz; 251 MHz, 3.98 Hz
- 17.61 100 dB, 1 kHz, 1 MHz; $(-0.637 \pm j9.98)$ Hz, $(-6.37 \pm j100)$ MHz; $(-2.20 \pm j19.9)$ Hz, $(-6.37 \pm j49.8)$ MHz
- 17.63 19.0 Hz, 3.04 MHz
- 17.65 +1, 9.99%
- 17.67 8.1°; 5.1°
- 17.69 110 kHz; $A \leq 2048$; larger
- 17.71 yes, but almost no phase margin; 0.4°
- 17.74 90.0°

- 17.75 yes, but almost no phase margin; 1.83°
- 17.76 12° , yes, 50°
- 17.81 26°
- 17.83 phase margin is undefined; $|T(j\omega)| < 1$ for all ω
- 17.85 1.8°
- 17.86 38.4°
- 17.87 10.6 MHz, 33.3 V/ μ s
- 17.89 8.1 MHz, -100° ; 8.0 MHz, -92°
- 17.91 159 MHz, 50 V/ μ s
- 17.93 12.5 V/ μ s
- 17.94 21.2 MHz
- 17.96 $1/RC$, $2R$
- 17.97 $0.5774/RC$, 1.83
- 17.98 63.7 kHz, 6.85 V
- 17.100 18.4 kHz, 10.7 V
- 17.102 17.5 MHz, 20.1 MHz, 36.3 MHz, 0.211 mS, 5.28 μ A
- 17.103 5.17 MHz, 4.53 MHz
- 17.105 9.00 MHz, 1.20
- 17.107 7.96 MHz, 8.11 MHz, 1.05
- 17.109 7.5 MHz, 80 V_{p-p}
- 17.110 7.96 MHz
- 17.111 11.1 MHz, 18.1 MHz, 1.00
- 17.112 15.9155 mH, 15.9155 fF; 10.008 MHz, 10.003 MHz
- 17.113 9.190 MHz; 9.190 MHz
- 17.114 9.28 MHz; 9.19 MHz