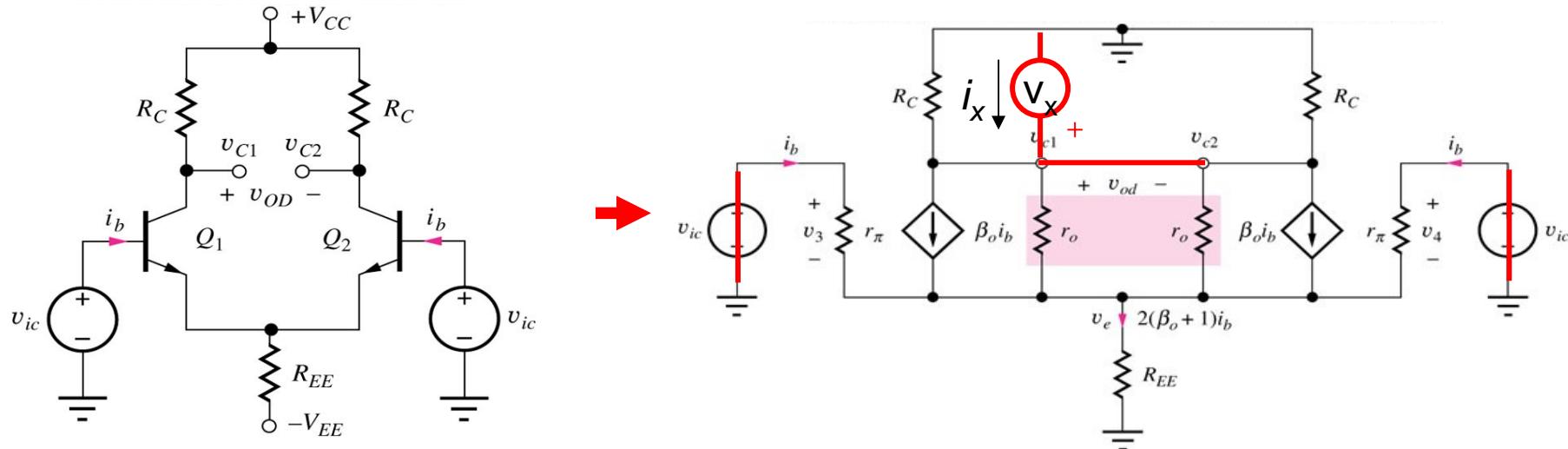


Output Resistance – for CM output



To find CM R_{out} , tie v_{C1} and v_{C2} together and apply a test voltage between v_{C1} and ground.

KCL at collector:

$$\text{KCL at emitter: } \frac{-v_e}{r_\pi}(1+\beta)2 + 2\frac{v_x - v_e}{r_o} = \frac{v_e}{R_{EE}}$$

$$v_e 2 \left[\frac{1+\beta}{r_\pi} + \frac{1}{r_o} + \frac{1}{2R_{EE}} \right] = 2 \frac{v_x}{r_o}$$

$$v_e = v_x \frac{1}{r_o} \left[\frac{\beta}{r_\pi} + \frac{1}{2R_{EE}} \right]^{-1} \quad \text{for } \frac{1+\beta}{r_\pi} \gg \frac{1}{r_o} \quad (1)$$

and $\beta \gg 1$

$$\begin{aligned} i_x &= 2 \left(\beta \frac{-v_e}{r_\pi} + \frac{v_x - v_e}{r_o} \right) + 2 \frac{v_x}{R_C} \\ &= -2v_e \left(\frac{\beta}{r_\pi} + \frac{1}{r_o} \right) + 2 \left(\frac{1}{R_C} + \frac{1}{r_o} \right) v_x \\ &\approx -2v_e \frac{\beta}{r_\pi} + 2 \left(\frac{1}{R_C} + \frac{1}{r_o} \right) v_x \end{aligned} \quad (2)$$



Output Resistance – for CM output

Put (2) into (1), we obtain:

$$R_{out} \equiv \frac{v_x}{i_x} = \frac{1}{2} \left[\frac{1}{r_o} \frac{1}{1 + 2\beta \frac{R_{EE}}{r_\pi}} + \frac{1}{R_c} \right]^{-1}$$
$$\approx \frac{1}{2} R_c$$

