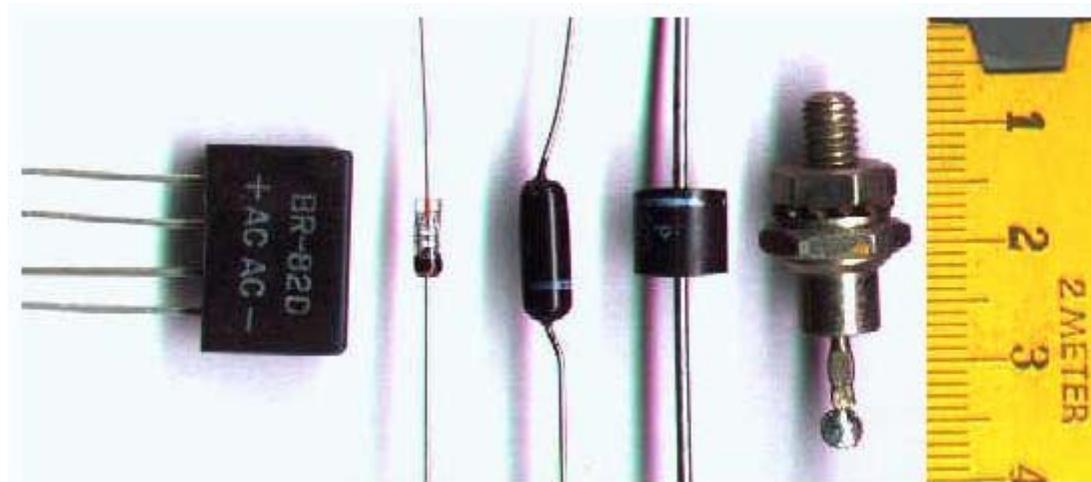


Week 2: PN Junction Diode



types of diodes - from the German wikipedia



Topics to cover...


- Physical operation of pn junction diode
- Terminal I-V characteristics
- Breakdown and junction capacitances
- Diode circuits analysis

- *Reading Assignment: Chap 3.1-3.7, 3.10-3.13 of Jaeger & Blalock*



Why diodes?

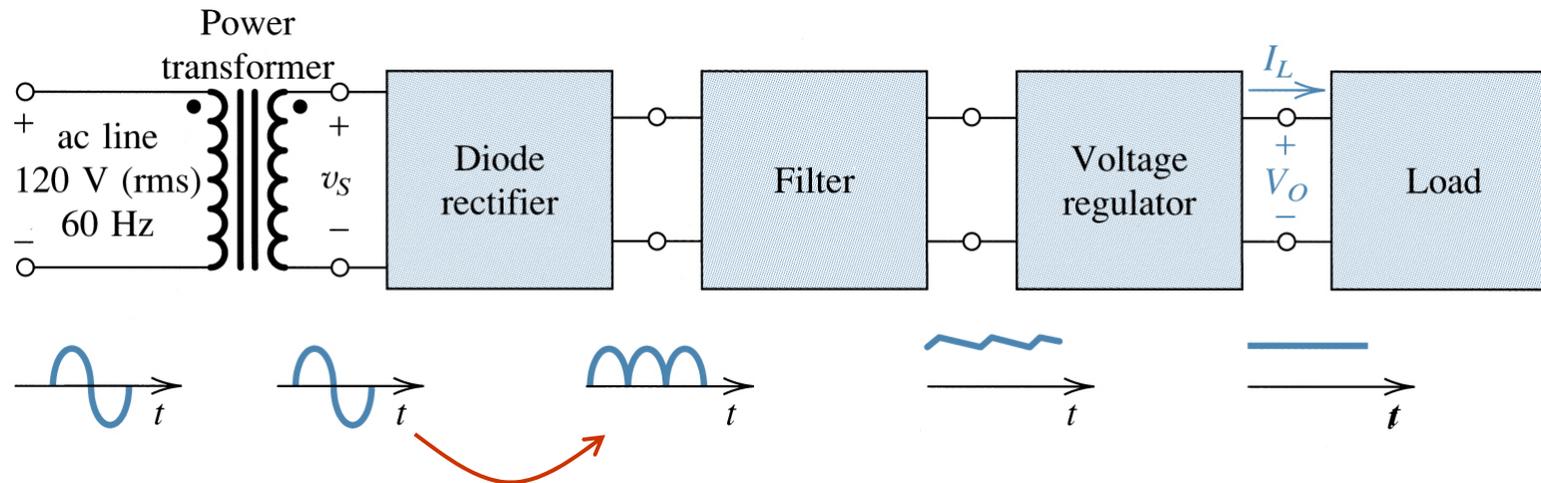- R, C, L are linear circuit elements
- Many signal processing functions need non-linear elements, like signal rectification (to convert negative signal to be positive).




Nonlinear signal processing

An AC-DC converter




Why diodes?

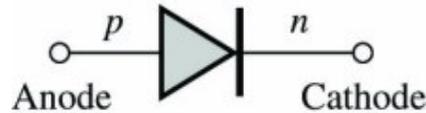- Basic function of diode: to allow current to flow only in one direction.




Diode symbol

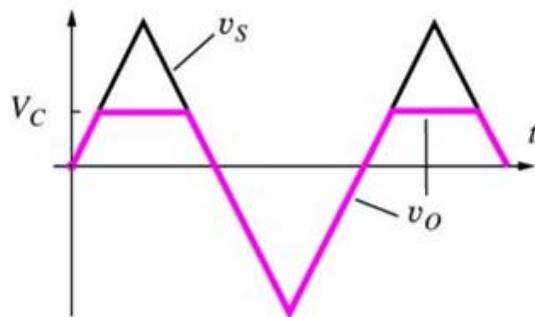- Applications:
 - Rectifiers
 - Waveform clipping and clamping circuits
 - DC-DC converters





Waveform clipping

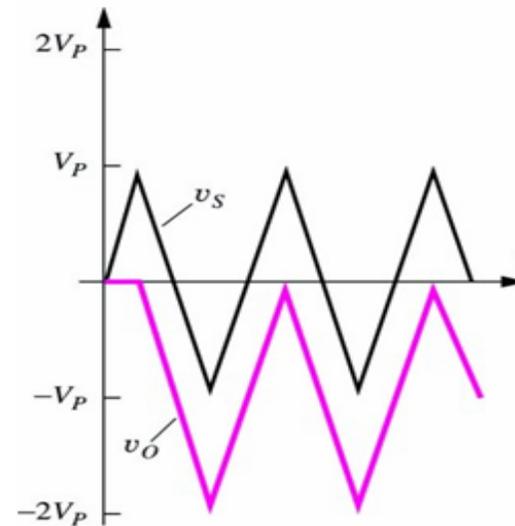


Waveform clamping



Physical Structure of pn Junction Diode

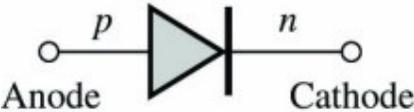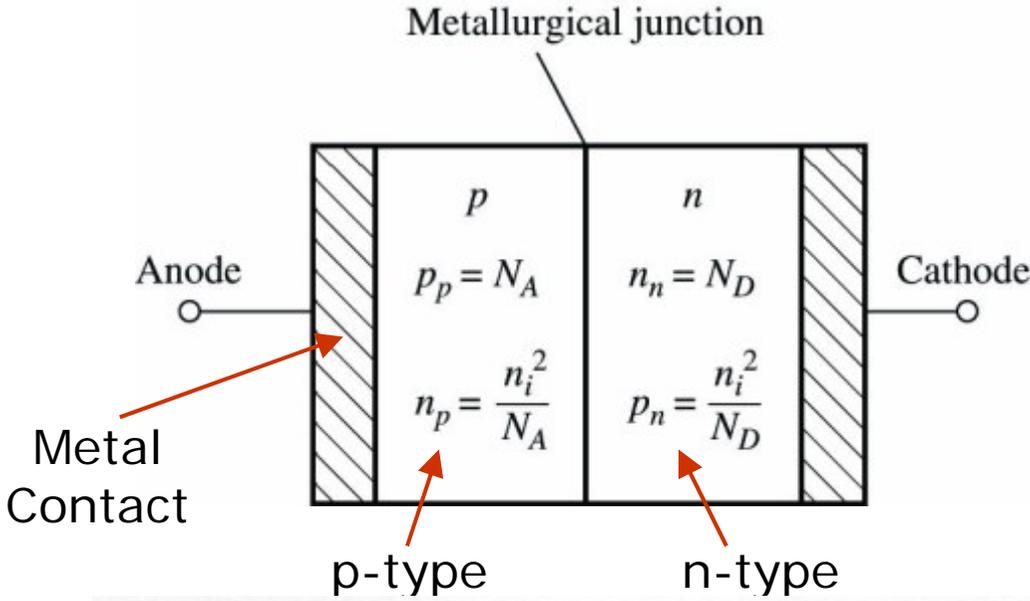

Diode symbol

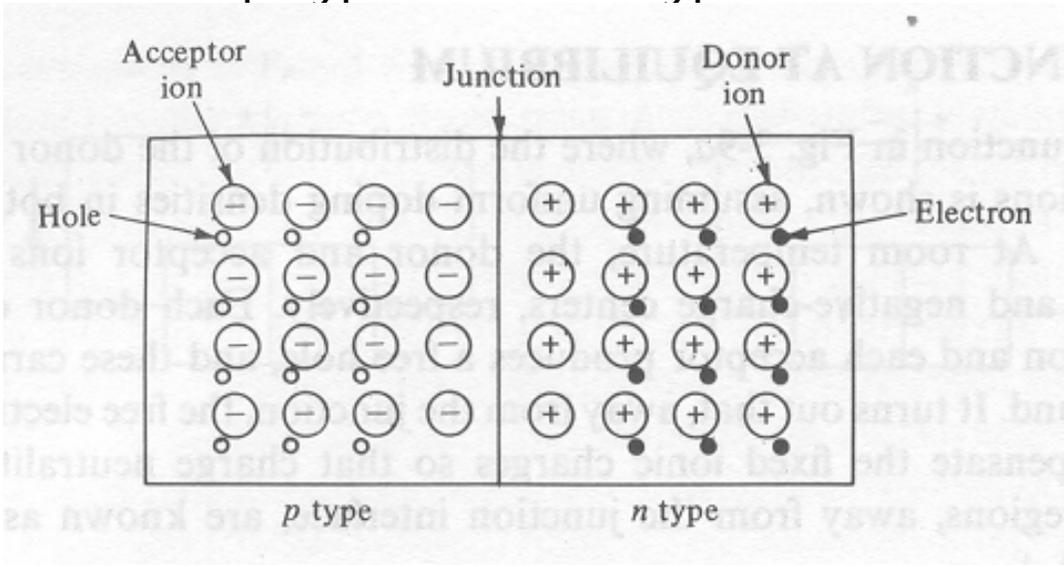


Note:
both p and n regions
are charge neutral.




Diffusion of Electrons and Holes

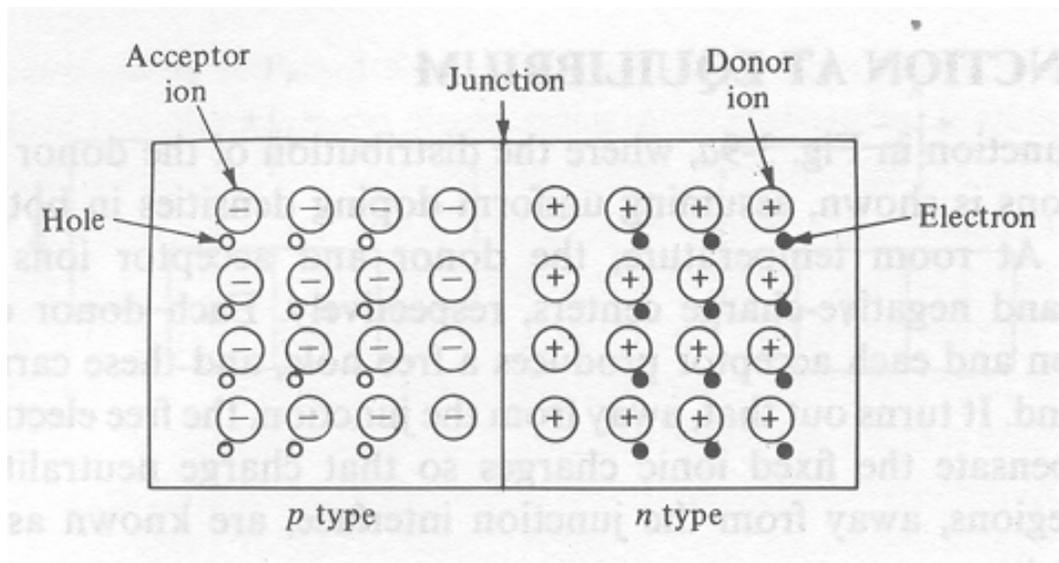- Electrons tend to diffuse from n side to p side
- Holes tend to diffuse from p side to n side
- The resulted current is diffuse current. It is due to the movement of majority carriers.
- Q: What are the directions of electron and hole diffusion currents?




Diffusion of Electrons and Holes

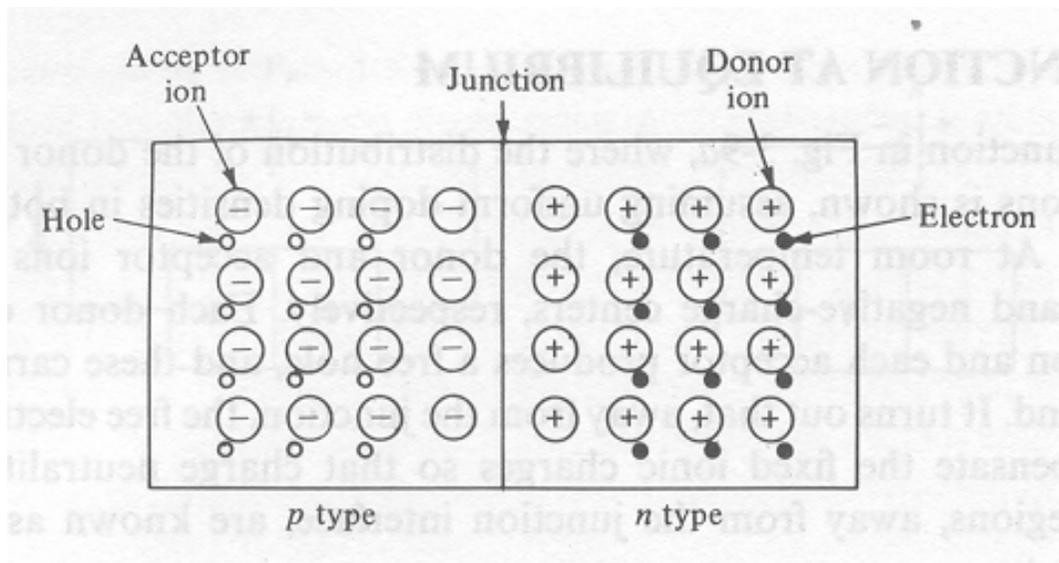- If diffusion processes were to continue unabated, there would eventually be a uniform distribution of electrons and holes.
- But there is a counter force...




Formation of Depletion Region

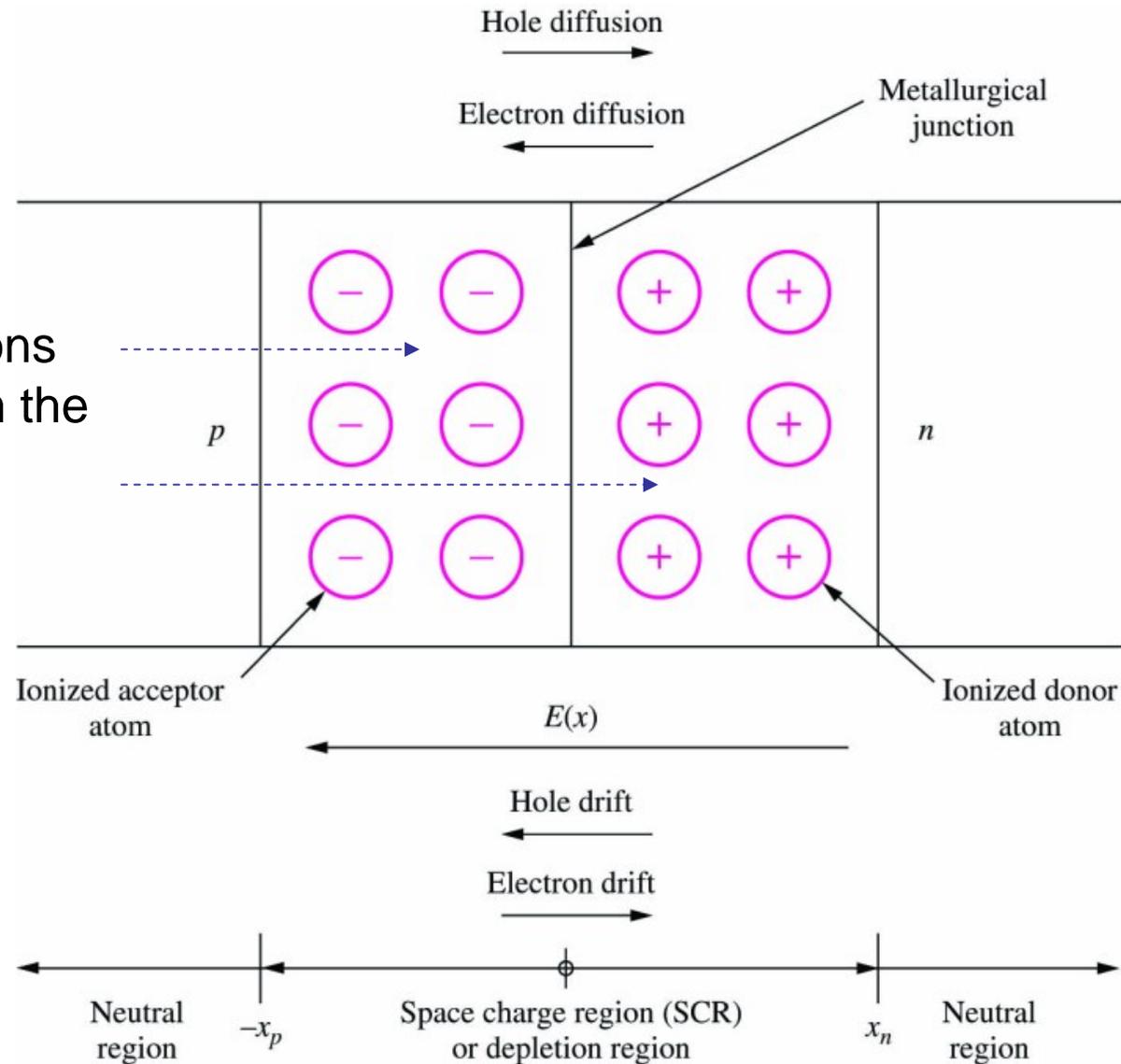Holes and electrons are depleted from the dopant atoms



Built-in Electric Field

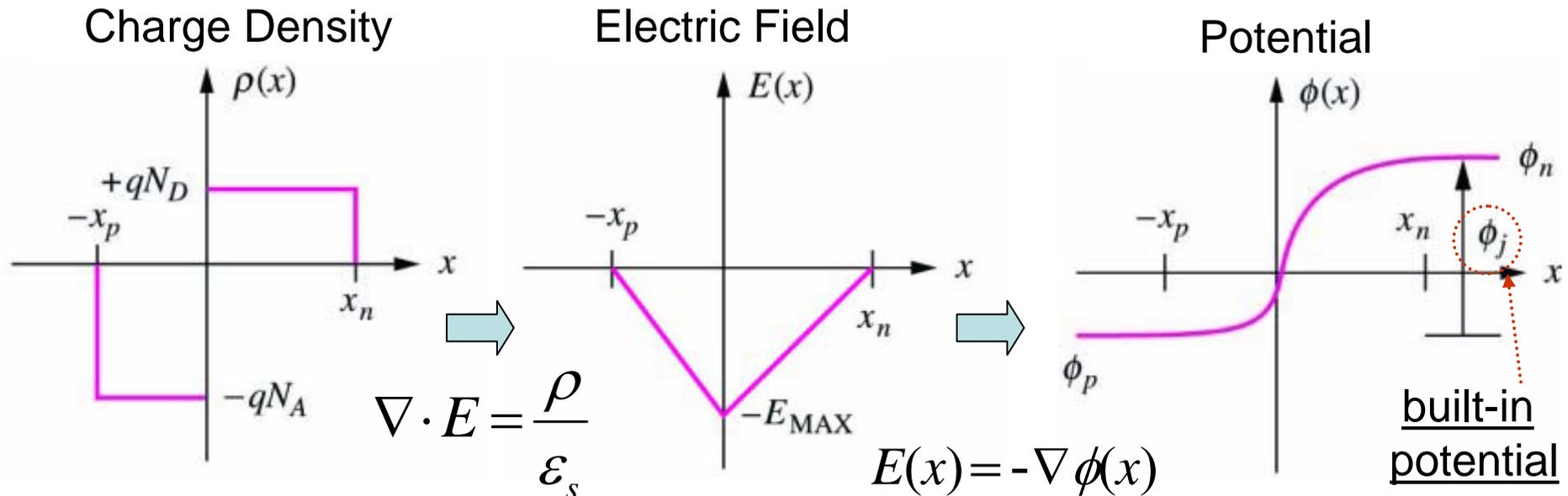

$$E(x) = \frac{1}{\epsilon_s} \int \rho(x) dx$$

(1 dimension)


Solid-state physics tells us that:

$$\phi_j = \frac{kT}{q} \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

The resulting potential gives rise to *drift currents*.



Built-in Electric Field

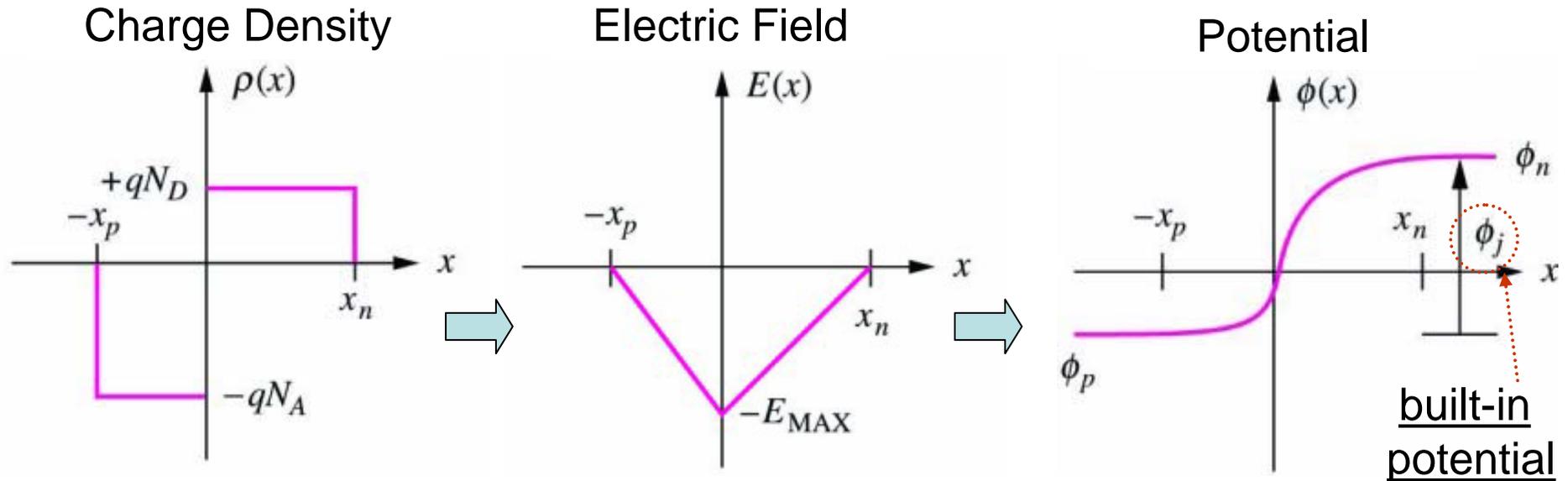


Direction of drift current:

Drift current is due to the movement of minorities.

For a diode with no external connections, the total current through it must be zero. Therefore, under thermal equilibrium (no external voltage), drift and diffusion currents have the same magnitude but opposite direction.



Width of Depletion Region


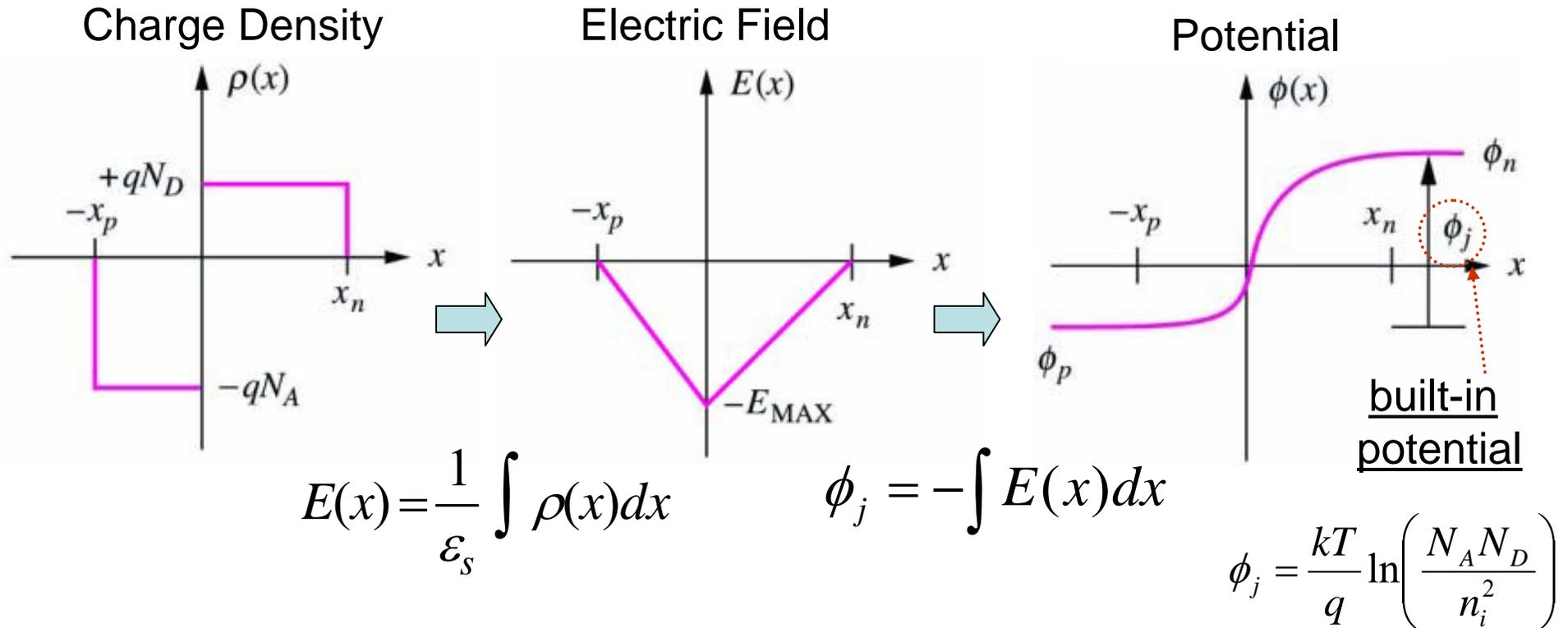


Depletion width is an important device parameter.
It can be shown that:

$$w_{d0} = (x_n + x_p) = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) \phi_j}$$



Forward-Biased PN Junction

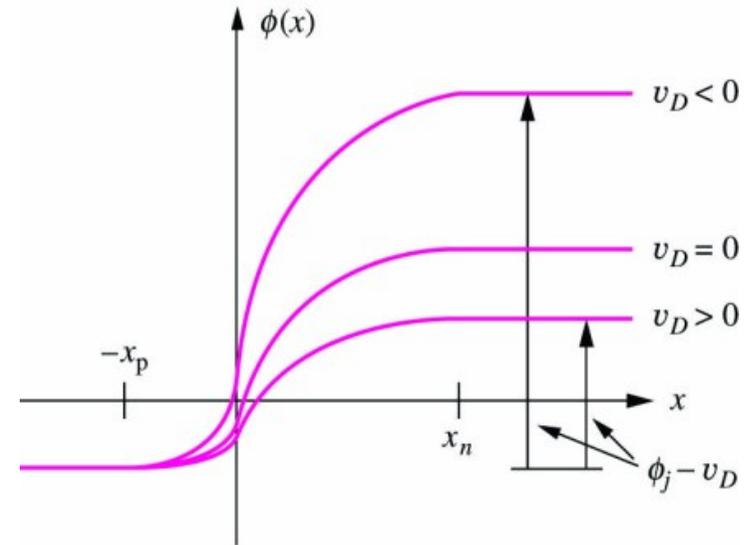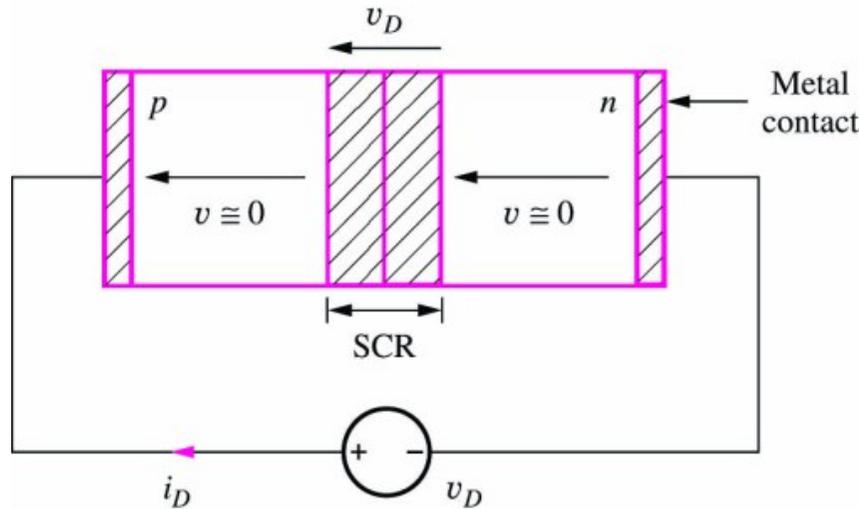

Forward biasing means applying an external voltage $v_D > 0$:


- Built-in potential drops (barrier lowers)
- Majority electrons and holes easily cross the junction
- Balance between diffusion and drift breaks
- Current appears at the terminals:

$$i_D = I_{\text{diffusion}} - I_{\text{drift}} > 0$$

In fact, $I_{\text{diffusion}}$ increases exponentially with V_D .



Reverse-Biased PN Junction

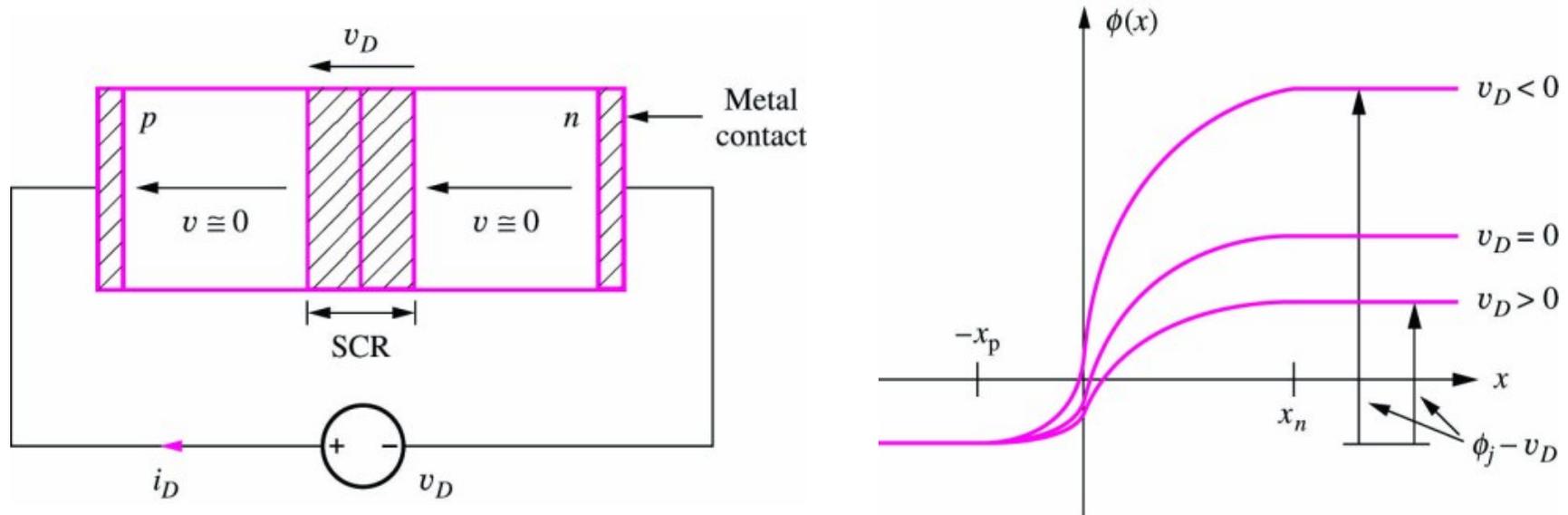

Reverse biasing means applying an external voltage $v_D < 0$:

- Built-in potential increases/barrier increases;
- Majority electrons and holes can hardly cross the junction
 - Diffusion decreases
- Drift current almost unchanged as there are little supply of carriers (minorities).

$$\therefore i_D = I_{\text{diffusion}} - I_{\text{drift}} < 0 \text{ and tends to } -I_{\text{drift}}$$




Topics to cover...

- Physical operation of pn junction diode
- Terminal I-V characteristics
- Breakdown and junction capacitances
- Diode circuits analysis



Diode Terminal I-V Characteristics

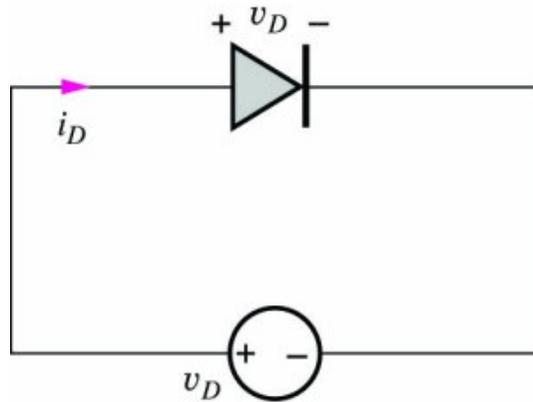

$$i_D = I_S \left[\exp\left(\frac{v_D}{V_T}\right) - 1 \right]$$

where I_S = reverse saturation current [A]

v_D = voltage applied to diode [V]

$V_T = kT/q$ = thermal voltage [V] (25 mV at room temp.)

q = electronic charge [1.60×10^{-19} C]

k = Boltzmann's constant [1.38×10^{-23}

J/K]

T = absolute temperature [K]



Diode Current for Reverse, Zero, and Forward Bias

- Reverse bias:

$$i_D = I_S \left[\exp\left(\frac{v_D}{V_T}\right) - 1 \right] \approx I_S [0 - 1] \approx -I_S \quad \text{for } v_D < -4V_T$$

- Zero bias:

$$i_D = I_S \left[\exp\left(\frac{v_D}{V_T}\right) - 1 \right] = I_S [1 - 1] = 0$$

- Forward bias:

$$i_D = I_S \left[\exp\left(\frac{v_D}{V_T}\right) - 1 \right] \approx I_S \exp\left(\frac{v_D}{V_T}\right) \quad \text{for } v_D > 4V_T$$



Example 1

Problem: Find diode voltage for diode with given specifications

Given data: $I_S=0.1 \text{ fA}$, $I_D= 300 \text{ } \mu\text{A} / 1\text{mA}$

Assumptions: Room-temperature dc operation with $V_T=25\text{mV}$

Analysis:



With $I_S=0.1 \text{ fA}$, $I_D= 300 \text{ } \mu\text{A}$

$$V_D = V_T \ln\left(1 + \frac{I_D}{I_S}\right) = (0.025\text{V}) \ln\left(1 + \frac{3 \times 10^{-4} \text{A}}{10^{-16} \text{A}}\right) = 0.718\text{V}$$

With $I_D= 1 \text{ mA}$, $I_S=0.1 \text{ fA}$ $V_D=0.748\text{V}$



Diode i - v Characteristics

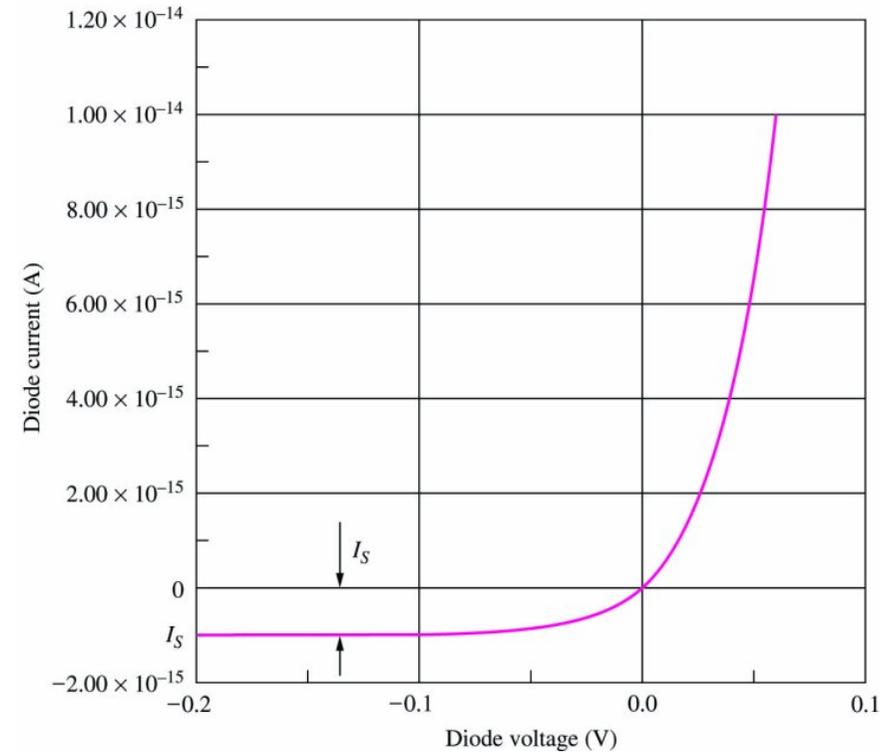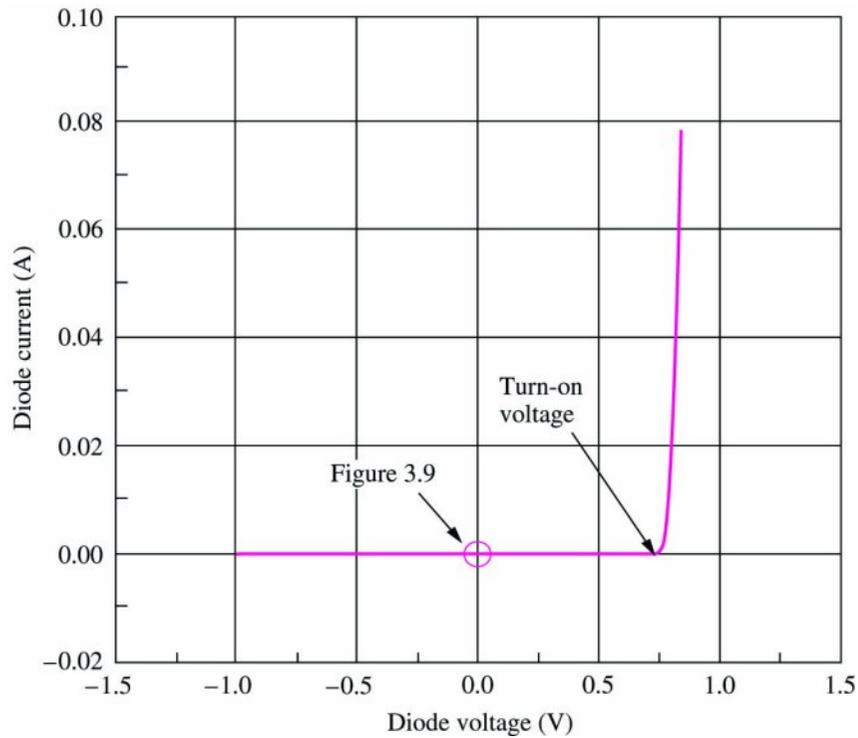


Turn-on voltage marks point of significant current flow.

I_s : reverse saturation current



Semi-log Plot of Diode Current

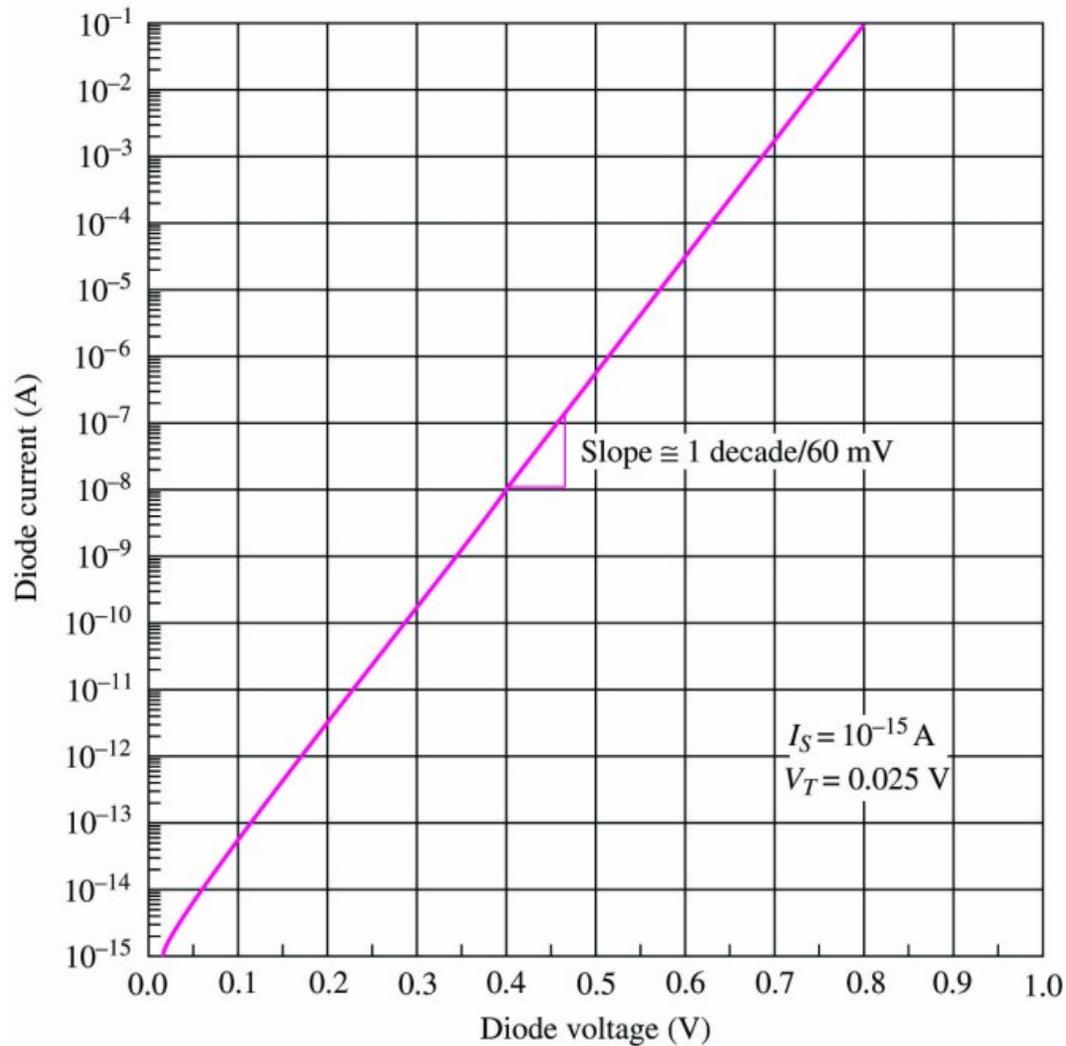


$$i_D = I_S \exp\left(\frac{v_D}{V_T}\right)$$

$$\text{Let } \frac{i_{D1}}{i_{D2}} = \exp\left(\frac{v_{D1} - v_{D2}}{V_T}\right) = 10$$

$$\begin{aligned} v_{D1} - v_{D2} &= V_T \ln 10 \\ &= 2.3V_T \\ &\approx 60 \text{ mV} \end{aligned}$$



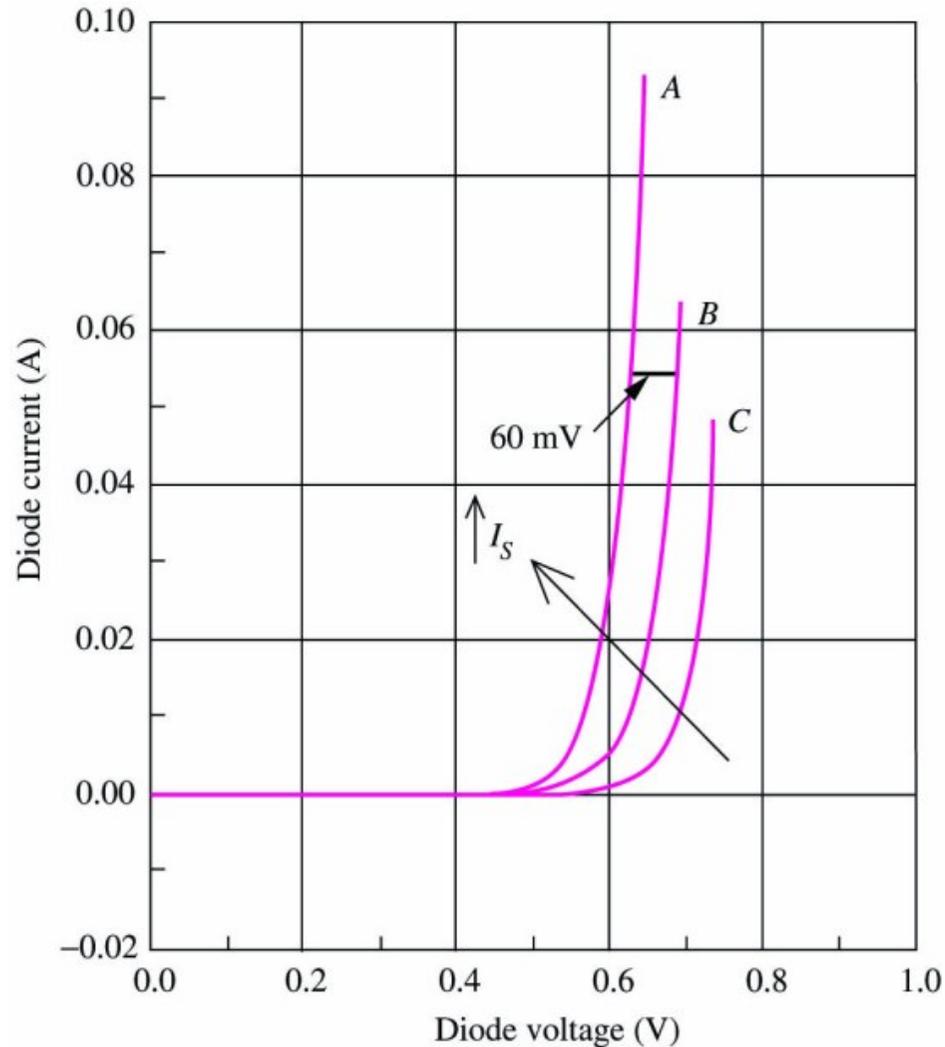Current for Three Different Values of I_S



$$I_{SA} = 10I_{SB} = 100I_{SC}$$

$$i_D = I_S \exp\left(\frac{v_D}{V_T}\right)$$

$$\text{Let } i_{DA} = i_{DB}$$

$$\frac{i_{SA}}{i_{SB}} = \exp\left(\frac{v_{DB} - v_{DA}}{V_T}\right) = 10$$

$$v_{DB} - v_{DA} = V_T \ln 10 \approx 60 \text{ mV}$$



Topics to cover...

- Physical operation of pn junction diode
- Terminal I-V characteristics
- Breakdown and junction capacitances
- Diode circuits analysis




Reverse Breakdown


Breakdown region:

Rapid increase in I_D when reverse bias voltage exceeds a break down voltage V_Z

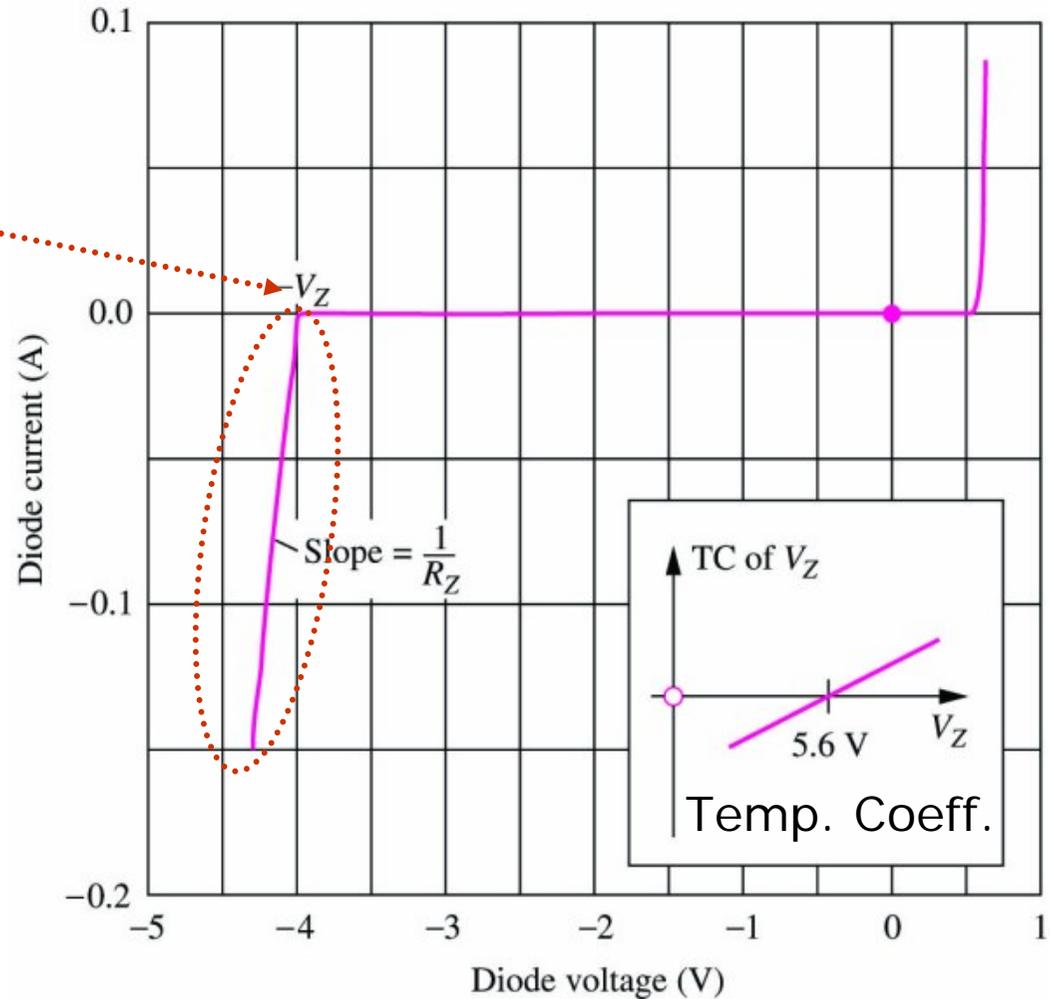Typical value of V_Z :
 $2\text{ V} \leq V_Z \leq 2000\text{ V}$



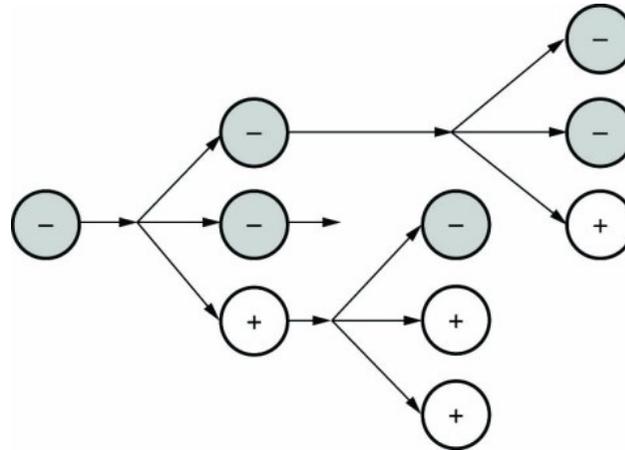Breakdown Mechanism 1: Avalanche Breakdown



- Carriers in the SCR are accelerated by the internal electric field and collide with fixed atoms
- As the reverse bias increases, the energy of the accelerated carriers increases, eventually breaking covalent bonds and generating electron-hole pairs
- The newly created carriers also accelerate, collide with atoms, and generate other electron-hole pairs. This process feeds on itself and leads to avalanche breakdown
- Si diodes with $V_Z > 5.6 \text{ V}$ enter breakdown through this mechanism




Breakdown Mechanism 2: Zener Breakdown

- Zener breakdown: occurs when the electric field in the depletion region increases to the point where it can break covalent bonds and generate electron-hole pairs.
- $V_Z < 5.6$ V for diodes entering breakdown through this mechanism
- In avalanche breakdown, V_Z increases with temperature
- In Zener breakdown, V_Z decreases with temperature
- Breakdown is not a destructive process provided that the maximum specified power dissipation is not exceeded




pn Junction Capacitance: Reverse Bias

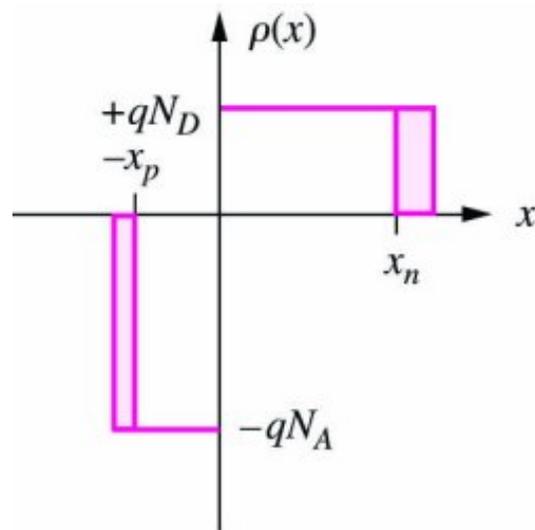
- External reverse bias leads to:
 - Increases of the built-in potential
 - Increases of the SCR, and thus fixed space charges
- This behaviors like a capacitor, and is referred to as depletion capacitance.



(a) Space charge density

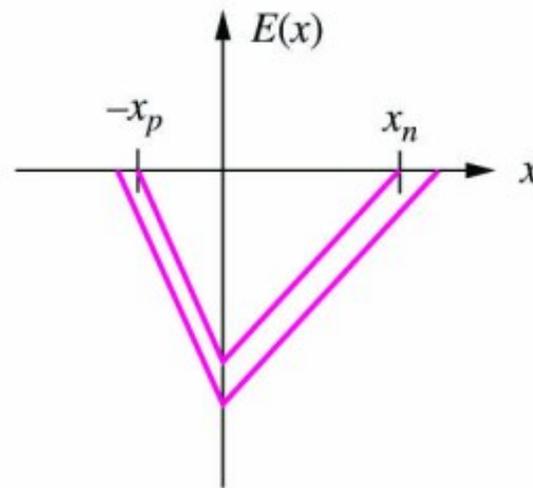


(b) Electric field

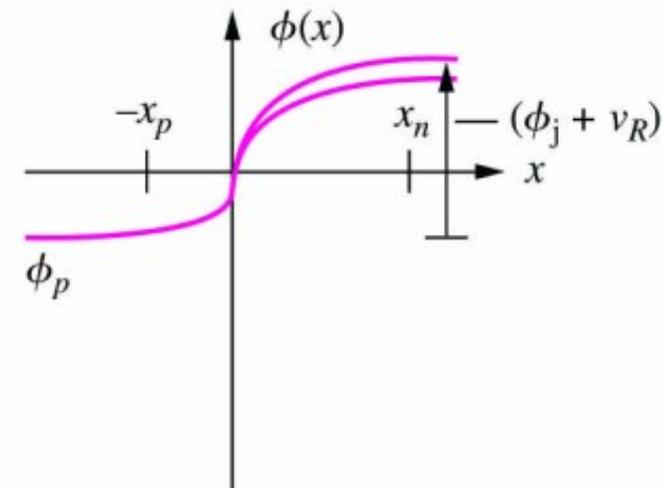

(c) Electrostatic potential



pn Junction Capacitance: Forward Bias

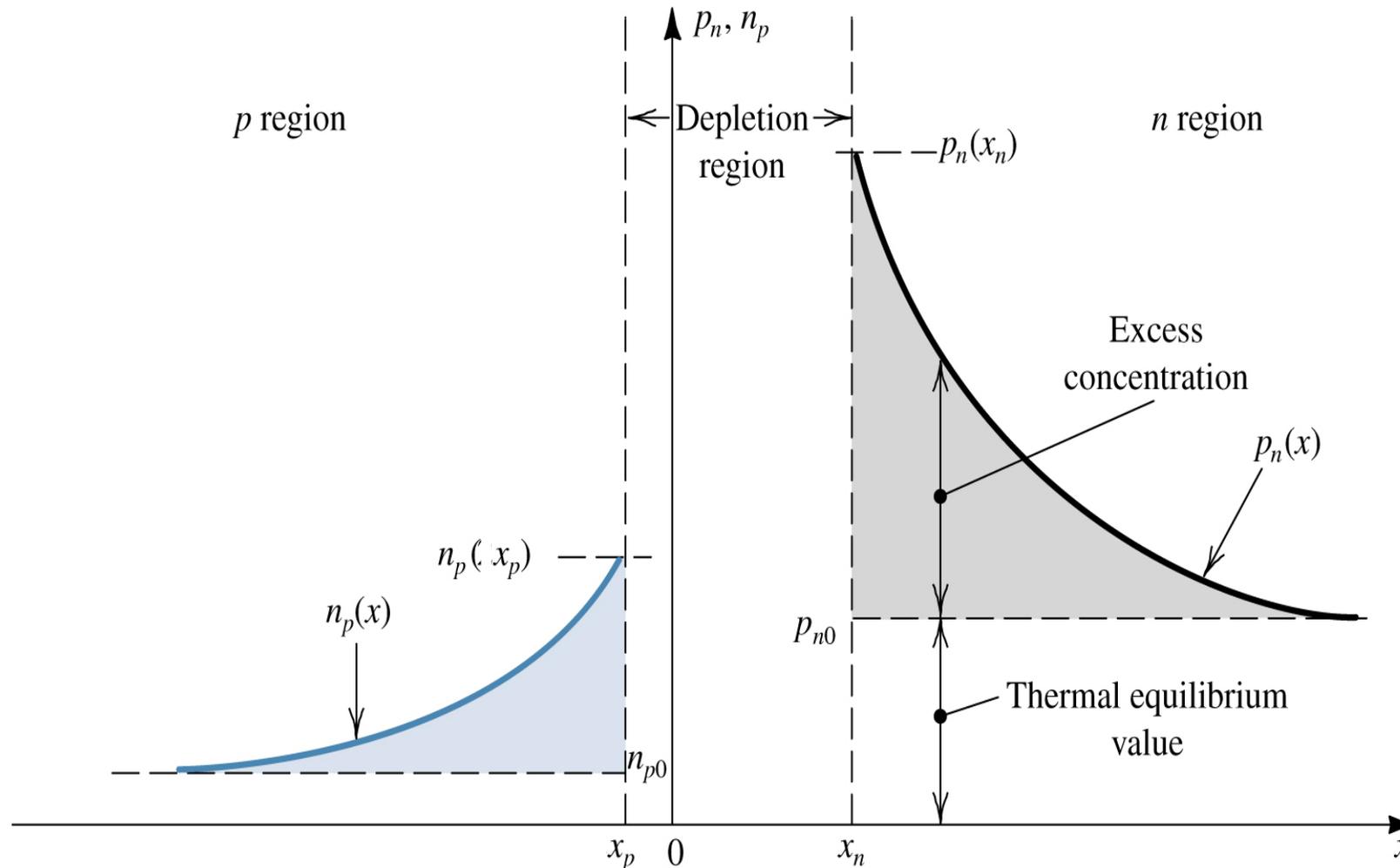

Forward bias minority distribution in neutral regions



pn Junction Capacitance: Forward Bias

Excess charge stored in neutral region near edges of space charge region is

$$Q_D = i_D \tau_T \text{ Coulombs}$$

t_T is called diode transit time and depends on size and type of diode.

The Q depends on i_D and in turn on v_D . This capacitance behavior is referred to as diffusion capacitance and given by:


$$C_j = \frac{dQ_D}{dv_D} = \frac{dQ_D}{di_D} \frac{di_D}{dv_D} \cong \frac{i_D \tau_T}{V_T} \text{ [F]}$$
$$\left| i_D = I_S \left[\exp\left(\frac{v_D}{V_T}\right) - 1 \right] \approx I_S \exp\left(\frac{v_D}{V_T}\right) \right.$$

Diffusion capacitance is proportional to current and becomes quite large at high currents.



Diode Circuit Analysis: Basics

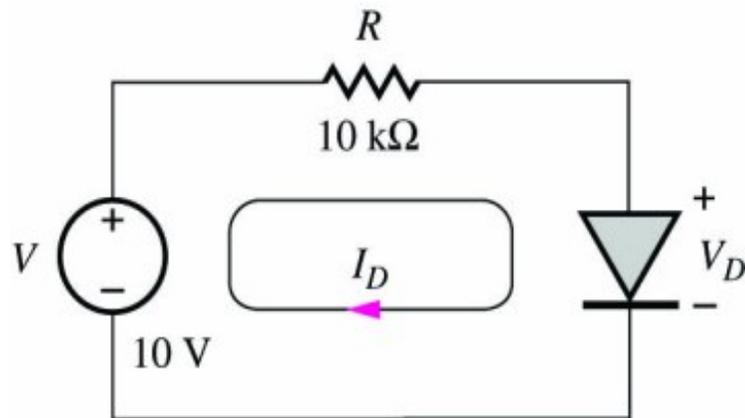Objective: to find the DC current (I_D) and voltage (V_D), or **quiescent operating point (Q-point)** of the diode.



V and R may represent Thevenin equivalent of a more complex 2-terminal network.

Full set of equations:

1. Diode equation:

$$\Rightarrow I_D = I_S \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]$$

2. KVL along the loop:

$$\Rightarrow V = I_D R + V_D$$

nonlinear

This is also called the **load line** equation of the diode, as if the V-source and R were the load of the diode.



Topics to cover...

- Physical operation of pn junction diode
- Terminal I-V characteristics
- Breakdown and junction capacitances
- Diode circuits analysis




Diode Circuit Analysis Approaches

- Graphical analysis (load-line method)
- Numerical Analysis with diode's mathematical model
- Simplified analysis with ideal diode model.
- Simplified analysis using constant voltage drop model.



Load-Line Analysis (Example 2)

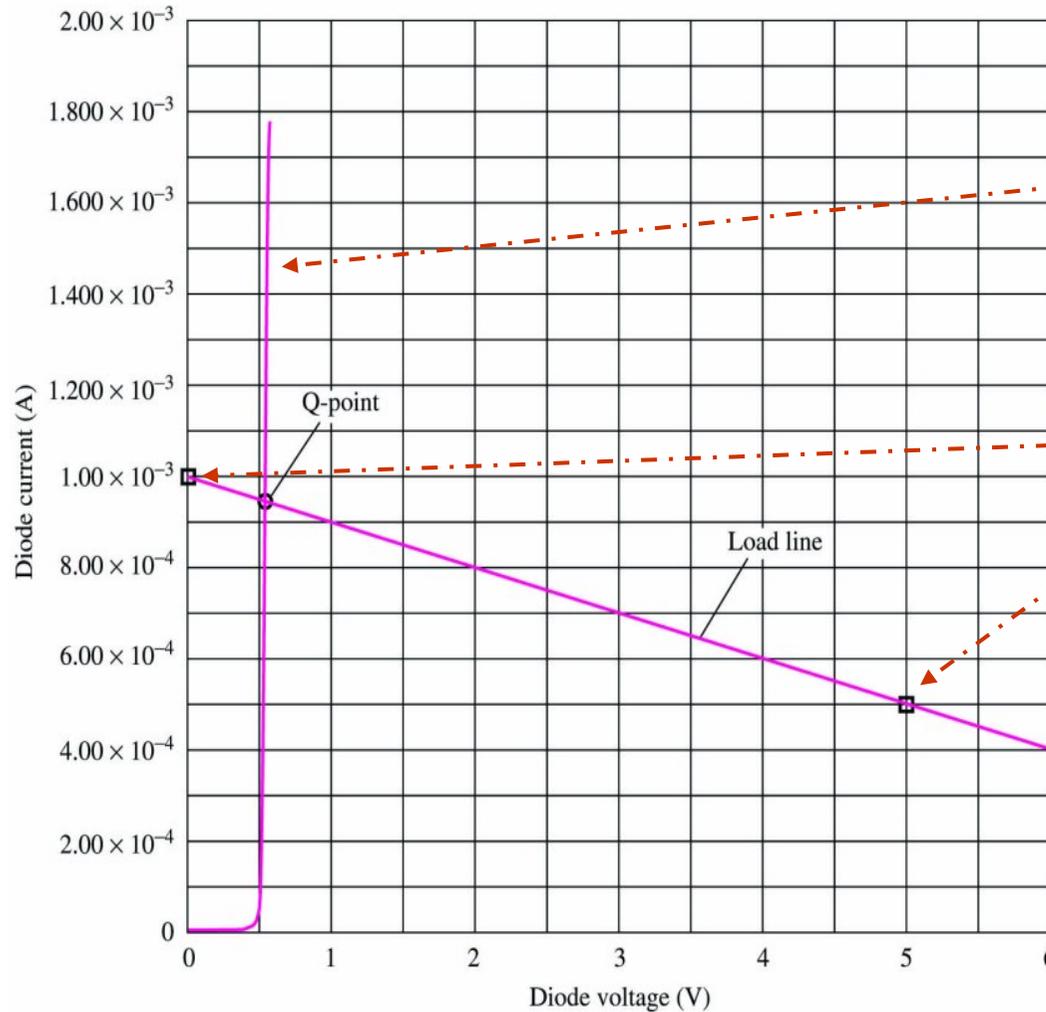

Problem: Find Q-point

Given data: $V=10$ V, $R=10$ k Ω .

Diode I-V curve.

Analysis:

$$10 = I_D 10^4 + V_D$$

To define the load line we use,

$$V_D = 0, \quad I_D = (10\text{V} / 10\text{k}\Omega) = 1 \text{ mA}$$

$$V_D = 5, \quad I_D = 0.5 \text{ mA}$$

These points and the resulting load line are plotted. Q-point is given by **intersection** of load line and diode characteristic:

Q-point = (0.95 mA, 0.6 V)



Numerical Analysis (Example 3)

Problem: Find Q-point for given diode characteristics.

Given data: $I_S = 10^{-13} \text{A}$, $V_T = 25 \text{ mV}$, $V = 10 \text{ V}$, $R = 10 \text{ k}\Omega$.

Analysis:

$$\begin{cases} I_D = I_S [\exp(V_D / V_T) - 1] = 10^{-13} [\exp(40V_D) - 1] \\ 10 = I_D 10^4 + V_D \end{cases}$$
$$\Rightarrow 10 = 10^4 10^{-13} [\exp(40V_D) - 1] + V_D$$

This is a *transcendental equation* and does not have analytical solutions. A numerical answer can be found by using *Newton's iterative method*.

Let: $f = 10 - 10^{-9} [\exp(40V_D) - 1] - V_D$


We desire to find V_D for which $f=0$.



Newton's Iteration Method for $f(v_D) = 0$

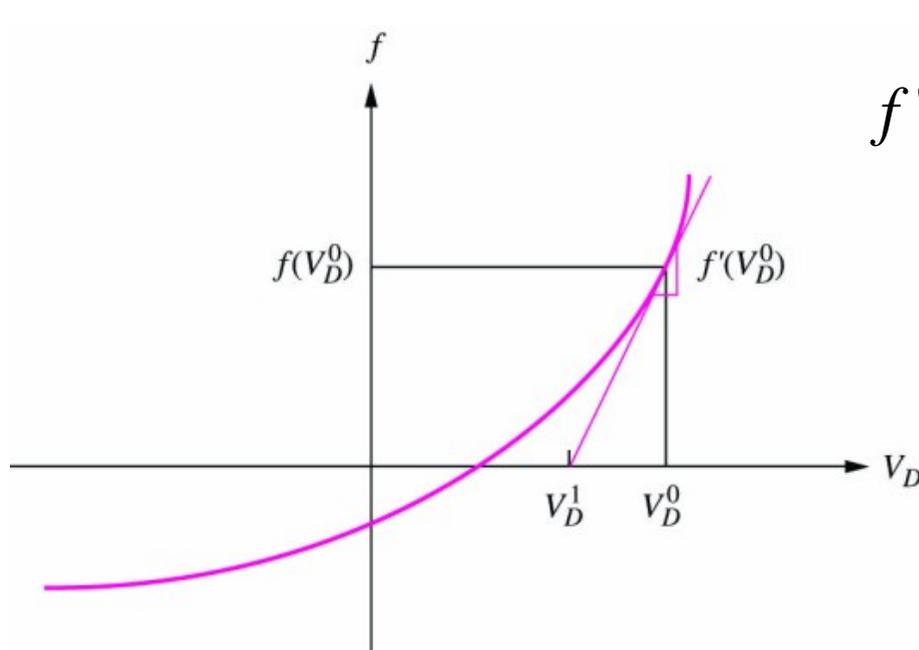1. Make initial guess V_D^0
2. Evaluate f and its derivative f' for this value of V_D
3. Calculate new guess for V_D using
4. Repeat steps 2 and 3 till convergence

$$V_D^1 = V_D^0 - \frac{f(V_D^0)}{f'(V_D^0)}$$



$$f'(V_D^0) = \frac{f(V_D^0) - 0}{V_D^0 - V_D^1}$$




Solution from a Spreadsheet

Iteration #	V_D [V]	f	f'	I_D [A]
0	0.8000	-7.895E+04	-3.159E+06	7.896E+00
1	0.7750	-2.904E+04	-1.162E+06	2.905E+00
2	0.7500	-1.068E+04	-4.276E+05	1.069E+00
3	0.7250	-3.927E+03	-1.575E+05	3.936E-01
4	0.7001	-1.442E+03	-5.806E+04	1.452E-01
5	0.6753	-5.281E+02	-2.150E+04	5.374E-02
6	0.6507	-1.918E+02	-8.048E+03	2.012E-02
7	0.6269	-6.817E+01	-3.103E+03	7.754E-03
8	0.6049	-2.281E+01	-1.289E+03	3.220E-03
9	0.5872	-6.455E+00	-6.357E+02	1.587E-03
10	0.5770	-1.148E+00	-4.238E+02	1.057E-03
11	0.5743	-5.989E-02	-3.804E+02	9.486E-04
12	0.5742	-1.876E-04	-3.780E+02	9.426E-04
13	0.5742	-1.858E-09	-3.780E+02	9.426E-04

← Q-point



Analysis using Ideal Diode Model

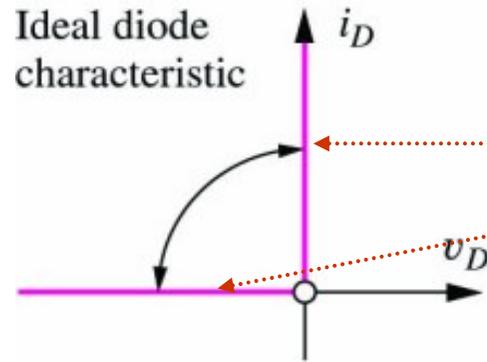

Ideal diode model:


Forward-biased: voltage = zero, $i_D > 0$

Reverse-biased: current = zero, $v_D < 0$

Diode is assumed to be either on or off.


I-V curve is **linear** in both regions.

Ideal diode symbol

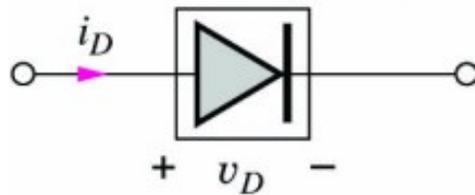


Analysis steps:


1. Identify anode and cathode of diode and label v_D and i_D .
2. Guess diode's region of operation from circuit.
3. Analyze circuit using diode model appropriate for assumed operation region.
4. Check results to check consistency with assumptions.

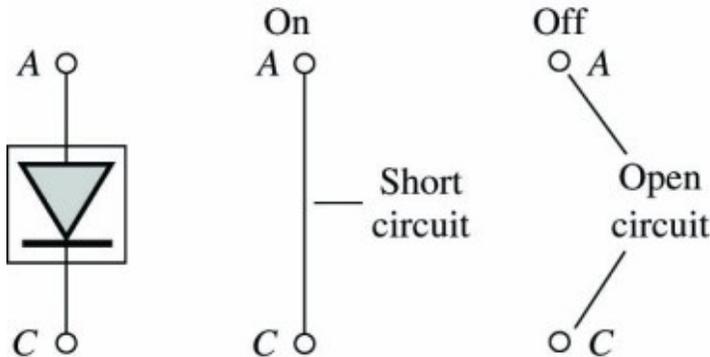

Example 4

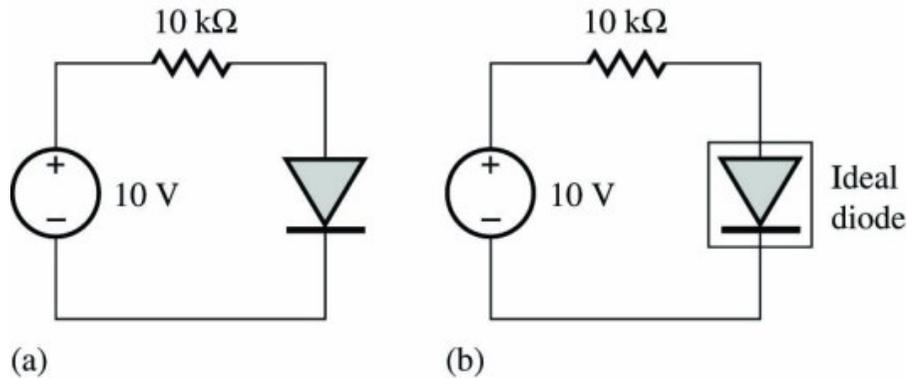

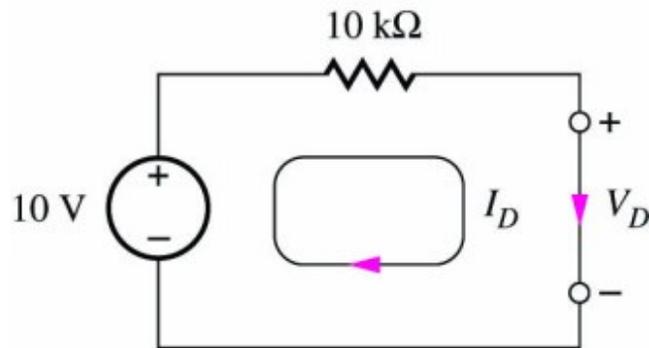Since source is forcing positive current through diode, assume diode is **on**. So $V_D=0$.




$$I_D = \frac{(10 - 0)\text{V}}{10\text{k}\Omega} = 1\text{ mA}$$


Since $I_D > 0$, our assumption is correct.
Q-point is (1 mA, 0V).



Example 5

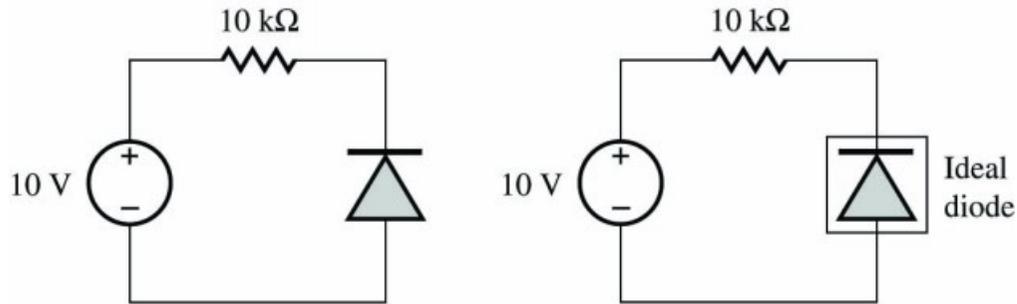

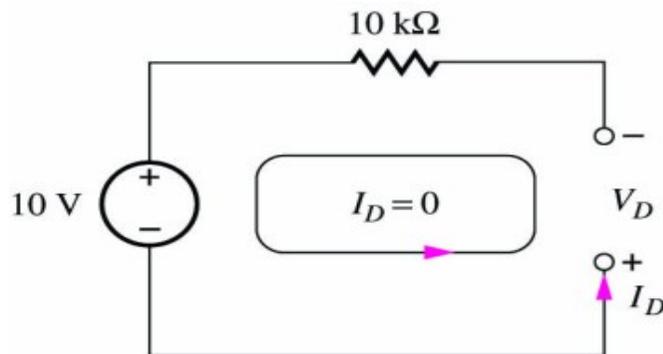Since source is forcing current backward through diode, assume diode is off. Hence $I_D = 0$.






$$10 + V_D + 10^4 I_D = 0$$
$$\therefore V_D = -10V$$

Since $V_D < 0$, our assumption is right.

Q-point is (0, -10 V)



Constant Voltage Drop Model

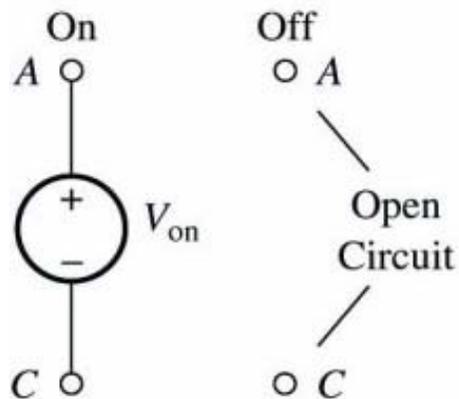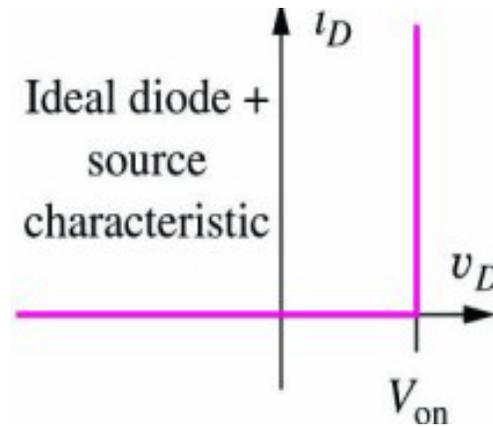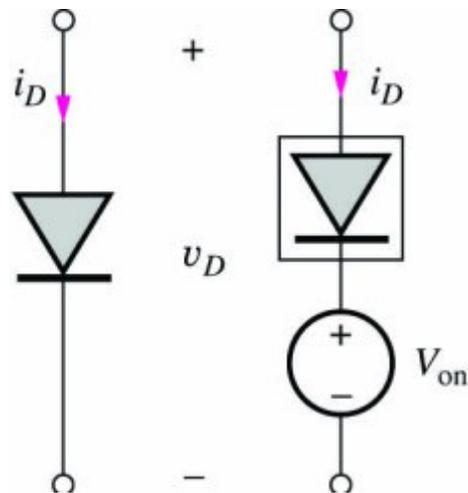


Forward-bias: $v_D = V_{on}$, $i_D > 0$


Reverse-bias: $i_D = 0$, $v_D < V_{on}$



Example 6

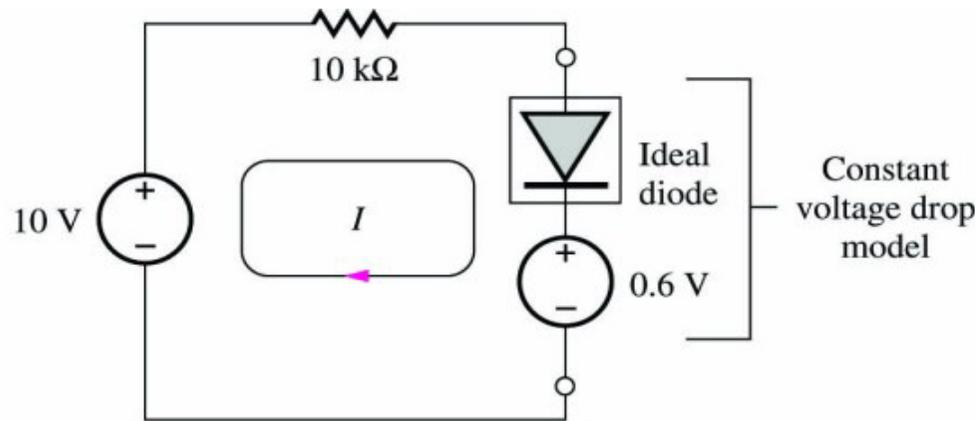

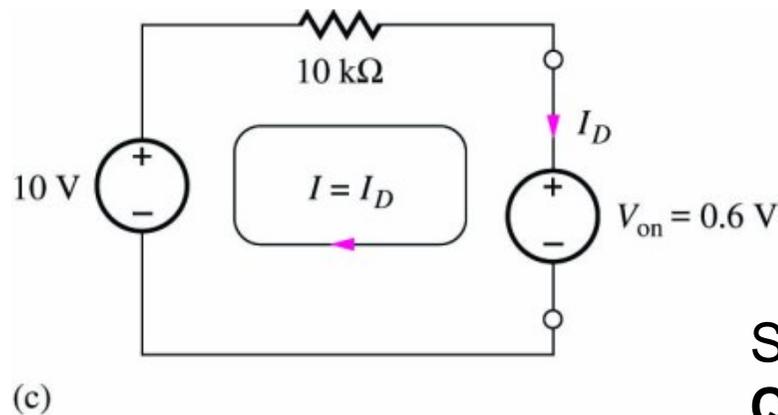Analysis: Since 10V source is forcing positive current through diode, we assume diode is on.




$$\begin{aligned} I_D &= \frac{(10 - V_{on})V}{10\text{k}\Omega} \\ &= \frac{(10 - 0.6)V}{10\text{k}\Omega} = 0.94\text{mA} \end{aligned}$$

Since $I_D > 0$, our assumption is correct.
Q-point is (0.94 mA, 0.6V).



Two-Diode Circuit Analysis (Example 7)

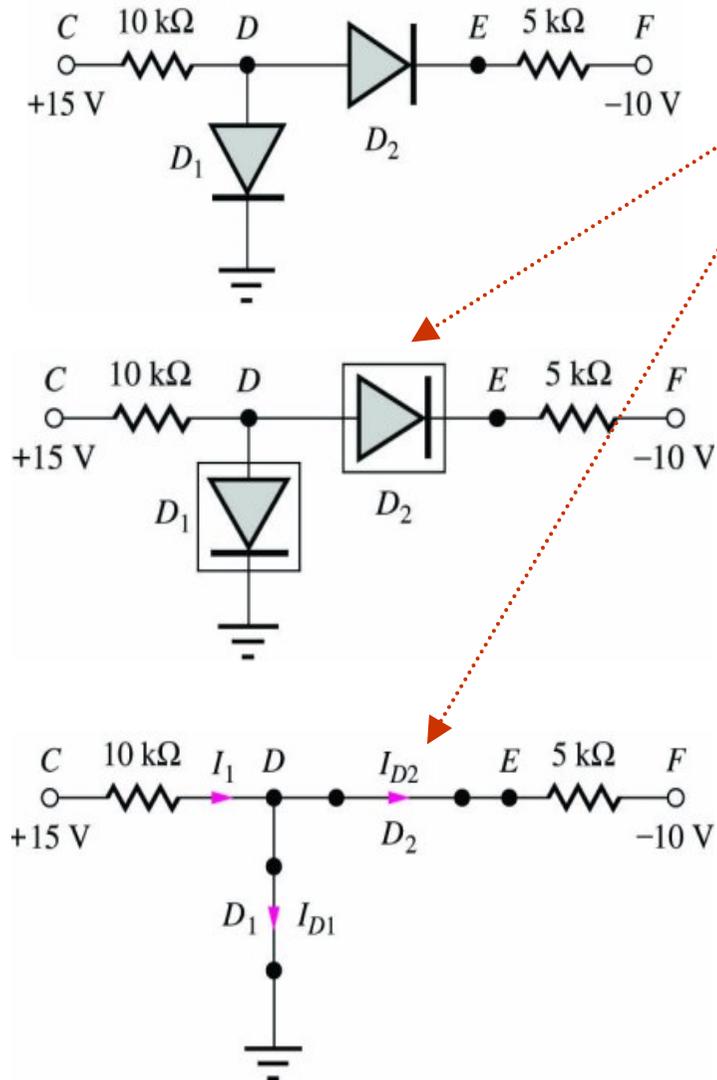

Analysis:

Choose ideal diode model.

Assume both diodes are on.

Since $V_{D1} = 0$,

$$I_1 = \frac{(15 - 0) \text{ V}}{10 \text{ k}\Omega} = 1.50 \text{ mA}$$

$$I_{D2} = \frac{0 - (-10) \text{ V}}{5 \text{ k}\Omega} = 2.00 \text{ mA}$$

$$I_{D1} = I_1 - I_{D2} = 1.5 - 2 = -0.5 \text{ mA}$$


Q-points are $(-0.5 \text{ mA}, 0 \text{ V})$ and $(2.0 \text{ mA}, 0 \text{ V})$

But, $I_{D1} < 0$ is not consistent with the assumption of D1 is ON, so try again.



Example 7 (Cont.)

The second guess is D_1 off and D_2 on:

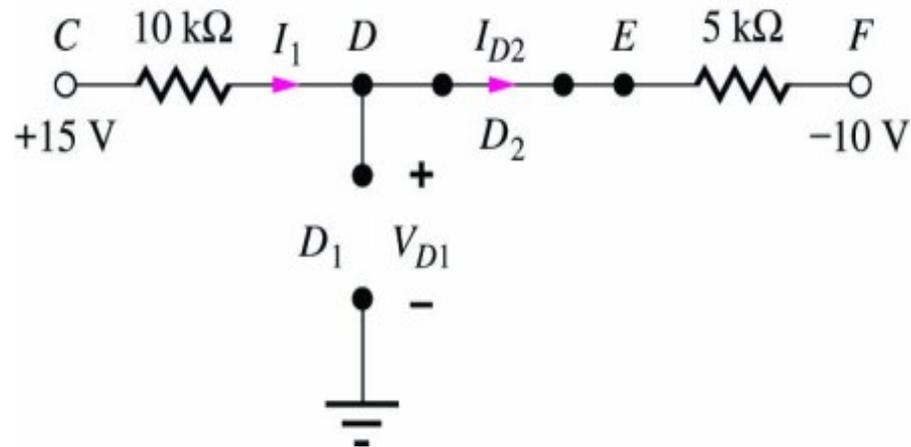

Since $I_{D2} = I_1$,

$$I_1 = \frac{15 - (-10)}{10\text{k}\Omega + 5\text{k}\Omega} = 1.67\text{mA}$$

$$V_{D1} = 15 - 10,000I_1 = -1.67\text{V}$$



Q-points are D_1 : (0 mA, -1.67 V): off

D_2 : (1.67 mA, 0 V) : on

This is consistent with our assumptions and analysis is finished.



Breakdown Region Diode Model

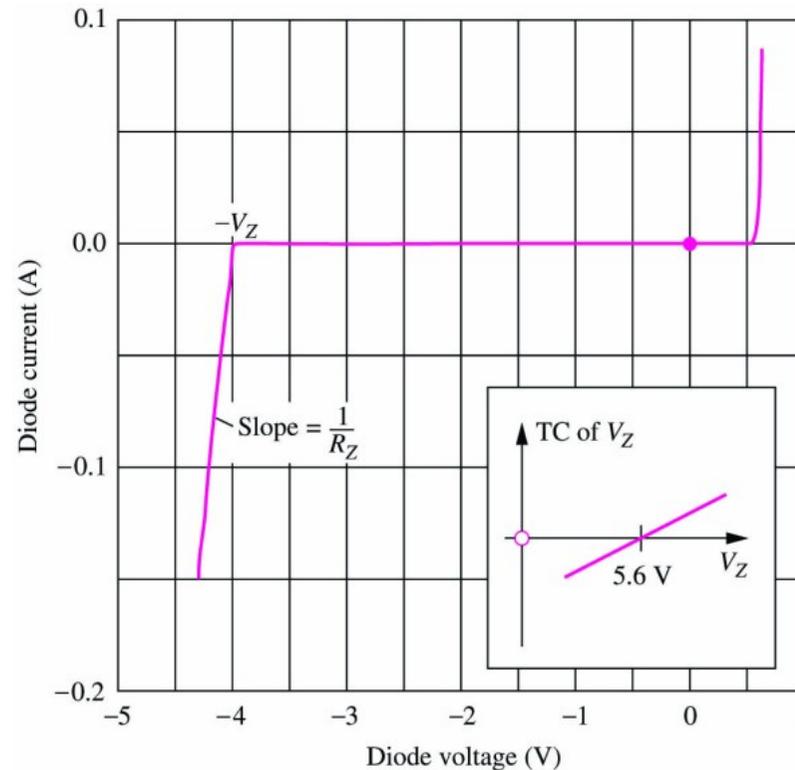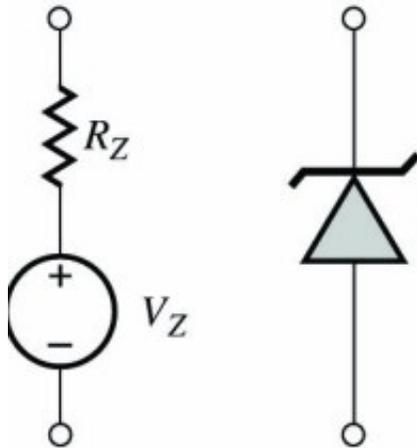


In breakdown, the diode is modeled with a DC voltage source, V_Z , and a series resistance, R_Z . R_Z models the slope of the i - v characteristic.

Diodes designed to operate in reverse breakdown are called **Zener diodes** and use the indicated symbol



Zener Diode Circuit Analysis (Example 8)

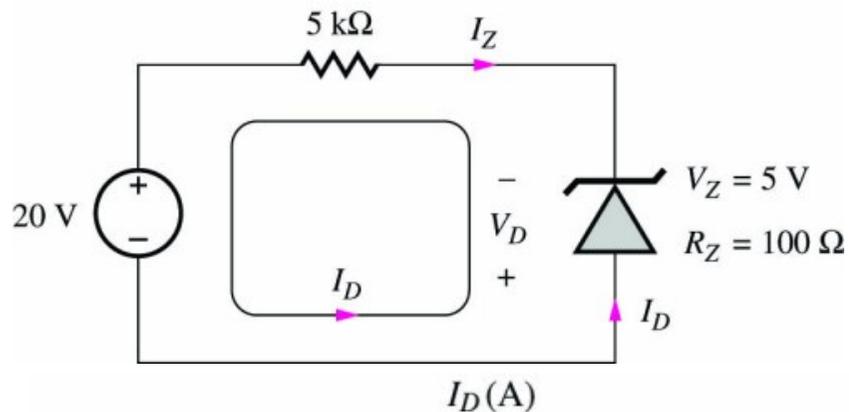


Load-line equation :
(KVL along the loop)

$$V_D + 5000I_D + 20 = 0$$



Using graphic analysis:

Choose 2 points (0V, -4mA) and (-5V, -3mA) to draw the load line.

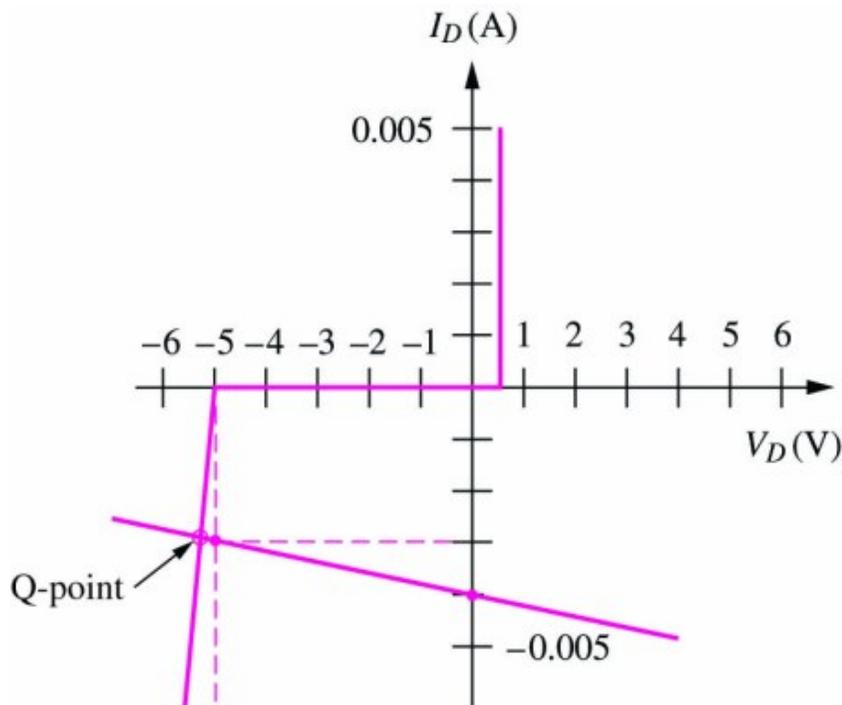
It intersects with *i-v* characteristic at **Q-point (-2.9 mA, -5.2 V).**



Zener Diode Circuit Analysis (Example 9)

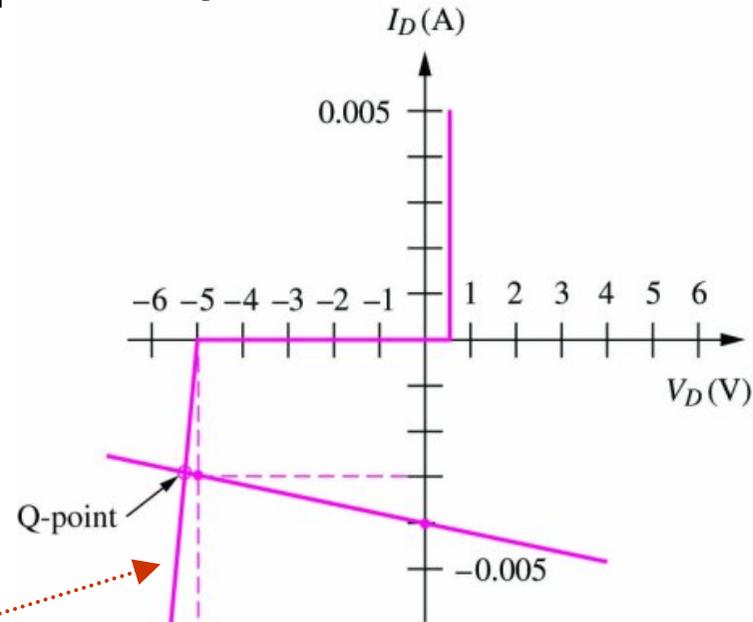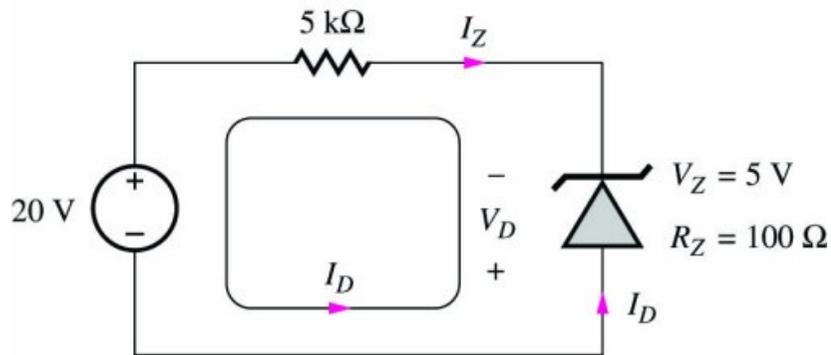

Using piecewise linear model:

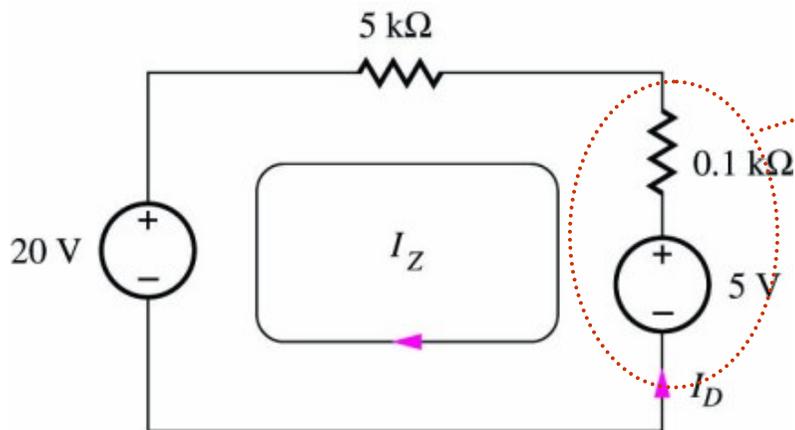

$$I_Z = -I_D > 0$$

Assume in breakdown region


$$-20 + 5100I_Z + 5 = 0$$

$$I_Z = \frac{(20 - 5)V}{5100\Omega} = 2.94\text{mA}$$


Since $I_Z > 0$ ($I_D < 0$), solution is consistent with Zener breakdown assumption.



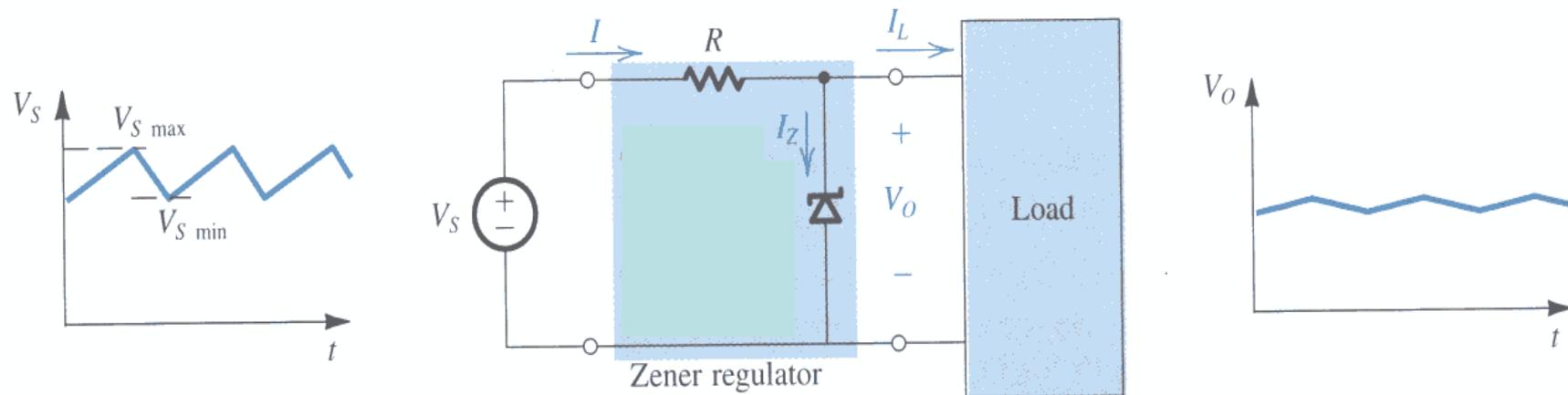Zener Diode Applications: Voltage Regulator



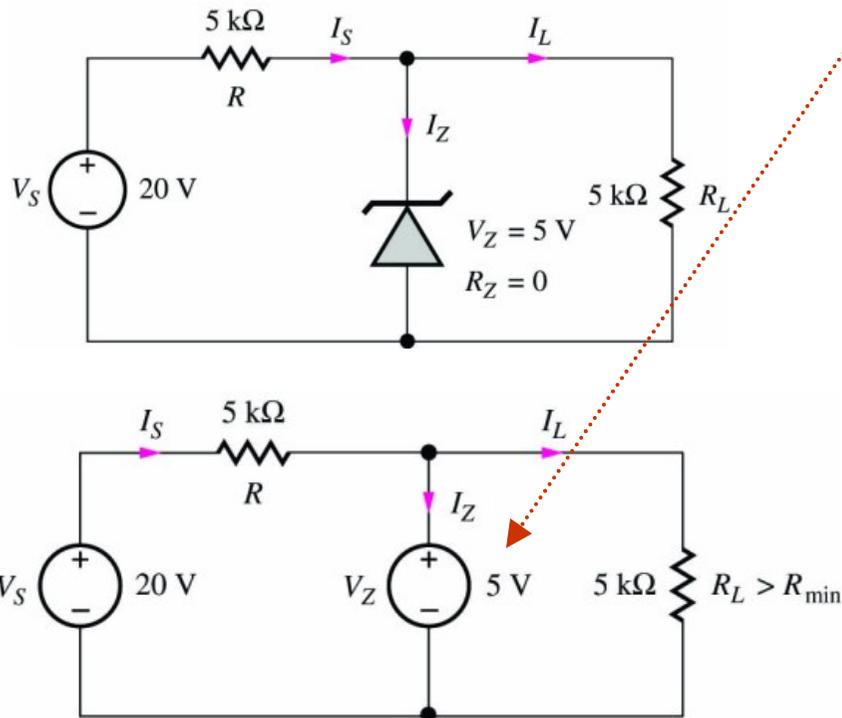Zener Diode Applications: Voltage Regulator



Use constant voltage drop model:

$$I_S = \frac{V_S - V_Z}{R} = \frac{(20 - 5)V}{5k\Omega} = 3\text{mA}$$

$$I_L = \frac{V_Z}{R_L} = \frac{5V}{5k\Omega} = 1\text{mA}$$

$$I_Z = I_S - I_L = 2\text{mA}$$

For proper regulation, $I_Z > 0$. If $I_Z < 0$, Zener diode no longer controls voltage across load resistor and the regulator is said to have “dropped out of regulation”.


Zener diode keeps voltage across load resistor constant

$$\therefore I_Z = \frac{V_S}{R} - V_Z \left(\frac{1}{R} + \frac{1}{R_L} \right) > 0 \quad R_L > \frac{R}{\left(\frac{V_S}{V_Z} - 1 \right)} = R_{\min}$$



Example 10

Zener diode model

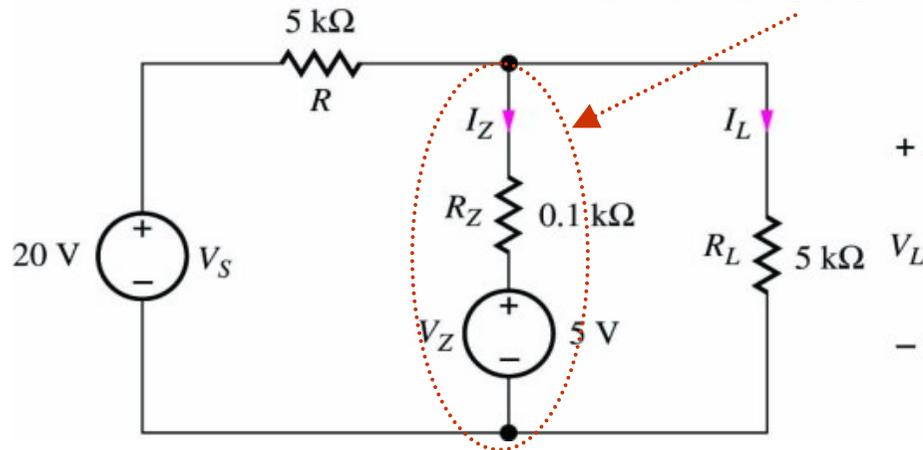

Problem: Find V_L and I_Z using the piece-wise linear model.

Given data:

$$V_S = 20 \text{ V}, \quad R = 5 \text{ k}\Omega,$$

$$R_Z = 0.1 \text{ k}\Omega, \quad V_Z = 5 \text{ V}$$

Analysis:

KCL at output node:

$$\frac{V_L - 20}{5000} + \frac{V_L - 5}{100} + \frac{V_L}{5000} = 0$$


$$\therefore V_L = 5.19 \text{ V}$$

$$I_Z = \frac{V_L - 5}{100} = \frac{5.19 - 5}{100} = 1.9 \text{ mA} > 0$$

Diode is actually operating in breakdown region as assumed.



Line and Load Regulation

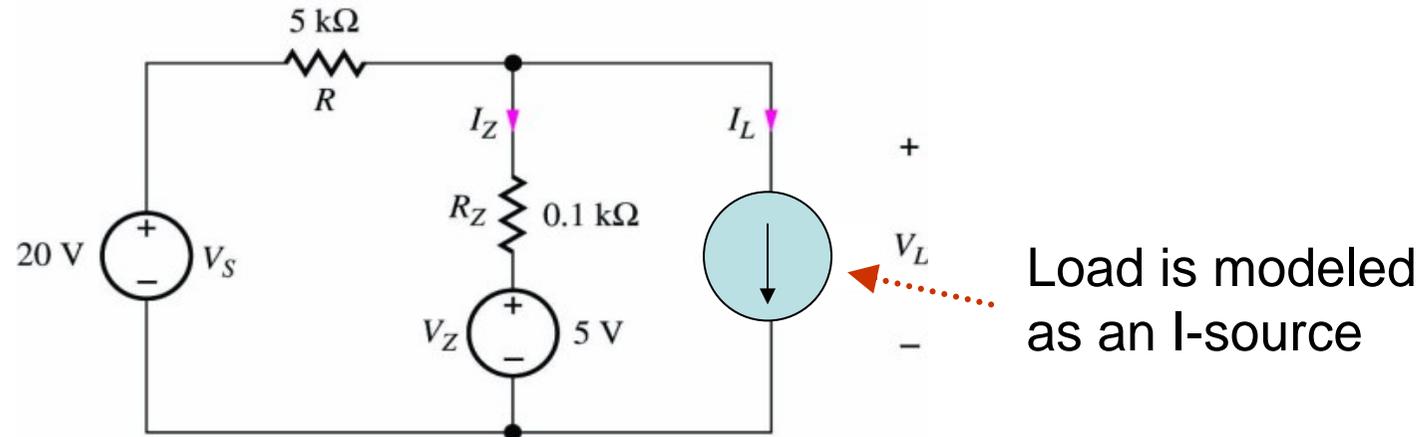

By superposition:

$$V_L = \frac{R}{R + R_z} V_Z + \frac{R_z}{R + R_z} V_S - (R_z // R) I_L$$

Line regulation $\equiv \frac{\partial V_L}{\partial V_S} = \frac{R_z}{R + R_z}$ (characterizes how sensitive output voltage is to input voltage changes)

Load regulation $\equiv \frac{\partial V_L}{\partial I_L} = -(R_z // R) [\Omega]$ (characterizes how sensitive output voltage is to load current changes)

