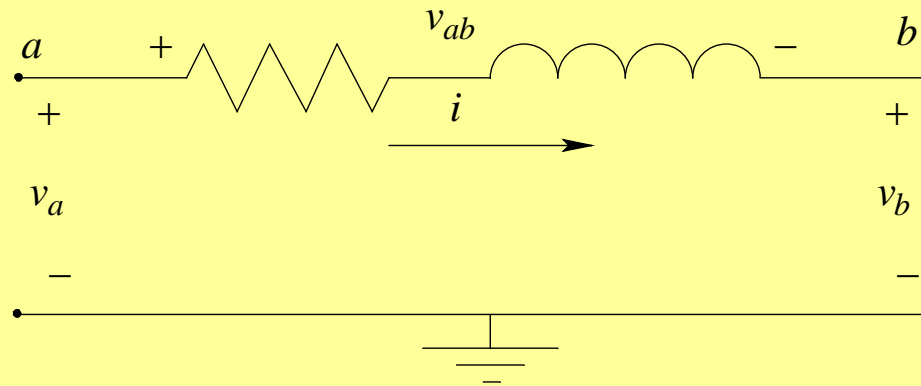


# Review of Basic Electric Circuits

- Convention and Symbols
- Use of Phasors
- Power, Reactive Power, Power Factor
- Inductive and Capacitive Loads



# Conventions

- ◆ MKS (SI) Units
- ◆ lower case  $v$  and  $i$  for instantaneous quantities
- ◆ upper case  $V$  and  $I$  for average and rms
- ◆ voltage and current subscripts




- ◆ voltage polarities and current directions
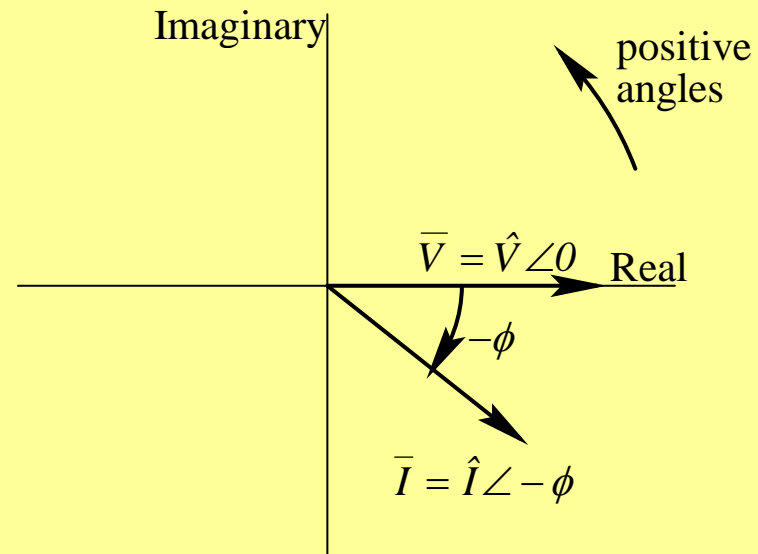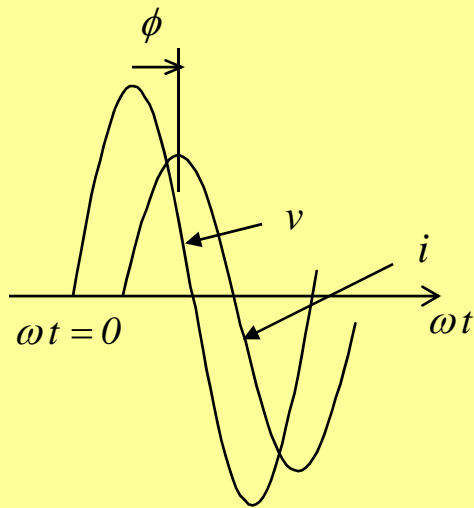
# Phasor Domain Representation for Sinusoidal Steady State AC





$$\begin{aligned}
 v(t) = \hat{V} \cos(\omega t) & \Leftrightarrow \bar{V} = \hat{V} \angle 0 \\
 i(t) = \hat{I} \cos(\omega t - \phi) & \Leftrightarrow \bar{I} = \hat{I} \angle -\phi
 \end{aligned}$$

# Time-Domain Analysis

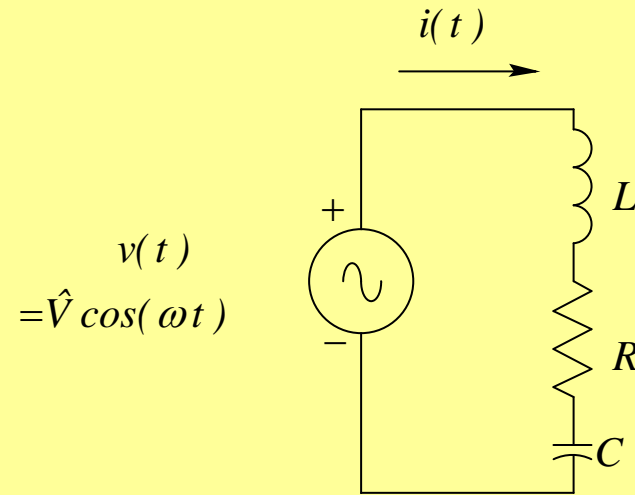

$$Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) \cdot dt = \hat{V} \cos(\omega t)$$

# Phasor Domain Analysis

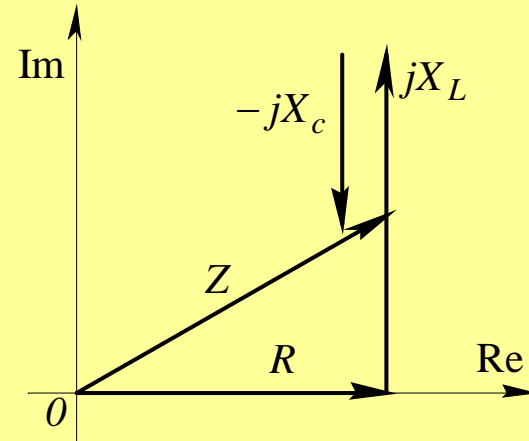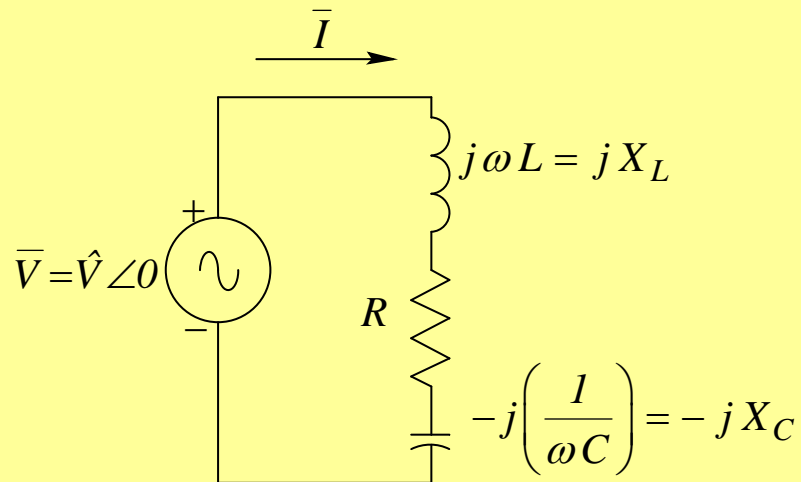


$$Z = R + jX_L - jX_C = |Z| \angle \phi$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \quad ; \quad \phi = \tan^{-1} \left[ \frac{\left(\omega L - \frac{1}{\omega C}\right)}{R} \right]$$



$$i(t) = \frac{\hat{V}}{|Z|} \cos(\omega t - \phi) \quad \Leftrightarrow \quad \bar{I} = \frac{\bar{V}}{Z} = \frac{\hat{V}}{|Z|} \angle -\phi$$

# Instantaneous Power

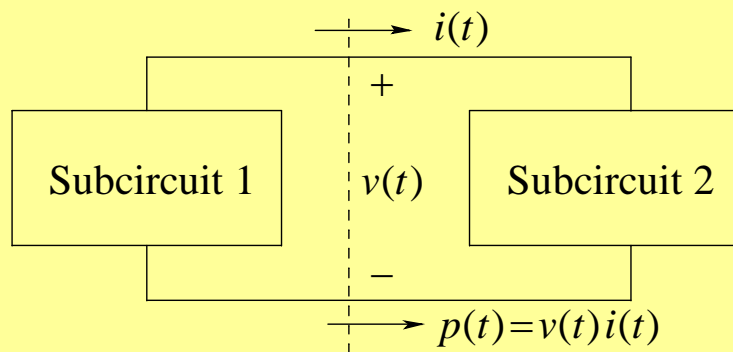

$$v(t) = \hat{V} \cos(\omega t + \phi_v)$$
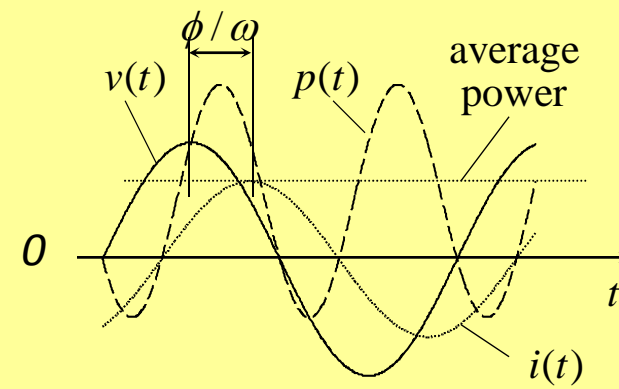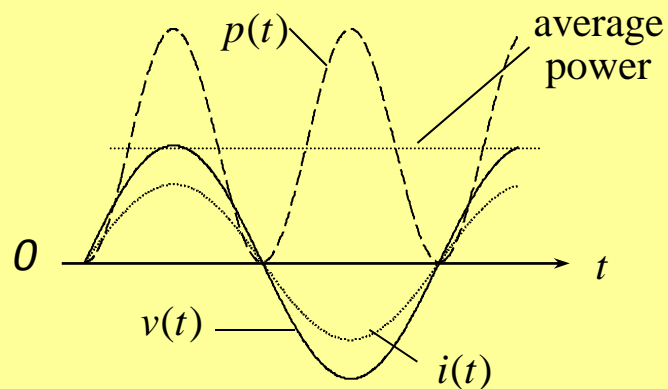
$$i(t) = \hat{I} \cos(\omega t + \phi_i)$$



- ◆  $v$  and  $i$  in phase ( $\phi_v = \phi_i$ )
- ◆ power flows in one direction
- ◆ maximum average power for given  $V$  and  $I$

- ◆  $v$  and  $i$  out of phase ( $\phi_v \neq \phi_i$ )
- ◆ power flow reverses periodically
- ◆ average power lower than maximum possible

# Real Power, Reactive Power and Power factor

- Complex Power

$$S = \bar{V} \bar{I}^* \quad (S \text{ is a complex number})$$

$$= V I \angle(\phi_v - \phi_i) = V I \angle\phi$$

$$S = P + jQ = |S| \angle\phi$$

- Real Power (average power)

$$P = V I \cos\phi \quad [W]$$

- Reactive Power




$$Q = V I \sin\phi \quad [VAR]$$

- Apparent Power

$$|S| = \sqrt{P^2 + Q^2} = VI \quad [VA]$$

- Power Factor

$$PF = \frac{P}{|S|} = \frac{P}{VI} = \cos\phi$$

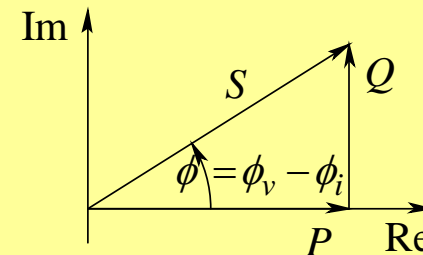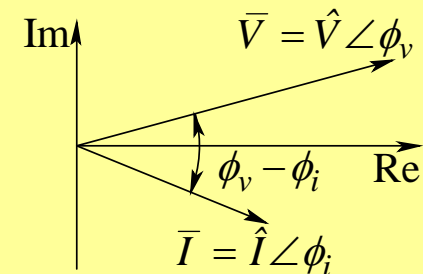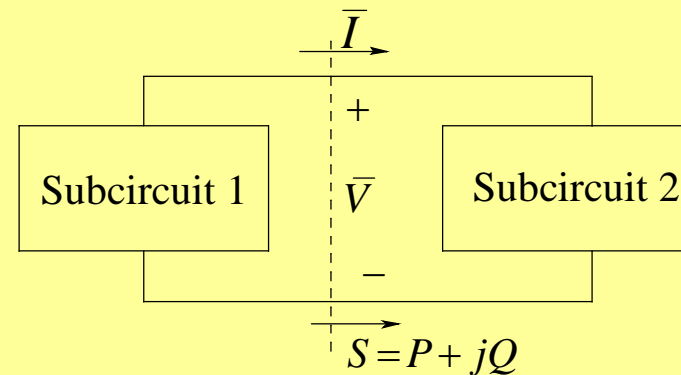

# Inductive Load

- The impedance is  $Z = |Z| \angle \phi$  where  $\phi$  is positive
- The current lags the voltage by the impedance angle  $\phi$
- Corresponds to a lagging power factor of operation
- In the power triangle, the same angle  $\phi$  relates P,Q and  $|S|$
- An inductive load draws positive reactive power (VARs)
- Most loads are inductive, particularly motors and transformers



# Summary

## Review of Basic Electric Circuits

- Convention and Symbols
- Use of Phasors
- Power, Reactive Power, Power Factor
- Inductive and Capacitive Loads