

ELE 2110A Electronic Circuits

Week 13: Frequency Response, Feedback



Topics to cover ...


- Miller Effect
- Bode Plot
- Negative Feedback
 - Properties
 - Topologies
 - Stability issue

Reading Assignment:

Chap 16.6-16.9, 17.1-17.2, 17.11 of Jaeger and Blalock



Miller's Theorem

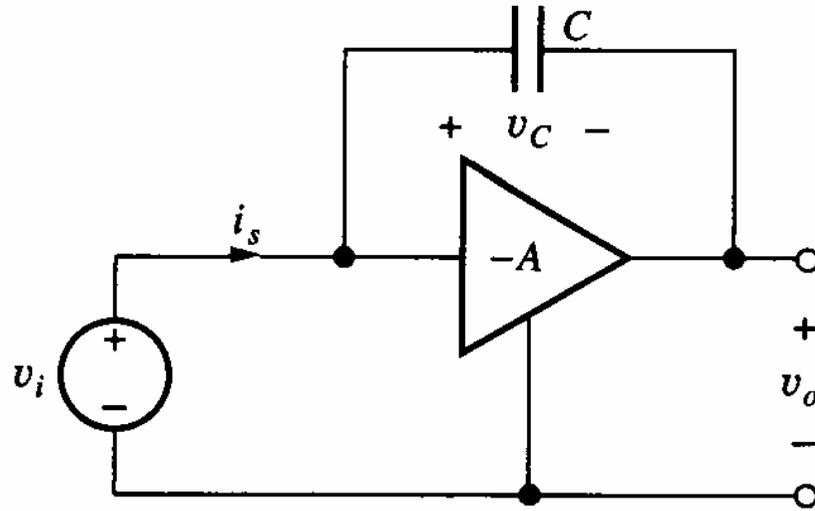

- Capacitor C is connected between the input and output of an inverting amplifier with gain $(-A)$
- Consider the input admittance ($Y=1/Z$) of the amplifier:


$$\mathbf{V}_o(s) = -A\mathbf{V}_i(s) \quad \text{and} \quad \mathbf{I}_s(s) = sC[\mathbf{V}_i(s) - \mathbf{V}_o(s)]$$

$$\rightarrow Y(s) \equiv \frac{\mathbf{I}_s(s)}{\mathbf{V}_i(s)} = sC(1 + A) \quad (\text{Miller's theorem})$$

- In general, the C can be any admittance element



Miller Effect

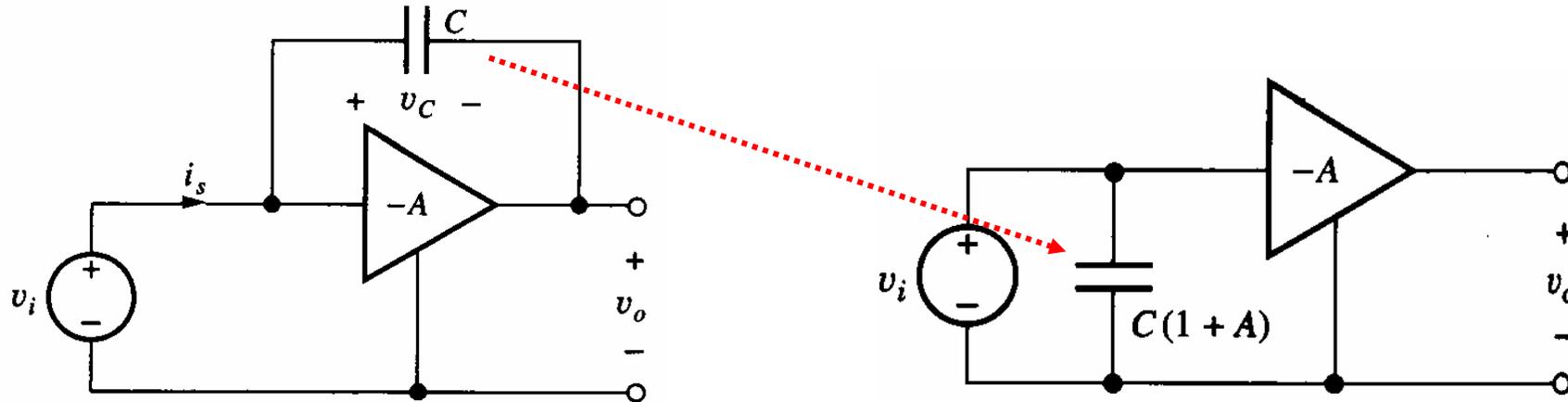


$$Y(s) \equiv \frac{\mathbf{I}_s(s)}{\mathbf{V}_i(s)} = sC(1+A)$$

- The capacitor C can be represented by an equivalent capacitor connected between input of the amplifier and the ground
- The input equivalent capacitance = $C \times (1+A)$
- This capacitance multiplication is referred to as **Miller effect**




Understanding the Miller Effect

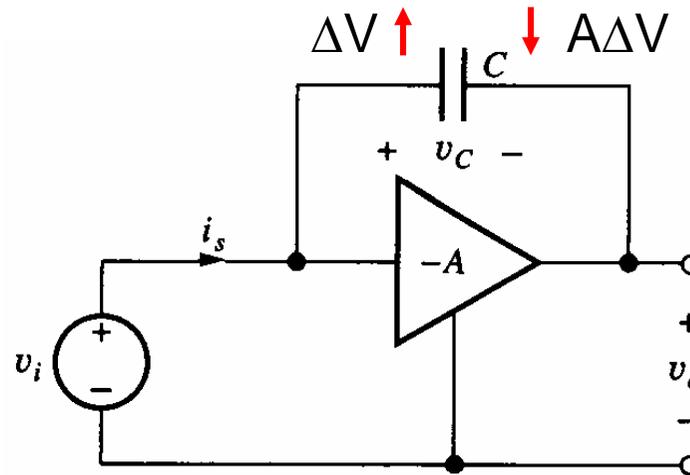


- If V_i changes by ΔV , V_o will change by $-A\Delta V$, so V_C will change by $(1+A)\Delta V \rightarrow$ amount of charges supplied to C is $C \times (1+A) \Delta V$
- If the capacitor were connecting between the input and ground, to absorb the same amount of charges, the equivalent capacitance must be $C \times (1+A)$




Miller Effect in C-E Amplifier

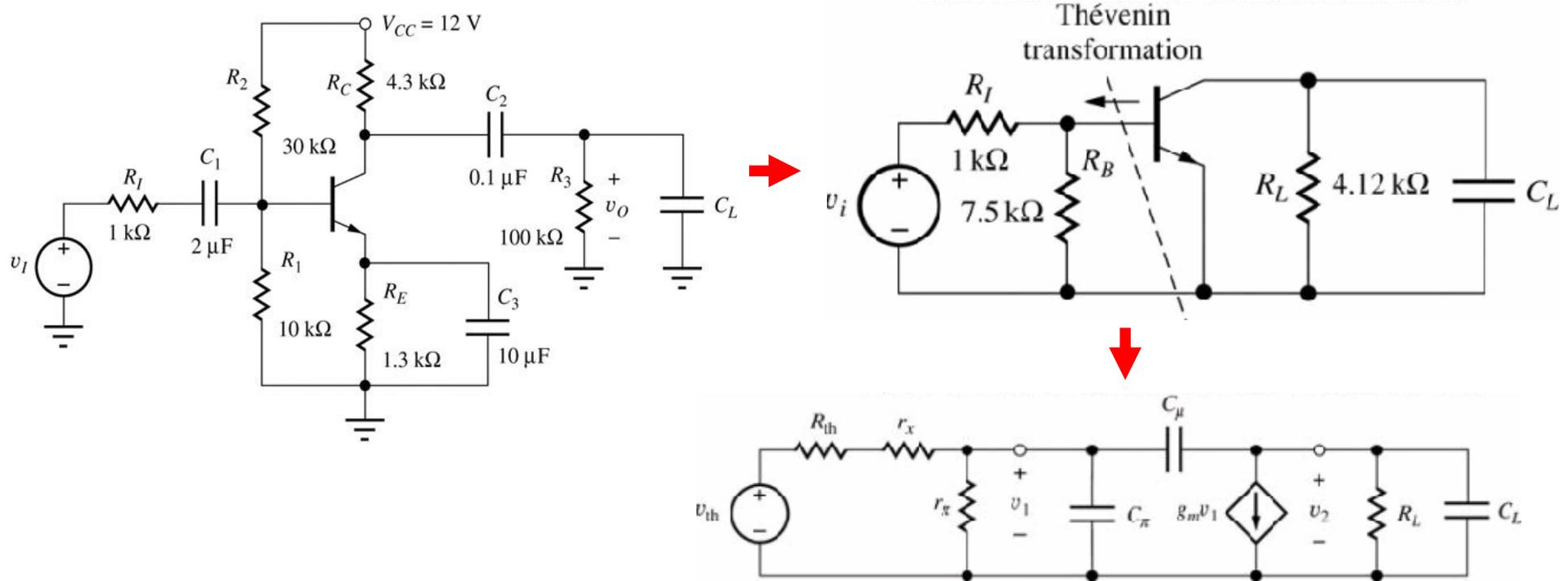

Miller Capacitor

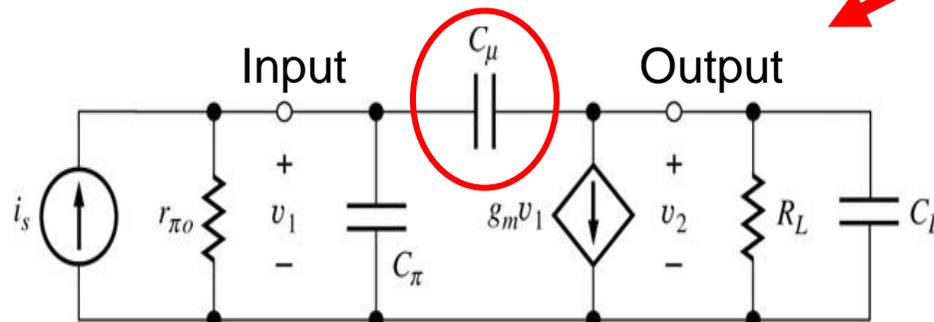

Miller Effect in CE amplifier


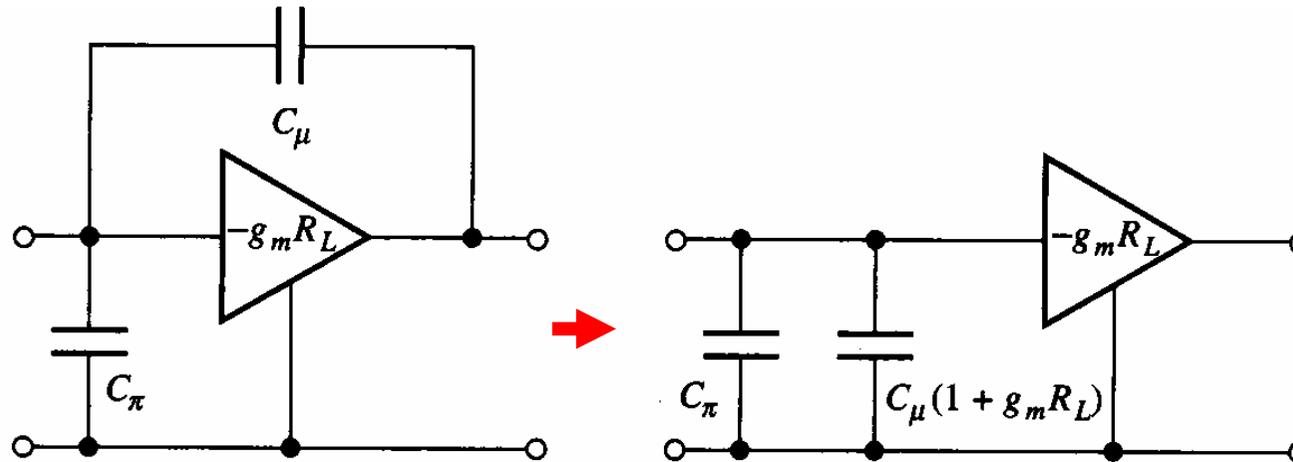


- C_μ is amplified by $(1 + g_m R_L)$ at the input \rightarrow Common emitter amplifiers generally have a low upper-cutoff frequency



Does Miller Effect exist in CB Amplifier?

CB Amplifier AC equivalent:

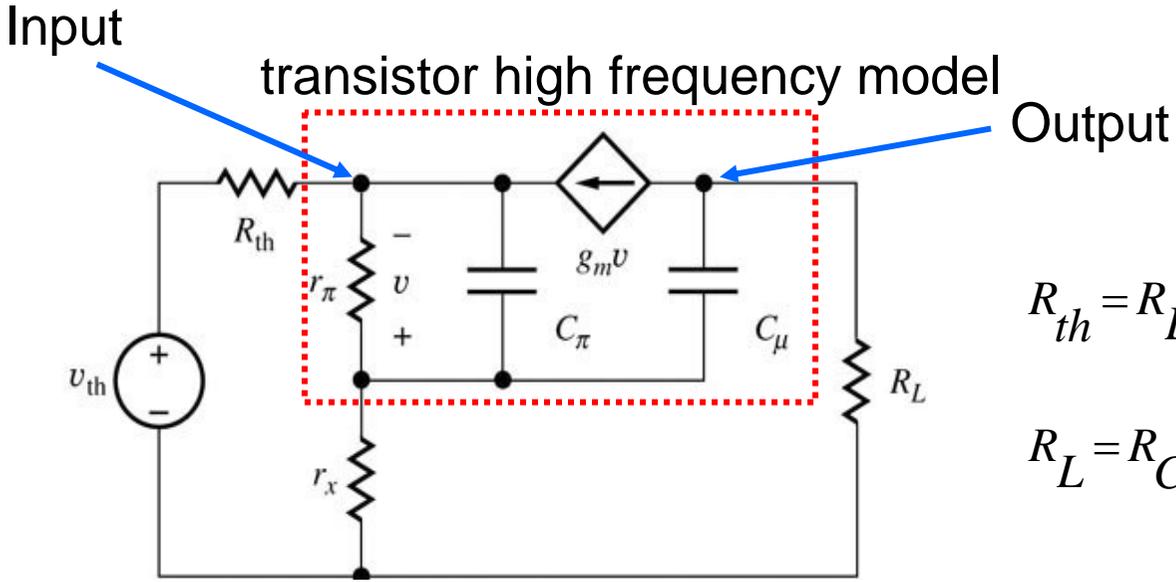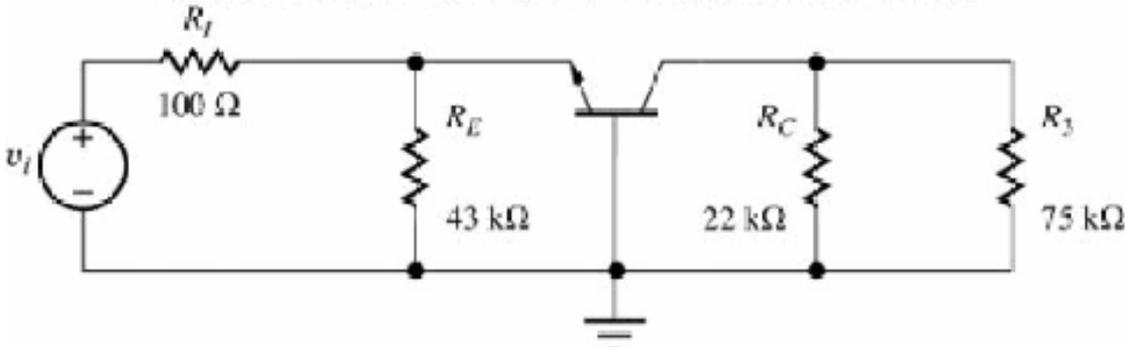


$$R_{th} = R_E \parallel R_I$$

$$R_L = R_C \parallel R_3$$





Does Miller Effect exist in Emitter Follower?

AC equivalent of emitter follower:

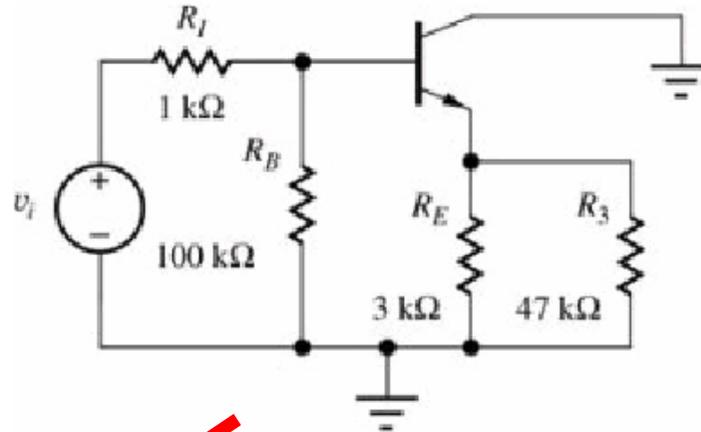

$$R_{th} = R_B \parallel R_I$$

$$R_L = R_E \parallel R_3$$

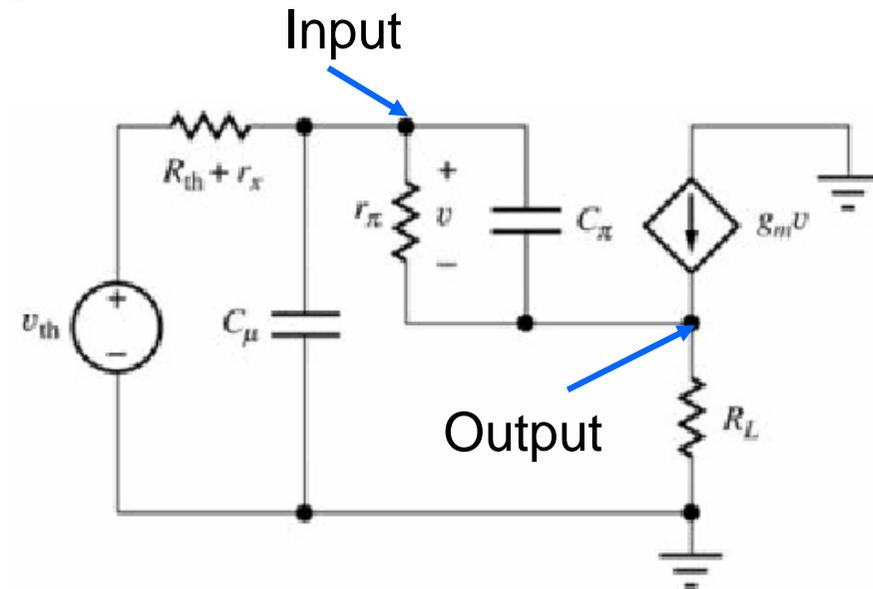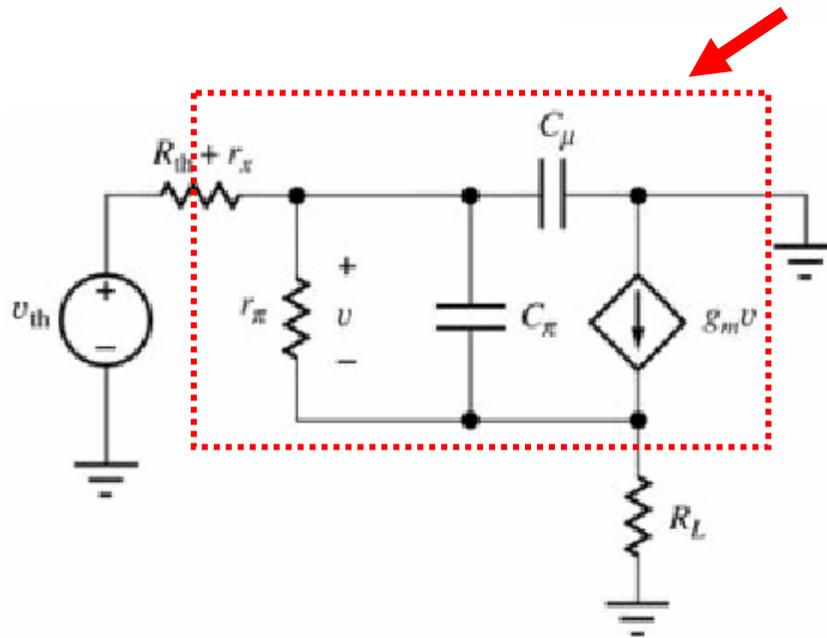

Re-arranged



Frequency Response of Single Stage Amplifiers

- C-E/C-S amplifier has a narrow bandwidth due to the Miller effect
- C-B/C-G amplifier has a wide bandwidth
- Emitter/Source follower has a wide bandwidth




Topics to cover ...

- Miller Effect
- Bode Plot
- Negative Feedback
 - Properties
 - Topologies
 - Stability issue



Transfer Function

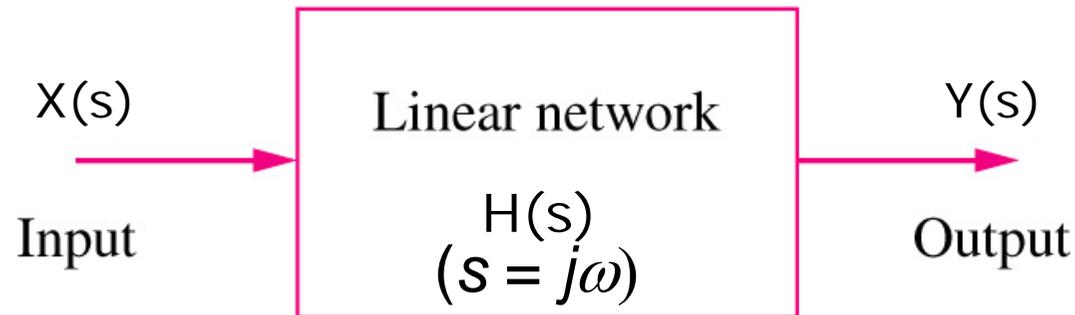

The transfer function of a circuit is the s-domain ratio of an output (voltage or current) to an input (voltage or current) :

$$H(s) = \frac{Y(s)}{X(s)}$$

$$H(s) = \text{Voltage Gain} = \frac{V_0(s)}{V_i(s)}$$

$$H(s) = \text{Transfer Impedance} = \frac{V_0(s)}{I_i(s)}$$

$$H(s) = \text{Current Gain} = \frac{I_0(s)}{I_i(s)}$$

$$H(s) = \text{Transfer Admittance} = \frac{I_0(s)}{V_i(s)}$$




Transfer Function Example

- Simple RC circuit

$$\mathbf{V}_o = \frac{1/j\omega C}{R + 1/j\omega C} \mathbf{V}_i$$
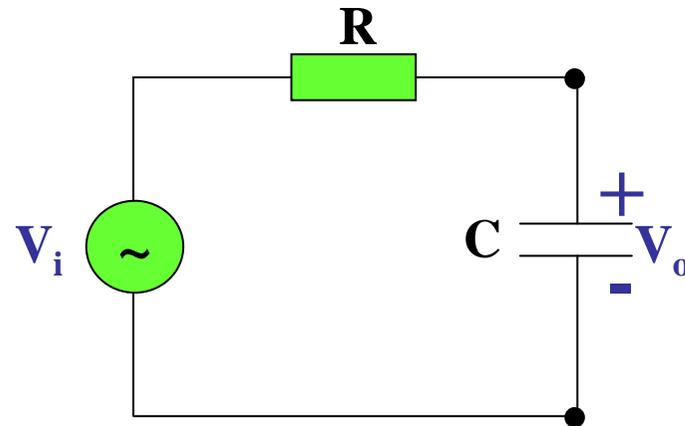
$$\frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1}{1 + j\omega RC}$$




is maximum when $\omega = 0$!


or $\frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle \phi$ **where** $\phi = -\tan^{-1}(\omega RC)$



Frequency response of RC circuit

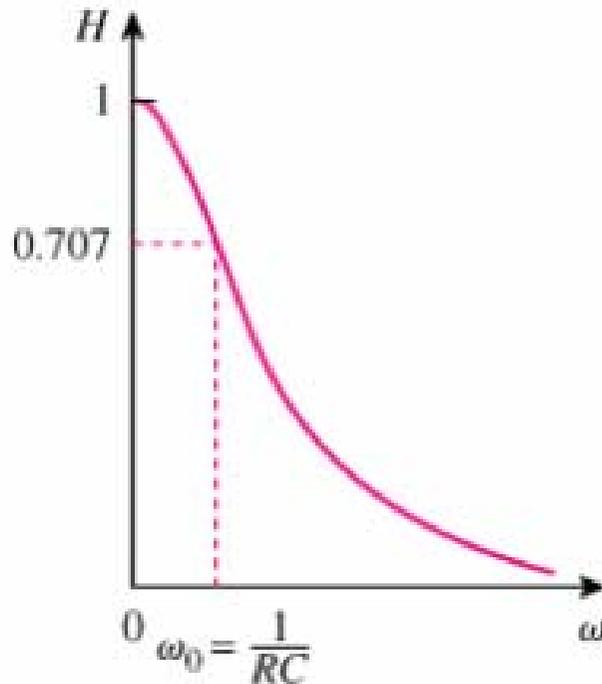

Magnitude

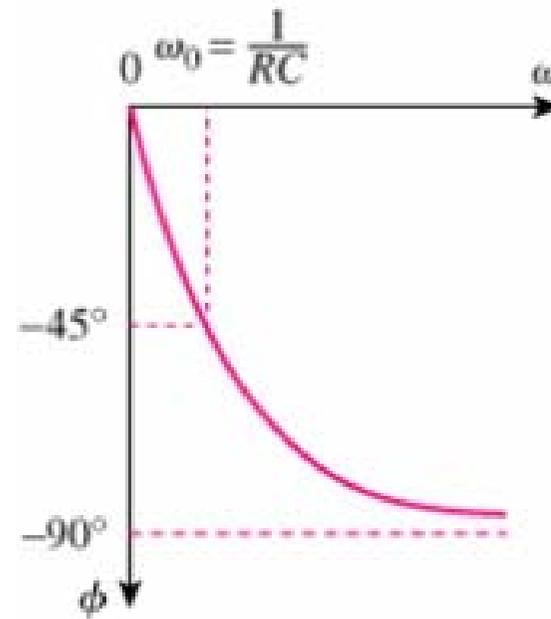


Phase

$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle \phi$$

$$\phi = -\tan^{-1}(\omega RC)$$




Frequency Response Example

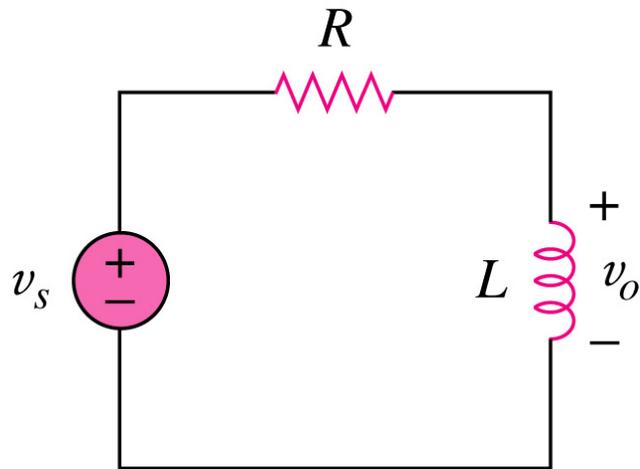


Transfer function of RL circuit:
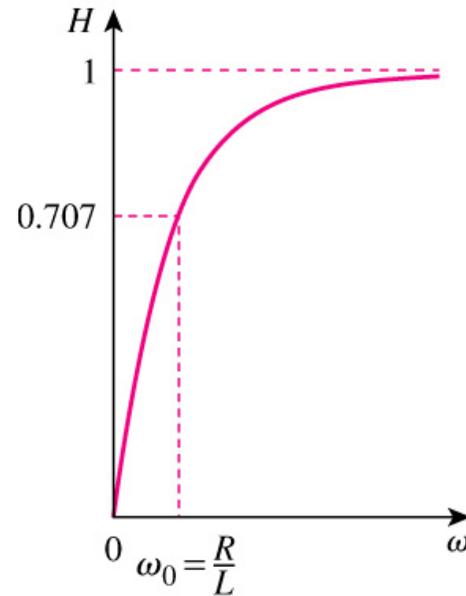
$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{j\omega L}{R + j\omega L}$$



(a)

Magnitude
response

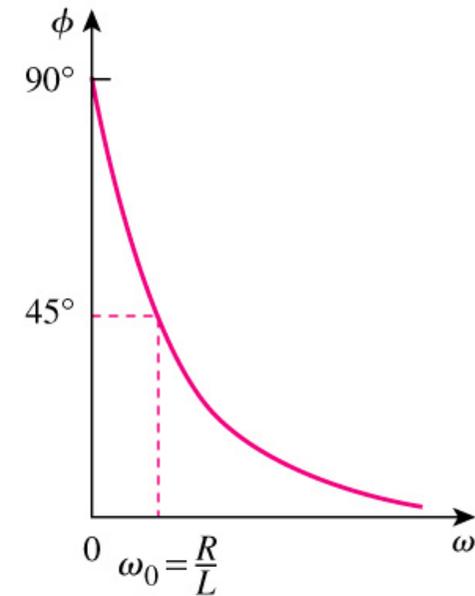

(b)

Phase
response



Pole and Zero in Transfer Functions

A circuit can have a general transfer function in the following form:

$$T(s) = \frac{K'(1 + s/\omega_{z_1})(1 + s/\omega_{z_2}) \cdots (1 + s/\omega_{z_m})}{(1 + s/\omega_{p_1})(1 + s/\omega_{p_2}) \cdots (1 + s/\omega_{p_n})} \quad s = j\omega$$

where $-\omega_{pk}$ and $-\omega_{zk}$ are called zeros and poles, respectively, of the transfer function



Logarithms

- Bode plot is a systematic way of plotting the magnitude and phase of a gain function as functions of frequency.
- Bode plots are based on logarithms. Some useful properties of logarithms are

$$1. \log P_1 \times P_2 = \log P_1 + \log P_2$$

$$2. \log P_1 / P_2 = \log P_1 - \log P_2$$

$$3. \log P^n = n \log P$$

$$4. \log 1 = 0$$



Decibel Scale

- In communications systems, gain is measured in *bels*. Historically, the bel is used to measure the ratio of two levels of *power* or power gain G :

$$G = \text{Number of bels} = \log_{10} P_2 / P_1$$

- The *decibel (dB)* is 1/10th of a bel:

$$G_{\text{dB}} = 10 \log_{10} \frac{P_2}{P_1}$$

- Alternatively, the gain can be expressed in terms of ratio of voltage or current amplitudes. For amplitude ratio, the decibel is defined as:

$$G_{\text{dB}} = 20 \log_{10} \frac{A_2}{A_1}$$

A_2 and A_1 are voltage or current amplitudes.

$$(P=I^2R = V^2/R)$$

So, 10dB voltage gain represents the same thing as 10dB power gain does



Magnitude Response

$$T(s) = \frac{K'(1 + s/\omega_{z_1})(1 + s/\omega_{z_2})\cdots(1 + s/\omega_{z_m})}{(1 + s/\omega_{p_1})(1 + s/\omega_{p_2})\cdots(1 + s/\omega_{p_n})}$$

For frequency response, put $s = j\omega$

The magnitude of the transfer function, in dB scale, is given by:

$$\therefore 20\log_{10}|T(j\omega)| = 20\log_{10} K' + \sum 20\log_{10} \sqrt{1 + (\omega/\omega_{z_k})^2} - \sum 20\log_{10} \sqrt{1 + (\omega/\omega_{p_k})^2}$$




Bode Magnitude Plot

$$20\log_{10}|T(j\omega)| = 20\log_{10} K' + \sum 20\log_{10} \sqrt{1 + (\omega / \omega_{z_k})^2} - \sum 20\log_{10} \sqrt{1 + (\omega / \omega_{p_k})^2}$$

Consider the general term

$$20\log_{10} \sqrt{1 + (\omega / \alpha)^2}$$

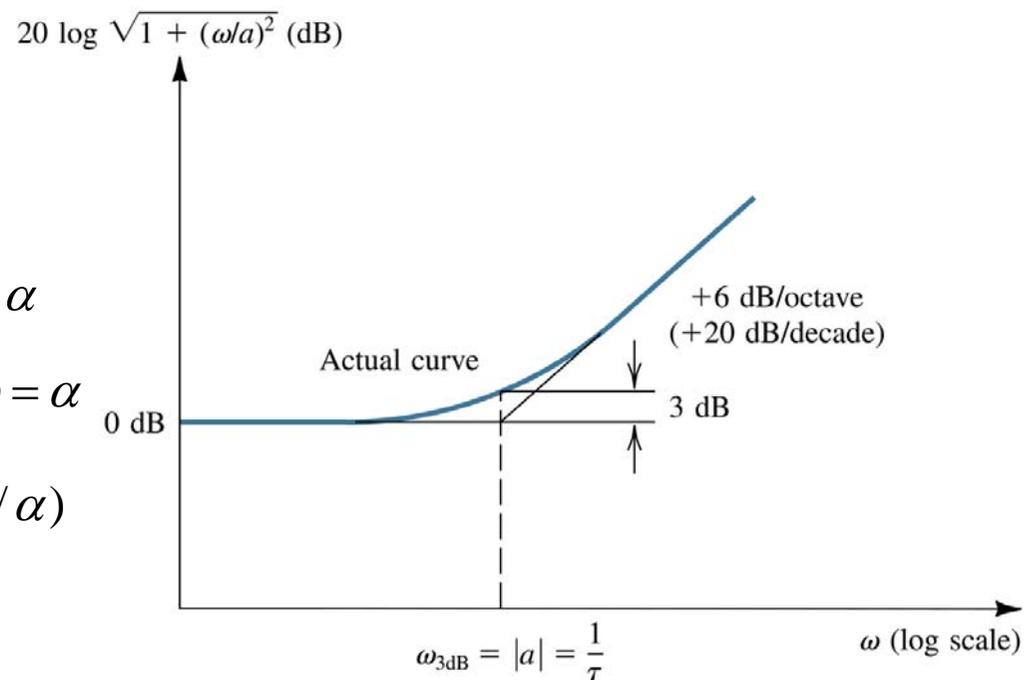- (i) $20\log_{10} \sqrt{1 + (\omega / \alpha)^2} \approx 0$ for $\omega \ll \alpha$
- (ii) $20\log_{10} \sqrt{1 + (\omega / \alpha)^2} = 3\text{dB}$ for $\omega = \alpha$
- (iii) $20\log_{10} \sqrt{1 + (\omega / \alpha)^2} \approx 20\log_{10}(\omega / \alpha)$
for $\omega \gg \alpha$



Bode Plot Example

Sketch the magnitude response of an amplifier with the transfer function of

$$T(s) = \frac{10s}{(1 + s/10^2)(1 + s/10^5)}$$

Curve 1: $T(s) = s$

A straight line with +20dB/decade,
passing through the point (1,0).

Curve 2:


$$T(s) = \frac{1}{(1 + s/10^2)}$$

Curve 3:

$$T(s) = \frac{1}{(1 + s/10^5)}$$

Curve 4: $T(s)=10$

$$20\log_{10} 10 = 20$$

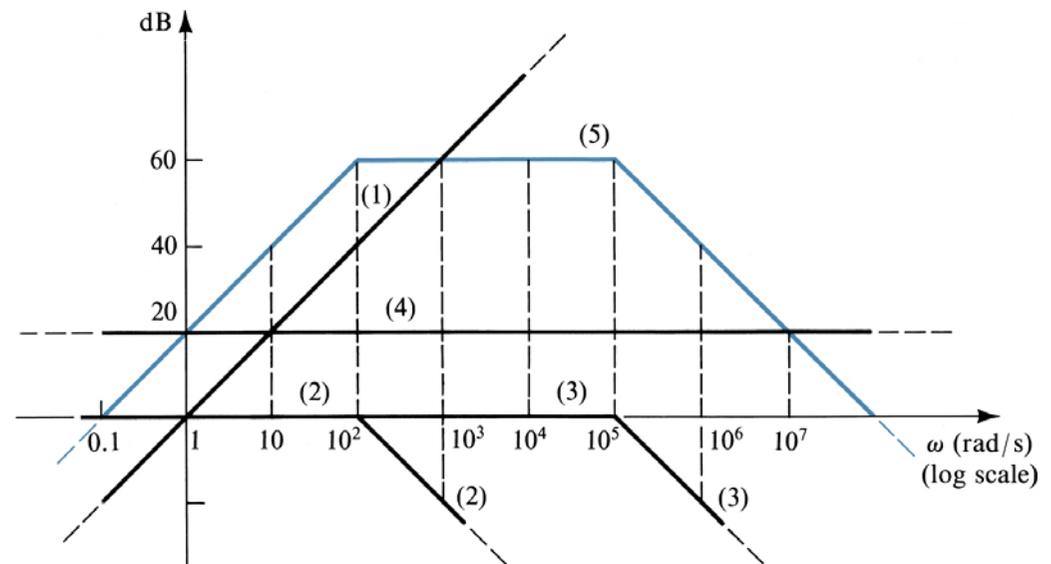

Adding four curves (1), (2), (3), (4), we have the overall magnitude response of curve (!



Phase Response

$$T(s) = \frac{K'(1 + s/\omega_{z_1})(1 + s/\omega_{z_2})\cdots(1 + s/\omega_{z_m})}{(1 + s/\omega_{p_1})(1 + s/\omega_{p_2})\cdots(1 + s/\omega_{p_n})} \quad s = j\omega$$

The phase of the transfer function is given by:

$$\begin{aligned} \angle T(j\omega) = & \angle(1 + j\omega/\omega_{z_1}) + \angle(1 + j\omega/\omega_{z_2}) + \dots + \angle(1 + j\omega/\omega_{z_m}) \\ & - \angle(1 + j\omega/\omega_{p_1}) - \angle(1 + j\omega/\omega_{p_2}) - \dots - \angle(1 + j\omega/\omega_{p_n}) \end{aligned}$$



Phase Response of a First Order Term


Consider the general term $T(s) = \frac{1}{1 + s/\alpha} \Big|_{s=j\omega} = \frac{1}{1 + j\omega/\alpha}$

$$\theta = \angle T = -\tan^{-1} \frac{\omega}{\alpha}$$

(i) $\omega = 0.1\alpha \Rightarrow \theta = -\tan^{-1} 0.1 = -5.7^\circ$

(ii) $\omega = \alpha \Rightarrow \theta = -\tan^{-1} 1 = -45^\circ$

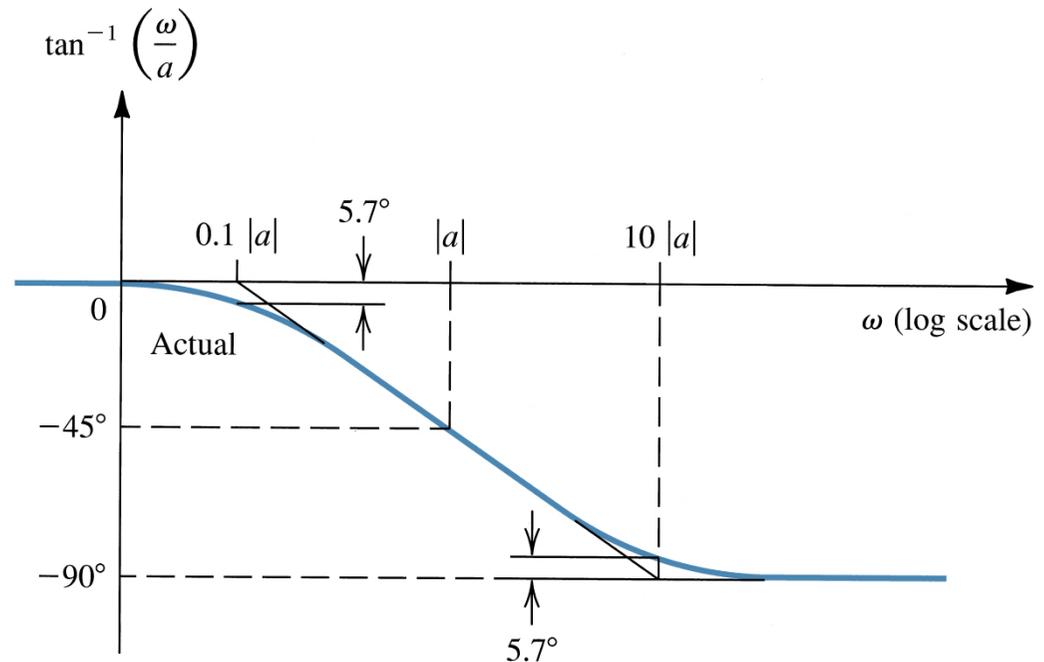(iii) $\omega = 10\alpha$
 $\Rightarrow \theta = -\tan^{-1} 10$
 $= -(90^\circ - \tan^{-1} 0.1)$
 $= -(90^\circ - 5.7^\circ)$



Example

Find the Bode plot for the phase response of $T(s) = \frac{10s}{(1+s/10^2)(1+s/10^5)}$

Curve 1: For $T(s)=s$, $s=j\omega$,


$$\theta = 90^\circ$$

Curve 2:

$$T(s) = \frac{1}{(1+s/10^2)}$$

Curve 3:

$$T(s) = \frac{1}{(1+s/10^5)}$$

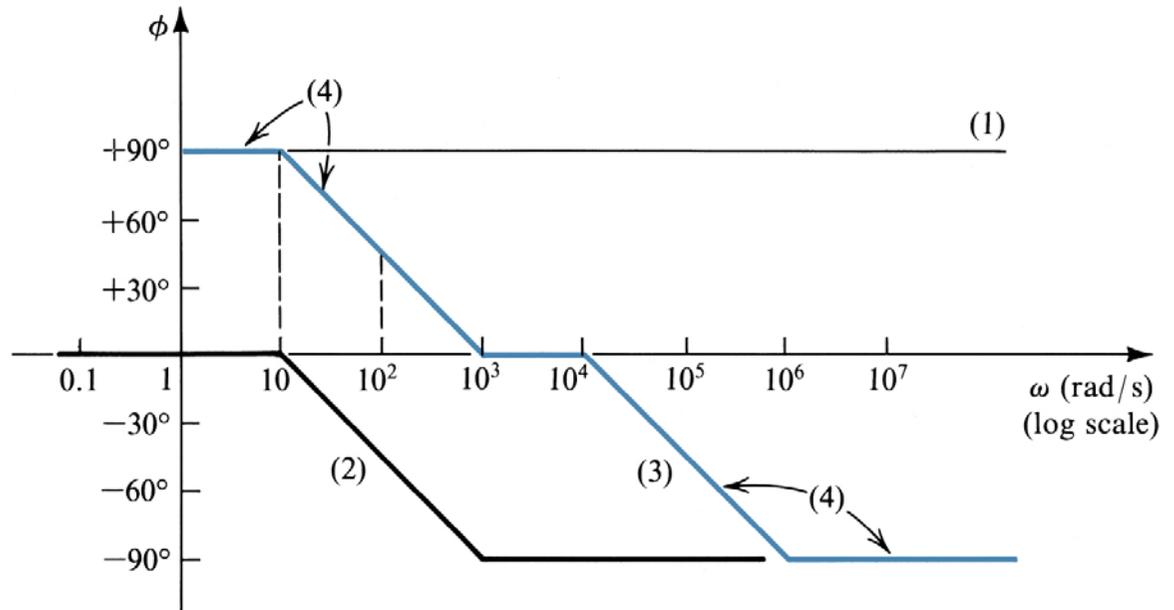

Adding curves (1), (2), and (3), we have curve (4), the Bode plot for the phase response.



Topics to cover ...


- Miller Effect
- Bode Plot
- Negative Feedback
 - Properties
 - Topologies
 - Stability issue



Background

Passive circuits

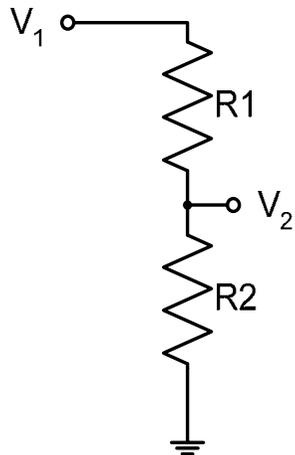- Gain < 1
- “Gain” can be very accurate
 - E.g., in 2-resistor string:



$$A = \frac{V_2}{V_1} = \frac{R_2}{R_1 + R_2}$$

A depends only on resistance ratio, which is independent on temperature, etc.

Active circuits

- Can provide large gain $\gg 1$
- But gain is inaccurate
 - E.g., in CS amplifier:


$$|A| = g_m R_L$$
$$g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_D}$$

- g_m depends on mobility (which in turn depends on Temp, doping level), W/L and I_D . All have large tolerance except W/L
- $|A|$ can vary by $\pm 50\%$

Feedback circuits: combine the advantages of both!



Classical Feedback System

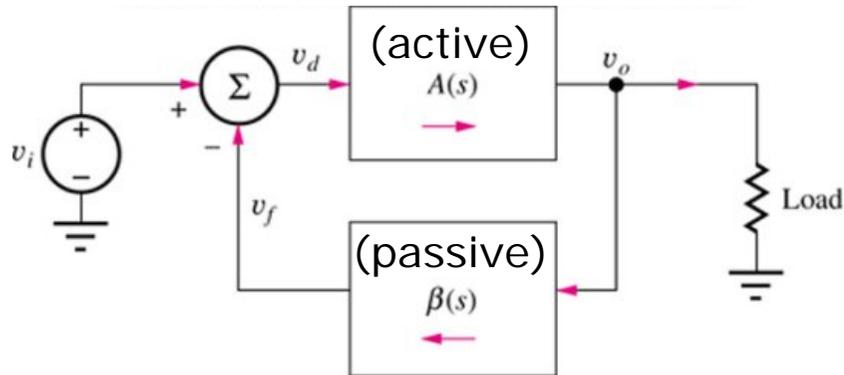

$$V_o(s) = V_d(s)A(s)$$

$$V_f(s) = V_o(s)\beta(s)$$

$$V_d(s) = V_i(s) - V_f(s)$$

- $A(s)$ = transfer function of open-loop amplifier, or **open-loop gain**
- $\beta(s)$ = transfer function of feedback network

Assumptions:

1. Feedback network and amplifier do not load each other
2. Signal flows are unidirectional

Closed-loop gain:

$$A_f(s) = \frac{V_o(s)}{V_i(s)} = \frac{A(s)}{1 + A(s)\beta(s)} = \frac{A(s)}{1 + T(s)}$$

$T(s) = A(s)\beta(s)$ is called **loop gain**

For negative feedback: $T(s) > 0$

For positive feedback: $T(s) < 0$

A_f is smaller than A by $1/[1 + A(s)\beta(s)]$



Closed-Loop Gain

- For $A\beta \gg 1$:

$$A_f = \frac{A}{1+A\beta} \approx \frac{1}{\beta}$$

- β is realized by accurate passive network
- Since $\beta < 1$, we have $A_f > 1$
- The closed-loop gain >1 and is accurate

Feedback combines the advantages of both passive and active circuits!



Topics to cover ...

- Miller Effect
- Bode Plot
- Negative Feedback

– Properties

– Topologies

– Stability issue



Desensitize the gain

$$A_f = \frac{A}{1 + A\beta}$$

Assume that β is constant. Taking differentials of both sides of the closed-loop gain with respect to A results in

$$\frac{dA_f}{dA} = \frac{1}{(1 + A\beta)} - \frac{A\beta}{(1 + A\beta)^2} = \frac{1}{(1 + A\beta)^2}$$

$$\rightarrow \frac{dA_f}{A_f} = \frac{1}{(1 + A\beta)} \frac{dA}{A}$$

which says that the percentage change in A_f (due to variations in some circuit parameter) is smaller than the percentage change in A by the amount of feedback.



Extend the Bandwidth

Consider an amplifier whose high-freq response is characterized by a single pole:

$$A(s) = \frac{A_M}{1 + s / \omega_H}$$

Therefore,

$$A_f(s) = \frac{A(s)}{1 + A(s)\beta} = \frac{\frac{A_M}{1 + s / \omega_H}}{1 + \frac{\beta A_M}{1 + s / \omega_H}} = \frac{A_M}{1 + \beta A_M + s / \omega_H}$$
$$= \frac{A_M / (1 + A_M \beta)}{1 + s / \omega_H (1 + A_M \beta)}$$

The upper-cutoff frequency ω_{Hf} of the closed loop amplifier is given by:


$$\omega_{Hf} = \omega_H (1 + A_M \beta)$$

Similarly, it can be proven that the lower cutoff frequency ω_{Lf} is given by

$$\omega_{Lf} = \omega_L / (1 + A_M \beta)$$



Reduce Nonlinear Distortion

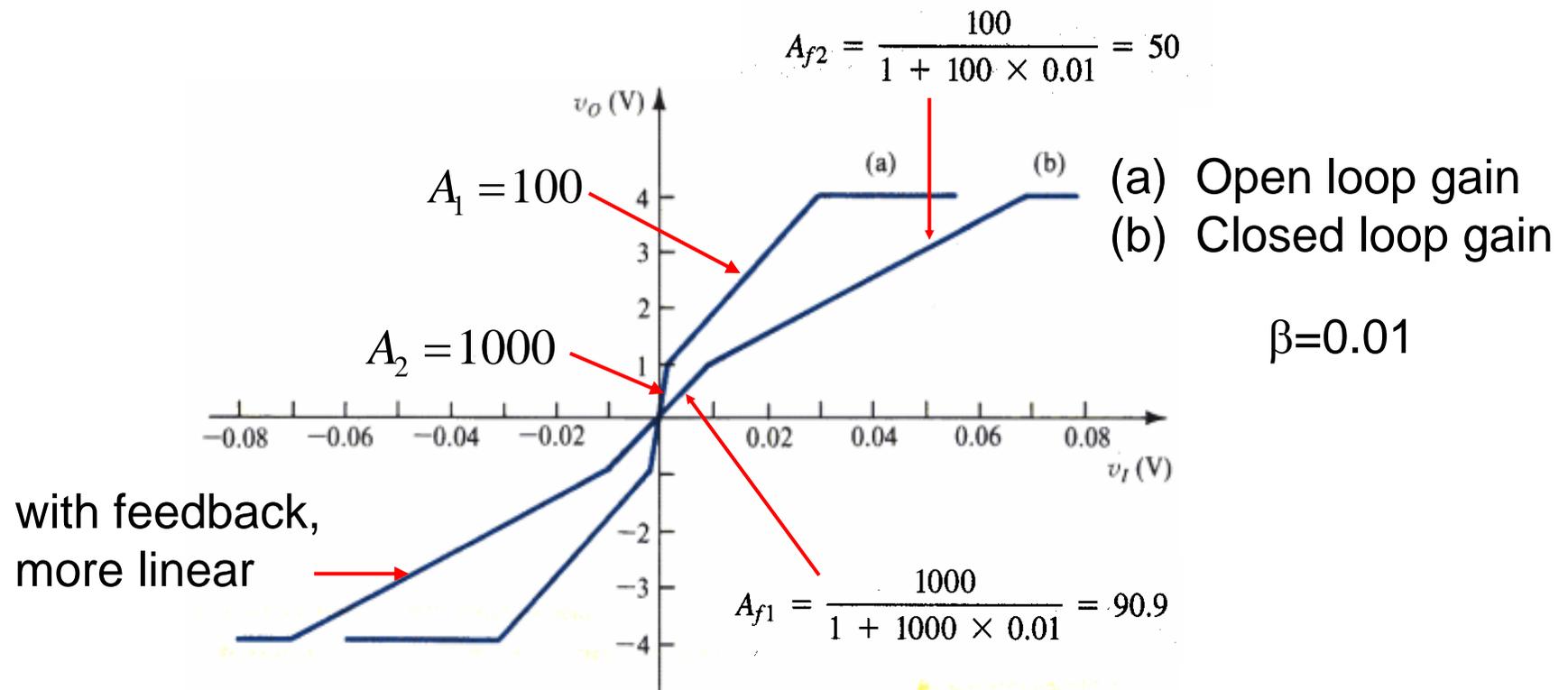

Effects of Negative Feedback

- ***Gain Sensitivity***
 - Feedback reduces sensitivity of gain to variations in values of transistor parameters and circuit elements.
- ***Bandwidth***
 - Bandwidth of amplifier can be extended using feedback.
- ***Nonlinear Distortion***
 - Feedback reduces effects of nonlinear distortion.

In short, the basic idea of negative feedback is to trade off gain for other desirable properties.




Topics to cover ...

- Miller Effect
- Bode Plot
- Negative Feedback
 - Properties
 - Topologies
 - Stability issue




Feedback Topologies

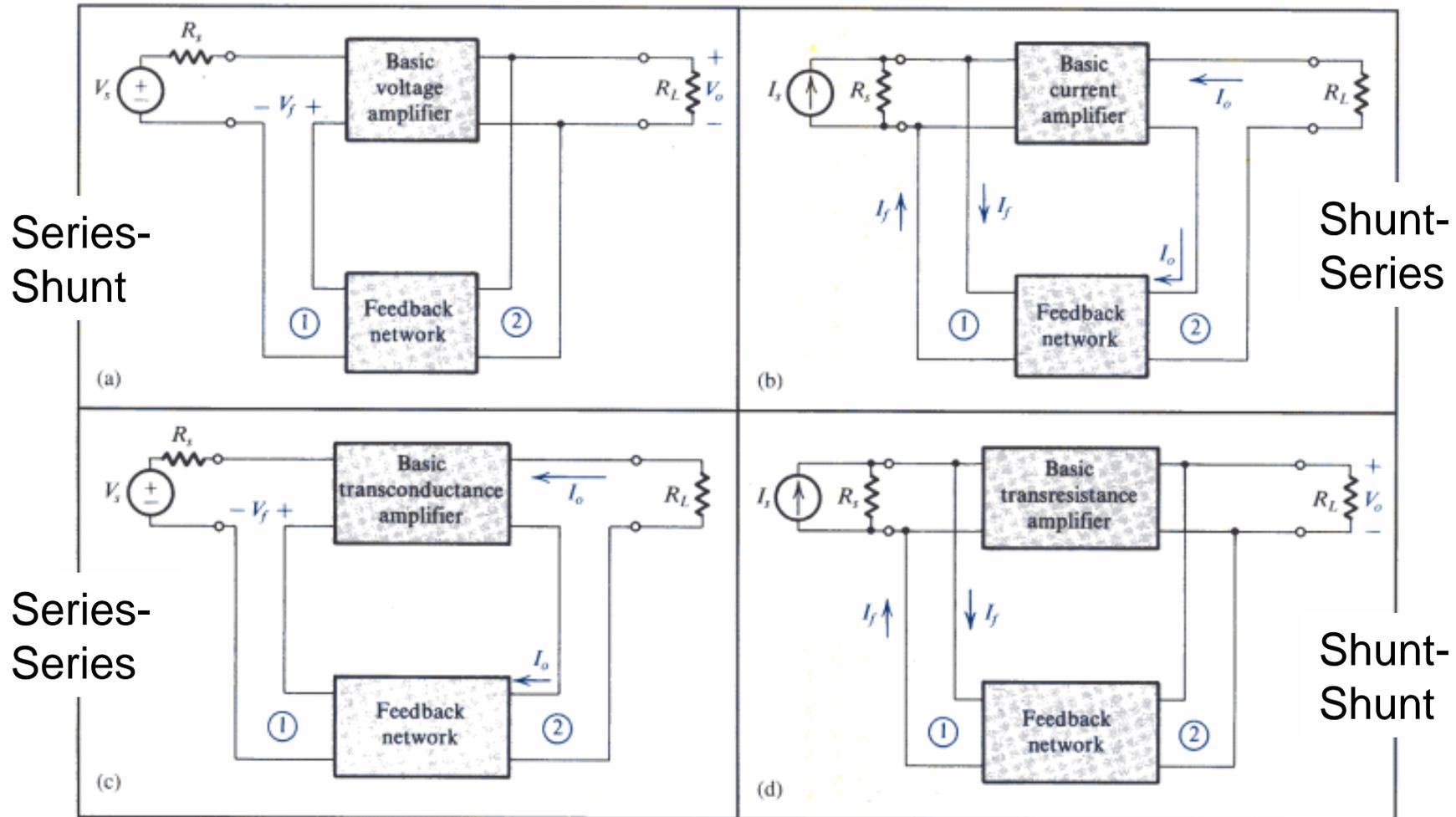

Shunt = Parallel




Series-Shunt Topology

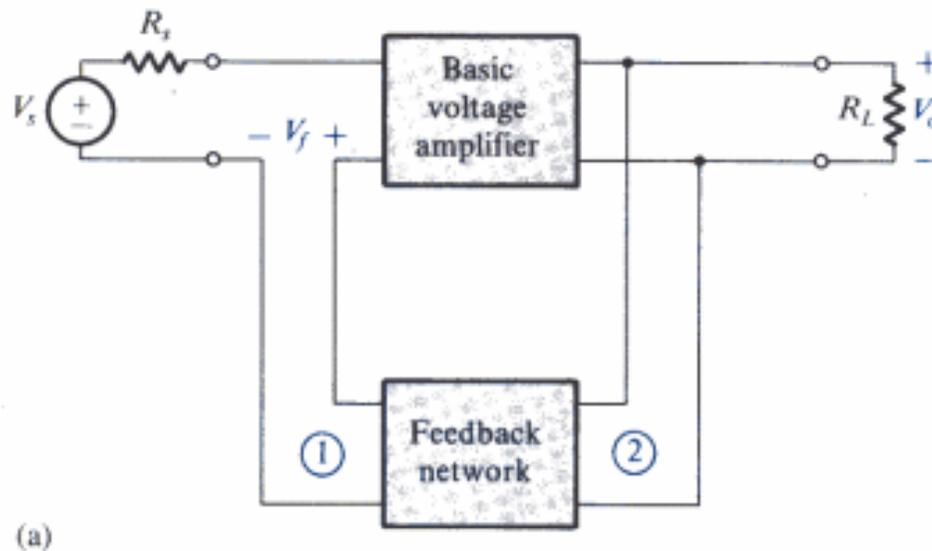


- Measure the output voltage, subtract a voltage quantity from input
- Input resistance \uparrow due to series connection
- Output resistance \downarrow due to shunt connection
- Used in voltage amplifier




Series-Shunt Example

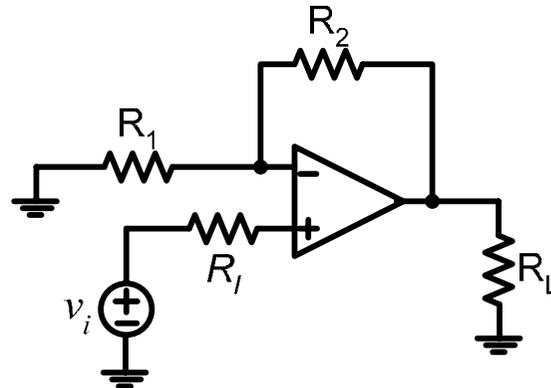

With two ports identified:

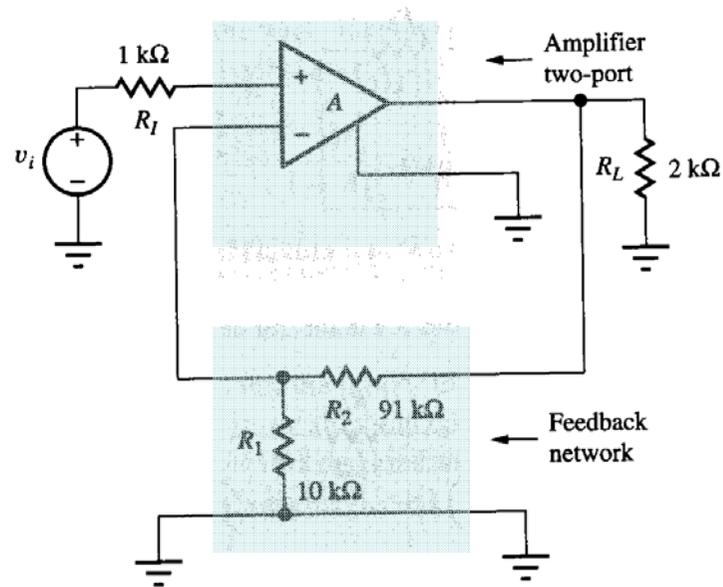



Shunt-Series Topology

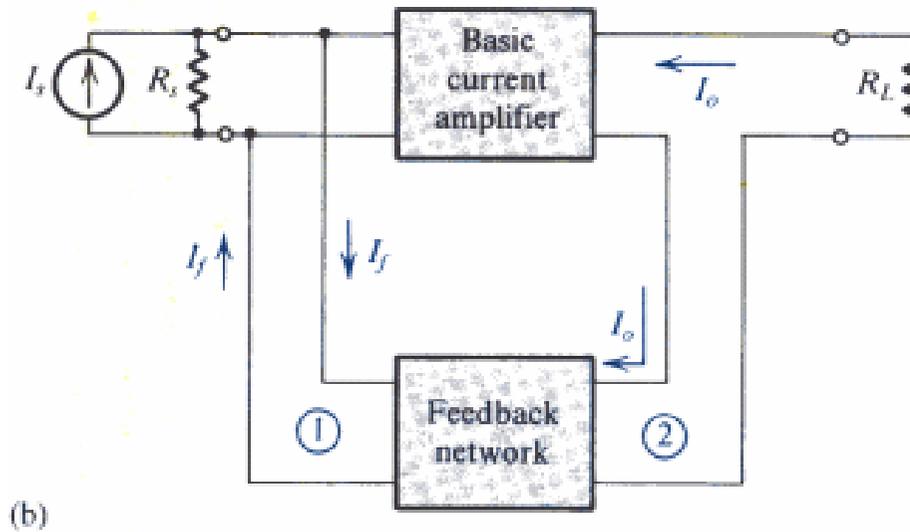

- Measure the output current, subtract a current quantity from input
- Input resistance \downarrow
- Output resistance \uparrow
- Used in current amplifier




Shunt-Series Example

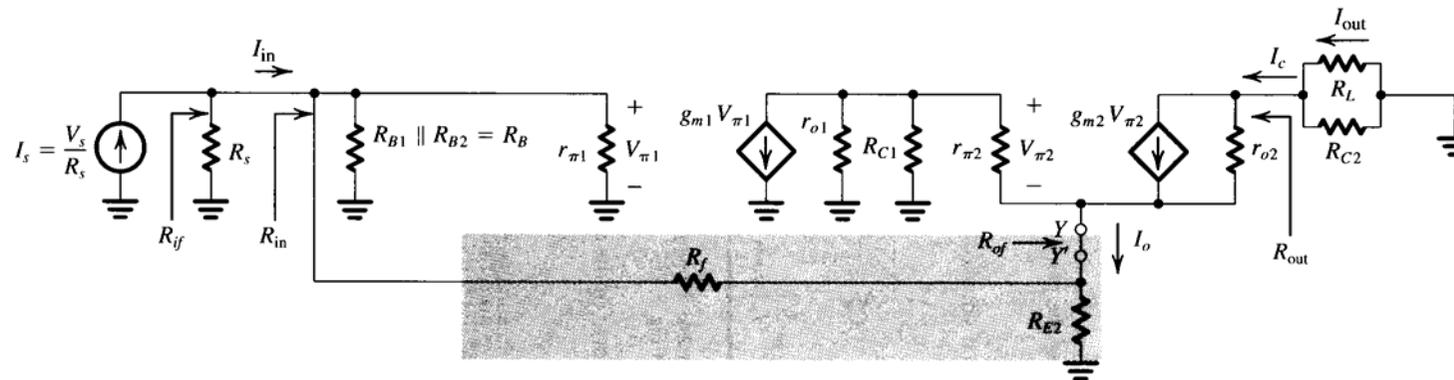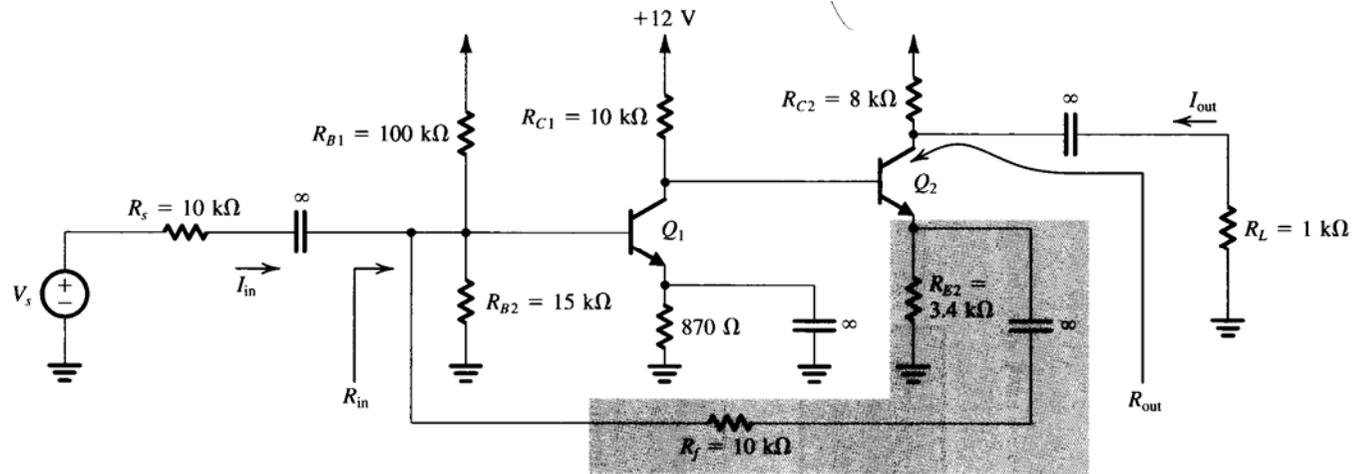

Small signal equivalent




Shunt-Shunt Topology

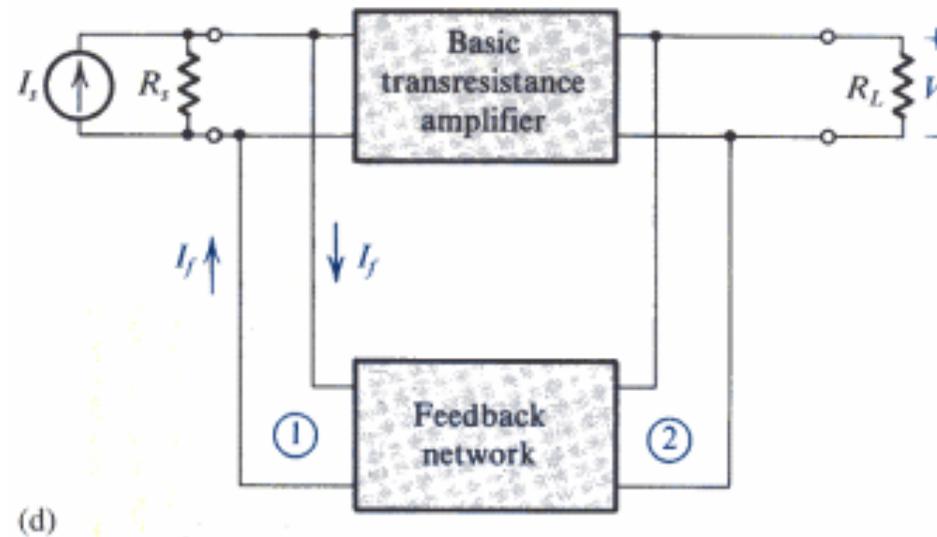


- Measure the output voltage, subtract a current quantity from input
- Input resistance ↓
- Output resistance ↓
- Used in trans-resistance (or more general, trans-impedance) amplifier




Shunt-Shunt Example

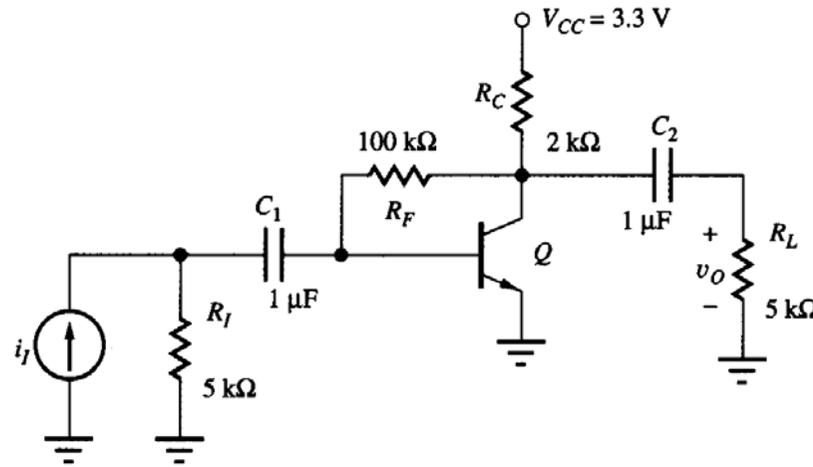

Two-port
representation:

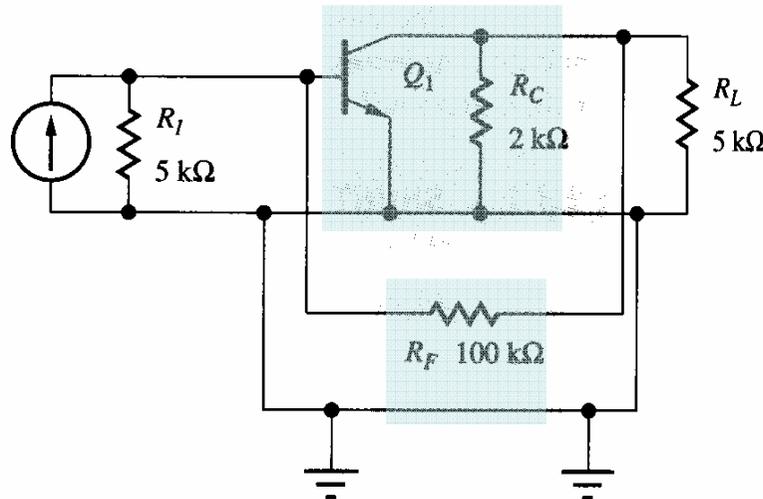


Series-Series Topology

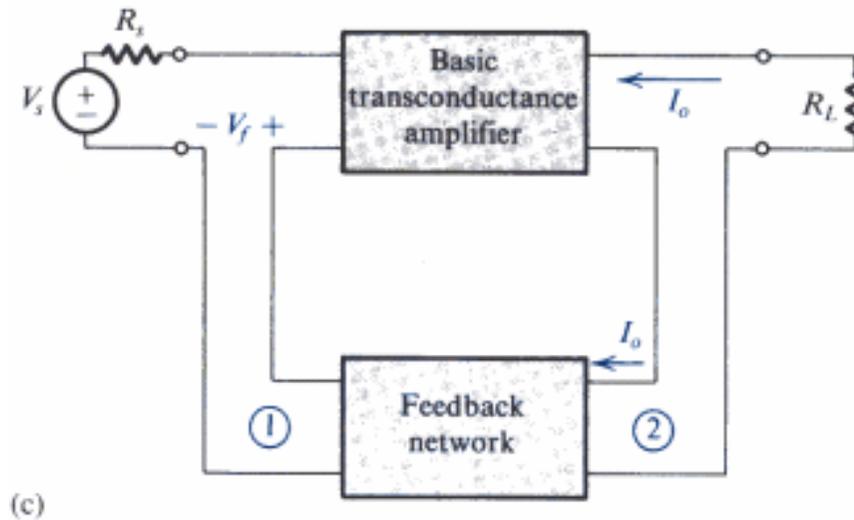


- Measure the output current, subtract a voltage quantity from input
- Input resistance \uparrow
- Output resistance \uparrow
- Used in transconductance amplifier



Series-Series Example

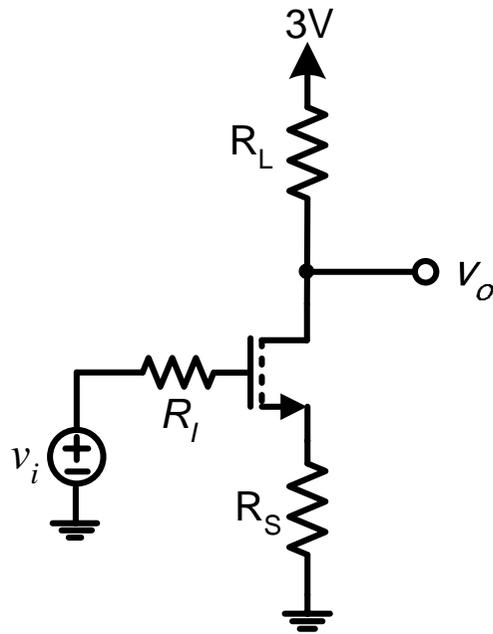

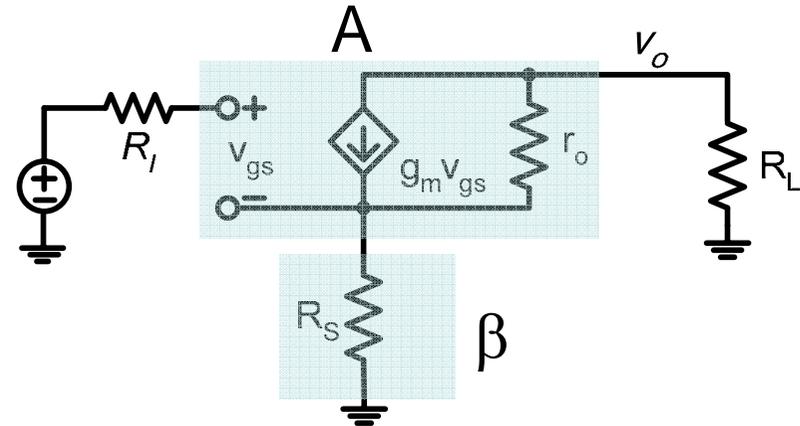Source-degenerated
common-source amplifier



Small signal equivalent



Topics to cover ...

- Miller Effect
- Bode Plot
- Negative Feedback
 - Properties
 - Topologies
 - Stability issue




Stability of Feedback Amplifiers

Closed-loop gain ($s=j\omega$):
$$A_f(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)\beta(j\omega)}$$

Loop gain:
$$T(j\omega) \equiv A(j\omega)\beta(j\omega) = |A(j\omega)\beta(j\omega)| e^{j\Phi(\omega)}$$

At the frequency where $\Phi(\omega)$ becomes 180° :

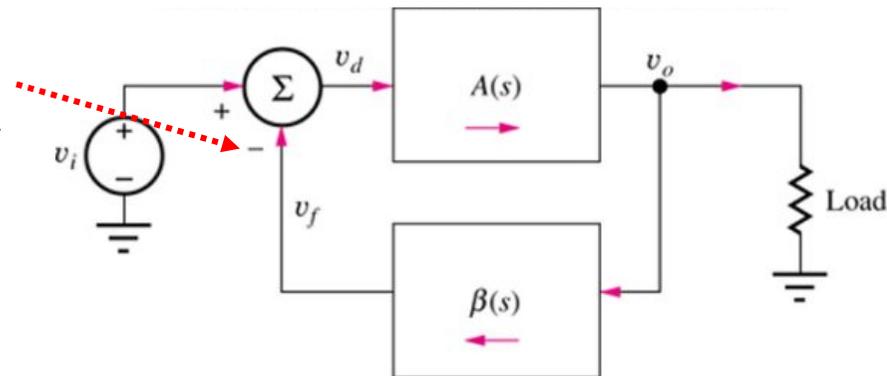Subtraction becomes addition;
Feedback becomes effectively
positive.




Signal adds to itself in-phase
every time it travels the loop.

Case 1: $|T| < 1$,
feedback amplifier
will be stable.

Case 2: $|T| \geq 1$,
feedback amplifier will
become unstable.



Determine Stability: Nyquist plot

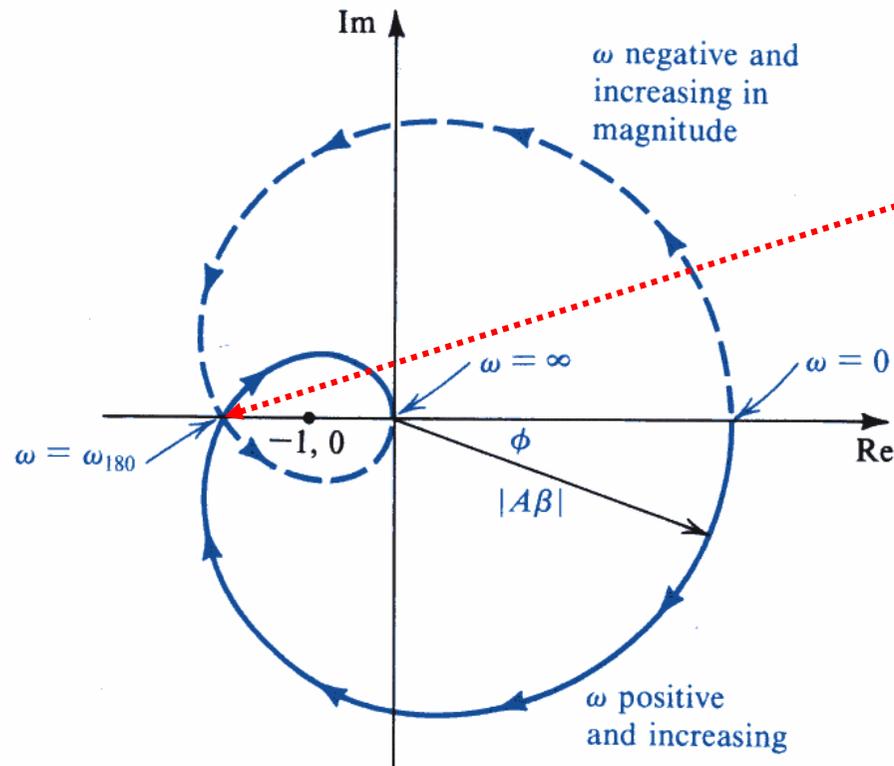

- If the intersection occurs to the left of the point $(-1,0)$, the amplifier is unstable
- Otherwise, the amplifier is stable

Plot the value of $T(j\omega)$ in the complex plane for ω increasing from 0 to infinity






Stability and Pole Location


The impulse response for a transfer function with poles at $\sigma_o \pm j\omega_n$ will contain the term:

$$v(t) = e^{\sigma_o t} [e^{+j\omega_n t} + e^{-j\omega_n t}] = 2e^{\sigma_o t} \cos(\omega_n t)$$

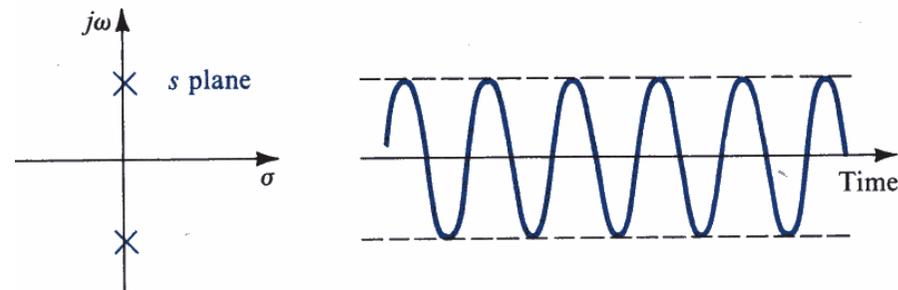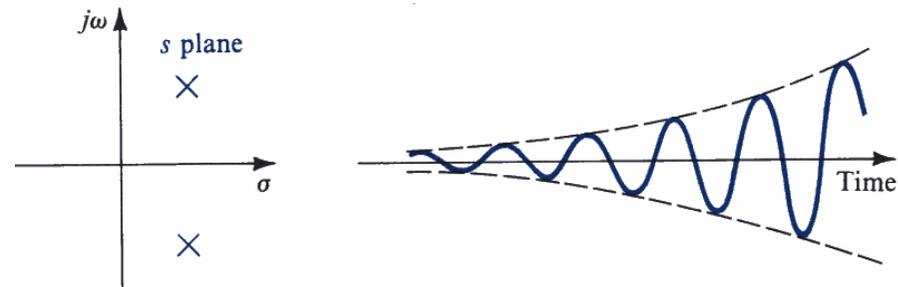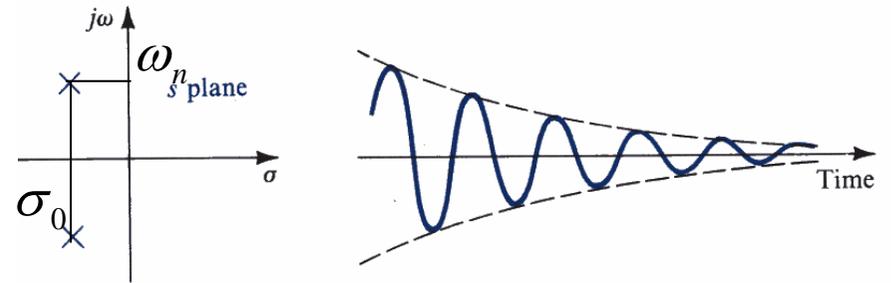- Poles lie in the left half of the s-plane:
Stable, Decaying Oscillations
- Poles lie in the right half of the s-plane:
Unstable, Growing Oscillations
- A pair of complex conjugate poles on the $j\omega$ axis:
Sustained Oscillations



Determine Stability: Root Locus

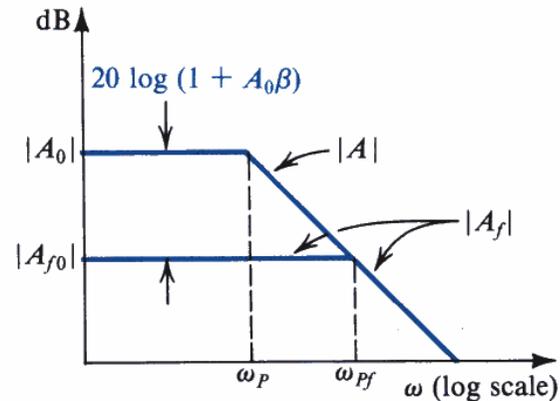

Considering an amplifier with single pole: $A(s) = \frac{A_0}{1 + s / \omega_p}$


Pole location: ω_p

The closed-loop gain is: $A_f(s) = \frac{A(s)}{1 + A(s)\beta} = \frac{A_0 / (1 + A_0\beta)}{1 + s / \omega_p (1 + A_0\beta)}$

Pole location: $\omega_{pf} = \omega_p (1 + A_0\beta)$



Determine Stability: Root Locus

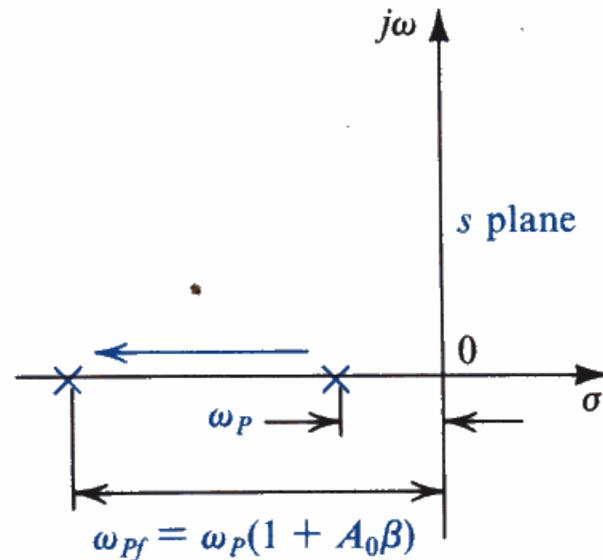

Root locus: pole location of $A_f(s)$ while increasing $A_0\beta$

Single-pole amplifier is ***unconditionally stable*** as pole location is always in LHS. This can be understood because the phase lag associated with a single-pole response can never be greater than 90° .



Root Locus: Two-pole Amplifier

For an amplifier with two poles

$$A(s) = \frac{A_0}{(1 + s/\omega_{P1})(1 + s/\omega_{P2})}$$

Set $1 + A(s)\beta = 0$ to find the closed-loop poles:


$$s^2 + s(\omega_{P1} + \omega_{P2}) + (1 + A_0\beta)\omega_{P1}\omega_{P2} = 0$$

The standard form is:

$$s^2 + s\frac{\omega_o}{Q} + \omega_o^2 = 0 \quad Q = \frac{\sqrt{(1 + A_0\beta)\omega_{P1}\omega_{P2}}}{\omega_{P1} + \omega_{P2}}$$

The closed-loop poles are:

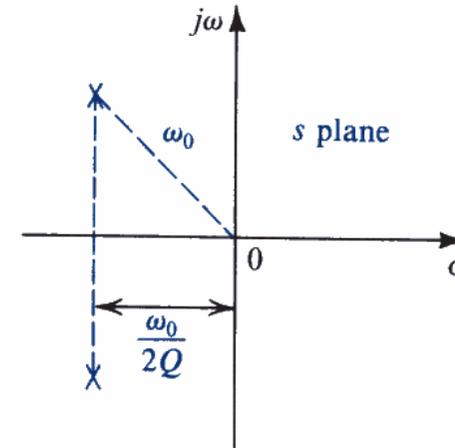
$$s = -\frac{1}{2}(\omega_{P1} + \omega_{P2}) \pm \frac{1}{2}\sqrt{(\omega_{P1} + \omega_{P2})^2 - 4(1 + A_0\beta)\omega_{P1}\omega_{P2}}$$



Pole location of A(s)



Root Locus: Two-pole Amplifier

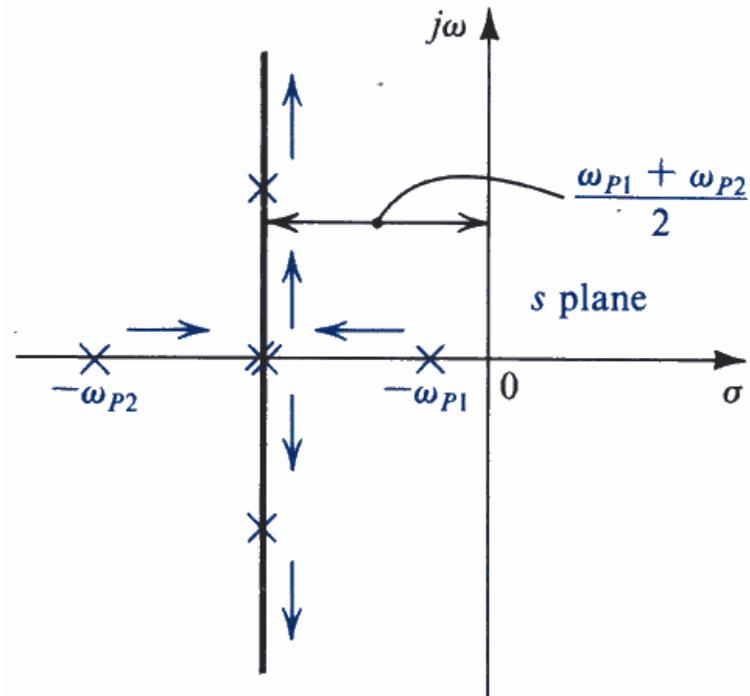


Pole location of $A_f(s)$ while increasing $A_0\beta$


The two-pole feedback amplifier is also ***unconditionally stable***.



Root Locus: Three-pole Amplifier

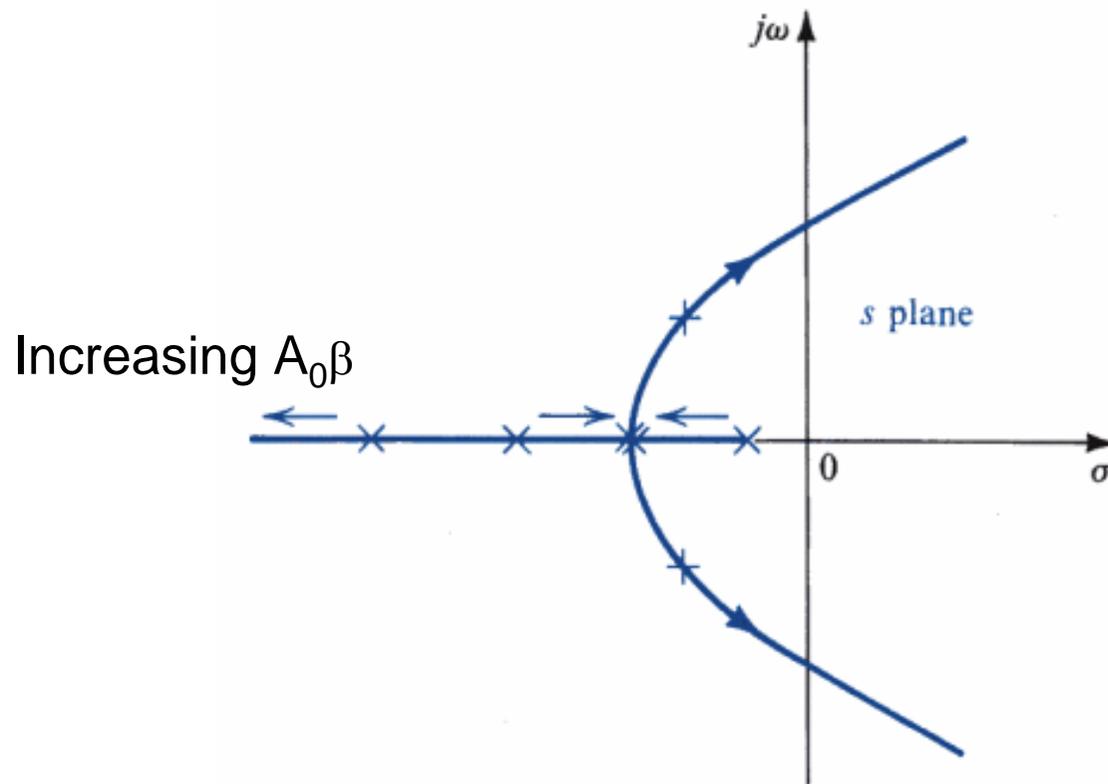

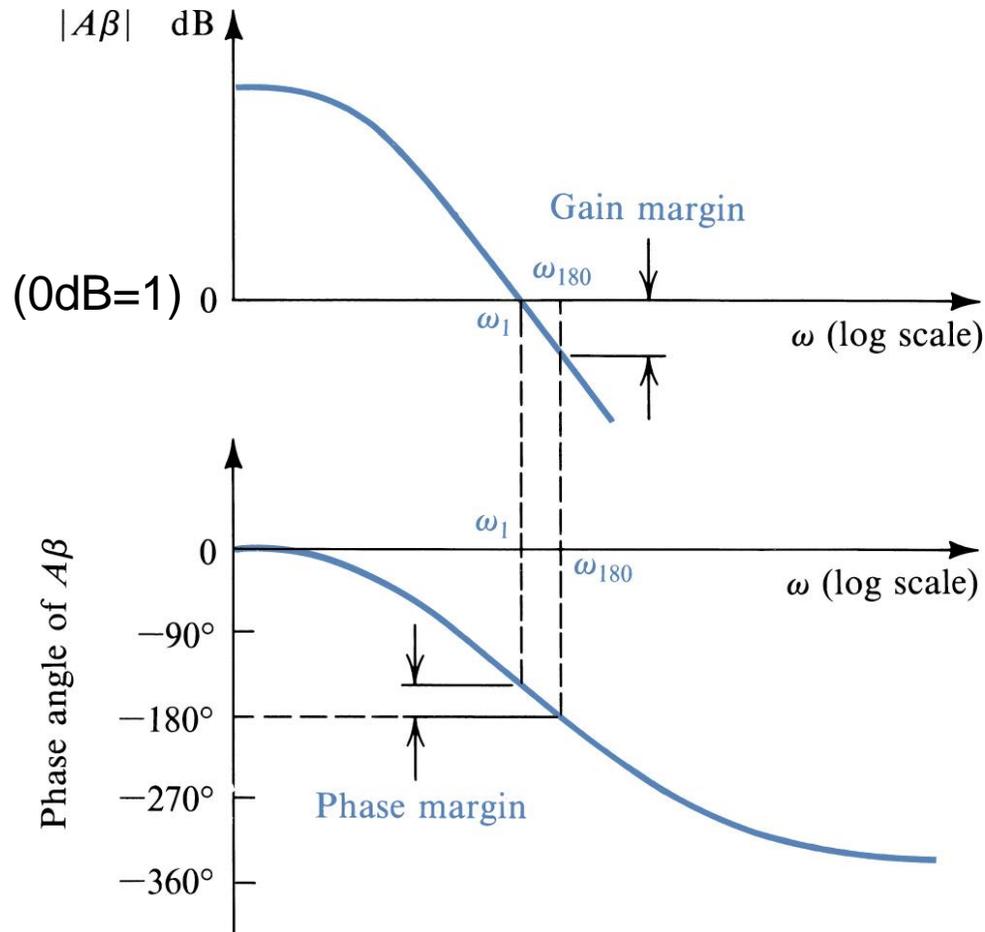Determine Stability from Bode Plot: Gain and Phase margins



- Gain margin = the difference between the value of $|A\beta|$ at ω_{180} and unity
 - ω_{180} : the frequency at which $\angle A\beta = 180^\circ$
- Phase margin = the difference between the phase angle at ω_1 and 180°
 - ω_1 : the frequency at which $|A\beta| = 1$
- Feedback amplifiers are normally designed with a phase margin of at least 45°



Example

- Evaluate the phase and gain margin of a feedback amplifier with the following loop gain:

$$A\beta = \frac{2 \times 10^{19}}{(s + 10^5)(s + 10^6)(s + 10^7)}$$

- A Matlab™ script is given in the next slide to generate the gain and phase response of the above loop gain



```

% Phase margin example for ELE2110A
% 17 April 2007, by KP Pun/EE/CUHK, free for distribution

clear all

% build loop gain function in zero-pole-gain form
Abeta_zpk=zpk([],[-1e5 -1e6 -1e7],2e19) % no zero
Abeta_tf=tf(Abeta_zpk)

w=logspace(4,7); % a vector storing the angular frequencies

% evaluate loop gain for s=j*w
Abeta_val=polyval(Abeta_tf.num{1},j*w)./polyval(Abeta_tf.den{1},j*w);


% evaluate the magnitude and phase of the loop gain
Abeta_db=20*log10(abs(Abeta_val));
Abeta_angle=unwrap(angle(Abeta_val))*180/pi;

% create the magnitude and phase plots
subplot(2,1,1);
semilogx(w,Abeta_db,'LineWidth',2); % plot the magnitude response
grid on; xlabel('Frequency (rad/s)','FontSize',14)
ylabel('Loop-gain A\beta (rad/s)','FontSize',14)
subplot(2,1,2);
semilogx(w,Abeta_angle,'LineWidth',2); % plot the phase response
xlabel('Frequency (rad/s)','FontSize',14);
ylabel('Phase (degree)','FontSize',14);grid on;

```



Phase and Gain Margins Example

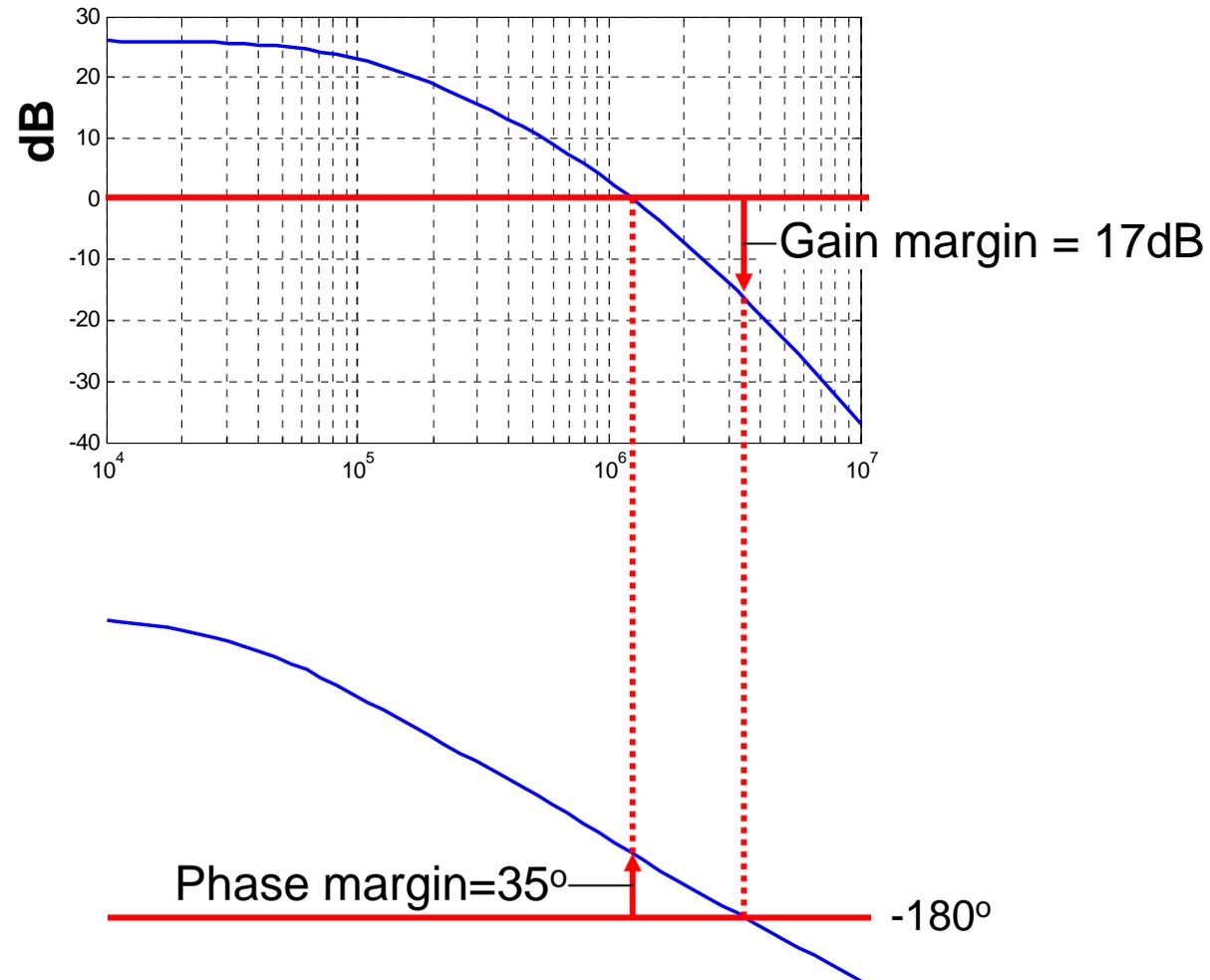

Phase Margin and Closed-Loop Gain

- Express loop gain in terms of open-loop gain and closed-loop gain:

$$20\log|A\beta| = 20\log|A| - 20\log\left|\frac{1}{\beta}\right|$$

– A: open loop gain

– $1/\beta$ = closed loop gain for $|A\beta| \gg 1$ $A_f = \frac{A}{1+A\beta} \cong \frac{1}{\beta}$

- Can plot open loop gain and closed loop gain separately
- The frequency at which these two curves intersect is the point $|A\beta| = 1$, or 0dB → Phase margin can be obtained



Phase Margin and Closed-Loop Gain

Example:

$$A = \frac{2 \times 10^{24}}{(s + 10^5)(s + 10^6)(s + 10^7)}$$

- Consider $1/\beta = 80\text{dB}$, 50dB and 0dB
- From the intersects we can find the corresponding phase margins

