

ELE 2110A Electronic Circuits

Week 14: Positive Feedback and Oscillator



Topics to cover ...

- Positive feedback
- Wien-Bridge Oscillator
- Phase Shift Oscillator

Reading assignment:
Chap 17.13 of Jeager and Blalock




Applications of Oscillators

- Clock input for CPU, DSP chips ...
- Local oscillator for radio receivers, mobile receivers, etc
- Signal generation for signal generators in your lab
- Clock input for analog-digital and digital-analog converters
- ...



Positive Feedback

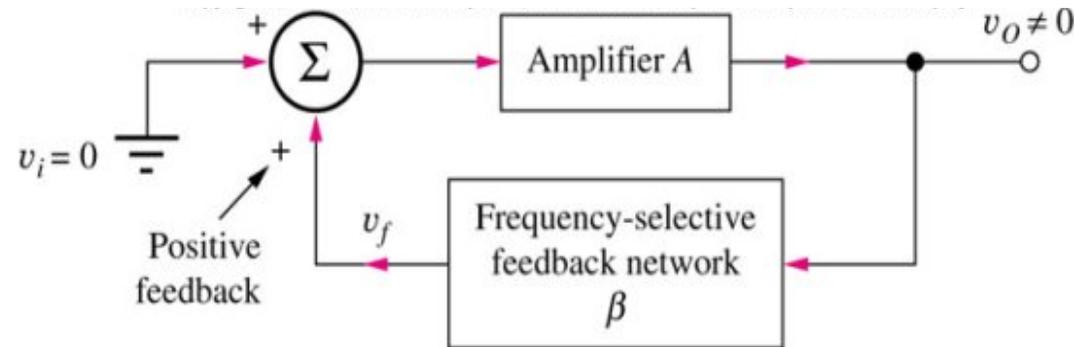


$$A_f(s) = \frac{A(s)}{1 - A(s)\beta(s)} = \frac{A(s)}{1 - T(s)}$$

- Designed to produce an output even though the input is zero
- Use positive feedback through frequency-selective feedback network to ensure sustained oscillation at ω_0



Barkhausen's Criteria for Oscillation

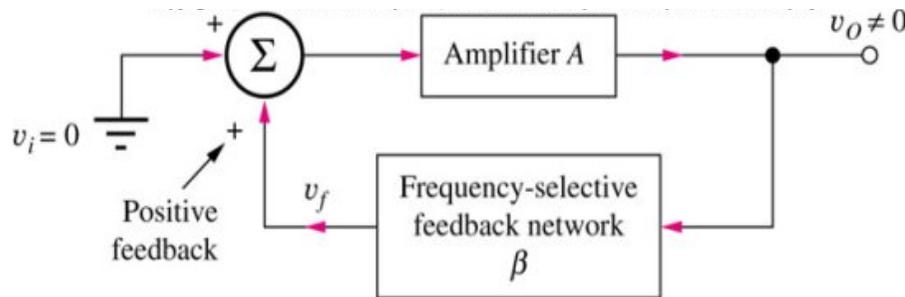

$$A_f(s) = \frac{A(s)}{1 - A(s)\beta(s)} = \frac{A(s)}{1 - T(s)}$$

- For sinusoidal oscillations,

$$1 - T(j\omega_o) = 0 \Rightarrow T(j\omega_o) = +1$$
- Barkhausen's criteria:

$$\angle T(j\omega_o) = 0^\circ \text{ or multiples of } 360^\circ$$

$$|T(j\omega_o)| = 1$$
- An impulse input starts the oscillation
 - Circuit noises, e.g., resistor thermal noise, serve this purpose
- Loop gain greater than unity causes a distorted oscillation to occur




Types of Oscillators

- Oscillators can be categorized as follows according to the types of feedback network used:
 - RC oscillator
 - LC oscillator
 - Crystal oscillator
- We will discuss the first type only



Wien-Bridge Oscillator

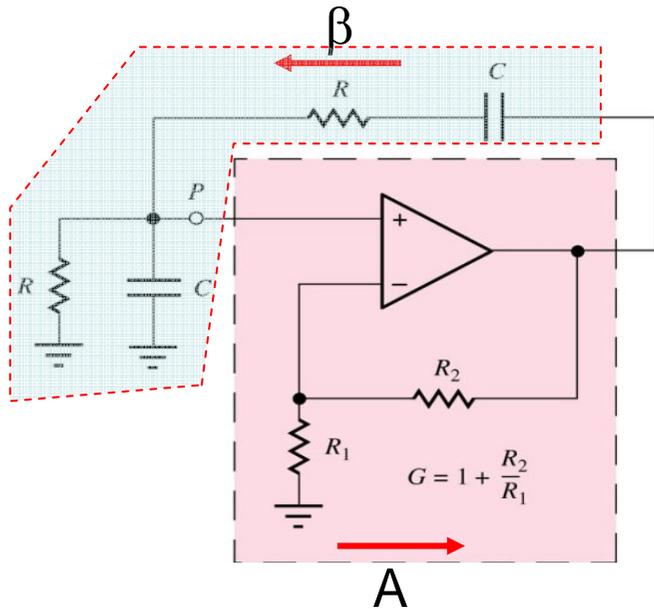

$$V_1(s) = \left(1 + \frac{R_2}{R_1}\right) V_I(s) = G V_I(s), \quad G = 1 + \frac{R_2}{R_1}$$

$$V_O(s) = V_1(s) \frac{Z_2(s)}{Z_1(s) + Z_2(s)}, \quad s = j\omega$$

Loop gain:

$$T(s) = \frac{V_O}{V_I} = \frac{j\omega R C G}{(1 - \omega^2 R^2 C^2) + 3j\omega R C}$$


Phase shift will be zero if $(1 - \omega^2 R^2 C^2) = 0$,

$$\text{At } \omega_0 = 1/RC, \quad T(j\omega_0) = +\frac{G}{3}$$


If $G=3$, sinusoidal oscillation is achieved.

This oscillator is used for frequencies up to few MHz, limited primarily by characteristics of amplifier.

Break the loop at P to find loop gain:

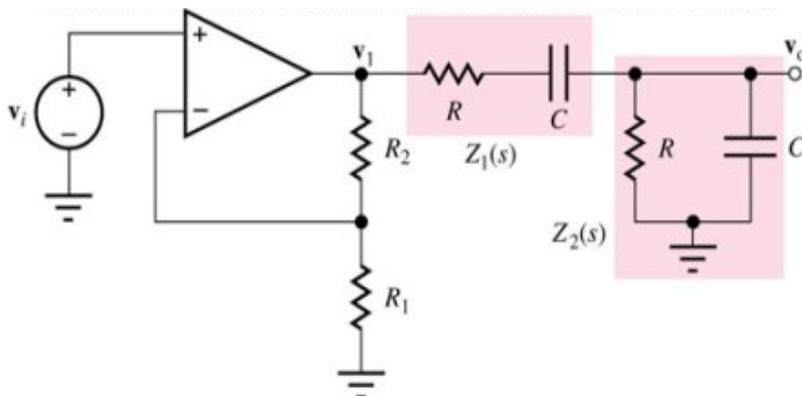

Phase-Shift Oscillator

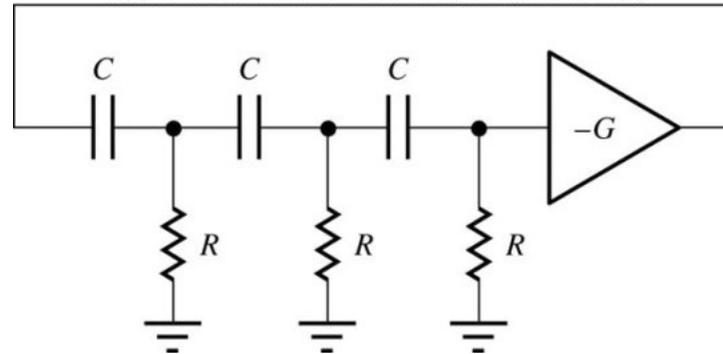

- The RC network is to provide 180° phase shift at the desired oscillation frequency
- At least three RC section is required:
 - One RC section can provide 90° phase shift at most:

$$H_{RC}(s) = \frac{R}{R + 1/j\omega C} = \frac{j\omega CR}{1 + j\omega CR}$$


$$\angle H_{RC}(s) = 90^\circ - \tan^{-1}(\omega RC) \leq 90^\circ$$

- Two RC sections provide 180° phase shift only at $\omega \rightarrow \infty$.



Phase-Shift Oscillator

One implementation:

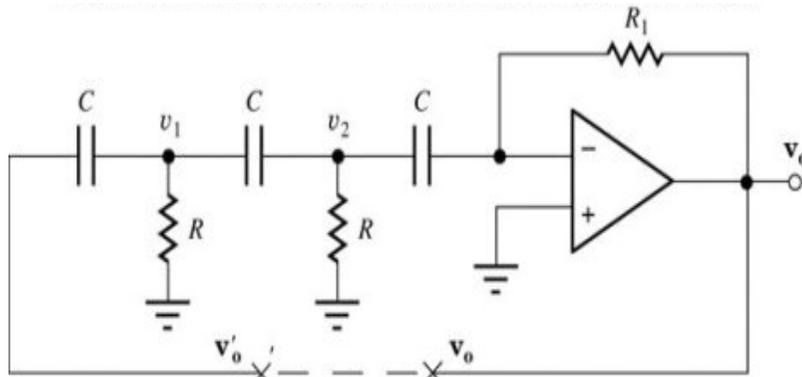

We have:

$$\therefore T(s) = \frac{V_O(s)}{V_O'(s)} = \frac{s^3 C^3 R^2 R_1}{3s^2 R^2 C^2 + 4sRC + 1}$$

Phase shift will be zero if $(1 - 3\omega_o^2 R^2 C^2) = 0$,

$$\therefore \omega_o = \frac{1}{\sqrt{3RC}}$$

At ω_o

$$T(j\omega_o) = \frac{\omega_o^2 C^2 R R_1}{4} = \frac{1}{12} \frac{R_1}{R}$$

KCL at v_1 and v_2 :

$$\begin{bmatrix} sCV_O'(s) \\ 0 \end{bmatrix} = \begin{bmatrix} (2sC+G) & -sC \\ -sC & (2sC+G) \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}$$

From v_2 to v_o :


$$\frac{V_O(s)}{V_2(s)} = -sCR_1$$

For $R_1 = 12R$, the Barkhausen's criterion is met.



Amplitude Stabilization

- As power supply voltage, component values and/or temperature change, the loop gain $|A\beta|$ deviates from 1 \rightarrow oscillation decays ($|A\beta| < 1$) or grows ($|A\beta| > 1$)
- Amplitude stabilization circuit \rightarrow automatically control the loop gain such that $A\beta=1$
- Example in Wien-bridge oscillator:

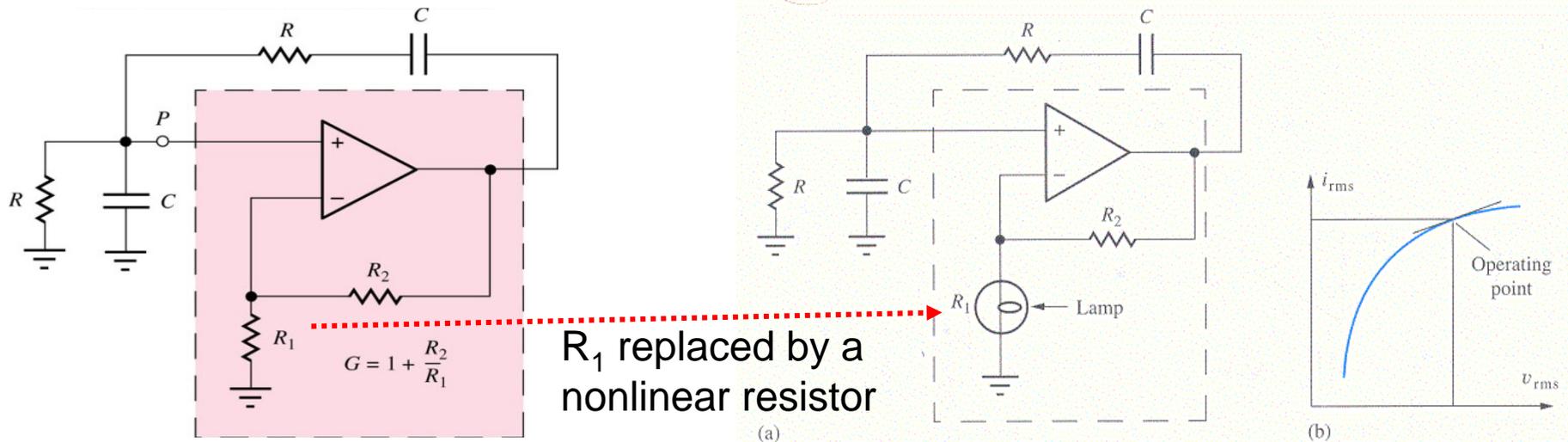


G must = 3
at oscillating freq.


When output amplitude increases
 $\rightarrow R_1$ increases due to heat
 $\rightarrow G$ decreases \rightarrow amplitude decreases



Amplitude Stabilization Circuit Example

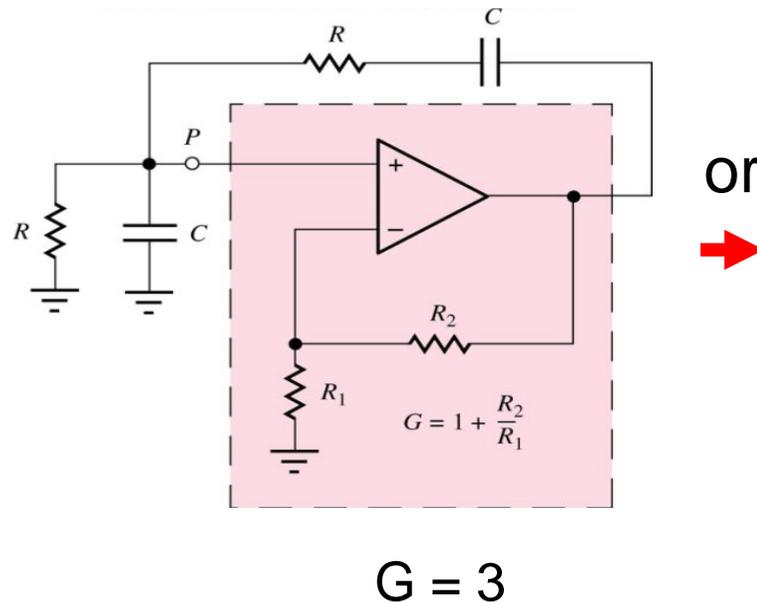

or
→

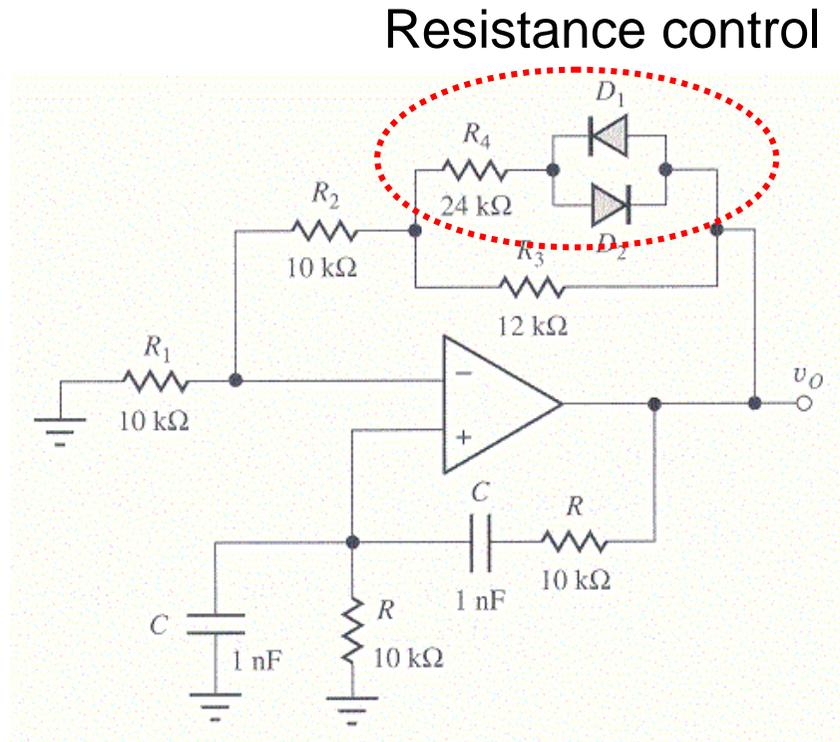

- R_4 and diodes D_1 and D_2 form a nonlinear resistor, whose value depends on output amplitude



Feedback Summary

- Feedback combines the advantages of passive circuits and active circuits
- Properties of negative feedback
 - Desensitize the gain
 - Extend the bandwidth
 - Reduce distortion
- Feedback circuits can be classified into four topologies
 - Series-series, series-shunt, shunt-series, shunt-shunt
- Stability is a special issue in feedback circuits. Stability can be determined by
 - Nyquist plot
 - Root locus diagram
 - Phase and gain margin in Bode plots
- Oscillators employ positive feedback circuits

