



Alexander-Sadiku

Fundamentals of Electric Circuits

Chapter 14

Frequency Response

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

1



Frequency Response

Chapter 14

- 14.1 Introduction
- 14.2 Transfer Function
- 14.3 Series Resonance
- 14.4 Parallel Resonance
- 14.5 Passive Filters

2

14.1 Introduction (1)


What is Frequency Response of a Circuit?

It is the variation in a circuit's behavior with change in signal frequency and may also be considered as the variation of the gain and phase with frequency.

3

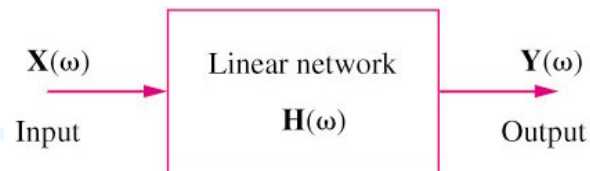14.2 Transfer Function (1)

The transfer function $H(\omega)$ of a circuit is the frequency-dependent ratio of a phasor output $Y(\omega)$ (an element voltage or current) to a phasor input $X(\omega)$ (source voltage or current).



$$H(\omega) = \frac{Y(\omega)}{X(\omega)} = |H(\omega)| \angle \phi$$


4

14.2 Transfer Function (2)

Four possible transfer functions:

$$H(\omega) = \text{Voltage gain} = \frac{V_o(\omega)}{V_i(\omega)}$$
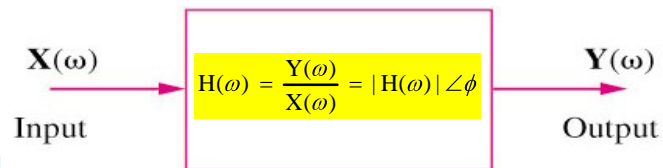
$$H(\omega) = \text{Transfer Impedance} = \frac{V_o(\omega)}{I_i(\omega)}$$



$$H(\omega) = \text{Current gain} = \frac{I_o(\omega)}{I_i(\omega)}$$

$$H(\omega) = \text{Transfer Admittance} = \frac{I_o(\omega)}{V_i(\omega)}$$


5

14.2 Transfer Function (3)


Example 1

For the RC circuit shown below, obtain the transfer function V_o/V_s and its frequency response.

Let $v_s = V_m \cos \omega t$.

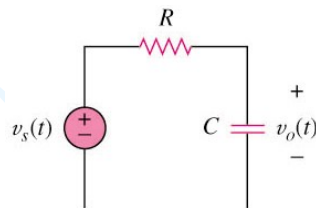

(a)

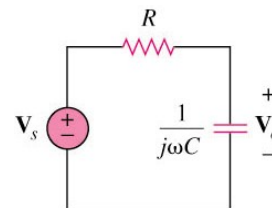

(b)

6

14.2 Transfer Function (4)




Solution:

The transfer function is

$$H(\omega) = \frac{V_o}{V_s} = \frac{1}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

The magnitude is $|H(\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_o)^2}}$

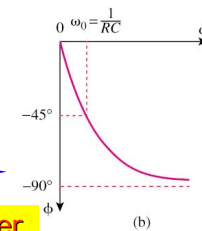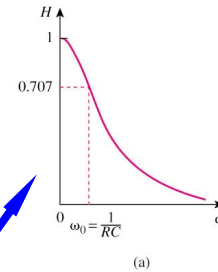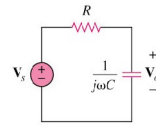The phase is $\phi = -\tan^{-1} \frac{\omega}{\omega_o}$
 $\omega_o = 1/RC$




Low Pass Filter

7

14.2 Transfer Function (5)

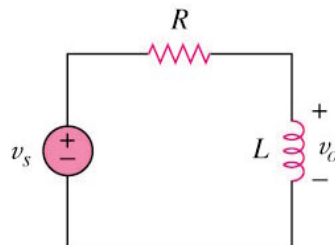Example 2

Obtain the transfer function V_o/V_s of the RL circuit shown below, assuming $v_s = V_m \cos \omega t$. Sketch its frequency response.




8

14.2 Transfer Function (6)

Solution:

The transfer function is
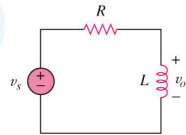
$$H(\omega) = \frac{V_o}{V_s} = \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{R}{j\omega L}}$$



The magnitude is


$$H(\omega) = \frac{1}{\sqrt{1 + \left(\frac{\omega_o}{\omega}\right)^2}}$$

The phase is

$$\phi = \angle 90^\circ - \tan^{-1} \frac{\omega}{\omega_o}$$

$$\omega_o = R/L$$


High Pass Filter

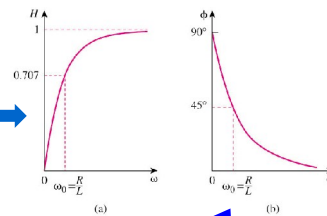

9

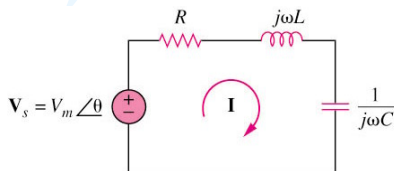14.3 Series Resonance (1)

Resonance is a condition in an RLC circuit in which the capacitive and inductive reactance are equal in magnitude, thereby resulting in **purely resistive** impedance.



$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$


Resonance frequency:

$$\omega_o = \frac{1}{\sqrt{LC}} \text{ rad/s} \quad \text{or}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

10

14.3 Series Resonance (2)

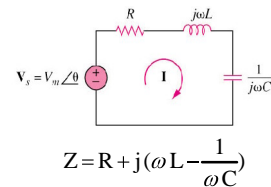

The features of series resonance:

The impedance is purely resistive, $Z = R$;

The supply voltage V_s and the current I are in phase, so $\cos \theta = 1$;

The magnitude of the transfer function $H(\omega) = Z(\omega)$ is minimum;

The inductor voltage and capacitor voltage can be much more than the source voltage.



11

14.3 Series Resonance (3)

Bandwidth B

The frequency response of the resonance circuit current is

$$I = |I| = \frac{V_m}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

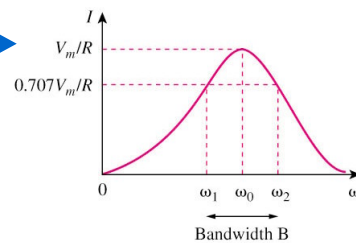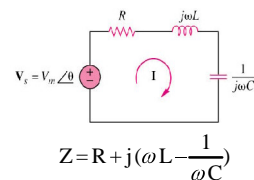

The average power absorbed by the RLC circuit is

$$P(\omega) = \frac{1}{2} I^2 R$$

The highest power dissipated occurs at resonance:

$$P(\omega_0) = \frac{1}{2} \frac{V_m^2}{R}$$

12

14.3 Series Resonance (4)

Half-power frequencies ω_1 and ω_2 are frequencies at which the dissipated power is **half the maximum value**:

$$P(\omega_1) = P(\omega_2) = \frac{1}{2} \frac{(V_m/\sqrt{2})^2}{R} = \frac{V_m^2}{4R}$$

The half-power frequencies can be obtained by setting Z equal to $\sqrt{2} R$.


$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_o = \sqrt{\omega_1 \omega_2}$$

Bandwidth B

$$B = \omega_2 - \omega_1$$

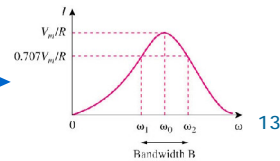

13

14.3 Series Resonance (5)

Quality factor, $Q = \frac{\text{Peak energy stored in the circuit}}{\text{Energy dissipated by the circuit in one period at resonance}} = \frac{\omega_o L}{R} = \frac{1}{\omega_o CR}$


The relationship between the B , Q and ω_o :

$$B = \frac{R}{L} = \frac{\omega_o}{Q} = \omega_o^2 CR$$

The quality factor is the **ratio** of its **resonant frequency** to its **bandwidth**.

If the bandwidth is **narrow**, the quality factor of the resonant circuit must be **high**.

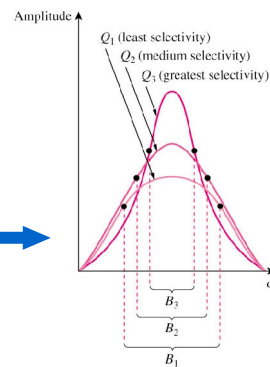If the band of frequencies is **wide**, the quality factor must be **low**.



14

14.3 Series Resonance (6)

Example 3


A series-connected circuit has $R = 4 \Omega$
and $L = 25 \text{ mH}$.

- Calculate the value of C that will produce a quality factor of 50.
- Find ω_1 and ω_2 , and B .
- Determine the average power dissipated at $\omega = \omega_0, \omega_1, \omega_2$. Take $V_m = 100\text{V}$.


15

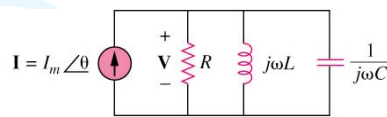14.4 Parallel Resonance (1)

It occurs when imaginary part of Y is zero


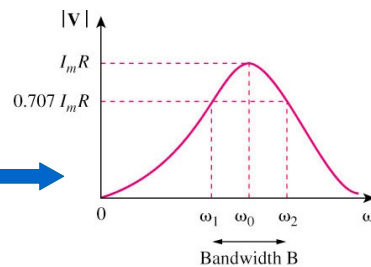
$$Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$



Resonance frequency:

$$\omega_o = \frac{1}{\sqrt{LC}} \text{ rad/s} \quad \text{or} \quad f_o = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

16

14.4 Parallel Resonance (2)

Summary of series and parallel resonance circuits:


<i>characteristic</i>	<i>Series circuit</i>	<i>Parallel circuit</i>
ω_0	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
Q	$\frac{\omega_0 L}{R}$ or $\frac{1}{\omega_0 RC}$	$\frac{R}{\omega_0 L}$ or $\omega_0 RC$
B	$\frac{\omega_0}{Q}$	$\frac{\omega_0}{Q}$
ω_1, ω_2	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$
$Q \geq 10, \omega_1, \omega_2$	$\omega_0 \pm \frac{B}{2}$	$\omega_0 \pm \frac{B}{2}$

17

14.4 Parallel Resonance (3)

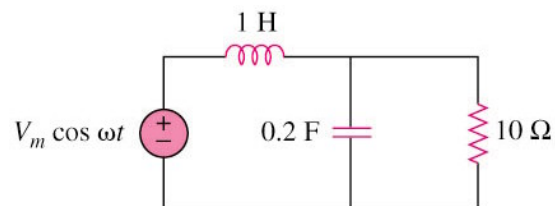Example 4

Calculate the resonant frequency of the circuit in the figure shown below.



Answer: $\omega = \frac{\sqrt{19}}{2} = 2.179 \text{ rad/s}$

18

14.5 Passive Filters (1)

A **filter** is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others.

Passive filter consists of only passive element R, L and C.


There are four types of filters.

Low Pass

High Pass

Band Pass

Band Stop

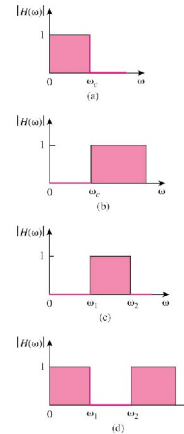


19

14.5 Passive Filters (2)

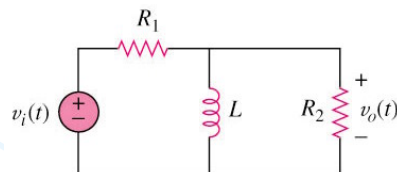Example 5

For the circuit in the figure below, obtain the transfer function $V_o(\omega)/V_i(\omega)$. Identify the type of filter the circuit represents and determine the corner frequency. Take $R_1=100\Omega =R_2$ and $L =2\text{mH}$.



Answer: $\omega = 25 \text{ krad/s}$

20

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.