

KIRCHHOFF VOLTAGE LAW

ONE OF THE FUNDAMENTAL CONSERVATION LAWS
IN ELECTRICAL ENGINEERING


THIS IS A CONSERVATION OF ENERGY PRINCIPLE
“ENERGY CANNOT BE CREATE NOR DESTROYED”




KIRCHHOFF VOLTAGE LAW (KVL)

KVL IS A CONSERVATION OF ENERGY PRINCIPLE

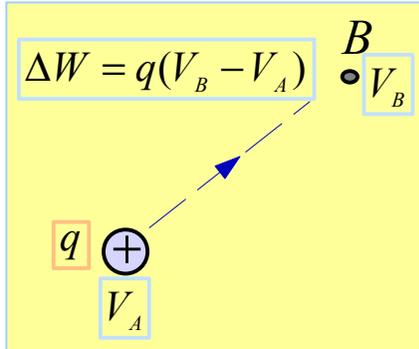A POSITIVE CHARGE GAINS ENERGY AS IT MOVES TO A POINT WITH HIGHER VOLTAGE AND RELEASES ENERGY IF IT MOVES TO A POINT WITH LOWER VOLTAGE



A "THOUGHT EXPERIMENT"

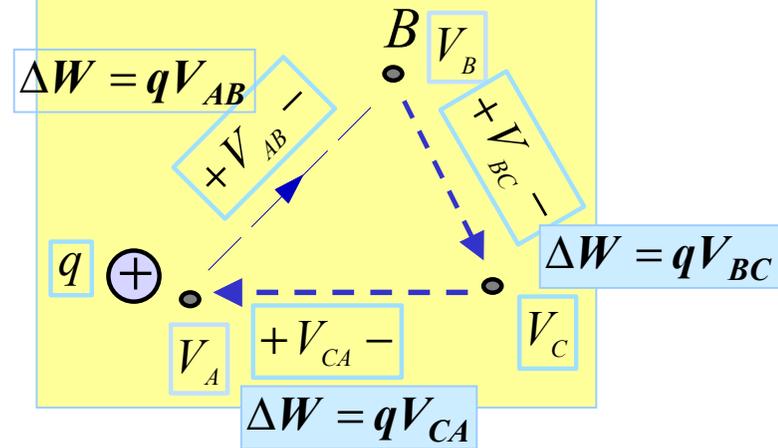

IF THE CHARGE COMES BACK TO THE SAME INITIAL POINT THE NET ENERGY GAIN MUST BE ZERO (Conservative network)


OTHERWISE THE CHARGE COULD END UP WITH INFINITE ENERGY, OR SUPPLY AN INFINITE AMOUNT OF ENERGY

$$q(V_{AB} + V_{BC} + V_{CD}) = 0$$


KVL: THE ALGEBRAIC SUM OF VOLTAGE DROPS AROUND ANY LOOP MUST BE ZERO

$$\text{A } -V \text{ from } A \text{ to } B \equiv \text{A } +(-V) \text{ from } A \text{ to } B$$

A VOLTAGE RISE IS
A NEGATIVE DROP

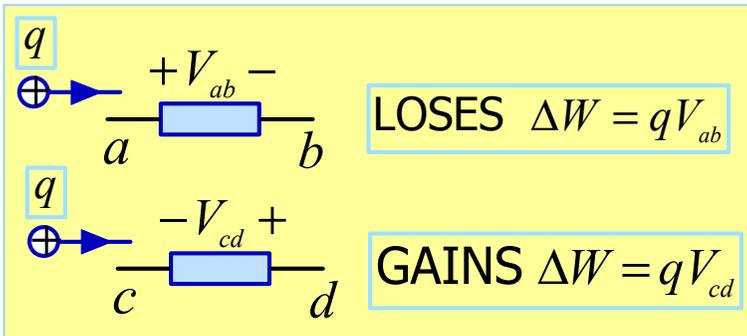

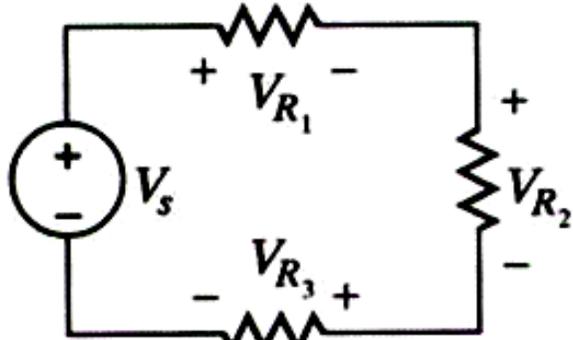
D2.4 Write the KVL equation for the following loop, traveling clockwise:



$$-V_S + V_{R_1} + V_{R_2} + V_{R_3} = 0$$


PROBLEM SOLVING TIP: KVL IS USEFUL TO DETERMINE A VOLTAGE - FIND A LOOP INCLUDING THE UNKNOWN VOLTAGE

THE LOOP DOES NOT HAVE TO BE PHYSICAL

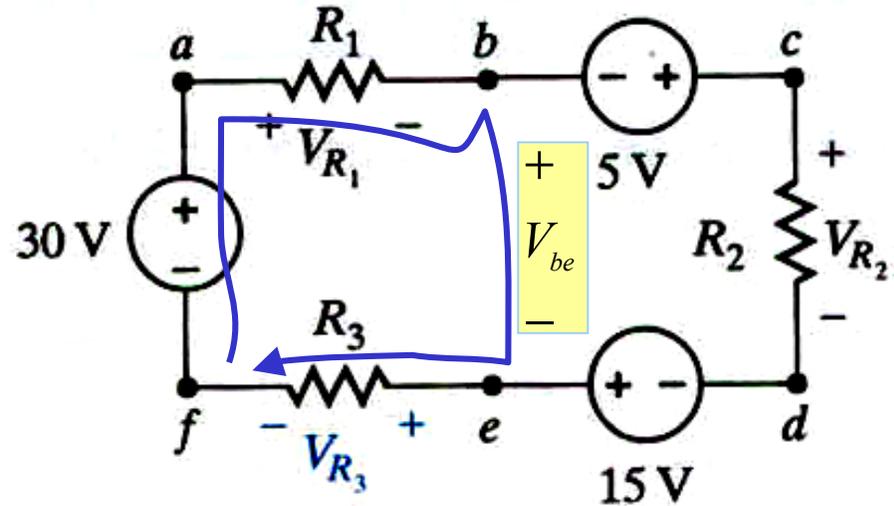

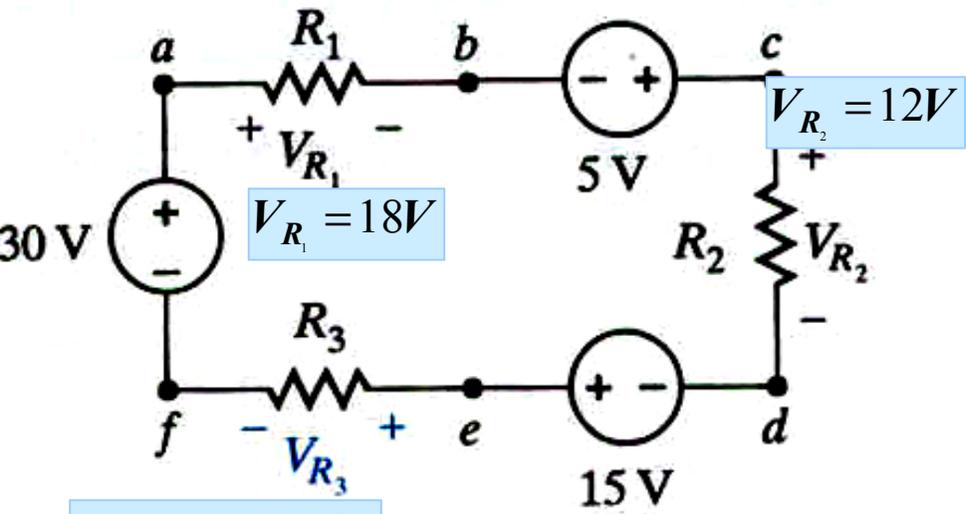EXAMPLE: V_{R_1}, V_{R_3} ARE KNOWN
DETERMINE THE VOLTAGE V_{be}

$$V_{R_1} + V_{be} + V_{R_3} - 30[V] = 0$$



LOOP *abcdefa*

$$+V_{R_1} - 5 + V_{R_2} - 15 + V_{R_3} - 30 = 0$$



BACKGROUND: WHEN DISCUSSING KCL WE SAW THAT NOT ALL POSSIBLE KCL EQUATIONS ARE INDEPENDENT. WE SHALL SEE THAT THE SAME SITUATION ARISES WHEN USING KVL

A SNEAK PREVIEW ON THE NUMBER OF LINEARLY INDEPENDENT EQUATIONS


IN THE CIRCUIT DEFINE

N NUMBER OF NODES

B NUMBER OF BRANCHES

$N - 1$ LINEARLY INDEPENDENT KCL EQUATIONS

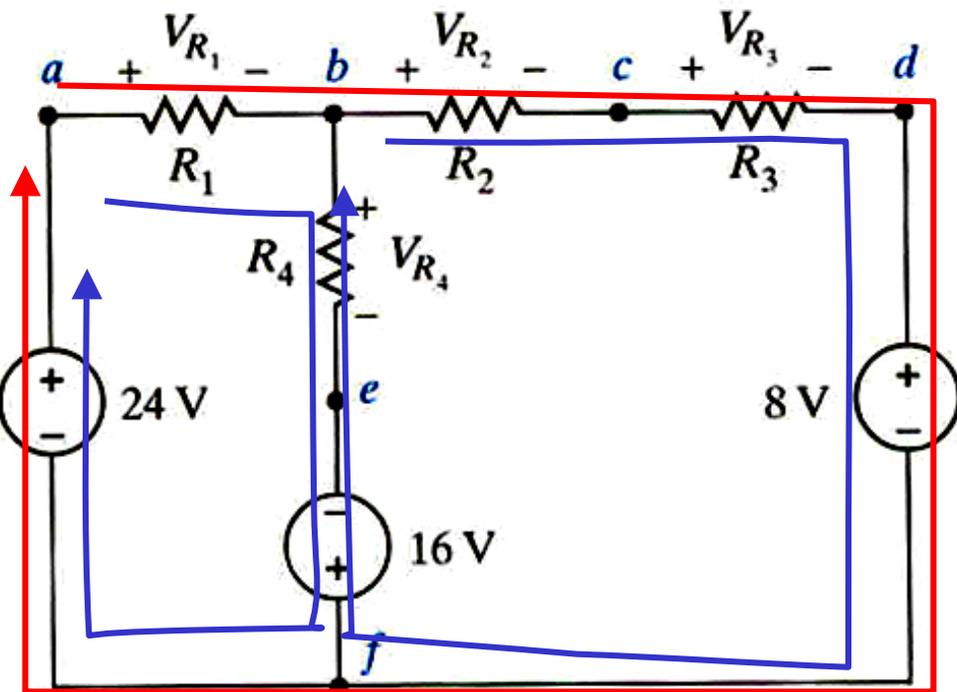$B - (N - 1)$ LINEARLY INDEPENDENT KVL EQUATIONS




EXAMPLE: FOR THE CIRCUIT SHOWN WE HAVE $N = 6$, $B = 7$. HENCE THERE ARE ONLY TWO INDEPENDENT KVL EQUATIONS

$$V_{R_1} + V_{R_4} - 16 - 24 = 0$$


$$V_{R_2} + V_{R_3} + 8 + 16 - V_{R_4} = 0$$

$$V_{R_1} + V_{R_2} + V_{R_3} + 8 - 24 = 0$$

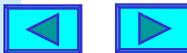THE THIRD EQUATION IS THE SUM OF THE OTHER TWO!!



FIND THE VOLTAGES V_{ae}, V_{ec}

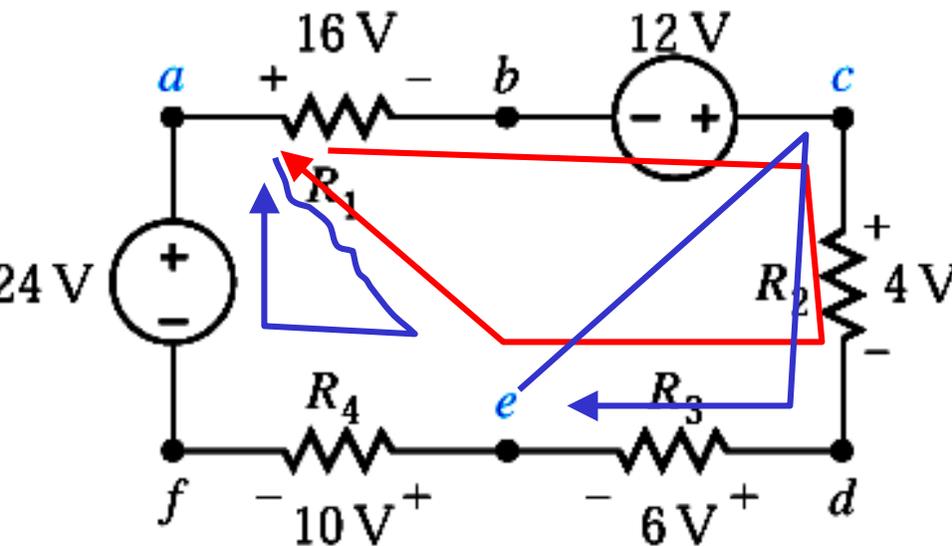


$$V_{ae} + 10 - 24 = 0$$

$$16 - 12 + 4 + 6 - V_{ae} = 0$$

GIVEN THE CHOICE USE THE SIMPLEST LOOP

$$4 + 6 + V_{ec} = 0$$


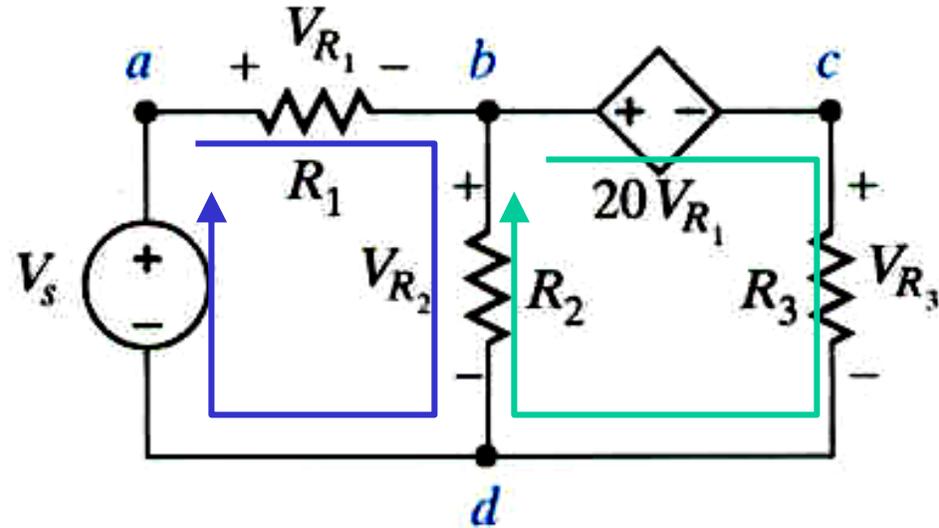
DEPENDENT SOURCES ARE HANDLED WITH THE SAME EASE




$$V_{R1} + V_{R2} - V_S = 0$$

$$20V_{R1} + V_{R3} - V_{R2} = 0$$



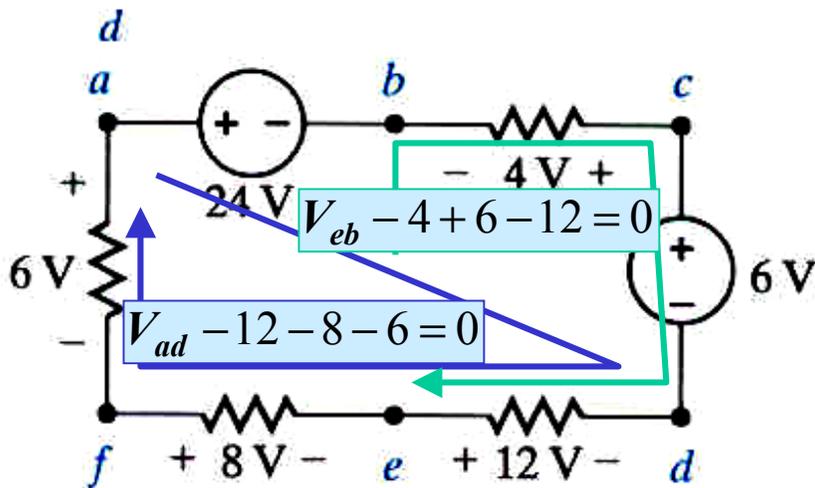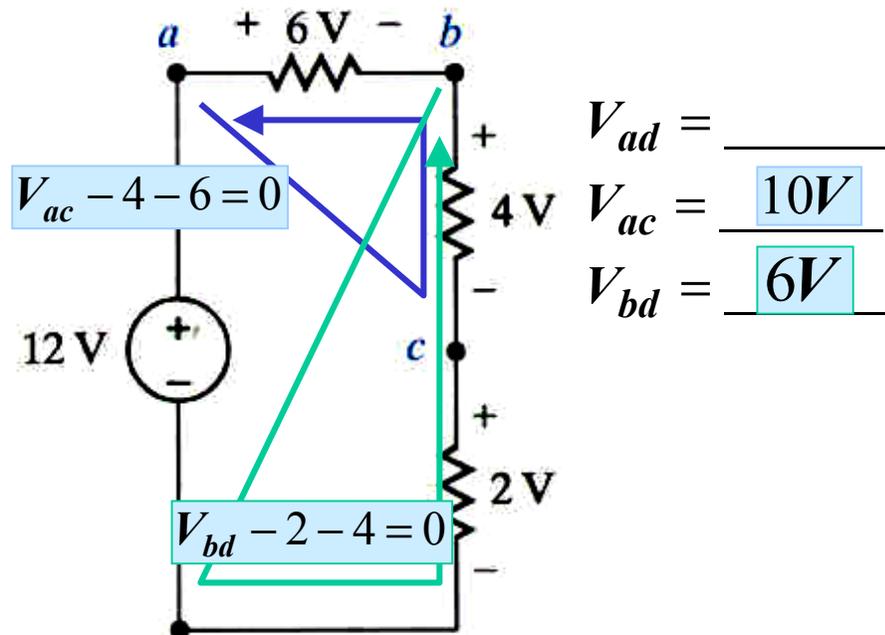

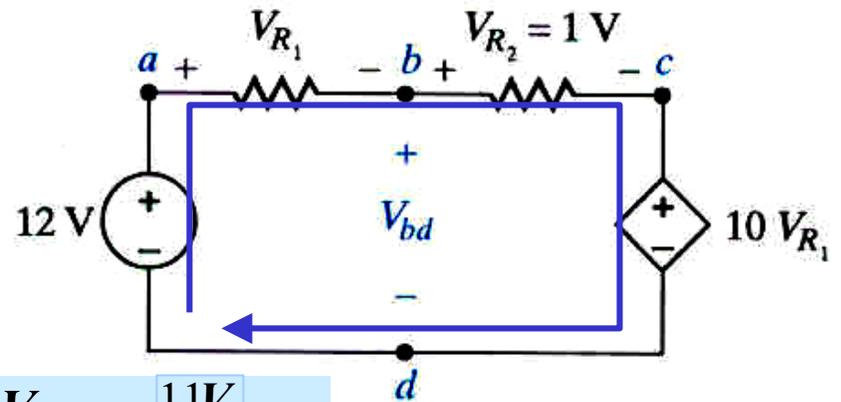$V_{ad} = \underline{\hspace{2cm}}, V_{eb} = \underline{\hspace{2cm}}$





MUST FIND V_{R_1} FIRST


$-12 + V_{R_1} + 1 + 10V_{R_1} = 0 \Rightarrow V_{R_1} = 1V$

DEPENDENT SOURCES ARE NOT REALLY DIFFICULT TO ANALYZE

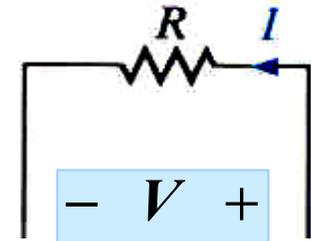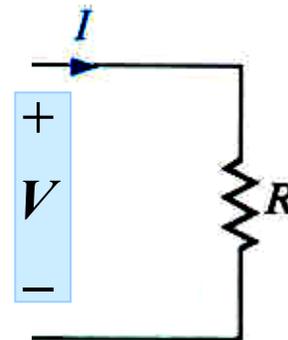REMINDER: IN A RESISTOR THE VOLTAGE AND CURRENT DIRECTIONS MUST SATISFY THE PASSIVE SIGN CONVENTION



SAMPLE PROBLEM

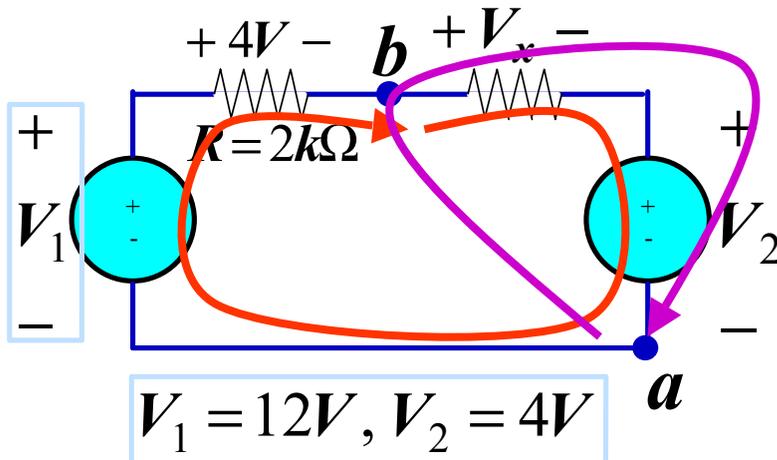

DETERMINE

$$V_x = 4V$$

$$V_{ab} = -8V$$

Power dissipated on
the 2k resistor

$$P_{2k} =$$

Remember
past topics

We need to find a closed path where only one voltage is unknown

FOR V_X

$$V_X + V_2 - V_1 + 4 = 0$$


$$V_X + 4 - 12 + 4 = 0$$

$$V_X + V_2 + V_{ab} = 0$$

$$V_{ab} = -V_X - V_2$$



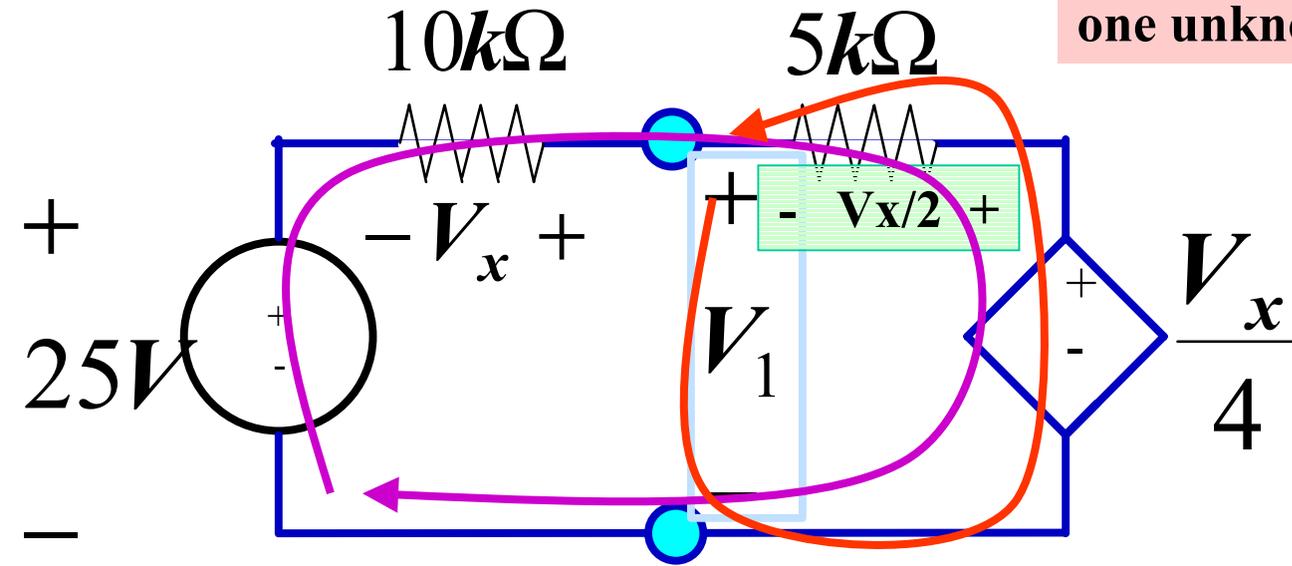There are no loops with only one unknown!!!



The current through the 5k and 10k resistors is the same. Hence the voltage drop across the 5k is one half of the drop across the 10k!!!

$$-25[V] - V_x - \frac{V_x}{2} + \frac{V_x}{4} = 0$$

$$V_x = -20[V]$$

$$V_1 - \frac{V_x}{4} + \frac{V_x}{2} = 0$$

$$V_1 = -\frac{V_x}{4} = 5[V]$$

