

LOOP ANALYSIS


The second systematic technique to determine all currents and voltages in a circuit

IT IS DUAL TO NODE ANALYSIS - IT FIRST DETERMINES ALL CURRENTS IN A CIRCUIT AND THEN IT USES OHM'S LAW TO COMPUTE NECESSARY VOLTAGES

THERE ARE SITUATION WHERE NODE ANALYSIS IS NOT AN EFFICIENT TECHNIQUE AND WHERE THE NUMBER OF EQUATIONS REQUIRED BY THIS NEW METHOD IS SIGNIFICANTLY SMALLER



Apply node analysis to this circuit

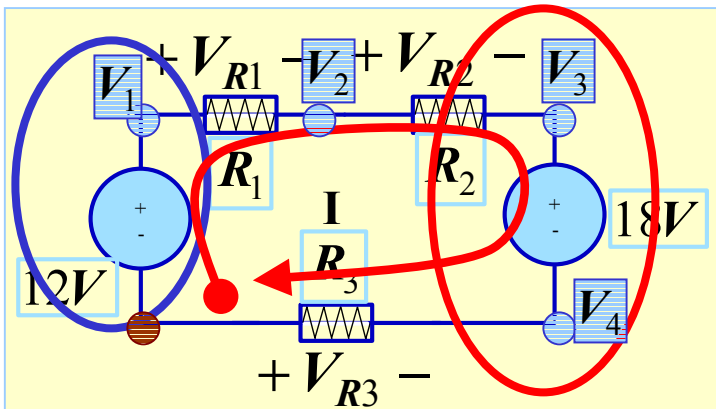

There are 4 non reference nodes

There is one supernode

There is one node connected to the reference through a voltage source

We need three equations to compute all node voltages

...BUT THERE IS ONLY ONE CURRENT FLOWING THROUGH ALL COMPONENTS AND IF THAT CURRENT IS DETERMINED ALL VOLTAGES CAN BE COMPUTED WITH OHM'S LAW

STRATEGY:

1. Apply KVL
(sum of voltage drops = 0)

$$-12[V] + V_{R1} + V_{R2} + 18[V] - V_{R3} = 0$$

Skip this equation

2. Use Ohm's Law to express voltages in terms of the "loop current."

$$-12[V] + R_1 I + R_2 I + 18[V] + R_3 I = 0$$


Write this one directly

RESULT IS ONE EQUATION IN THE LOOP CURRENT!!!

SHORTCUT



LOOPS, MESHES AND LOOP CURRENTS

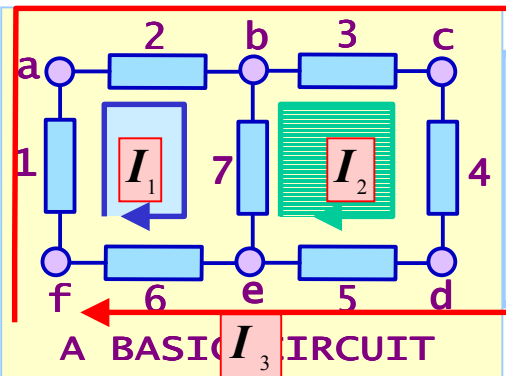

EACH COMPONENT IS CHARACTERIZED BY ITS VOLTAGE ACROSS AND ITS CURRENT THROUGH

CLAIM: IN A CIRCUIT, THE CURRENT THROUGH ANY COMPONENT CAN BE EXPRESSED IN TERMS OF THE LOOP CURRENTS

EXAMPLES

$$I_{af} = -I_1 - I_3$$

$$I_{be} = I_1 - I_2$$

$$I_{bc} = I_2 + I_3$$

THE DIRECTION OF THE LOOP CURRENTS IS SIGNIFICANT

A LOOP IS A CLOSED PATH THAT DOES NOT GO TWICE OVER ANY NODE. THIS CIRCUIT HAS THREE LOOPS

fabef

ebcde


fabcdef

A MESH IS A LOOP THAT DOES NOT ENCLOSE ANY OTHER LOOP. fabef, ebcde ARE MESHES

A LOOP CURRENT IS A (FICTICIOUS) CURRENT THAT IS ASSUMED TO FLOW AROUND A LOOP

FACT: NOT EVERY LOOP CURRENT IS REQUIRED TO COMPUTE ALL THE CURRENTS THROUGH COMPONENTS

USING TWO LOOP CURRENTS

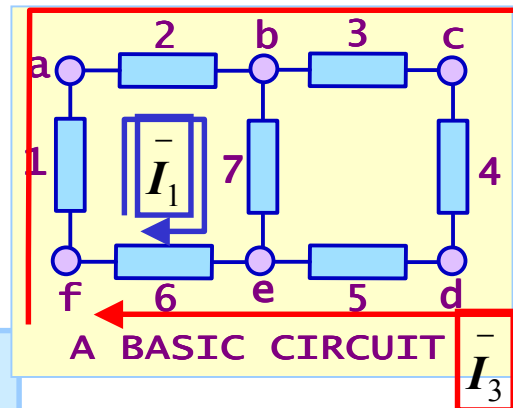

$$I_{af} = -\bar{I}_1 - \bar{I}_3$$

$$I_{be} = \bar{I}_1$$

$$I_{bc} = \bar{I}_3$$

I_1, I_2, I_3 ARE LOOP CURRENTS

A MESH CURRENT IS A LOOP CURRENT ASSOCIATED TO A MESH. I_1, I_2 ARE MESH CURRENTS

FOR EVERY CIRCUIT THERE IS A MINIMUM NUMBER OF LOOP CURRENTS THAT ARE NECESSARY TO COMPUTE EVERY CURRENT IN THE CIRCUIT. SUCH A COLLECTION IS CALLED A MINIMAL SET (OF LOOP CURRENTS).




FOR A GIVEN CIRCUIT LET
 B NUMBER OF BRANCHES
 N NUMBER OF NODES

THE MINIMUM REQUIRED NUMBER OF
 LOOP CURRENTS IS

$$L = B - (N - 1)$$

MESH CURRENTS ARE ALWAYS INDEPENDENT

AN EXAMPLE

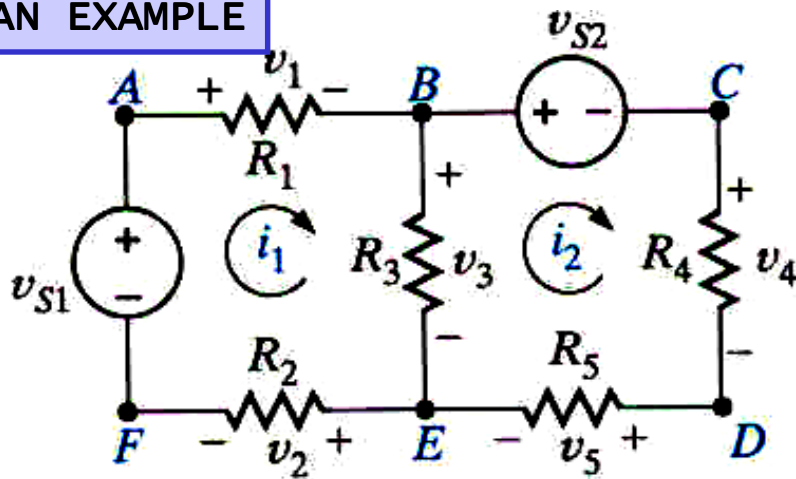

TWO LOOP CURRENTS ARE
 REQUIRED.
 THE CURRENTS SHOWN ARE
 MESH CURRENTS. HENCE
 THEY ARE INDEPENDENT AND
 FORM A MINIMAL SET

$$B = 7$$

$$N = 6$$

$$L = 7 - (6 - 1) = 2$$

DETERMINATION OF LOOP CURRENTS

KVL ON LEFT MESH

$$+v_1 + v_3 + v_2 - v_{S1} = 0$$

KVL ON RIGHT MESH

$$+v_{S2} + v_4 + v_5 - v_3 = 0$$

USING OHM'S LAW

$$v_1 = i_1 R_1, v_2 = i_1 R_2, v_3 = (i_1 - i_2) R_3$$

$$v_4 = i_2 R_4, \text{ and } v_5 = i_2 R_5$$

REPLACING AND REARRANGING

$$\begin{aligned} i_1(R_1 + R_2 + R_3) - i_2(R_3) &= v_{S1} \\ -i_1(R_3) + i_2(R_3 + R_4 + R_5) &= -v_{S2} \end{aligned}$$

IN MATRIX FORM

$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_3 \\ -R_3 & R_3 + R_4 + R_5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_{S1} \\ -v_{S2} \end{bmatrix}$$

THESE ARE LOOP EQUATIONS FOR THE
 CIRCUIT

LEARNING BY DOING: WRITE THE MESH EQUATIONS


BOOKKEEPING

BRANCHES = 8

NODES = 7

LOOP CURRENTS NEEDED = 2

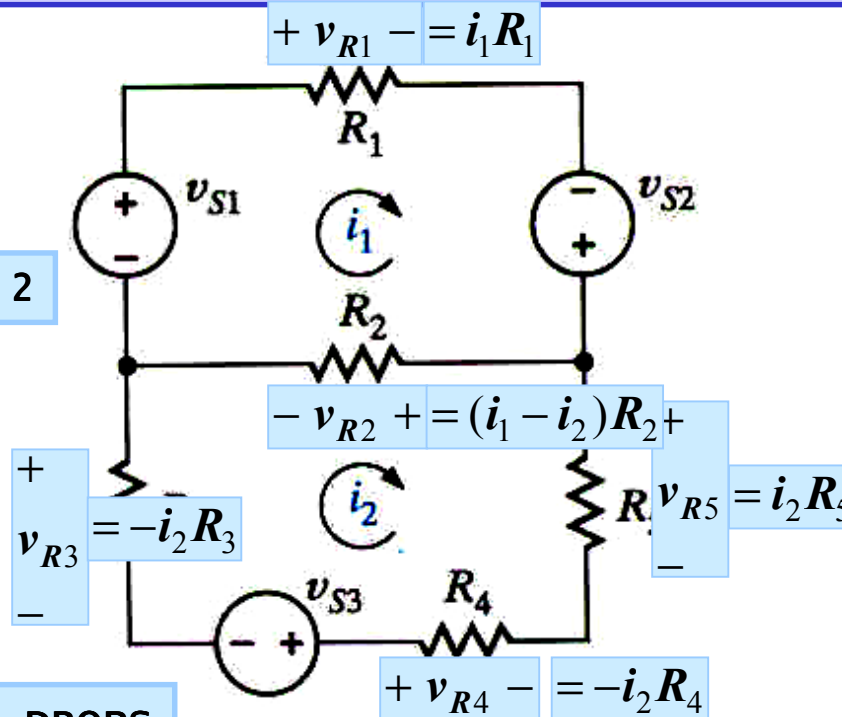AND WE ARE TOLD TO USE MESH CURRENTS! THIS DEFINES THE LOOP CURRENTS TO BE USED



IDENTIFY ALL VOLTAGE DROPS

WRITE KVL ON EACH MESH

TOP MESH: $-v_{S1} + v_{R1} - v_{S2} + v_{R2} = 0$


BOTTOM: $-v_{R2} + v_{R5} - v_{R4} + v_{S3} - v_{R3} = 0$

USE OHM'S LAW

$$-v_{S1} + i_1 R_1 - v_{S2} + (i_1 - i_2)R_2 = 0$$
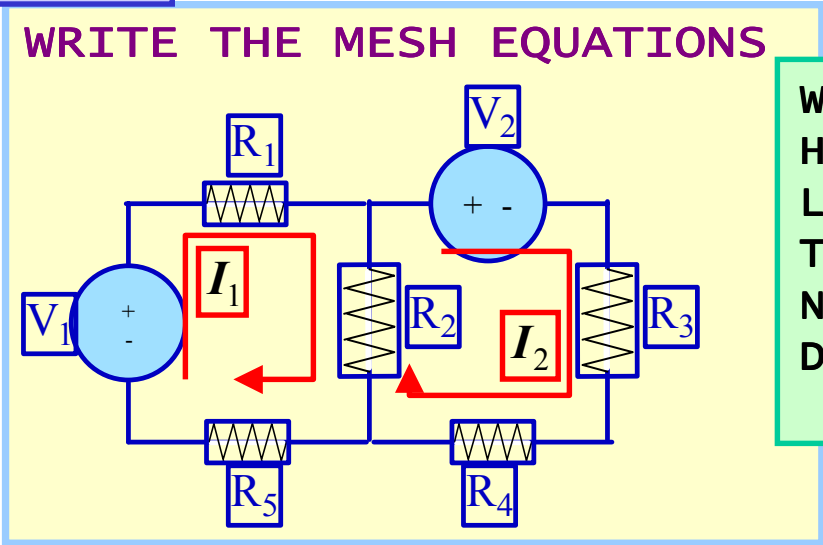
$$i_2 R_3 + (i_2 - i_1)R_2 + i_2 R_5 + i_2 R_4 + v_{S3} = 0$$





WHENEVER AN ELEMENT HAS MORE THAN ONE LOOP CURRENT FLOWING THROUGH IT WE COMPUTE NET CURRENT IN THE DIRECTION OF TRAVEL

DRAW THE MESH CURRENTS. ORIENTATION CAN BE ARBITRARY. BUT BY CONVENTION THEY ARE DEFINED CLOCKWISE


NOW WRITE KVL FOR EACH MESH AND APPLY OHM'S LAW TO EVERY RESISTOR.

AT EACH LOOP FOLLOW THE PASSIVE SIGN CONVENTION USING LOOP CURRENT REFERENCE DIRECTION


$$-V_1 + I_1 R_1 + (I_1 - I_2) R_2 + I_1 R_5 = 0$$
$$V_2 + I_2 R_3 + I_2 R_4 + (I_2 - I_1) R_2 = 0$$



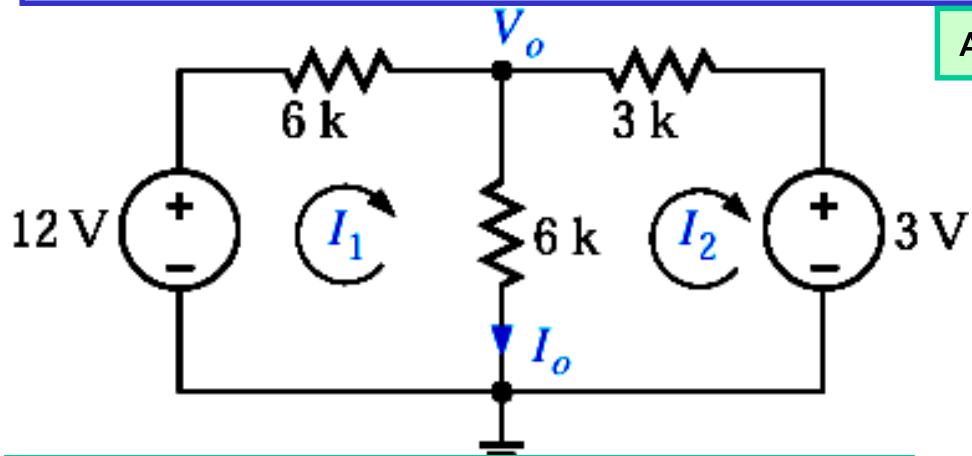LEARNING EXAMPLE: FIND I_o USING LOOP ANALYSIS II



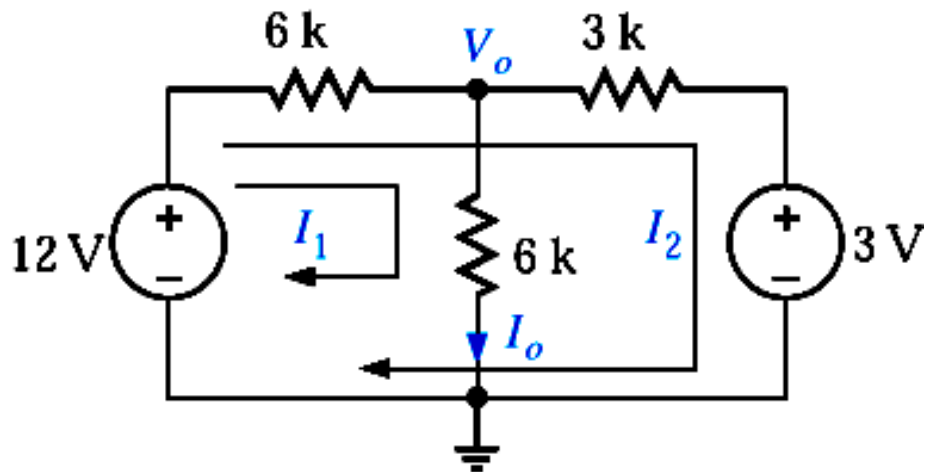AN ALTERNATIVE SELECTION OF LOOP CURRENTS



SHORTCUT: POLARITIES ARE NOT NEEDED. APPLY OHM'S LAW TO EACH ELEMENT AS KVL IS BEING WRITTEN

KVL @ I_1 $-12 + 6kI_1 + 6k(I_1 - I_2) = 0$

KVL @ I_2 $6k(I_2 - I_1) + 3kI_2 + 3 = 0$

REARRANGE $12kI_1 - 6kI_2 = 12$
 $-6kI_1 + 9kI_2 = -3$ * /2 and add

$12kI_2 = 6 \Rightarrow I_2 = 0.5mA$

$12kI_1 = 12 + 6kI_2 \Rightarrow I_1 = \frac{5}{4}mA$

EXPRESS VARIABLE OF INTEREST AS FUNCTION OF LOOP CURRENTS $I_o = I_1 - I_2$

KVL @ I_1 $-12 + 6k(I_1 + I_2) + 6kI_1 = 0$

KVL @ I_2 $-12 + 6k(I_1 + I_2) + 3kI_2 + 3 = 0$

NOW $I_o = I_1$

THIS SELECTION IS MORE EFFICIENT


REARRANGE $12kI_1 + 6kI_2 = 12$ * /3
 $6kI_1 + 9kI_2 = 9$ * /2 and subtract

$24kI_1 = 18 \Rightarrow I_1 = \frac{3}{4}mA$



IF THE CIRCUIT CONTAINS ONLY INDEPENDENT SOURCE THE MESH EQUATIONS CAN BE WRITTEN "BY INSPECTION"

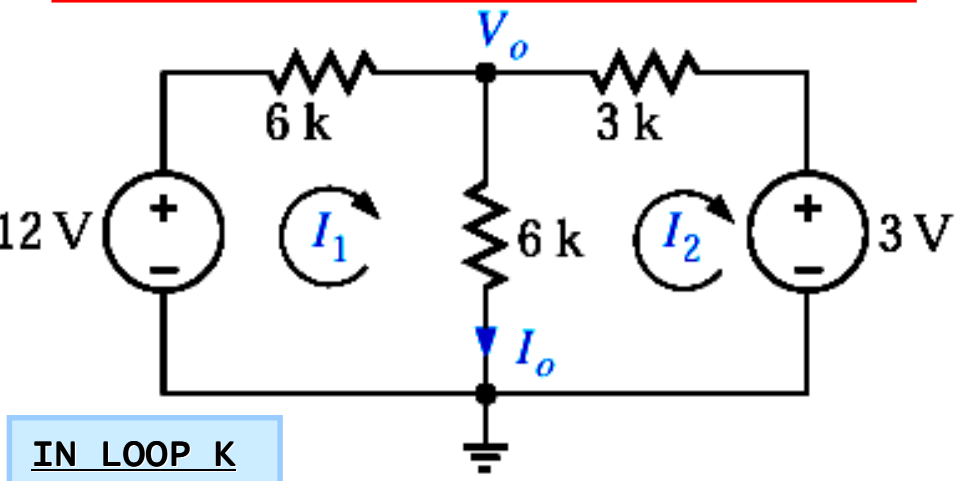MUST HAVE ALL MESH CURRENTS WITH THE SAME ORIENTATION



IN LOOP K


THE COEFFICIENT OF I_k IS THE SUM OF RESISTANCES AROUND THE LOOP.

THE RIGHT HAND SIDE IS THE ALGEBRAIC SUM OF VOLTAGE SOURCES AROUND THE LOOP (VOLTAGE RISES - VOLTAGE DROPS)

THE COEFFICIENT OF I_j IS THE SUM OF RESISTANCES COMMON TO BOTH k AND j AND WITH A NEGATIVE SIGN.

LOOP 1 $12kI_1 - 6kI_2 = 12$

LOOP 2 $-6kI_1 + 9kI_2 = -3$

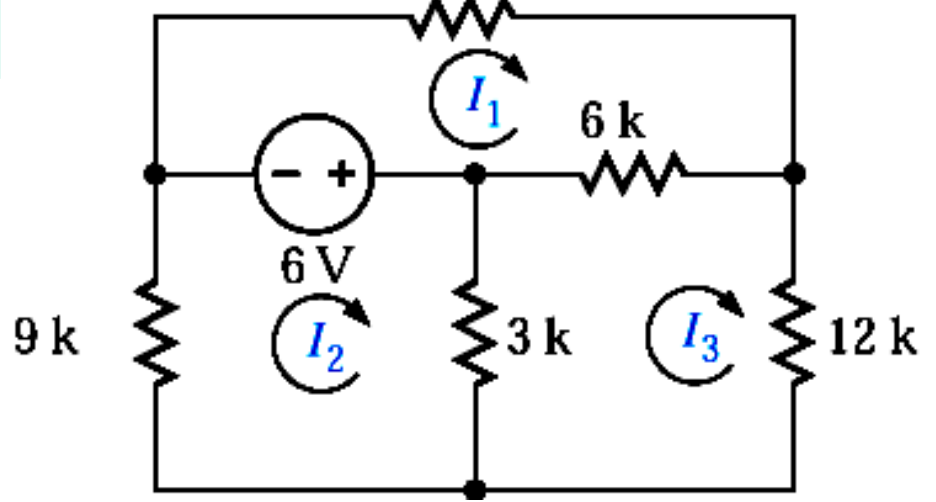

LOOP 1 coefficient of $I_1 = 4k + 6k$
 coefficient of $I_2 = 0$
 coefficient of $I_3 = -6k$ RHS = $-6[V]$

$$(4k + 6k)I_1 - (0)I_2 - (6k)I_3 = -6$$

LOOP 2 coefficient of $I_1 = 0$
 coefficient of $I_2 = 9k + 3k$
 coefficient of $I_3 = -3k$ RHS = $6[V]$


$$-(0)I_1 + (9k + 3k)I_2 - (3k)I_3 = 6$$

Loop 3 $-(6k)I_1 - (3k)I_2 + (3k + 6k + 12k)I_3 = 0$



Use mesh equations to find V_o

LEARNING EXTENSION

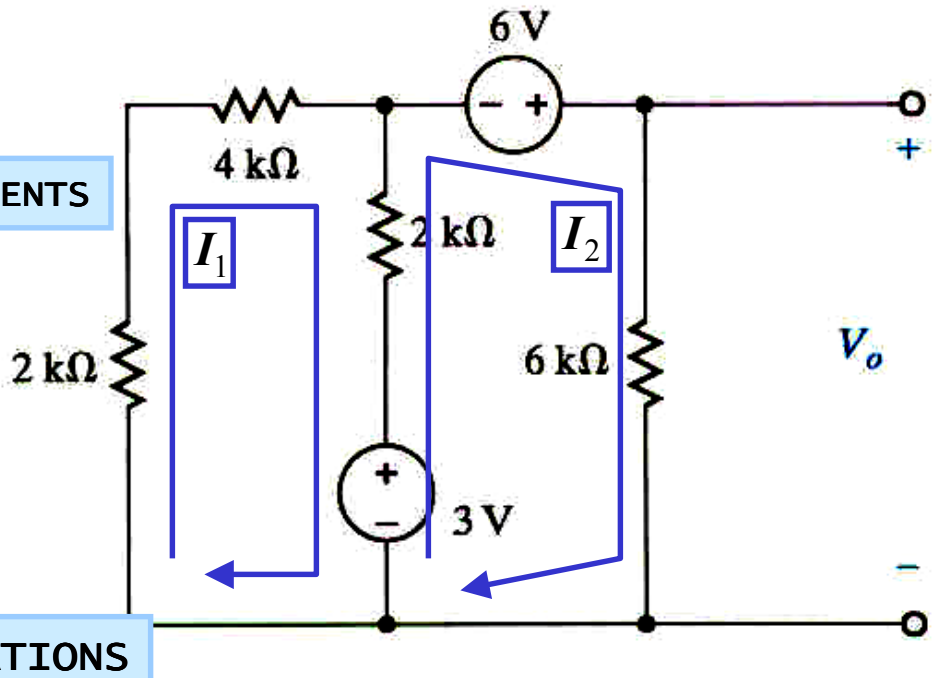

1. DRAW THE MESH CURRENTS

2. WRITE MESH EQUATIONS

$$\text{MESH 1 } (2k + 4k + 2k)I_1 - 2kI_2 = -3[V]$$

$$\text{MESH 2 } -2kI_1 + (2k + 6k)I_2 = (6V + 3V)$$

DIVIDE BY 1k. GET NUMBERS FOR COEFFICIENTS ON THE LEFT AND mA ON THE RHS

3. SOLVE EQUATIONS

$$8I_1 - 2I_2 = -3[mA]$$


$$-2I_1 + 8I_2 = 9[mA] \text{ */4 and add}$$

$$30I_2 = 33[mA]$$

$$V_o = 6kI_2 = \frac{33}{5}[V]$$



WRITE THE MESH EQUATIONS

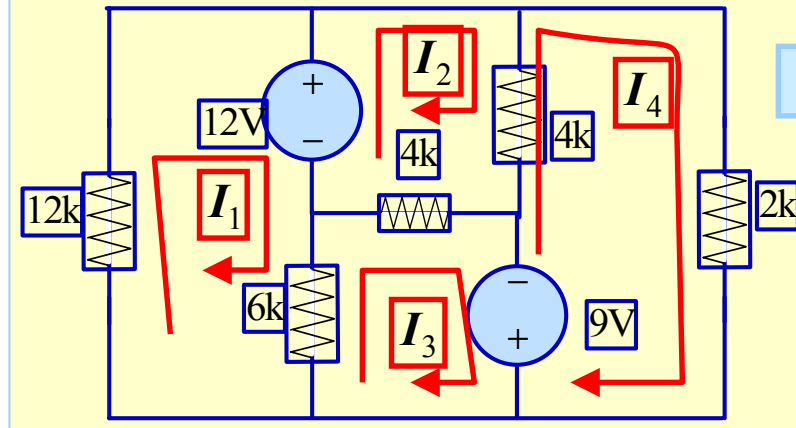

1. DRAW MESH CURRENTS

BOOKKEEPING: $B = 7$, $N = 4$

2. WRITE MESH EQUATIONS. USE KVL

$$\text{MESH 1: } 12kI_1 + 12V + 6k(I_1 - I_3) = 0$$

$$\text{MESH 2: } -12V + 4k(I_2 - I_4) + 4k(I_2 - I_3) = 0$$

$$\text{MESH 3: } -9V + 6k(I_3 - I_1) + 4k(I_3 - I_2) = 0$$

$$\text{MESH 4: } 9V + 4k(I_4 - I_2) + 2kI_4 = 0$$

EQUATIONS BY INSPECTION

$$18kI_1 - 6kI_3 = -12V$$

$$8kI_2 - 4kI_3 - 4kI_4 = 12V$$

$$-6kI_1 - 4kI_2 + 10kI_3 = 9V$$


$$-4kI_2 + 6kI_4 = -9V$$

CHOOSE YOUR FAVORITE TECHNIQUE
TO SOLVE THE SYSTEM OF EQUATIONS



CIRCUITS WITH INDEPENDENT CURRENT SOURCES

find both V_o and V_1 in the circuit

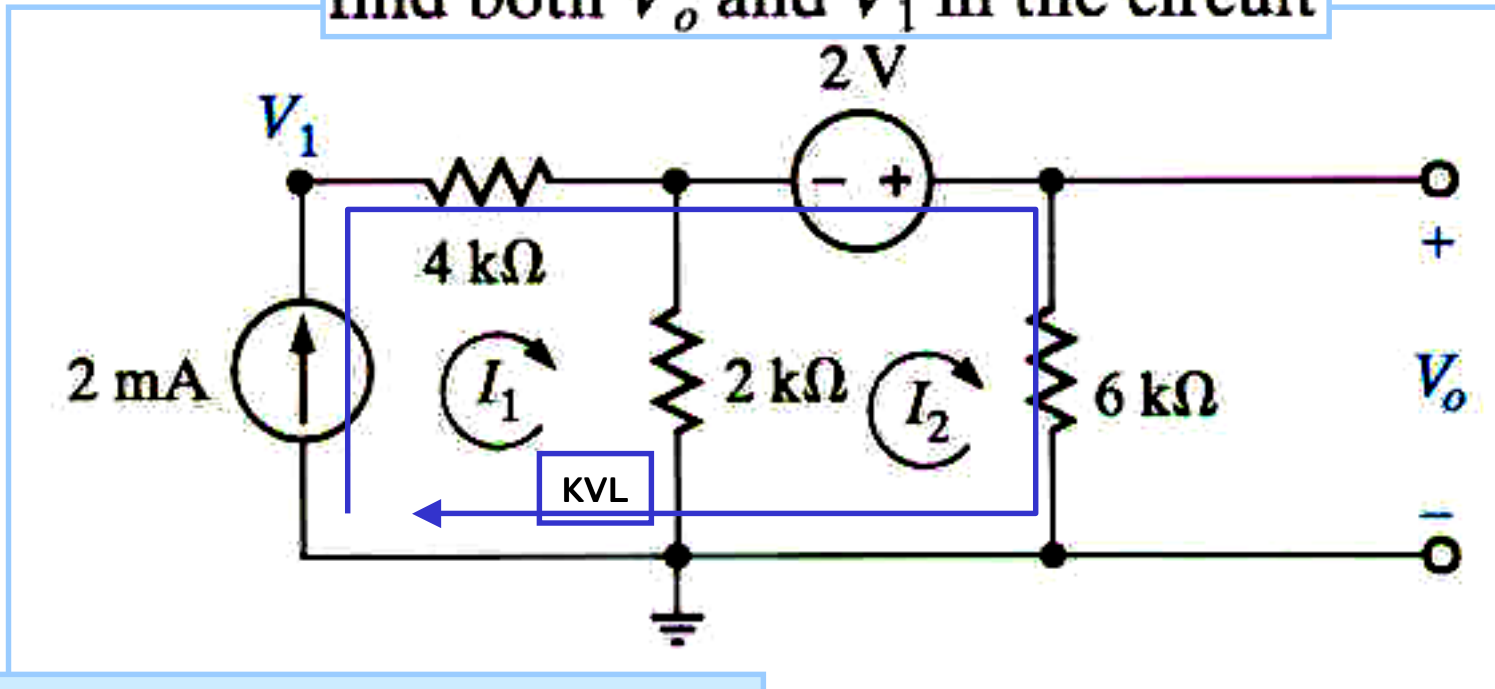

THERE IS NO RELATIONSHIP BETWEEN V_1 AND THE SOURCE CURRENT! HOWEVER ...

MESH 1 CURRENT IS CONSTRAINED

MESH 1 EQUATION $I_1 = 2mA$

MESH 2 $2k(I_2 - I_1) - 2 + 6kI_2 = 0$

"BY INSPECTION" $-2kI_1 + 8kI_2 = 2V$

$$I_2 = \frac{2k \times (2mA) + 2V}{8k} = \frac{3}{4} mA \Rightarrow V_o = 6kI_2 = \frac{9}{2} [V]$$

CURRENT SOURCES THAT ARE NOT SHARED BY OTHER MESHES (OR LOOPS) SERVE TO DEFINE A MESH (LOOP) CURRENT AND REDUCE THE NUMBER OF REQUIRED EQUATIONS


TO OBTAIN V_1 APPLY KVL TO ANY CLOSED PATH THAT INCLUDES V_1

$$-V_1 + 4kI_1 - 2 + 6kI_2 = 0$$



LEARNING EXAMPLE

COMPUTE V_o USING MESH ANALYSIS

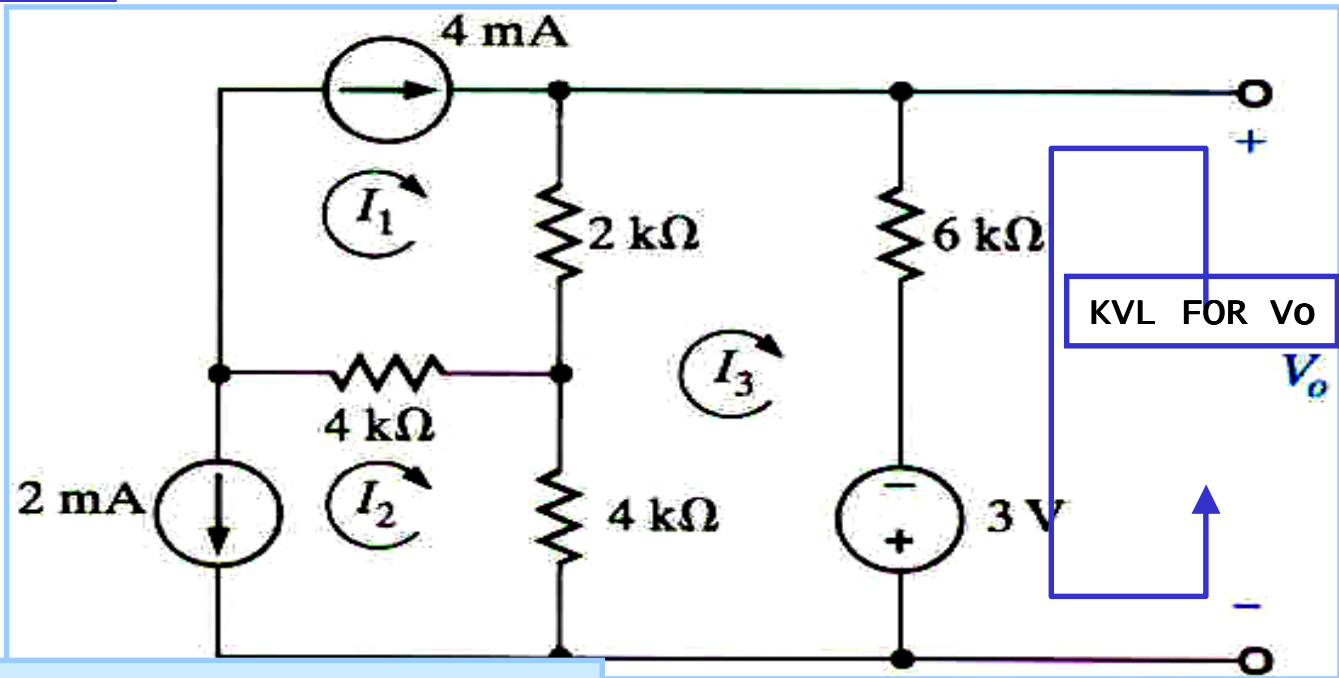

TWO MESH CURRENTS ARE DEFINED BY CURRENT SOURCES

$$I_1 = 4mA \quad I_2 = -2mA$$

MESH 3

$$4k(I_3 - I_2) + 2k(I_3 - I_1) + 6kI_3 - 3 = 0$$

“BY INSPECTION” $-2kI_1 - 4kI_2 + 12kI_3 = 3V$

$$I_3 = \frac{3V + 2k(4mA) + 4k(-2mA)}{12k} = \frac{1}{4}mA$$


USE KVL TO COMPUTE V_o

$$V_o = 6kI_3 - 3 = \frac{-3}{2}V$$



LEARNING EXTENSIONS

Find V_o

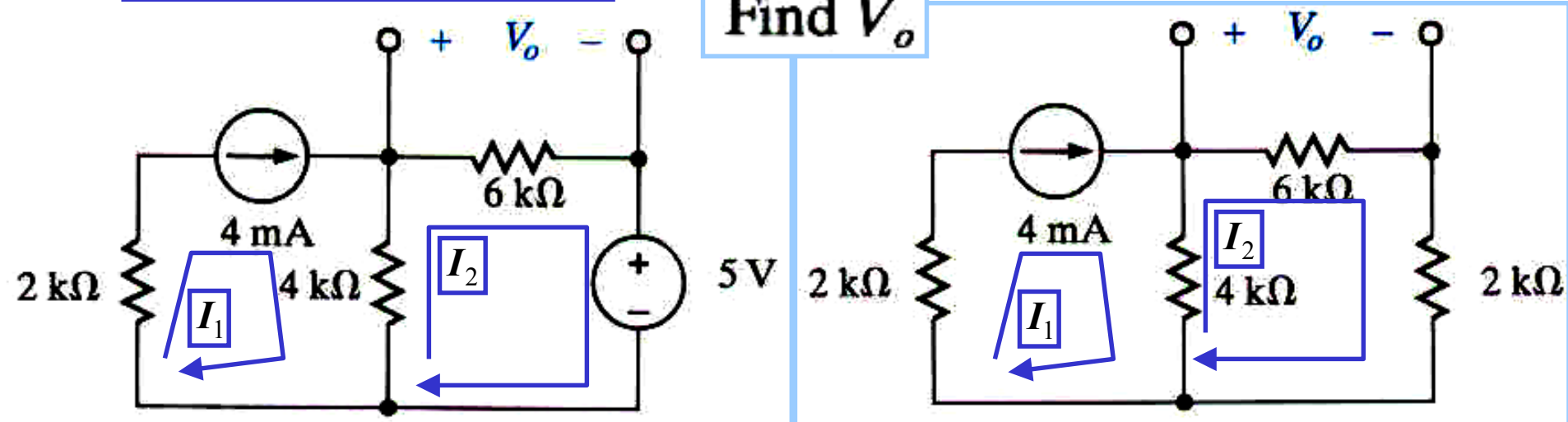

WE ACTUALLY NEED THE CURRENT ON THE RIGHT MESH. HENCE, USE MESH ANALYSIS

MESH 1: $I_1 = 4mA$

MESH 2: $5[V] + 4k(I_2 - I_1) + 6kI_2 = 0$

$$10I_2 = -5mA + 4 \times 4mA = 11mA$$

$$V_o = 6kI_2 = \frac{33}{5}[V]$$

MESH 1: $I_1 = 4mA$

MESH 2: $-4kI_1 + 12kI_2 = 0$


$$I_2 = \frac{16}{12} = \frac{4}{3}mA$$

$$V_o = 6kI_2 = 8[V]$$



Problem 3.46 (6th Ed)

Determine V_O

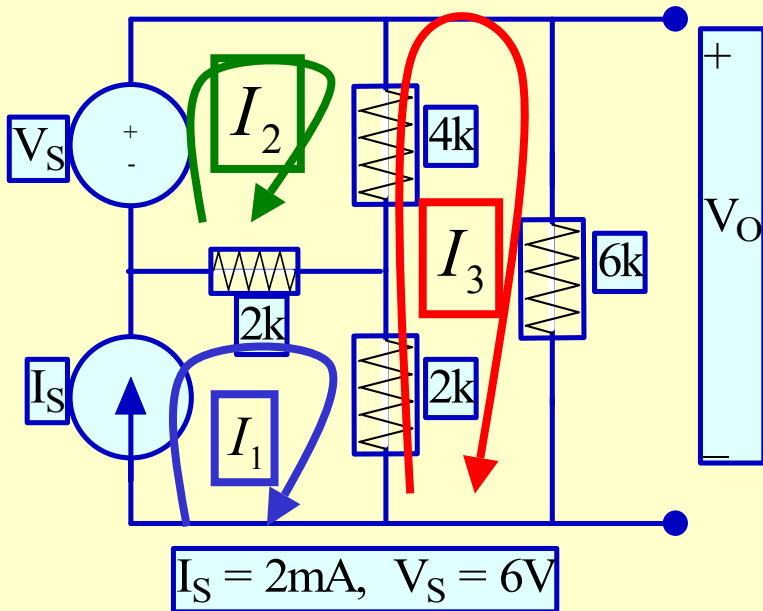

2. write loop equations.

Loop 1 $I_1 = I_S$

Loop 2 $-V_S + 4k(I_2 - I_3) + 2k(I_2 - I_1) = 0$

Loop 3 $4k(I_3 - I_2) + 6kI_3 + 2k(I_3 - I_1) = 0$

Since we need to compute V_O it is efficient to solve for I_3 only.

HINT: Divide the loop equations by 1k. Coefficients become numbers and voltage source becomes mA.

We use the fact that $I_1 = I_S$

Loop 2 $6I_2 - 4I_3 = \frac{V_S}{1k} + 2I_1 = (6 + 4)[mA] \quad */2$

Loop 3 $-4I_2 + 12I_3 = 2I_S = 4mA \quad */3$ and add eq

$$28I_3 = 10 \times 2 + 4 \times 3 \Rightarrow I_3 = \frac{32}{28} mA$$

$$V_O = 6kI_3 = \frac{48}{7} V$$

SELECTING THE SOLUTION METHOD

3 non-reference nodes. 3 meshes

One current source, one super node


BOTH APPROACHES SEEM COMPARABLE. CHOOSE LOOP ANALYSIS

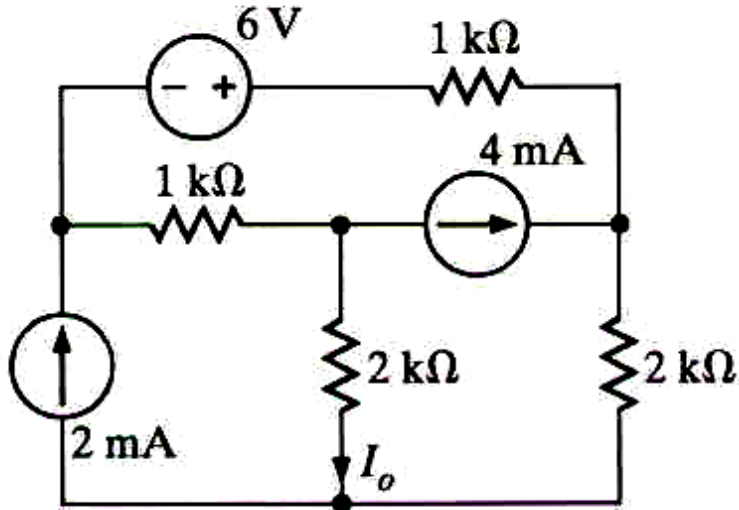1. select loop currents.


In this case we use meshes. We note that the current source could define one mesh.



CURRENT SOURCES SHARED BY LOOPS - THE SUPERMESH APPROACH



1. SELECT MESH CURRENTS

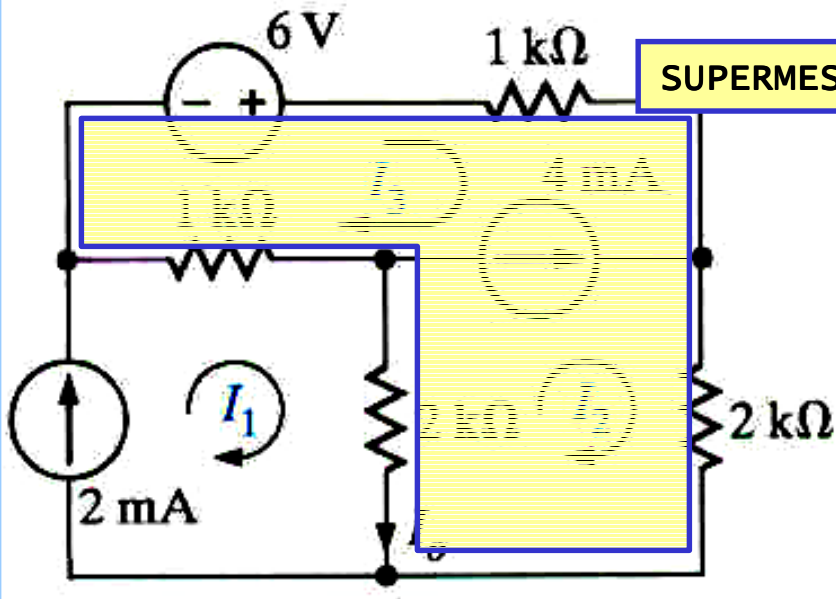

2. WRITE CONSTRAINT EQUATION DUE TO MESH CURRENTS SHARING CURRENT SOURCES

$$I_2 - I_3 = 4mA$$

3. WRITE EQUATIONS FOR THE OTHER MESHES

$$I_1 = 2mA$$

4. DEFINE A SUPERMESH BY (MENTALLY) REMOVING THE SHARED CURRENT SOURCE



5. WRITE KVL FOR THE SUPERMESH

$$-6 + 1kI_3 + 2kI_2 + 2k(I_2 - I_1) + 1k(I_3 - I_1) = 0$$

NOW WE HAVE THREE EQUATIONS IN THREE UNKNOWN. THE MODEL IS COMPLETE



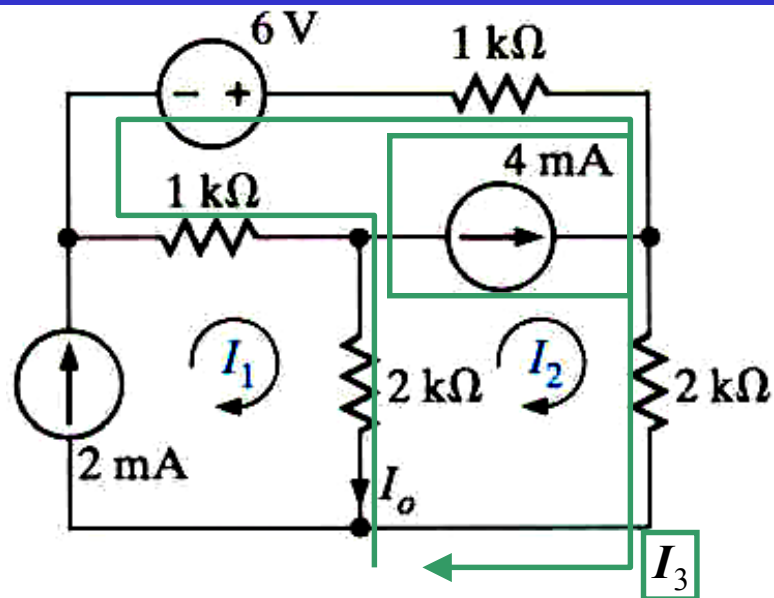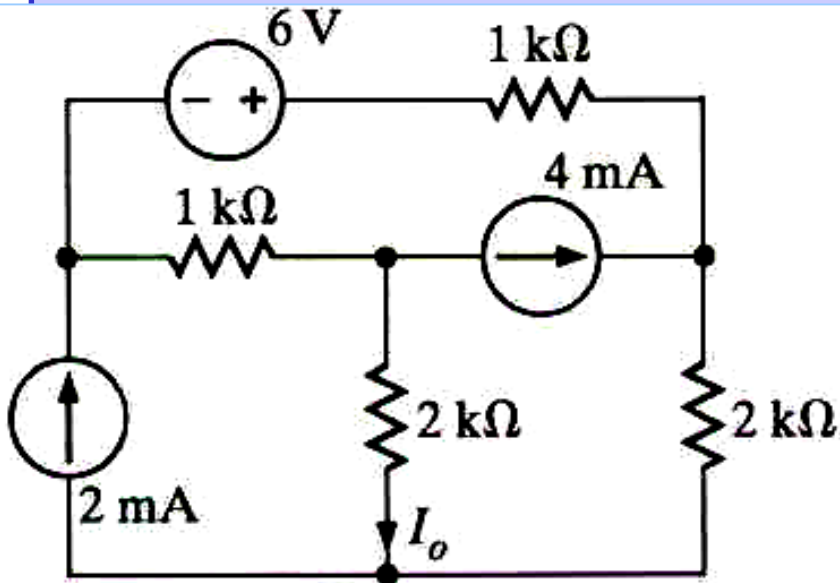CURRENT SOURCES SHARED BY MESHES - THE GENERAL LOOP APPROACH



THE STRATEGY IS TO DEFINE LOOP CURRENTS THAT DO NOT SHARE CURRENT SOURCES -

EVEN IF IT MEANS ABANDONING MESHES

FOR CONVENIENCE START USING MESH CURRENTS UNTIL REACHING A SHARED SOURCE. AT THAT POINT DEFINE A NEW LOOP.

IN ORDER TO GUARANTEE THAT IT GIVES AN INDEPENDENT EQUATION ONE MUST MAKE SURE THAT THE LOOP INCLUDES COMPONENTS THAT ARE NOT PART OF PREVIOUSLY DEFINED LOOPS

A POSSIBLE STRATEGY IS TO CREATE A LOOP BY OPENING THE CURRENT SOURCE

THE LOOP EQUATIONS FOR THE LOOPS WITH CURRENT SOURCES ARE

$$I_1 = 2mA$$

$$I_2 = 4mA$$


THE LOOP EQUATION FOR THE THIRD LOOP IS

$$-6[V] + 1kI_3 + 2k(I_3 + I_2) + 2k(I_3 + I_2 - I_1) + 1k(I_3 - I_1) = 0$$

THE MESH CURRENTS OBTAINED WITH THIS METHOD ARE DIFFERENT FROM THE ONES OBTAINED WITH A SUPERMESH. EVEN FOR THOSE DEFINED USING MESHES.



FIND VOLTAGES ACROSS RESISTORS

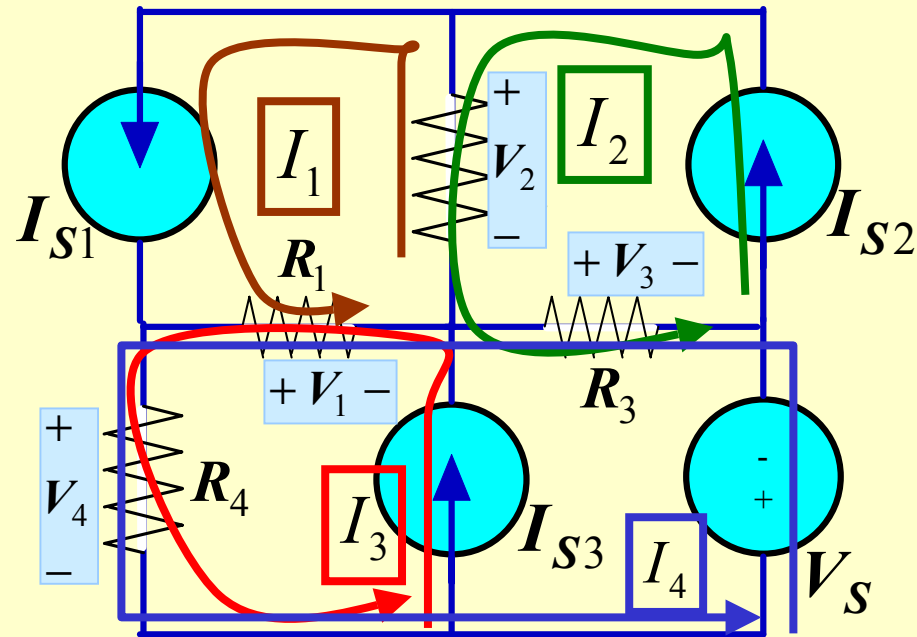

Now we need a loop current that does not go over any current source and passes through all unused components.

HINT: IF ALL CURRENT SOURCES ARE REMOVED THERE IS ONLY ONE LOOP LEFT

MESH EQUATIONS FOR LOOPS WITH CURRENT SOURCES

$$I_1 = I_{S1}$$

$$I_2 = I_{S2}$$

$$I_3 = I_{S3}$$

KVL OF REMAINING LOOP

$$V_S + R_3(I_4 - I_2) + R_1(I_4 + I_3 - I_1) + R_4(I_4 + I_3) = 0$$

For loop analysis we notice...

Three independent current sources.
Four meshes.
One current source shared by two meshes.

Careful choice of loop currents should make only one loop equation necessary. Three loop currents can be chosen using meshes and not sharing any source.

SOLVE FOR THE CURRENT I4.
USE OHM'S LAW TO COMPUTE REQUIRED VOLTAGES

$$V_1 = R_1(I_1 - I_3 - I_4)$$

$$V_2 = R_2(I_2 - I_1)$$


$$V_3 = R_3(I_2 - I_4)$$

$$V_4 = R_4(I_3 + I_4)$$



A COMMENT ON METHOD SELECTION

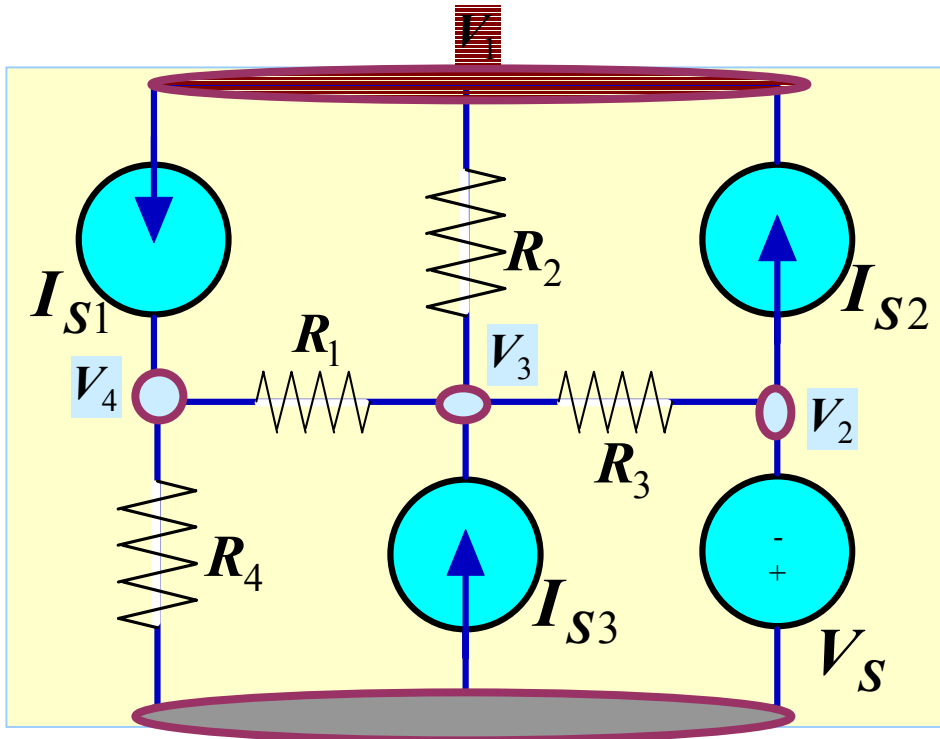The same problem can be solved by node analysis but it requires 3 equations



$$V_2 = -V_S$$


$$\frac{V_1 - V_3}{R_2} + I_{S1} - I_{S2} = 0$$

$$-I_{S3} + \frac{V_3 - V_2}{R_3} + \frac{V_3 - V_1}{R_2} + \frac{V_3 - V_4}{R_1} = 0$$

$$-I_{S1} + \frac{V_4}{R_1} + \frac{V_4 - V_1}{R_1} = 0$$

CIRCUITS WITH DEPENDENT SOURCES

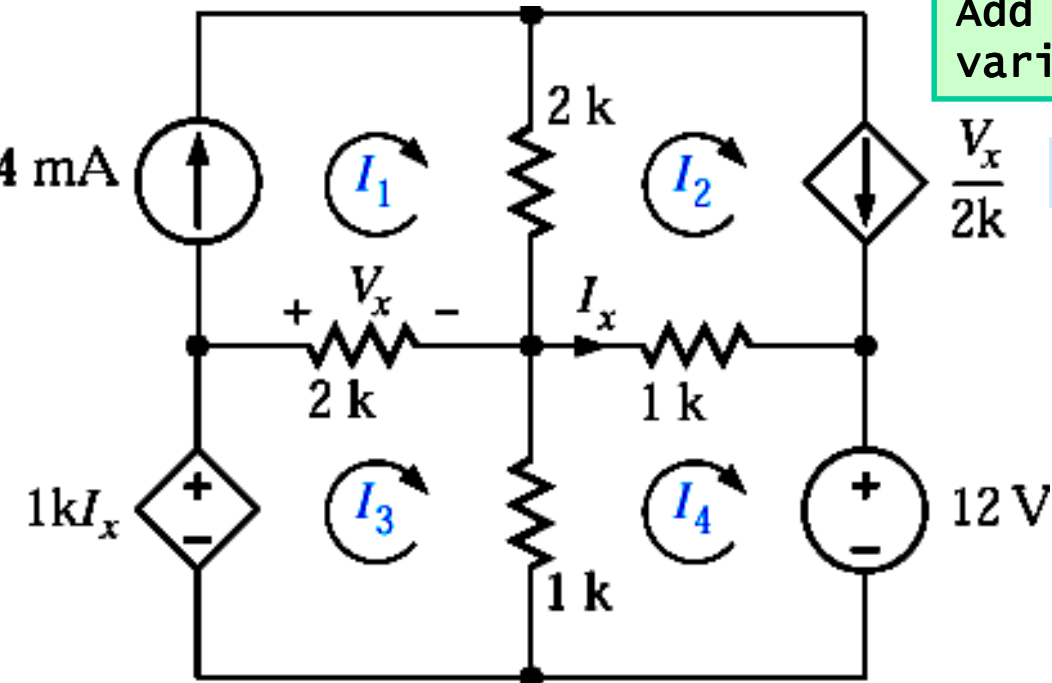Treat the dependent source as though it were independent.
Add one equation for the controlling variable



COMBINE EQUATIONS. DIVIDE BY 1k

$$\begin{aligned} I_1 &= 4 \\ I_1 + I_2 - I_3 &= 0 \\ I_2 + 3I_3 - 2I_4 &= 8 \\ -I_2 - I_3 + 2I_4 &= -12 \end{aligned}$$

MESH CURRENTS
DETERMINED BY SOURCES

$$I_1 = 4 \text{ mA}$$

$$I_2 = \frac{V_x}{2k}$$

MESH 3: $-1kI_x + 2k(I_3 - I_1) + 1k(I_3 - I_4) = 0$

MESH 4: $1k(I_4 - I_3) + 1k(I_4 - I_2) + 12V = 0$

CONTROLLING VARIABLES

$$I_x = I_4 - I_2 \quad V_x = 2k(I_3 - I_1)$$



SOLVE USING MATLAB

$$I_1 = 4$$

$$I_1 + I_2 - I_3 = 0$$

$$I_2 + 3I_3 - 2I_4 = 8$$

$$-I_2 - I_3 + 2I_4 = -12$$

Since we divided by 1k the RHS is mA and all the coefficients are numbers

PUT IN MATRIX FORM

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 1 & 1 & -1 & 0 \\ 0 & 1 & 3 & -2 \\ 0 & -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \\ 8 \\ -12 \end{bmatrix}$$

>> is the MATLAB prompt. What follows is the command entered

DEFINE THE MATRIX

```
» R=[1,0,0,0; %FIRST ROW  
1,1,-1,0; %SECOND ROW  
0,1,3,-2; %THIRD ROW  
0,-1,-1,2] %FOURTH ROW
```

```
R =  
1 0 0 0  
1 1 -1 0  
0 1 3 -2  
0 -1 -1 2
```

DEFINE THE RIGHT HAND SIDE VECTOR

```
» V=[4;0;8;12]
```

```
V =  
  
4  
0  
8  
-12
```

SOLVE AND GET THE ANSWER

The answers are in mA



```
» I=R\V
```

```
I =  
  
4  
-6  
-2  
-10
```



LEARNING EXTENSION: Dependent Sources

Find V_o

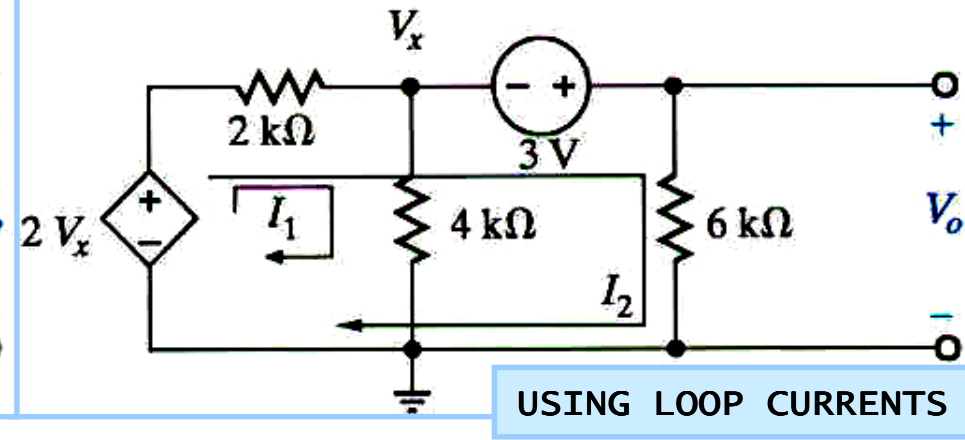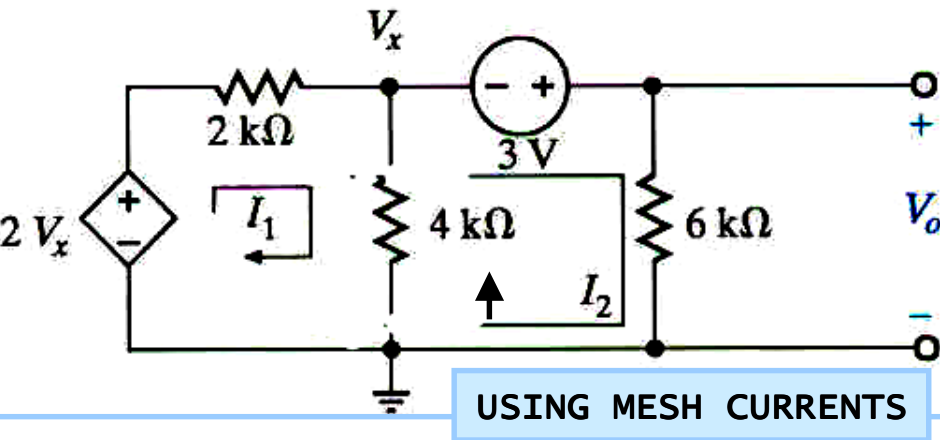

We treat the dependent source as one more voltage source

MESH 1 $-2V_x + 2kI_1 + 4k(I_1 - I_2) = 0$

LOOP 1 $-2V_x + 2k(I_1 + I_2) + 4kI_1 = 0$

MESH 2 $-3 + 6kI_2 + 4k(I_2 - I_1) = 0$

LOOP 2 $-2V_x + 2k(I_1 + I_2) - 3 + 6kI_2 = 0$

NOW WE EXPRESS THE CONTROLLING VARIABLE IN TERMS OF THE LOOP CURRENTS

$V_x = 4k(I_1 - I_2)$

and solve...

$V_x = 4kI_1$

$-2kI_1 + 4kI_2 = 0$

REPLACE AND REARRANGE

$-6kI_1 + 6kI_2 = 0$

$-4kI_1 + 10kI_2 = 3$

$-6kI_1 + 8kI_2 = 3$

$I_1 = 3mA, I_2 = 1.5mA$

SOLUTIONS


$I_1 = 1.5mA, I_2 = 1.5mA$

$V_o = 6kI_2 = 9[V]$

NOTICE THE DIFFERENCE BETWEEN MESH CURRENT I1 AND LOOP CURRENT I1 EVEN THOUGH THEY ARE ASSOCIATED TO THE SAME PATH

The selection of loop currents simplifies expression for V_x and computation of V_o .

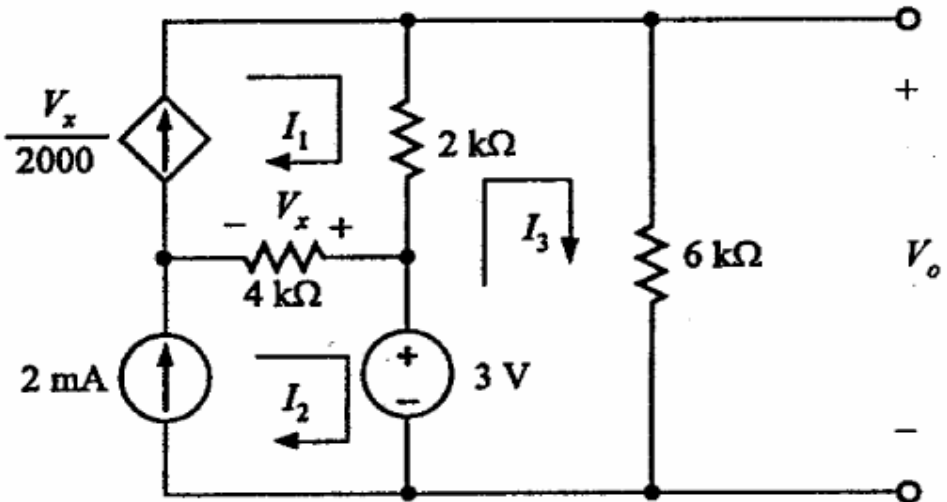DEPENDENT CURRENT SOURCE. CURRENT SOURCES NOT SHARED BY MESHES



WE ARE ASKED FOR V_o . WE ONLY NEED TO SOLVE FOR I_3

REPLACE AND REARRANGE

$$\left. \begin{aligned} V_x &= 2kI_1 \\ V_x &= 4k(I_1 - I_2) \end{aligned} \right\} \Rightarrow I_1 = 2I_2 = 4mA$$

$$8kI_3 = 3 + 2kI_2 \Rightarrow I_3 = \frac{11}{8}mA$$

$$V_o = 6kI_3 = \frac{33}{4}[V]$$

We treat the dependent source as a conventional source

Equations for meshes with current sources

$$I_1 = \frac{V_x}{2000}$$

$$I_2 = 2 \times 10^{-3}$$

Then KVL on the remaining loop(s)


$$-3 + 2k(I_3 - I_1) + 6kI_3 = 0$$

And express the controlling variable, V_x , in terms of loop currents

$$V_x = 4k(I_1 - I_2)$$



Use mesh analysis to find V_o

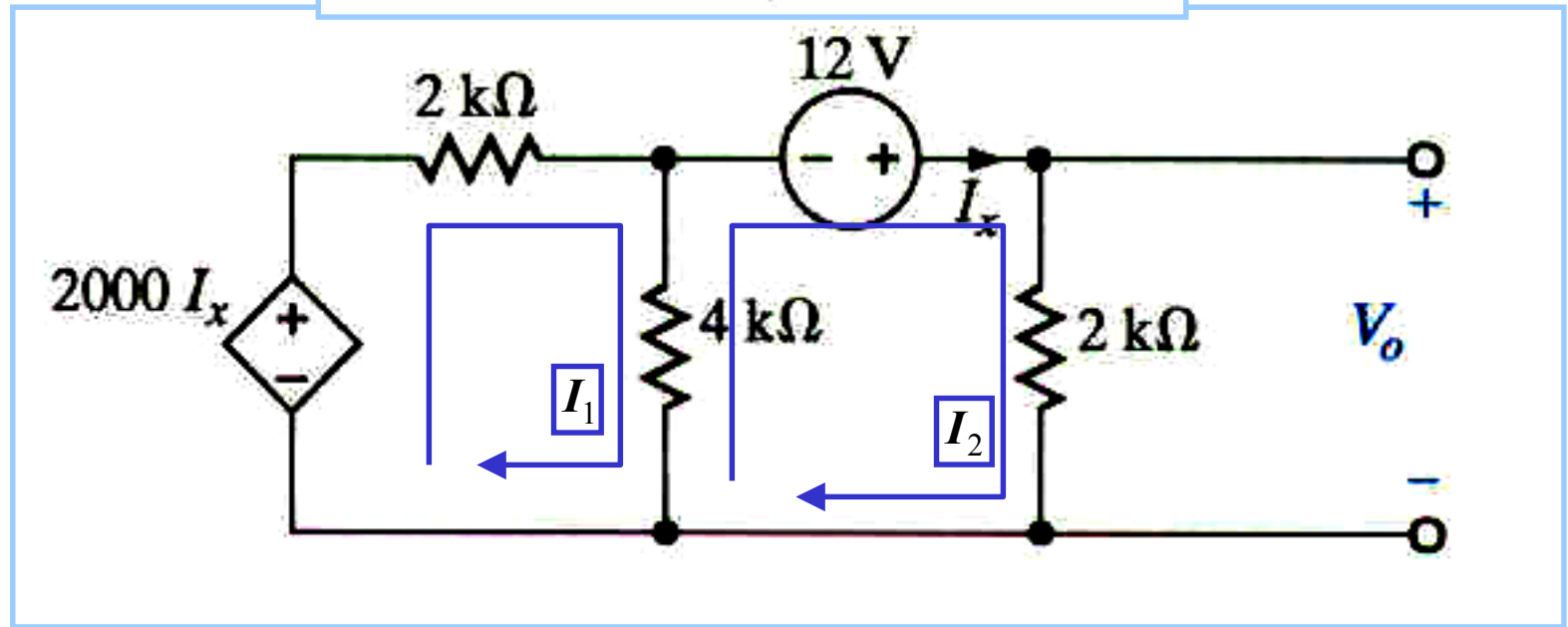

DRAW MESH CURRENTS

WRITE MESH EQUATIONS.

$$\text{MESH 1: } -2kI_x + 2kI_1 + 4k(I_1 - I_2) = 0$$

$$\text{MESH 2: } -12 + 2kI_2 + 4k(I_2 - I_1) = 0$$

CONTROLLING VARIABLE IN TERMS OF LOOP CURRENTS

$$I_x = I_2$$

REPLACE AND REARRANGE

$$6kI_1 - 6kI_2 = 0$$

$$-4kI_1 + 6kI_2 = 12$$

SOLVE FOR I2

$$2kI_2 = 12 \Rightarrow I_2 = 6mA$$

$$V_o = 2kI_2 = 12[V]$$

