

FIRST AND SECOND-ORDER TRANSIENT CIRCUITS

IN CIRCUITS WITH INDUCTORS AND CAPACITORS VOLTAGES AND CURRENTS CANNOT CHANGE INSTANTANEOUSLY.
EVEN THE APPLICATION, OR REMOVAL, OF CONSTANT SOURCES CREATES A TRANSIENT BEHAVIOR

LEARNING GOALS

FIRST ORDER CIRCUITS

Circuits that contain a single energy storing elements.
Either a capacitor or an inductor

SECOND ORDER CIRCUITS

Circuits with two energy storing elements in any combination




ANALYSIS OF LINEAR CIRCUITS WITH INDUCTORS AND/OR CAPACITORS

THE CONVENTIONAL ANALYSIS USING MATHEMATICAL MODELS REQUIRES THE DETERMINATION OF (A SET OF) EQUATIONS THAT REPRESENT THE CIRCUIT.

ONCE THE MODEL IS OBTAINED ANALYSIS REQUIRES THE SOLUTION OF THE EQUATIONS FOR THE CASES REQUIRED.

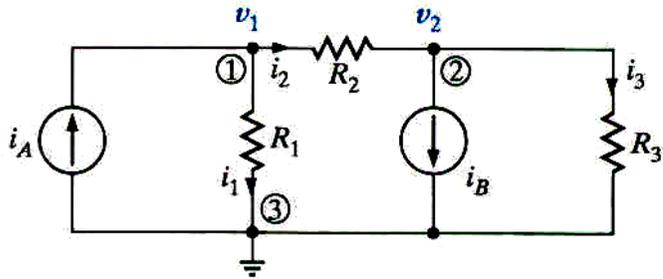FOR EXAMPLE IN NODE OR LOOP ANALYSIS OF RESISTIVE CIRCUITS ONE REPRESENTS THE CIRCUIT BY A SET OF ALGEBRAIC EQUATIONS



THE MODEL

$$\begin{aligned}(G_1 + G_2)v_1 - G_2v_2 &= i_A \\ -G_2v_1 + (G_2 + G_3)v_2 &= -i_B\end{aligned}$$

WHEN THERE ARE INDUCTORS OR CAPACITORS THE MODELS BECOME LINEAR ORDINARY DIFFERENTIAL EQUATIONS (ODEs). HENCE, IN GENERAL, ONE NEEDS ALL THOSE TOOLS IN ORDER TO BE ABLE TO ANALYZE CIRCUITS WITH ENERGY STORING ELEMENTS.

A METHOD BASED ON THEVENIN WILL BE DEVELOPED TO DERIVE MATHEMATICAL MODELS FOR ANY ARBITRARY LINEAR CIRCUIT WITH ONE ENERGY STORING ELEMENT.

THE GENERAL APPROACH CAN BE SIMPLIFIED IN SOME SPECIAL CASES WHEN THE FORM OF THE SOLUTION CAN BE KNOWN BEFOREHAND.

THE ANALYSIS IN THESE CASES BECOMES A SIMPLE MATTER OF DETERMINING SOME PARAMETERS.


TWO SUCH CASES WILL BE DISCUSSED IN DETAIL FOR THE CASE OF CONSTANT SOURCES. ONE THAT ASSUMES THE AVAILABILITY OF THE DIFFERENTIAL EQUATION AND A SECOND THAT IS ENTIRELY BASED ON ELEMENTARY CIRCUIT ANALYSIS... BUT IT IS NORMALLY LONGER

WE WILL ALSO DISCUSS THE PERFORMANCE OF LINEAR CIRCUITS TO OTHER SIMPLE INPUTS




AN INTRODUCTION

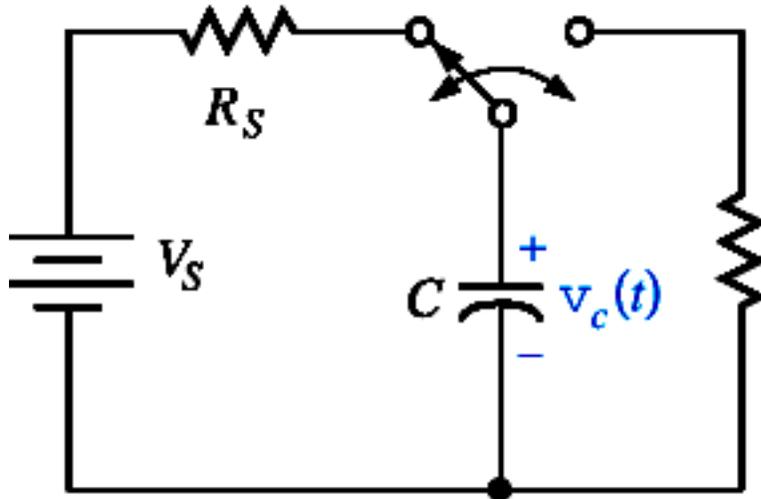INDUCTORS AND CAPACITORS CAN STORE ENERGY. UNDER SUITABLE CONDITIONS THIS ENERGY CAN BE RELEASED. THE RATE AT WHICH IT IS RELEASED WILL DEPEND ON THE PARAMETERS OF THE CIRCUIT CONNECTED TO THE TERMINALS OF THE ENERGY STORING ELEMENT




With the switch on the left the capacitor receives charge from the battery.

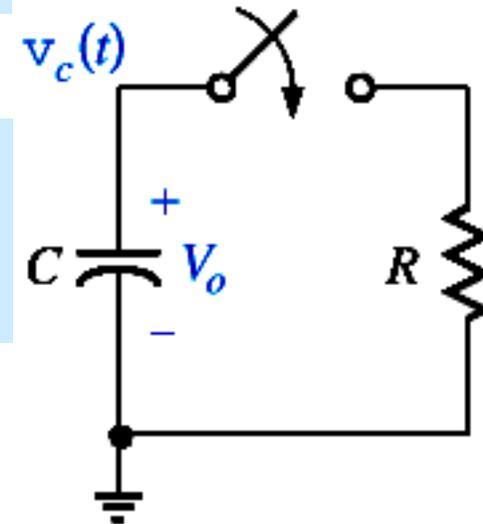Switch to the right and the capacitor discharges through the lamp



((R) Xenon lamp)

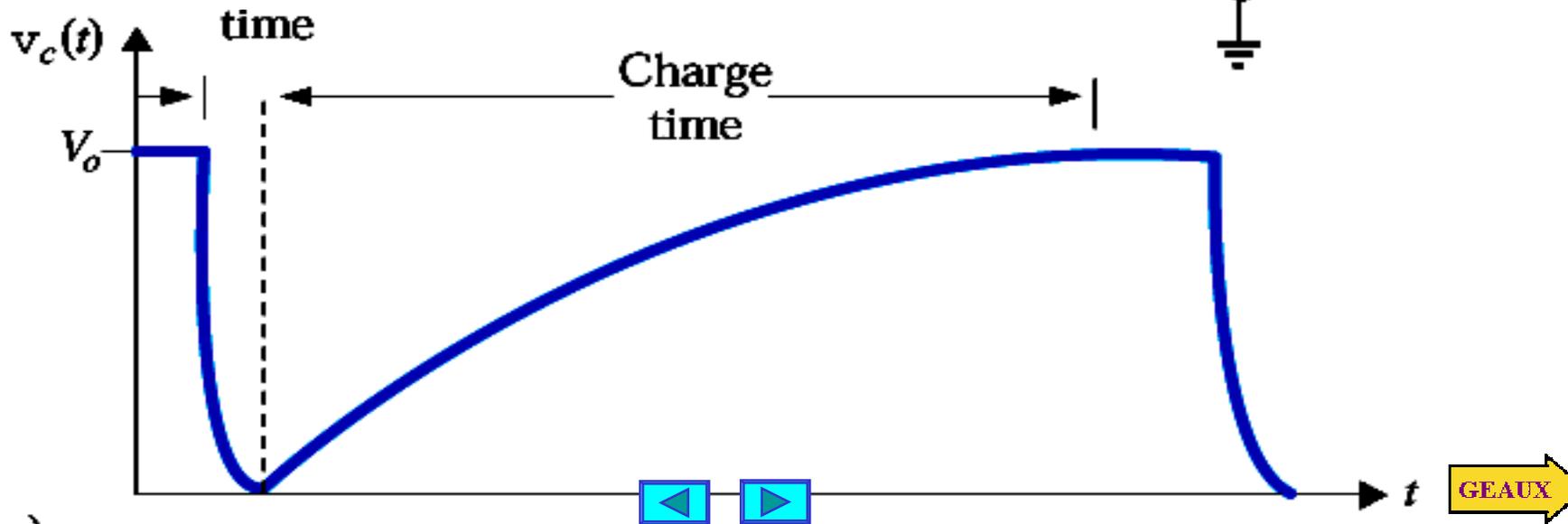

GENERAL RESPONSE: FIRST ORDER CIRCUITS

Including the initial conditions the model for the capacitor voltage or the inductor current will be shown to be of the form

$$e^{\frac{t}{\tau}} x(t) - e^{\frac{t_0}{\tau}} x(t_0) = \int_{t_0}^t \frac{1}{\tau} e^{\frac{x}{\tau}} f_{TH}(x) dx \quad * / e^{-\frac{t}{\tau}}$$

$$\frac{dx}{dt}(t) + ax(t) = f(t); \quad x(0+) = x_0$$

$$x(t) = e^{-\frac{t-t_0}{\tau}} x(t_0) + \frac{1}{\tau} \int_{t_0}^t e^{-\frac{t-x}{\tau}} f_{TH}(x) dx$$

$$\tau \frac{dx}{dt} + x = f_{TH}; \quad x(0+) = x_0$$

THIS EXPRESSION ALLOWS THE COMPUTATION OF THE RESPONSE FOR ANY FORCING FUNCTION. WE WILL CONCENTRATE IN THE SPECIAL CASE WHEN THE RIGHT HAND SIDE IS CONSTANT

Solving the differential equation using integrating factors, one tries to convert the LHS into an exact derivative

$$\tau \frac{dx}{dt} + x = f_{TH} \quad /* \frac{1}{\tau} e^{\frac{t}{\tau}}$$

τ is called the "time constant." it will be shown to provide significant information on the reaction speed of the circuit

$$e^{\frac{t}{\tau}} \frac{dx}{dt} + \frac{1}{\tau} e^{\frac{t}{\tau}} x = \frac{1}{\tau} e^{\frac{t}{\tau}} f_{TH}$$

The initial time, t_0 , is arbitrary. The general expression can be used to study sequential switchings.

$$\int_{t_0}^t \frac{d}{dt} \left(e^{\frac{t}{\tau}} x \right) = \frac{1}{\tau} e^{\frac{t}{\tau}} f_{TH}$$



FIRST ORDER CIRCUITS WITH CONSTANT SOURCES

$$\tau \frac{dx}{dt} + x = f_{TH}; \quad x(0+) = x_0$$

$$x(t) = e^{-\frac{t-t_0}{\tau}} x(t_0) + \frac{1}{\tau} \int_{t_0}^t e^{-\frac{t-x}{\tau}} f_{TH}(x) dx$$

If the RHS is constant

$$x(t) = e^{-\frac{t-t_0}{\tau}} x(t_0) + \frac{f_{TH}}{\tau} \int_{t_0}^t e^{-\frac{t-x}{\tau}} dx$$

$$e^{-\frac{t-x}{\tau}} = e^{-\frac{t}{\tau}} e^{\frac{x}{\tau}} \Rightarrow$$

$$x(t) = e^{-\frac{t-t_0}{\tau}} x(t_0) + \frac{f_{TH}}{\tau} e^{-\frac{t}{\tau}} \int_{t_0}^t e^{\frac{x}{\tau}} dx$$

$$x(t) = e^{-\frac{t-t_0}{\tau}} x(t_0) + \frac{f_{TH}}{\tau} e^{-\frac{t}{\tau}} \left(\tau e^{\frac{x}{\tau}} \right)_{t_0}^t$$

$$x(t) = e^{-\frac{t-t_0}{\tau}} x(t_0) + f_{TH} e^{-\frac{t}{\tau}} \left(e^{\frac{t}{\tau}} - e^{\frac{t_0}{\tau}} \right)$$

$$x(t) = f_{TH} + (x(t_0) - f_{TH}) e^{-\frac{t-t_0}{\tau}}$$

$$t \geq t_0$$

The form of the solution is

$$x(t) = K_1 + K_2 e^{-\frac{t-t_0}{\tau}}; \quad t \geq t_0$$

TIME
CONSTANT

TRANSIENT

Any variable in the circuit is of the form


$$y(t) = K_1 + K_2 e^{-\frac{t-t_0}{\tau}}; \quad t \geq t_0$$

Only the values of the constants K_1, K_2 will change



EVOLUTION OF THE TRANSIENT AND INTERPRETATION OF THE TIME CONSTANT


$$x_c(t) = K_2 e^{-t/\tau}$$

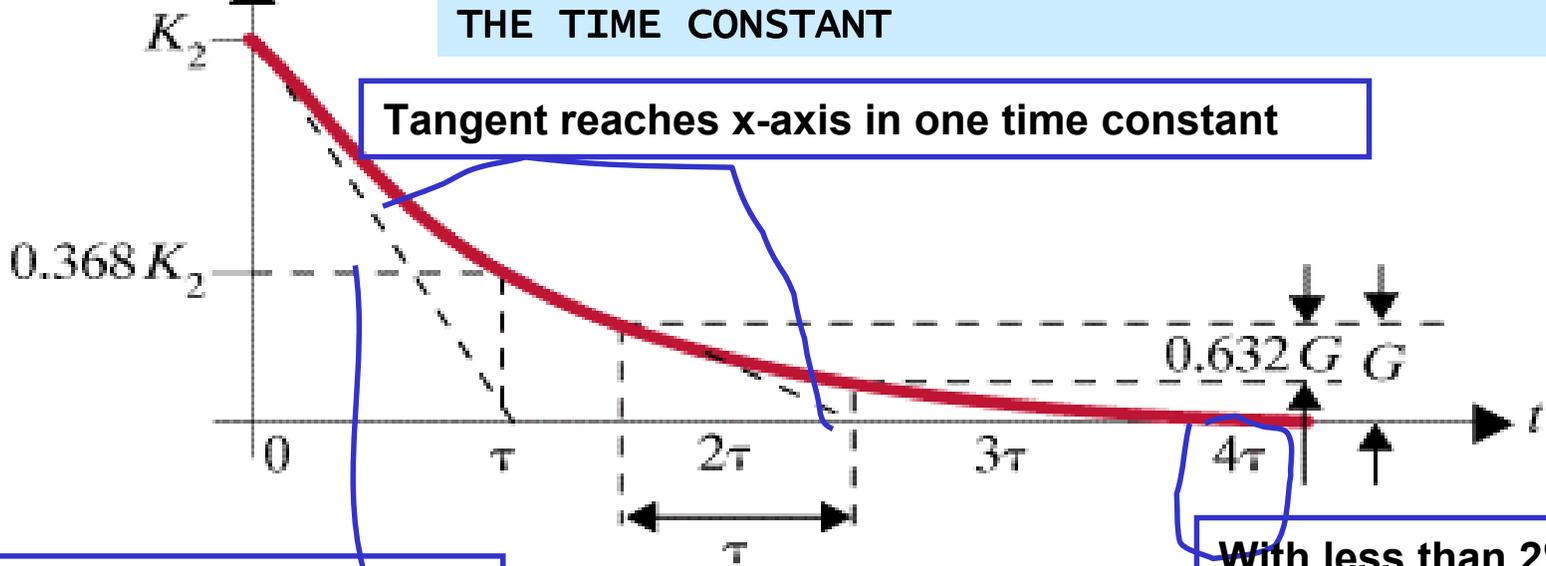

Drops 0.632 of initial value in one time constant

Tangent reaches x-axis in one time constant

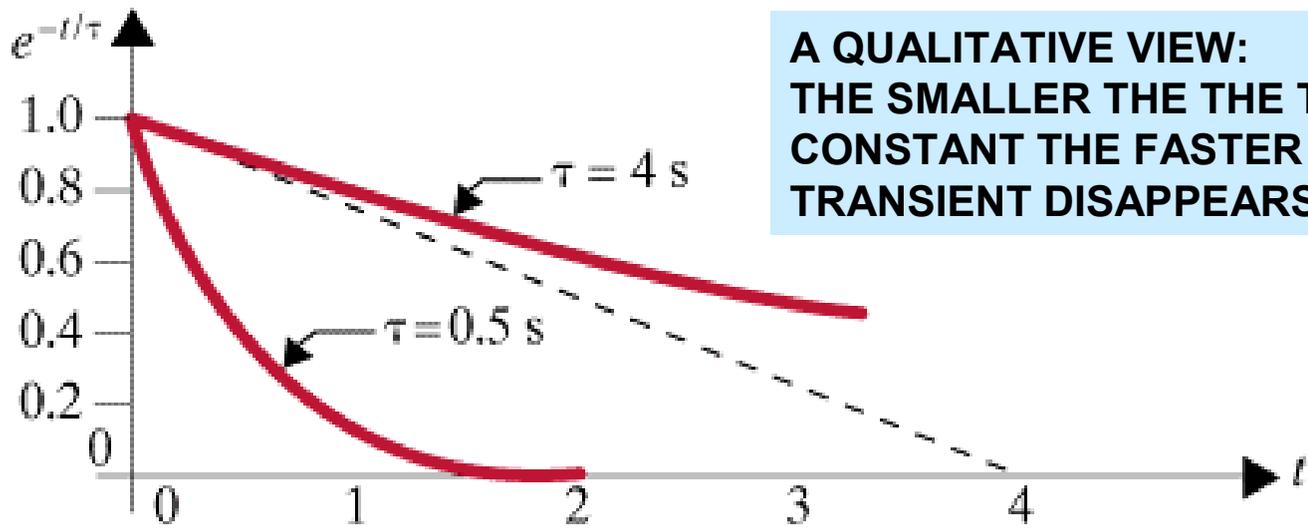With less than 2% error transient is zero beyond this point




A QUALITATIVE VIEW:
THE SMALLER THE THE TIME
CONSTANT THE FASTER THE
TRANSIENT DISAPPEARS



THE TIME CONSTANT

The following example illustrates the physical meaning of time constant

Charging a capacitor

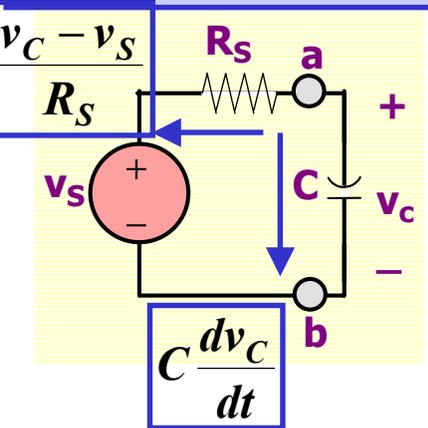

KCL@a:

$$C \frac{dv_c}{dt} + \frac{v_c - v_s}{R_s} = 0$$

The model

$$R_{TH} C \frac{dv_c}{dt} + v_c = v_{TH}$$

Assume $v_s = V_s, v_c(0) = 0$

$$\tau = R_{TH} C$$

The solution can be shown to be


$$v_c(t) = V_s - V_s e^{-\frac{t}{\tau}}$$

transient

For practical purposes the capacitor is charged when the transient is negligible

t	$e^{-\frac{t}{\tau}}$
τ	0.368
2τ	0.135
3τ	0.0498
4τ	0.0183
5τ	0.0067

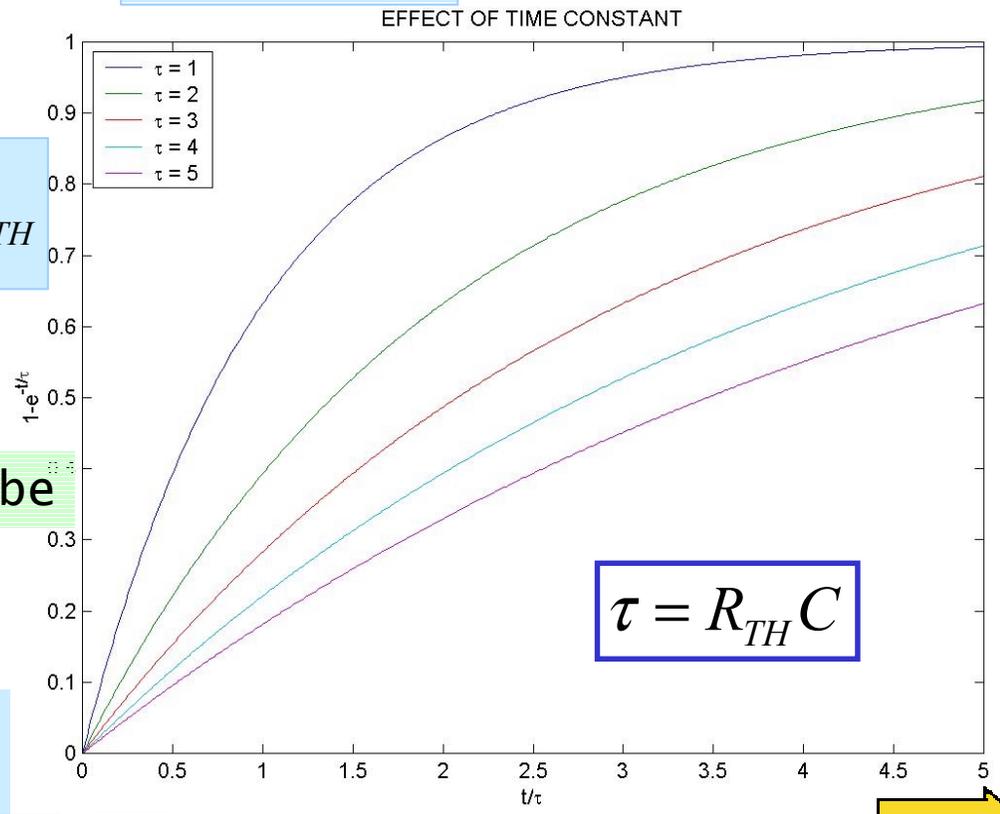with less than 1% error the transient is negligible after five time constants



$$\tau = R_{TH} C$$



CIRCUITS WITH ONE ENERGY STORING ELEMENT

THE DIFFERENTIAL EQUATION APPROACH

CONDITIONS

1. THE CIRCUIT HAS ONLY CONSTANT INDEPENDENT SOURCES
2. THE DIFFERENTIAL EQUATION FOR THE VARIABLE OF INTEREST IS SIMPLE TO OBTAIN. NORMALLY USING BASIC ANALYSIS TOOLS; e.g., KCL, KVL. . . OR THEVENIN
3. THE INITIAL CONDITION FOR THE DIFFERENTIAL EQUATION IS KNOWN, OR CAN BE OBTAINED USING STEADY STATE ANALYSIS

FACT : WHEN ALL INDEPENDENT SOURCES ARE CONSTANT FOR ANY VARIABLE, $y(t)$, IN THE CIRCUIT THE SOLUTION IS OF THE FORM

$$y(t) = K_1 + K_2 e^{-\frac{(t-t_0)}{\tau}}, t > t_0$$

SOLUTION STRATEGY: USE THE DIFFERENTIAL EQUATION AND THE INITIAL CONDITIONS TO FIND THE PARAMETERS K_1, K_2, τ



If the diff eq for y is known in the form

$$a_1 \frac{dy}{dt} + a_0 y = f$$

$$y(0+) = y_0$$

We can use this info to find the unknowns

Use the initial condition to get one more equation

$$y(0+) = K_1 + K_2$$

$$K_2 = y(0+) - K_1$$

Use the diff eq to find two more equations by replacing the form of solution into the differential equation

$$y(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0 \Rightarrow \frac{dy}{dt} = -\frac{K_2}{\tau} e^{-\frac{t}{\tau}}$$

$$a_1 \left(-\frac{K_2}{\tau} e^{-\frac{t}{\tau}} \right) + a_0 \left(K_1 + K_2 e^{-\frac{t}{\tau}} \right) = f$$

$$a_0 K_1 = f \Rightarrow K_1 = \frac{f}{a_0}$$

$$\left(-\frac{a_1}{\tau} + a_0 \right) K_2 e^{-\frac{t}{\tau}} = 0 \Rightarrow \tau = \frac{a_1}{a_0}$$

SHORTCUT: WRITE DIFFERENTIAL EQ. IN NORMALIZED FORM WITH COEFFICIENT OF VARIABLE = 1.


$$a_1 \frac{dy}{dt} + a_0 y = f \Rightarrow \frac{a_1}{a_0} \frac{dy}{dt} + y = \frac{f}{a_0}$$

τ K_1



LEARNING EXAMPLE FIND $v(t), t > 0$. ASSUME $v(0) = V_s/2$

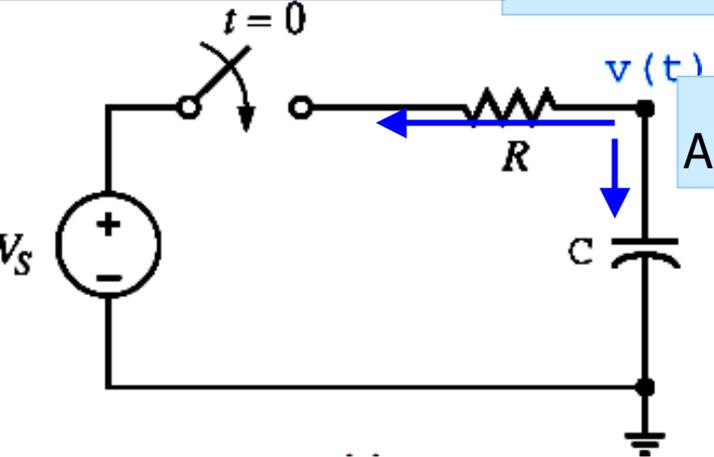$x(t) = K_1 + K_2 e^{-t/\tau}, t > 0$
 $K_1 = x(\infty); K_1 + K_2 = x(0+)$



ANSWER: $v(t) = V_s - (V_s/2)e^{-t/RC}, t > 0$

STEP 2 STEADY STATE ANALYSIS

SOLUTION IS $v(t) = K_1 + K_2 e^{-t/\tau}, t > 0$
 for $\tau > 0$ and $t \rightarrow \infty, v(t) \rightarrow K_1$ (steady state value)

IN STEADY STATE THE SOLUTION IS A CONSTANT. HENCE ITS DERIVATIVE IS ZERO. FROM DIFF EQ.

$\frac{dv}{dt} = 0 \Rightarrow v = V_s$ Steady state value from diff. eq.

\therefore (equating steady state values)
 $K_1 = V_s$

IF THE MODEL IS $\tau \frac{dy}{dt} + y = f$ THEN $K_1 = f$

STEP 3 USE OF INITIAL CONDITION

AT $t = 0$
 $v(0) = K_1 + K_2 \Rightarrow K_2 = v(0) - K_1$

$K_2 = v(0) - f$

$v(0) = V_s/2 \Rightarrow K_2 = -V_s/2$

MODEL FOR $t > 0$. USE KCL @ $v(t)$

$\frac{v(t) - V_s}{R} + C \frac{dv}{dt}(t) = 0$ ***/R**

initial condition $v(0) = V_s/2$

(DIFF. EQ. KNOWN, INITIAL CONDITION KNOWN)

STEP 1 TIME CONSTANT

$\tau \frac{dy}{dt} + y = f$


$RC \frac{dv}{dt}(t) + v(t) = V_s$

Get time constant as coefficient of derivative



LEARNING EXAMPLE

FIND $i(t), t > 0$

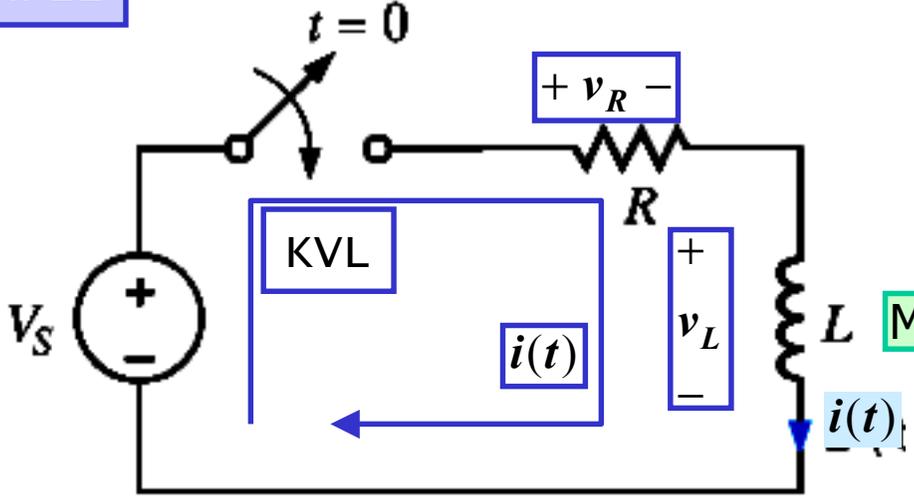

$$x(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$$

$$K_1 = x(\infty); K_1 + K_2 = x(0+)$$

$$i(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$$

MODEL. USE KVL FOR $t > 0$

$$V_S = v_R + v_L = Ri(t) + L \frac{di}{dt}(t)$$

INITIAL CONDITION
 $t < 0 \Rightarrow i(0-) = 0$
 inductor $\Rightarrow i(0-) = i(0+)$ } $i(0+) = 0$

STEP 1 $\frac{L}{R} \frac{di}{dt}(t) + i(t) = \frac{V_S}{R}$ $\tau = \frac{L}{R}$

STEP 2 STEADY STATE $i(\infty) = K_1 = \frac{V_S}{R}$

STEP 3 INITIAL CONDITION $i(0+) = K_1 + K_2$

ANS: $i(t) = \frac{V_S}{R} \left(1 - e^{-\frac{t}{L/R}} \right)$




LEARNING BY DOING

Find $i(t)$ for $t > 0$
in the following network:

$$i(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$$

MODEL. KCL FOR $t > 0$

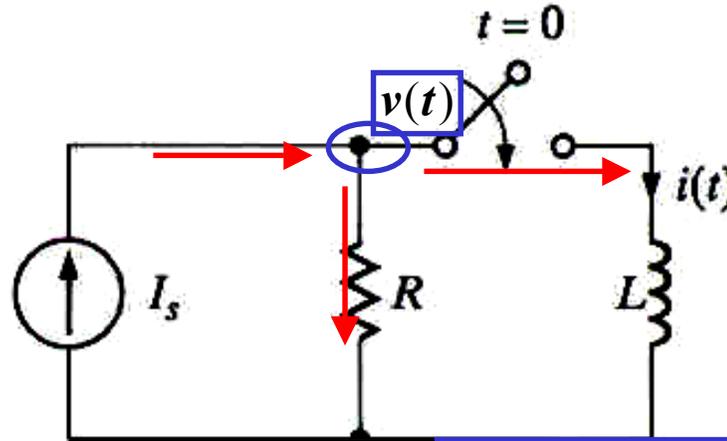

$$I_s = \frac{v(t)}{R} + i(t)$$

$$v(t) = L \frac{di}{dt}(t) \Rightarrow I_s = \frac{L}{R} \frac{di}{dt}(t) + i(t)$$


INITIAL CONDITION: $i(0+) = 0$

STEP 1 $\tau = \frac{L}{R}$

STEP 2 $i(\infty) = I_s \Rightarrow K_1 = I_s$

STEP 3 $i(0+) = 0 = K_1 + K_2$
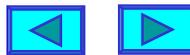
$$\text{ANS: } i(t) = I_s \left(1 - e^{-\frac{t}{L/R}} \right)$$





$$i(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$$


Assuming that the switch has been in position 1 for a long time, at time $t = 0$ the switch is moved to position 2. We wish to calculate the current $i(t)$ for $t > 0$.

INITIAL CONDITIONS

CIRCUIT IN STEADY STATE FOR $t < 0$

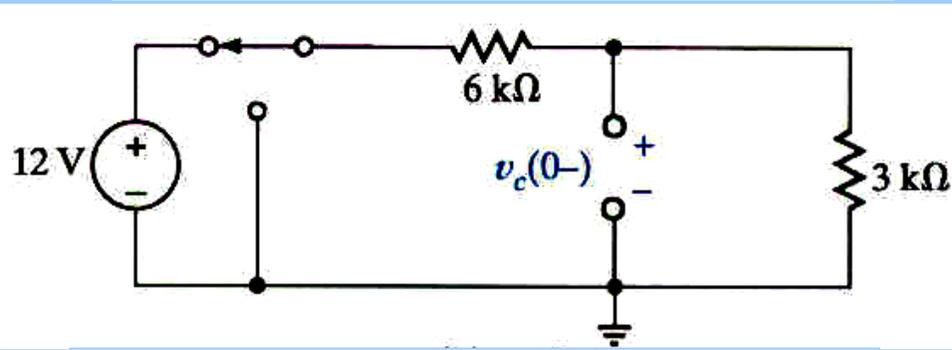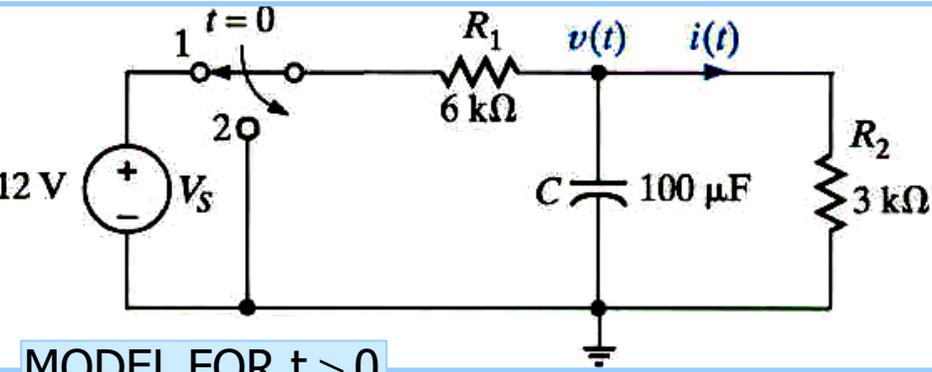

MODEL FOR $t > 0$

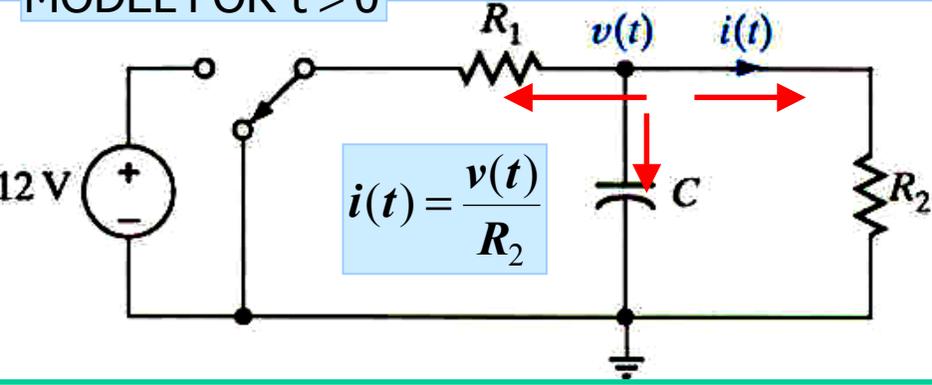

$$v_C(0^-) = \frac{3k}{3k + 6k} (12) = 4V \Rightarrow v(0^+) = 4V$$

STEP 1

$$\tau = R_P C = (2 \times 10^3 \Omega)(100 \times 10^{-6} F) = 0.2s$$

STEP 2

$$v(\infty) = K_1 = 0$$

STEP 3

$$v(0^+) = K_1 + K_2 = 4V \Rightarrow K_2 = 4V$$

IT IS SIMPLER TO DETERMINE MODEL FOR CAPACITOR VOLTAGE

$$v(t) = 4e^{-\frac{t}{0.2}} [V], t > 0$$

$$\frac{v(t)}{R_1} + C \frac{dv}{dt}(t) + \frac{v(t)}{R_2} = 0; R_P = R_1 \parallel R_2$$


$$R_P = 3k \parallel 6k = 2k\Omega$$

$$C \frac{dv}{dt}(t) + \frac{v(t)}{R_P} = 0$$

$$\text{ANS: } i(t) = \frac{4}{3} e^{-\frac{t}{0.2}} [mA], t > 0$$



LEARNING EXAMPLE

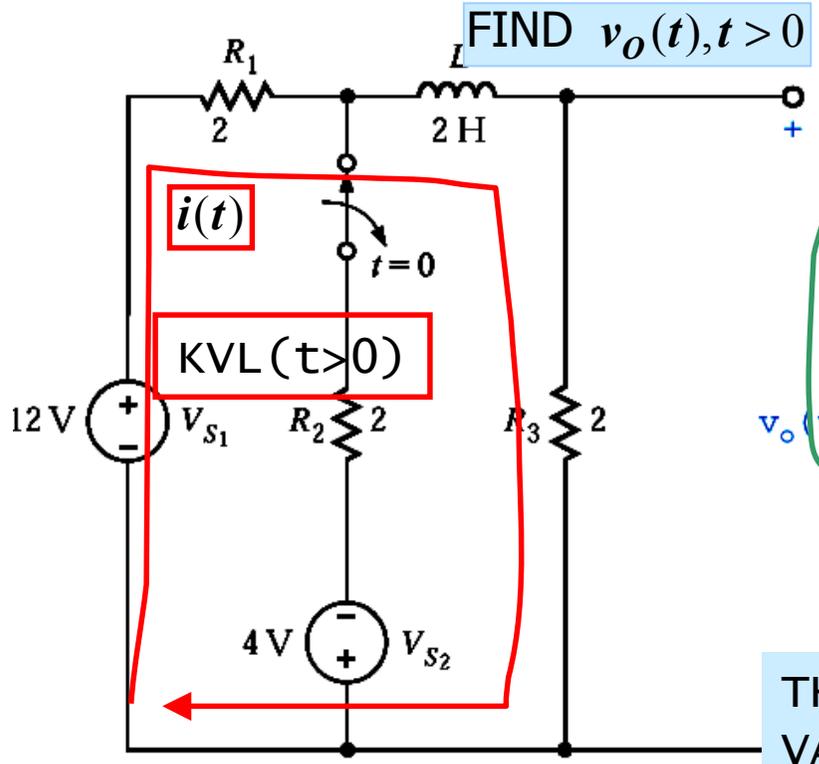

FIND $v_o(t), t > 0$

$$x(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$$

$$K_1 = x(\infty); K_1 + K_2 = x(0+)$$

$$v_o(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$$

STEP 2: FIND K1 USING STEADY STATE ANALYSIS

$$0.5 \frac{dv_o}{dt}(t) + v_o(t) = 6 \Rightarrow v_o(\infty) = 6V$$

$$v_o(\infty) = K_1$$

$$\therefore K_1 = 6V$$

THE NEXT STEP REQUIRES THE INITIAL VALUE OF THE VARIABLE, $v_o(0+)$

MODEL FOR $t > 0$. USE KVL

$$-V_{S1} + R_1 i(t) + L \frac{di}{dt}(t) + R_3 i(t) = 0$$

$$2 \frac{di}{dt}(t) + 4i(t) = 12 \quad v_o(t) = 2i(t)[V]$$

$$0.5 \frac{di}{dt}(t) + i(t) = 3[A]$$

$$0.5 \frac{dv_o}{dt}(t) + v_o(t) = 6V \quad \tau = 0.5$$


STEP 1

FOR THE INITIAL CONDITION ONE NEEDS THE INDUCTOR CURRENT FOR $t < 0$ AND USES THE CONTINUITY OF THE INDUCTOR CURRENT DURING THE SWITCHING .

THE STEADY STATE ASSUMPTION FOR $t < 0$ SIMPLIFIES THE ANALYSIS




CIRCUIT IN STEADY STATE ($t < 0$)

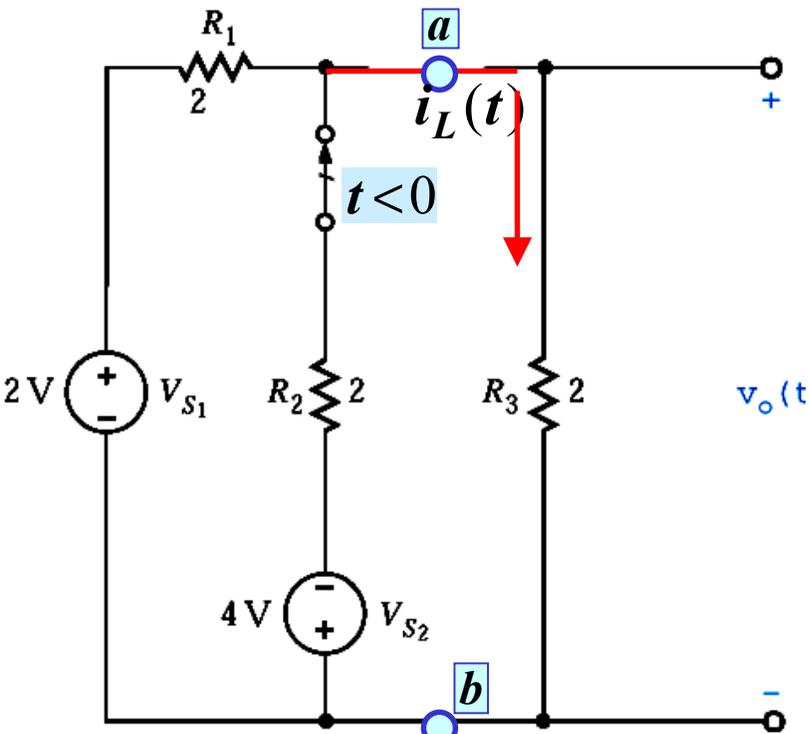

MUST FIND $i_L(t)$

FOR EXAMPLE USE THEVENIN ASSUMING INDUCTOR IN STEADY STATE
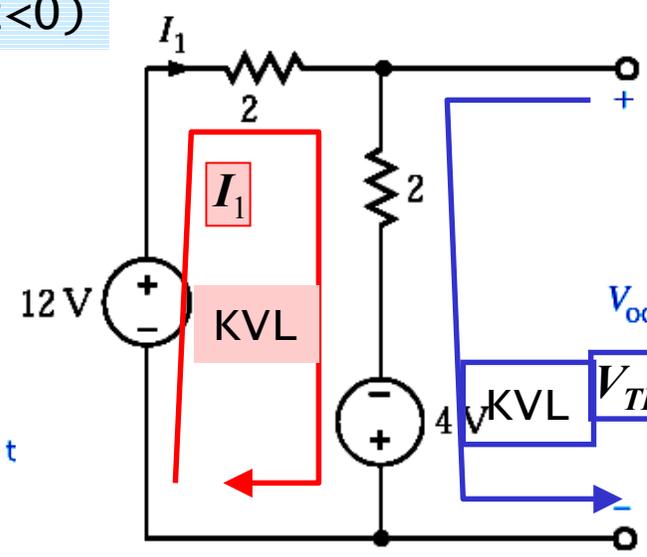
$$v_o(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$$




$$R_{TH} = 2 \parallel 2 = 1\Omega$$

$$-12 + 4I_1 - 4 = 0$$

$$I_1 = 4[A]$$

$$V_{TH} = V_{OC} = 2I_1 - 4 = 4[V]$$

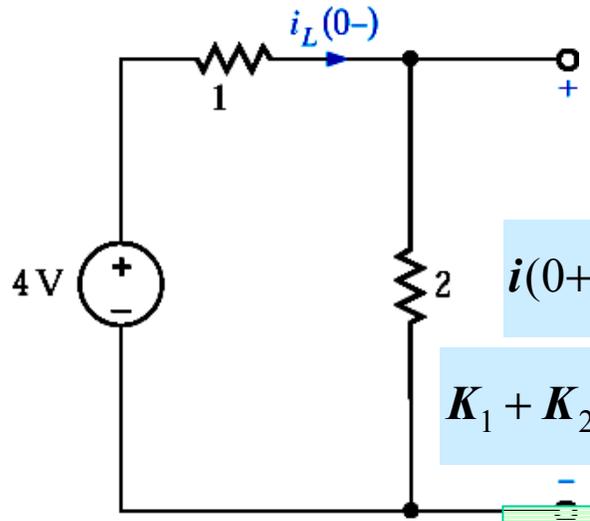

$$i_L(0-) = i(0+) = \frac{4}{3}[A]$$

$$i(0+) = \frac{4}{3} \Rightarrow v_o(0+) = \frac{8}{3}[V]$$

$$K_1 + K_2 = \frac{8}{3} = 6 - K_2 \Rightarrow K_2 = \frac{10}{3}$$


$$v_o(t) = 6 - \frac{10}{3} e^{-0.5t}[V], t > 0$$

$$i(t) = 3 - \frac{5}{3} e^{-0.5t}, t > 0$$



LEARNING EXTENSION FIND $v_o(t), t > 0$

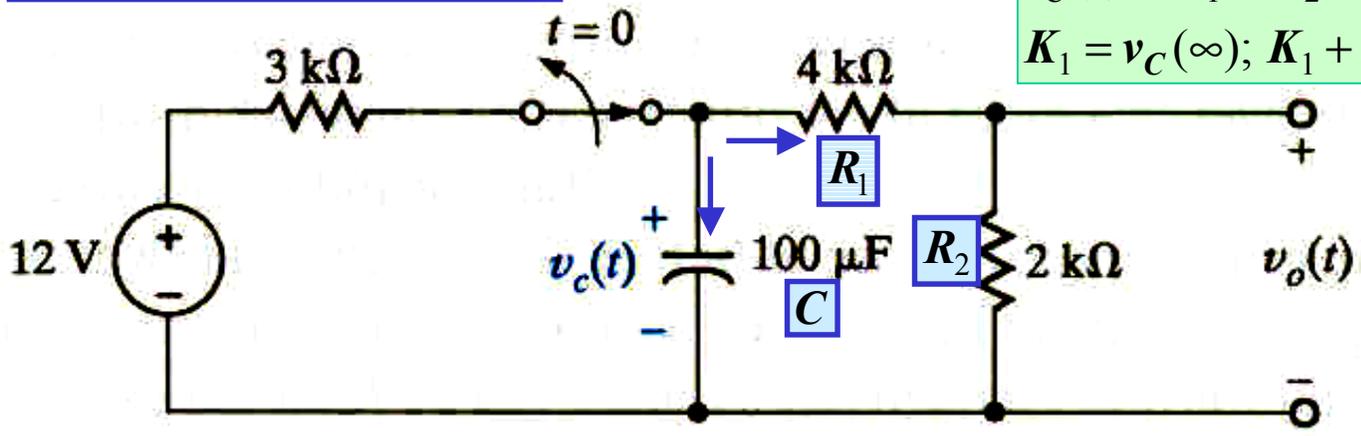$v_C(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$
 $K_1 = v_C(\infty); K_1 + K_2 = i_1(0+)$



MODEL FOR $t > 0$. USE KCL

DETERMINE $v_c(t)$

$C \frac{dv_C}{dt}(t) + \frac{v_C}{R_1 + R_2} = 0 \Rightarrow (R_1 + R_2)C \frac{dv_C}{dt}(t) + v_C = 0$

$v_o(t) = \frac{2}{2+4} v_C(t) = \frac{1}{3} v_C(t)$


STEP 1 $\tau = (R_1 + R_2)C = (6 \times 10^3 \Omega)(100 \times 10^{-6} F) = 0.6s$

$v_o(t) = \frac{8}{3} e^{-\frac{t}{0.6}} [V], t > 0$

STEP 2 $v_C(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$ $K_1 = 0$

INITIAL CONDITIONS. CIRCUIT IN STEADY STATE $t < 0$


STEP 3

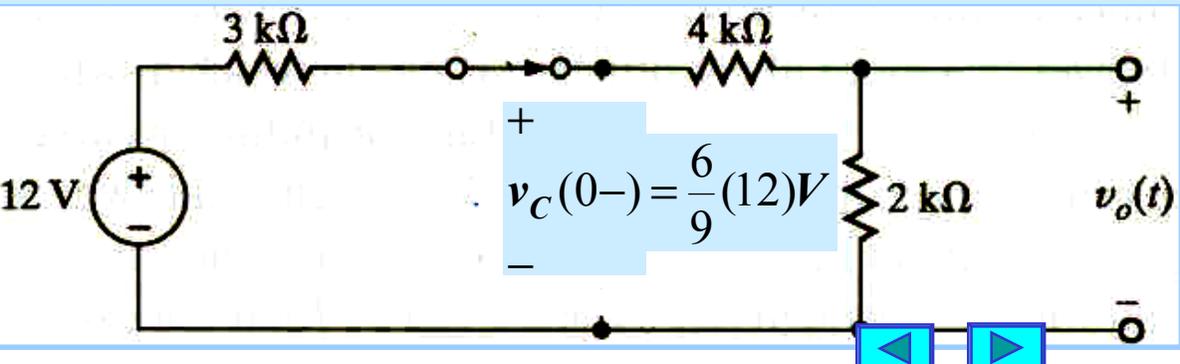

$v_C(0+) = 8 = K_1 + K_2 \Rightarrow K_2 = 8[V]$

$v_C(t) = 8e^{-\frac{t}{0.6}} [V], t > 0$


LEARNING EXTENSION FIND $i_1(t), t > 0$

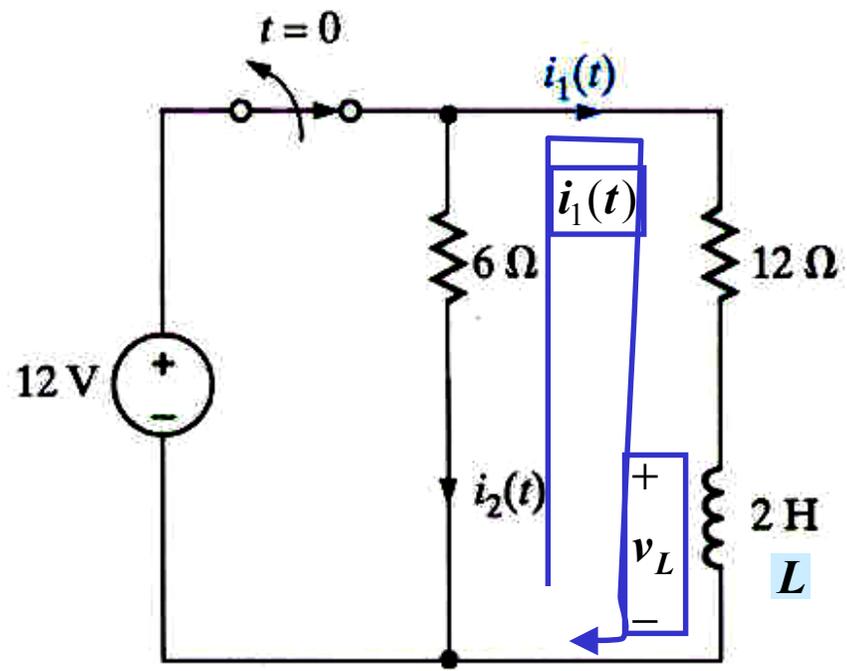

$$i_1(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$$

$$K_1 = i_1(\infty); K_1 + K_2 = i_1(0+)$$

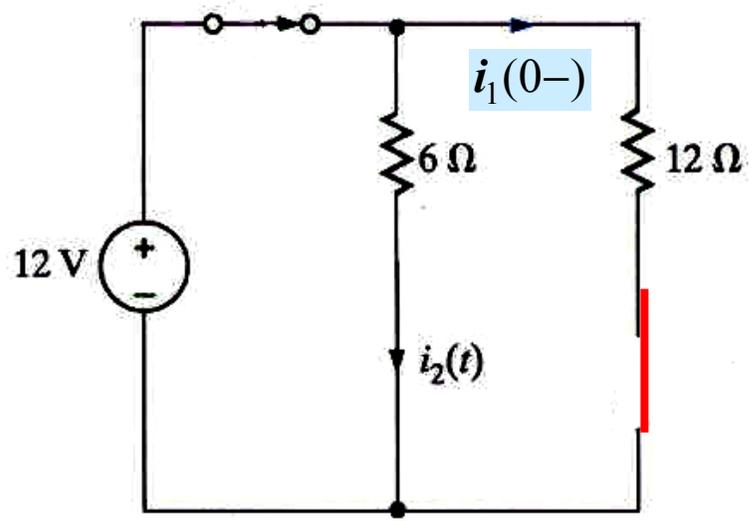CIRCUIT IN STEADY STATE PRIOR TO SWITCHING



$$i_1(0-) = \frac{12V}{12\Omega} = 1A$$

MODEL FOR $t > 0$. USE KVL

$$L \frac{di_1}{dt} + 18i_1(t) = 0 \Rightarrow \frac{1}{9} \frac{di_1}{dt}(t) + i_1(t) = 0$$

STEP 1 $\tau = \frac{1}{9} s$

STEP 2 $K_1 = 0$

STEP 3

$$i_1(0-) = i_1(0+) = K_1 + K_2 \Rightarrow K_2 = 1[A]$$


FOR INITIAL CONDITIONS ONE NEEDS INDUCTOR CURRENT FOR $t < 0$

$$\text{ANS: } i_1(t) = e^{-\frac{t}{1/9}} [A] = e^{-9t} [A], t > 0$$




USING THEVENIN TO OBTAIN MODELS

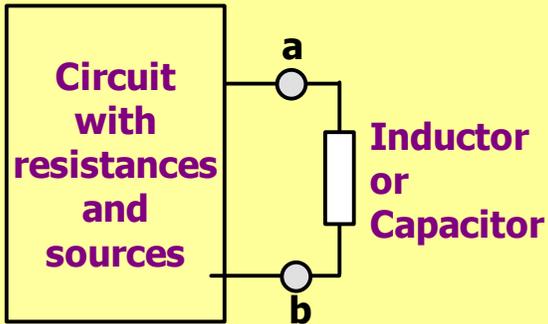
Obtain the voltage across the capacitor or the current through the inductor



→
Thevenin

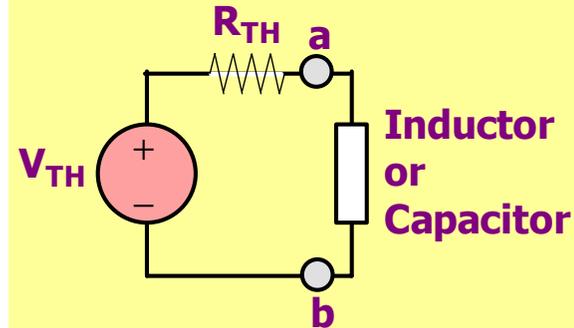

Representation of an arbitrary circuit with one storage element

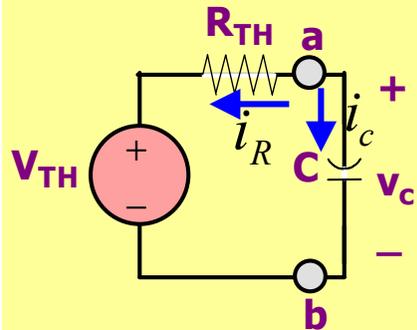

Case 1.1
Voltage across capacitor

KCL@ node a


$$i_c + i_R = 0$$

$$i_c = C \frac{dv_C}{dt}$$

$$i_R = \frac{v_C - v_{TH}}{R_{TH}}$$

$$C \frac{dv_C}{dt} + \frac{v_C - v_{TH}}{R_{TH}} = 0$$

$$R_{TH} C \frac{dv_C}{dt} + v_C = v_{TH}$$

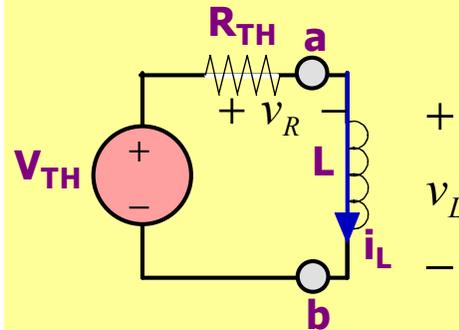

Case 1.2
Current through inductor

Use KVL

$$v_R + v_L = v_{TH}$$

$$v_R = R_{TH} i_L$$


$$v_L = L \frac{di_L}{dt}$$

$$L \frac{di_L}{dt} + R_{TH} i_L = v_{TH}$$


$$\left(\frac{L}{R_{TH}} \right) \frac{di_L}{dt} + i_L = \frac{v_{TH}}{R_{TH}} = i_{SC}$$

EXAMPLE

Find $i_o(t); t > 0$

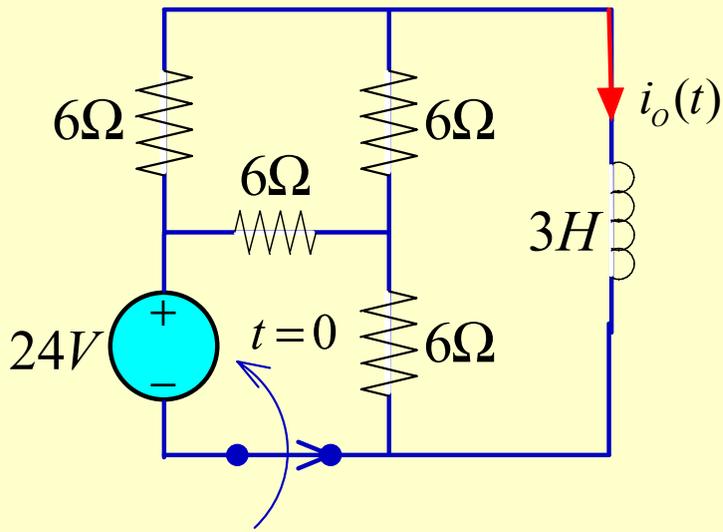

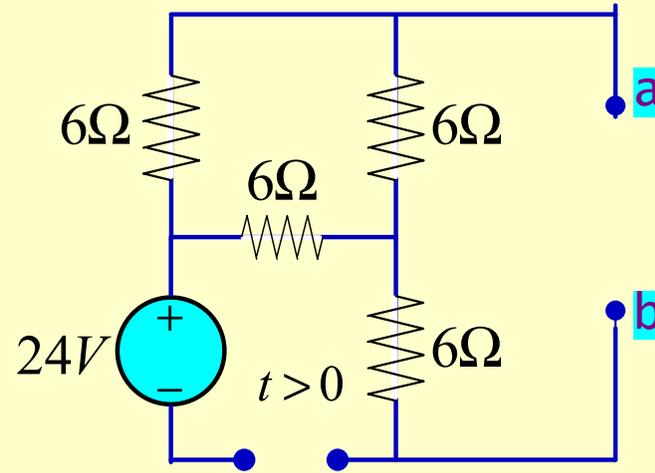Thevenin for $t > 0$
at inductor terminals



$$v_{TH} = 0 \quad R_{TH} = 6 + (6 \parallel (6 + 6))$$

$$\tau = \frac{L}{R_{TH}} = \frac{3H}{10\Omega} = 0.3s$$

$$0.3 \frac{di_o}{dt} + i_o = 0; t > 0$$

$$0.3 \left(-\frac{K_2}{0.3} e^{-\frac{t}{0.3}} \right) + K_1 + K_2 e^{-\frac{t}{0.3}} = 0$$

$$K_1 = 0 \Rightarrow i_o(t) = K_2 e^{-\frac{t}{0.3}}; t > 0$$

The variable of interest is the inductor current. The model is

$$\frac{L}{R_{TH}} \frac{di_o}{dt} + i_o = \frac{v_{TH}}{R_{TH}}$$

And the solution is of the form


$$i_o(t) = K_1 + K_2 e^{-\frac{t}{\tau}}; t > 0$$

Next: Initial Condition



Determine $i_o(0+)$. Use steady state assumption and continuity of inductor current

Circuit for $t < 0$

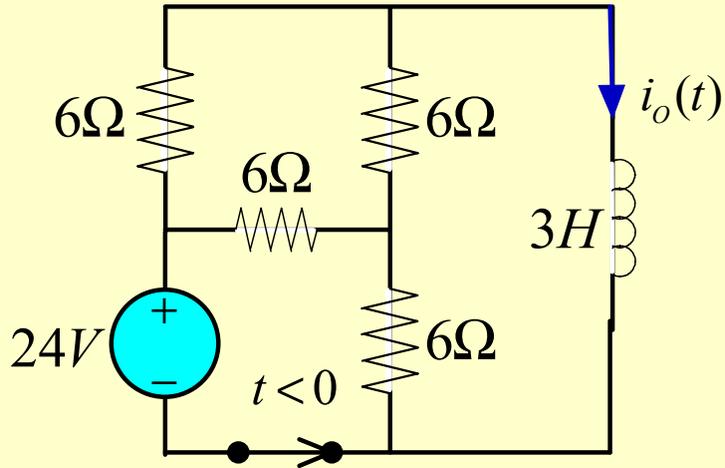

$$6i_1 + 6(i_1 - i_3) + 6(i_1 - i_2) = 0$$

Loop analysis

$$-24 + 6(i_2 - i_1) + 6(i_2 - i_3) = 0$$


$$i_c(0+) = i_3$$

$$6(i_3 - i_1) + 6(i_3 - i_2) = 0$$

$$\frac{v_1}{6} + \frac{v_1}{6} + \frac{v_1 - 24}{6} = 0 \Rightarrow v_1 = 8$$

Node analysis
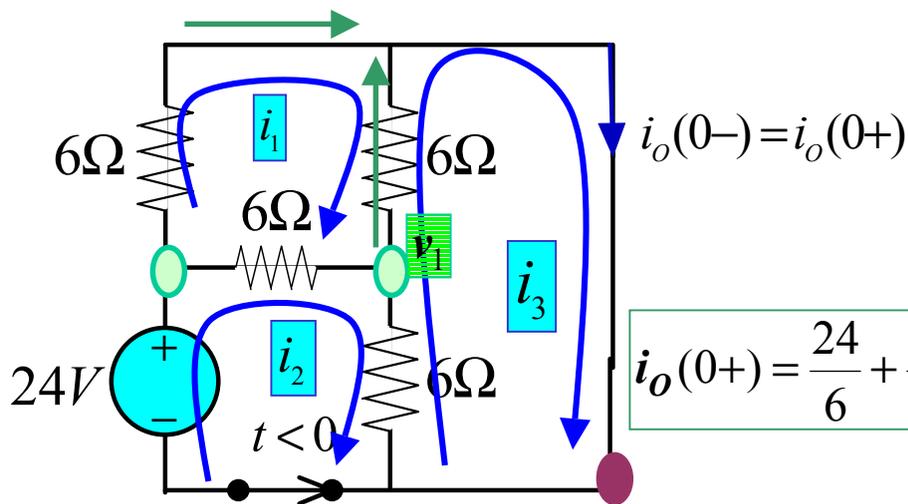
$$\text{solution: } i_c(0+) = \frac{32}{6} \text{ mA}$$



$$i_o(0+) = \frac{24}{6} + \frac{v_1}{6}$$

Since $K_1=0$ the solution is

$$i_o(t) = K_2 e^{-\frac{t}{0.3}}; t > 0$$


$$\text{Evaluating at } 0+ \quad K_2 = \frac{32}{6}$$

$$i_o(t) = \frac{32}{6} e^{-\frac{t}{0.3}}; t > 0$$



EXAMPLE

Find $i_o(t), t > 0$

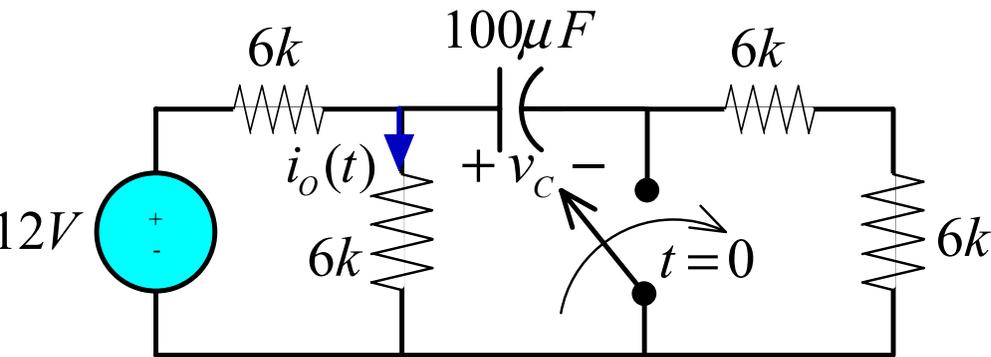


For $t > 0$ $i_o = \frac{v_c}{6k}$

Hence, if the capacitor voltage is known the problem is solved

Model for v_c
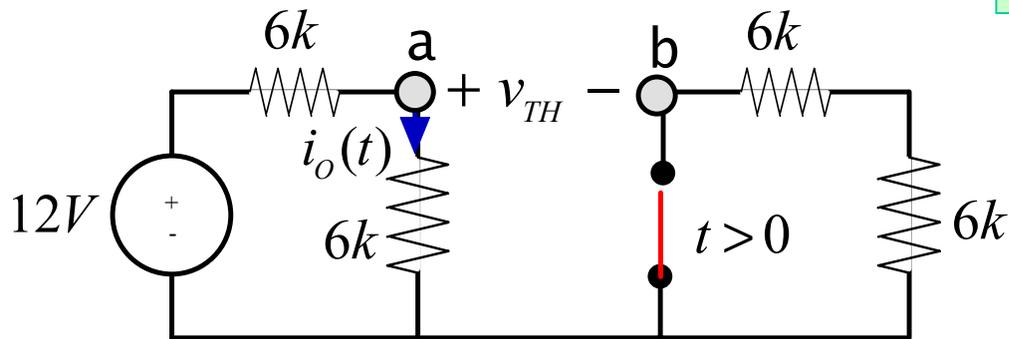
$$R_{TH} C \frac{dv_c}{dt} + v_c = v_{TH}$$



$$v_{TH} = 6V$$

$$R_{TH} = 6k \parallel 6k = 3k$$

$$\tau = 3 \cdot 10^3 \Omega \cdot 100 \cdot 10^{-6} F = 0.3s$$

Model for v_c

$$0.3 \frac{dv_c}{dt} + v_c = 6$$


$$v_c = K_1 + K_2 e^{-\frac{t}{0.3}}$$

$$1.5 \left(-\frac{K_2}{1.5} e^{-\frac{t}{1.5}} \right) + K_1 + K_2 e^{-\frac{t}{0.3}} = 6$$

$$K_1 = 6$$

Now we need to determine the initial value $v_c(0+)$ using continuity and the steady state assumption

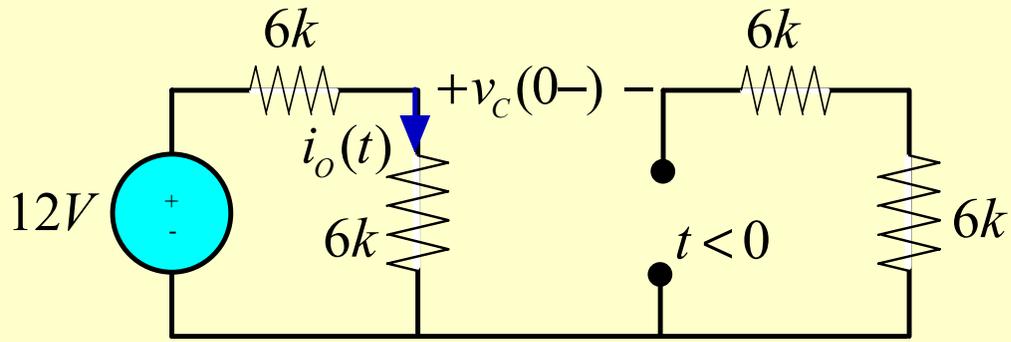circuit in steady state
before the switching



$$v_c(0-) = 6V$$

Continuity of capacitor voltage

$$v_c(0+) = 6V$$

$$K_1 + K_2 = v_c(0+)$$

$$K_1 = 6 \Rightarrow K_2 = 0$$

$$v_c(t) = 6V; t > 0 \Rightarrow$$

$$i_o(t) = \frac{v_c}{6k} = 1mA; t > 0$$

Diff Eq
Approach

