

# STEADY-STATE POWER ANALYSIS

## LEARNING GOALS

**Instantaneous Power**

For the special case of steady state sinusoidal signals

**Average Power**

Power absorbed or supplied during one cycle

**Maximum Average Power Transfer**

When the circuit is in sinusoidal steady state

**Effective or RMS Values**

For the case of sinusoidal signals

**Power Factor**

A measure of the angle between current and voltage phasors

**Power Factor Correction**

How to improve power transfer to a load by “aligning” phasors


**Single Phase Three-Wire Circuits**

Typical distribution method for households and small loads



GEAUX

# INSTANTANEOUS POWER

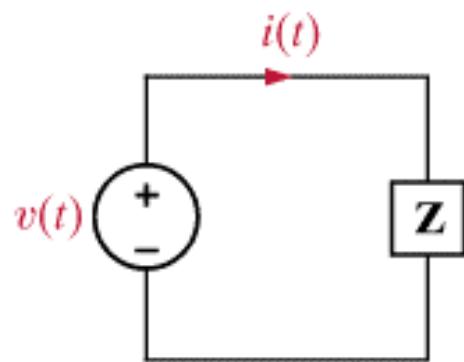

Instantaneous Power Supplied to Impedance  
 $p(t) = v(t)i(t)$

In steady State

$$v(t) = V_M \cos(\omega t + \theta_v)$$

$$i(t) = I_M \cos(\omega t + \theta_i)$$

$$p(t) = V_M I_M \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$\cos \phi_1 \cos \phi_2 = \frac{1}{2} [\cos(\phi_1 - \phi_2) + \cos(\phi_1 + \phi_2)]$$

$$p(t) = \frac{V_M I_M}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)]$$

constant

Twice the frequency

# LEARNING EXAMPLE

Assume:  $v(t) = 4 \cos(\omega t + 60^\circ)$ ,  
 $Z = 2 \angle 30^\circ \Omega$

Find:  $i(t), p(t)$


$$I = \frac{V}{Z} = \frac{4 \angle 60^\circ}{2 \angle 30^\circ} = 2 \angle 30^\circ (A)$$

$$i(t) = 2 \cos(\omega t + 30^\circ) (A)$$

$$V_M = 4, \theta_v = 60^\circ$$

$$I_M = 2, \theta_i = 30^\circ$$
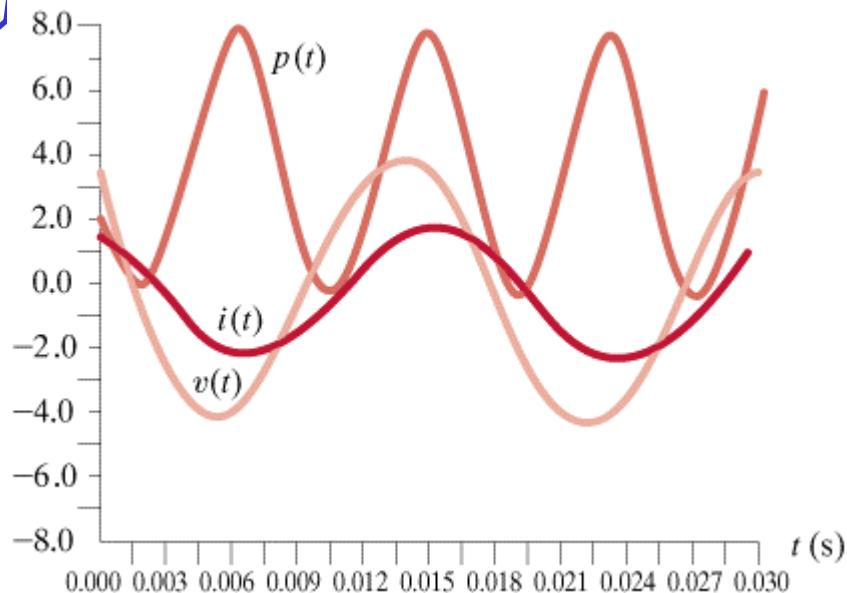
$$p(t) = 4 \cos 30^\circ + 4 \cos(2\omega t + 90^\circ)$$



## AVERAGE POWER

For sinusoidal (and other periodic signals) we compute averages over one period

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt$$

$$T = \frac{2\pi}{\omega}$$

$$p(t) = \frac{V_M I_M}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)]$$

$$P = \frac{V_M I_M}{2} \cos(\theta_v - \theta_i)$$

It does not matter who leads

If voltage and current are in phase

$$\theta_v = \theta_i \Rightarrow P = \frac{1}{2} V_M I_M$$


Purely resistive

If voltage and current are in quadrature

$$\theta_v - \theta_i = \pm 90^\circ \Rightarrow P = 0$$

Purely inductive or capacitive

## LEARNING EXAMPLE

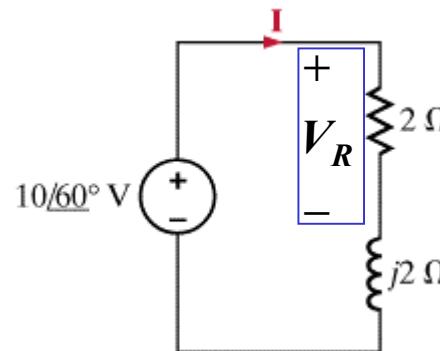

Find the average power absorbed by impedance

$$I = \frac{10\angle 60^\circ}{2 + j2} = \frac{10\angle 60^\circ}{2\sqrt{2}\angle 45^\circ} = 3.53\angle 15^\circ (A)$$

$$V_M = 10, I_M = 3.53, \theta_v = 60^\circ, \theta_i = 15^\circ$$

$$P = 35.3 \cos(45^\circ) = 12.5W$$


Since inductor does not absorb power one can use voltages and currents across the resistive part

$$V_R = \frac{2}{2 + j2} 10\angle 60^\circ = 7.06\angle 15^\circ (V)$$

$$P = \frac{1}{2} 7.06 \times 3.53 W$$
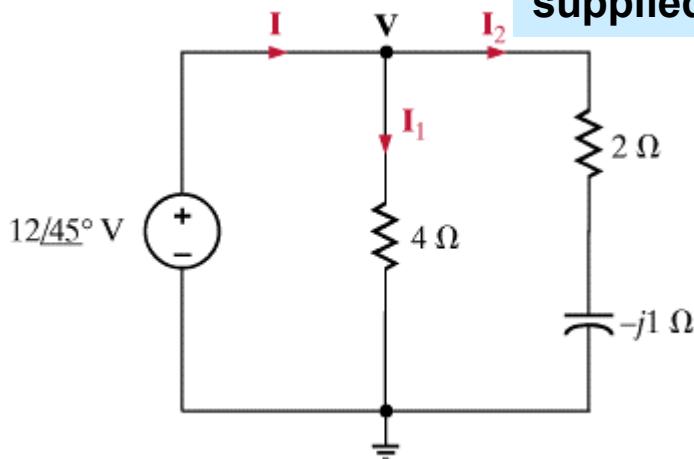
## LEARNING EXAMPLE

Determine the average power absorbed by each resistor, the total average power absorbed and the average power supplied by the source



If voltage and current are in phase

$$\theta_v = \theta_i \Rightarrow P = \frac{1}{2} V_M I_M = \frac{1}{2} R I_{1M}^2 = \frac{1}{2} \frac{V_M^2}{R}$$

$$I_1 = \frac{12\angle 45^\circ}{4} = 3\angle 45^\circ(A)$$

$$P_{4\Omega} = \frac{1}{2} 12 \times 3 = 18W$$

$$I_2 = \frac{12\angle 45^\circ}{2 - j1} = \frac{12\angle 45^\circ}{\sqrt{5}\angle -26.37^\circ} = 5.36\angle 71.57^\circ(A)$$

$$P_{2\Omega} = \frac{1}{2} \times 2 \times 5.36^2(W) = 28.7W$$

Inductors and capacitors do not absorb power in the average

$$P_{total} = 18 + 28.7W$$

$$P_{supplied} = P_{absorbed} \Rightarrow P_{supplied} = 46.7W$$

Verification

$$I = I_1 + I_2 = 3\angle 45^\circ + 5.36\angle 71.57^\circ$$


$$I = 8.15\angle 62.10^\circ(A)$$

$$P = \frac{V_M I_M}{2} \cos(\theta_v - \theta_i)$$

$$P_{supplied} = \frac{1}{2} 12 \times 8.15 \times \cos(45^\circ - 62.10^\circ)$$
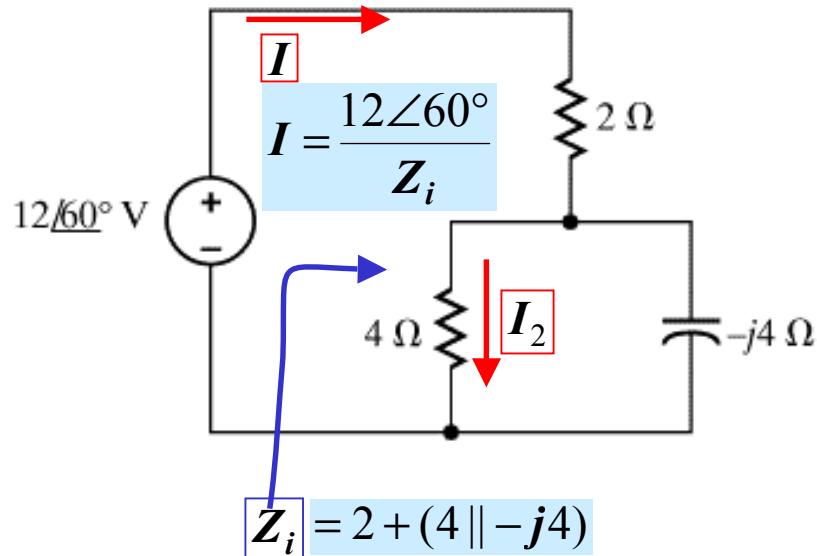
## LEARNING EXTENSION

Find average power absorbed by each resistor



$$I_2 = \frac{-j4}{4-j4} I = \frac{4\angle -90^\circ}{4\sqrt{2}\angle -45^\circ} \times 2.68\angle 86.6^\circ$$

$$I_2 = 1.90\angle 41.6^\circ$$

$$P_{4\Omega} = \frac{1}{2} \times 4 \times 1.90^2 (W)$$

$$Z_i = 2 + \frac{4(-j4)}{4-j4} = \frac{8-j8-j16}{4-j4} = \frac{25.3\angle -71.6^\circ}{4\sqrt{2}\angle -45^\circ}$$


$$Z_i = 4.47\angle -26.6^\circ \Omega$$

$$I = \frac{12\angle 60^\circ}{4.47\angle -26.6^\circ} = 2.68\angle 86.6^\circ (A)$$

$$P_{2\Omega} = \frac{1}{2} R I_M^2 = \frac{1}{2} \times 2 \times 2.68^2 = 7.20 W$$
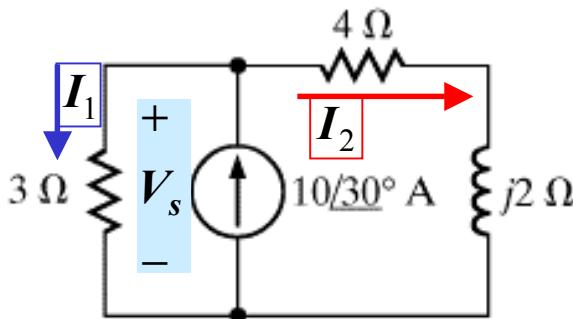
## LEARNING EXTENSION

Find the AVERAGE power absorbed by each PASSIVE component and the total power supplied by the source



$$I_1 = \frac{4 + j2}{3 + 4 + j2} 10\angle 30^\circ$$

$$I_1 = \frac{4.47\angle 26.57^\circ}{7.28\angle 15.95^\circ} 10\angle 30^\circ = 6.14\angle 40.62^\circ (A)$$

$$P_{3\Omega} = \frac{1}{2} RI_M^2 = \frac{1}{2} \times 3 \times 6.14^2 (W)$$

$$I_2 = 10\angle 30^\circ - 6.14\angle 40.62^\circ$$

$$I_2 = \frac{3}{3 + 4 + j2} 10\angle 30^\circ = \frac{30\angle 30^\circ}{7.28\angle 15.95^\circ} \\ = 4.12\angle 14.05^\circ (A)$$

$$P_{4\Omega} = \frac{1}{2} \times 4 \times 4.12^2 (W)$$

$$P_{j2\Omega} = 0(W)$$

**Power supplied by source**

**Method 1.**  $P_{\text{supplied}} = P_{\text{absorbed}}$

$$P_{\text{supplied}} = P_{3\Omega} + P_{4\Omega} = 90.50W$$


**Method 2:**  $P = \frac{1}{2} V_M I_M \cos(\theta_v - \theta_i)$

$$V_s = 3I_1 = 18.42\angle 40.62^\circ$$

$$P = \frac{1}{2} \times 18.42 \times 10 \times \cos(40.62^\circ - 30^\circ)$$
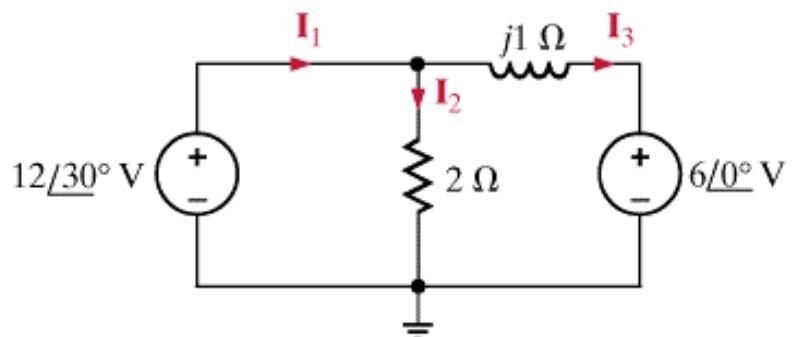
## LEARNING EXAMPLE

Determine average power absorbed or supplied by each element



$$I_2 = \frac{12\angle 30^\circ}{2} = 6\angle 30^\circ (A)$$

$$P_{2\Omega} = \frac{1}{2} RI_M^2 = \frac{1}{2} \times 2 \times 6^2 = 36(W)$$

$$P_{j1\Omega} = 0$$

To determine power absorbed/supplied by sources we need the currents I<sub>1</sub>, I<sub>2</sub>

Average Power

$$P = \frac{1}{2} V_M I_M \cos(\theta_v - \theta_i)$$

For resistors

$$P = \frac{1}{2} RI_M^2 = \frac{1}{2} \frac{V_M^2}{R}$$

$$\begin{aligned} I_3 &= \frac{12\angle 30^\circ - 6\angle 0^\circ}{j1} = \frac{10.39 + j6 - 6}{j} = 6 - j4.39 \\ &= 7.43\angle -36.19^\circ (A) \end{aligned}$$

$$P_{6\angle 0^\circ} = \frac{1}{2} \times 6 \times 7.43 \cos(0 + 36.19^\circ) = 18W$$


**Passive sign convention**

$$\begin{aligned} I_1 &= I_2 + I_3 = 5.20 + j3 + 6 - j4.39 = 11.2 - j1.39(A) \\ &= 11.28\angle -7.07^\circ \end{aligned}$$

$$\begin{aligned} P_{12\angle 30^\circ} &= -\frac{1}{2} \times 12 \times 11.28 \times \cos(30^\circ + 7.07^\circ) \\ &= -54(W) = -(36+18) \end{aligned}$$
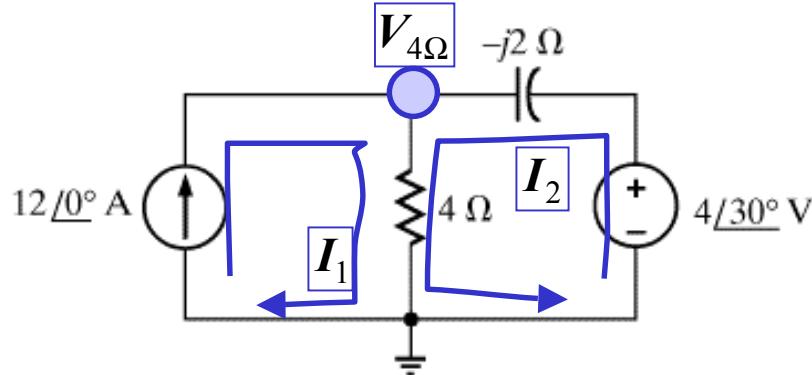
## LEARNING EXTENSION

Determine average power absorbed/supplied by each element



$$P_{12\angle 0^\circ} = -\frac{1}{2} \times 19.92 \times 12 \times \cos(-54.5^\circ - 0^\circ) = -69.4(W)$$

$$P_{4\angle 30^\circ} = -\frac{1}{2} \times 4 \times (9.97) \cos(30^\circ - 204^\circ) = 19.8(W)$$

**Check: Power supplied = power absorbed**

Loop Equations

$$I_1 = 12\angle 0^\circ$$

$$4\angle 30^\circ = -j2I_2 + 4(I_2 + 12\angle 0^\circ)$$

$$I_2 = \frac{4\angle 30^\circ - 48\angle 0^\circ}{4 - j2} = \frac{3.46 + j2 - 48}{4.47\angle -26.57^\circ}$$

$$I_2 = \frac{44.58\angle 177.43^\circ}{4.47\angle -26.57^\circ} = 9.97\angle 204^\circ(A)$$

$$\begin{aligned}V_{4\Omega} &= 4(I_1 + I_2) = 4(12 + 9.97\angle 204^\circ)(V) \\&= 4(12 - 9.108 - j4.055)(V) = 19.92\angle -54.5^\circ(V)\end{aligned}$$

$$P_{4\Omega} = \frac{1}{2} \frac{V_M^2}{R} = \frac{1}{2} \times \frac{19.92^2}{4} = 49.6W$$

$$P_{-2j\Omega} = 0(W)$$

Alternative Procedure

Node Equations

$$-12\angle 0^\circ + \frac{V_{4\Omega}}{4} + \frac{V_{4\Omega} - 4\angle 30^\circ}{-j2} = 0$$

$$I_2 = \frac{4\angle 30^\circ - V_{4\Omega}}{-2j}$$

Average Power


$$P = \frac{1}{2} V_M I_M \cos(\theta_v - \theta_i)$$

For resistors

$$P = \frac{1}{2} R I_M^2 = \frac{1}{2} \frac{V_M^2}{R}$$
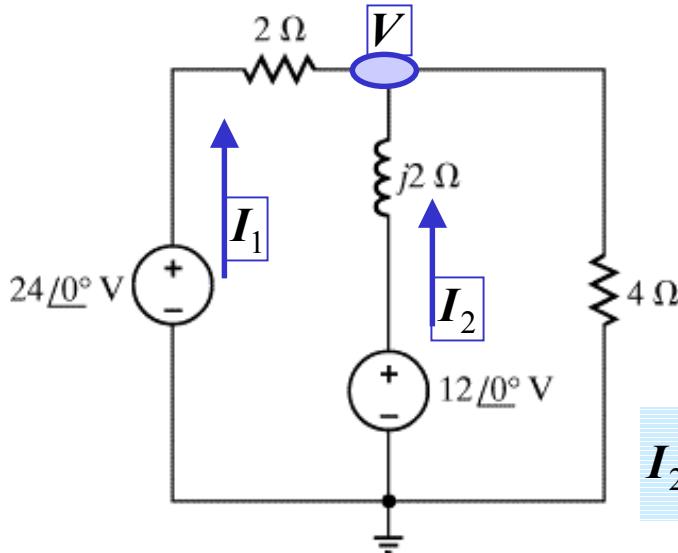
## LEARNING EXTENSION

Determine average power absorbed/supplied by each element



$$I_1 = \frac{24\angle 0^\circ - V}{2} = \frac{24 - 14.77 - j1.85}{2} = 4.62 - j0.925$$

$$I_1 = 4.71\angle -11.32^\circ(A)$$

$$I_2 = \frac{12\angle 0^\circ - V}{j2} = \frac{12 - 14.77 + j1.85}{j2} \times \frac{-j}{-j}$$

$$I_2 = \frac{-1.85 + j2.77}{2} = -0.925 + j1.385(A) = 1.67\angle 123.73^\circ(A)$$

Node Equation

$$\frac{V - 24\angle 0^\circ}{2} + \frac{V - 12\angle 0^\circ}{j2} + \frac{V}{4} = 0 \quad \times j4$$

$$2j(V - 24) + 2(V - 12) + JV = 0$$

$$(2 + 3j)V = 24 + j48$$

$$V = \frac{24 + j48}{2 + j3} \times \frac{2 - j3}{2 - j3} = \frac{192 + j24}{13}$$

$$= 14.88\angle 7.125^\circ(V)$$

$$= 14.77 + j1.85(V)$$

$$P_{2\Omega} = \frac{1}{2} \times 2 \times 4.71^2 = 22.18(W)$$

$$P_{4\Omega} = \frac{1}{2} \times \frac{14.88^2}{4} = 27.67(W)$$

For resistors

$$P = \frac{1}{2} RI_M^2 = \frac{1}{2} \frac{V_M^2}{R}$$

$$P_{12\angle 0^\circ} = -\frac{1}{2} \times 12 \times 1.67 \cos(0^\circ - 123.73^\circ) = 5.565(W)$$

$$P_{24\angle 0^\circ} = -\frac{1}{2} \times 24 \times 4.71 \times \cos(0^\circ + 11.32^\circ) = -55.42(W)$$

Average Power

$$P = \frac{1}{2} V_M I_M \cos(\theta_v - \theta_i)$$


Check:

$$P_{\text{absorbed}} = 22.18 + 27.67 + 5.565(W)$$

$$P_{\text{supplied}} = 55.42(W)$$

# MAXIMUM AVERAGE POWER TRANSFER

$$Z_{TH} = R_{TH} + jX_{TH}$$

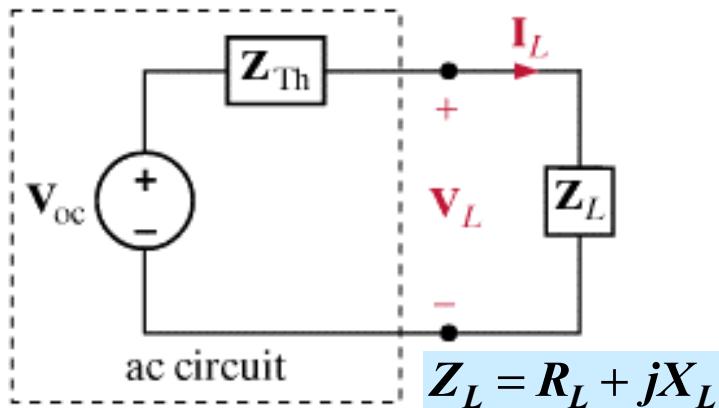

$$Z_L = R_L + jX_L$$

$$P_L = \frac{1}{2} V_{LM} I_{LM} \cos(\theta_{V_L} - \theta_{I_L})$$

$$= \frac{1}{2} |V_L \parallel I_L| \cos(\theta_{V_L} - \theta_{I_L})$$

$$V_L = \frac{Z_L}{Z_L + Z_{TH}} V_{oc} \Rightarrow |V_L| = \left| \frac{Z_L}{Z_L + Z_{TH}} \right| |V_{oc}|$$

$$I_L = \frac{V_L}{Z_L} \Rightarrow \angle I_L = \angle V_L - \angle Z_L \Rightarrow |I_L| = \frac{|V_L|}{|Z_L|}$$

$$Z_L = R_L + jX_L \Rightarrow \tan(\angle Z_L) = \frac{X_L}{R_L}$$

$$\cos \theta = \frac{1}{\sqrt{1 + \tan^2 \theta}} \therefore \cos(\theta_{V_L} - \theta_{I_L}) = \frac{R_L}{\sqrt{R_L^2 + X_L^2}}$$

$$P_L = \frac{1}{2} \frac{|Z_L \parallel V_{oc}|^2}{|Z_L + Z_{TH}|^2} \frac{R_L}{\sqrt{R_L^2 + X_L^2}}$$

$$Z_L + Z_{TH} = (R_L + R_{TH}) + j(X_L + X_{TH})$$

$$|Z_L + Z_{TH}|^2 = (R_L + R_{TH})^2 + (X_L + X_{TH})^2$$

$$P_L = \frac{1}{2} \frac{|V_{oc}|^2 R_L}{(R_L + R_{TH})^2 + (X_L + X_{TH})^2}$$

$$\begin{cases} \frac{\partial P_L}{\partial X_L} = 0 \\ \frac{\partial P_L}{\partial R_L} = 0 \end{cases} \Rightarrow \begin{cases} X_L = -X_{TH} \\ R_L = R_{TH} \end{cases}$$


$$\therefore Z_L^{opt} = Z_{TH}^*$$

$$P_L^{\max} = \frac{1}{2} \left( \frac{|V_{oc}|^2}{4R_{TH}} \right)$$
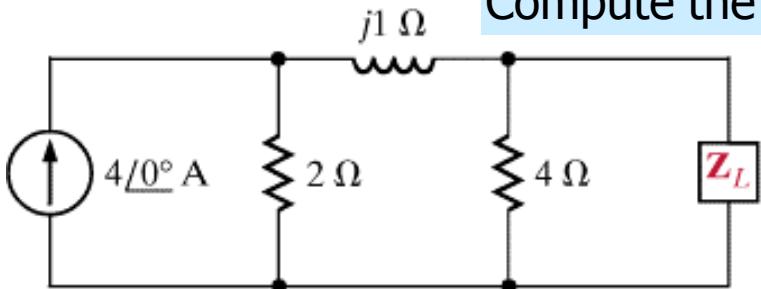
## LEARNING EXAMPLE

Find  $Z_L$  for maximum average power transfer.


Compute the maximum average power supplied to the load



$$\therefore Z_L^{opt} = Z_{TH}^*$$


$$P_L^{\max} = \frac{1}{2} \left( \frac{|V_{oc}|^2}{4R_{TH}} \right)$$

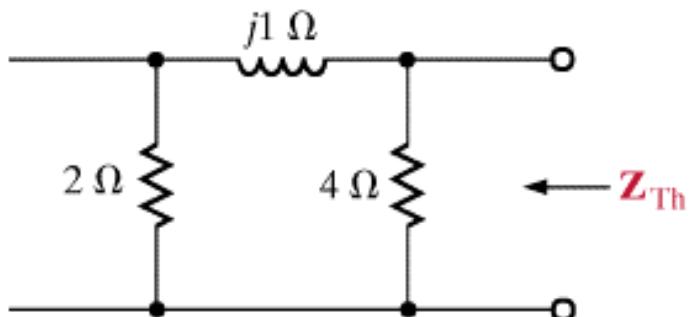Remove the load and determine the Thevenin equivalent of remaining circuit



$$\begin{aligned} Z_{TH} &= 4 \parallel (2 + j1) = \frac{8 + j4}{6 + j1} = \frac{(8 + j4)(6 - j1)}{37} = \frac{52 + j16}{37} \Omega \\ &= \frac{8 + j4}{6 + j1} = \frac{8.94 \angle 26.57^\circ}{6.08 \angle 9.64^\circ} = 1.47 \angle 16.93^\circ \Omega \end{aligned}$$
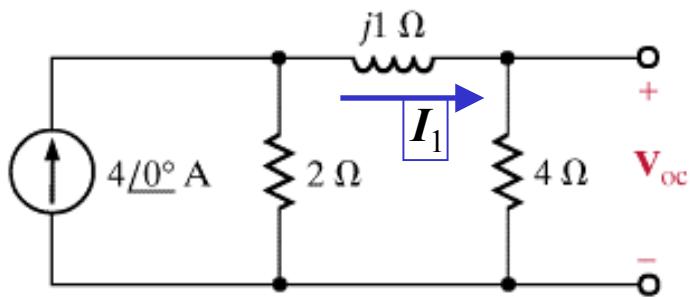
$$Z_L^* = 1.47 \angle -16.93^\circ = 1.41 - j0.43 \Omega$$



$$V_{oc} = 4 \times \frac{2}{2 + 4 + j1} 4 \angle 0^\circ = \frac{32 \angle 0^\circ}{6.08 \angle 9.64^\circ} = 5.26 \angle -9.64^\circ$$


$$P_L^{\max} = \frac{1}{2} \times \frac{5.26^2}{4 \times 1.41} = 2.45(W)$$

We are asked for the value of the power. We need the Thevenin voltage
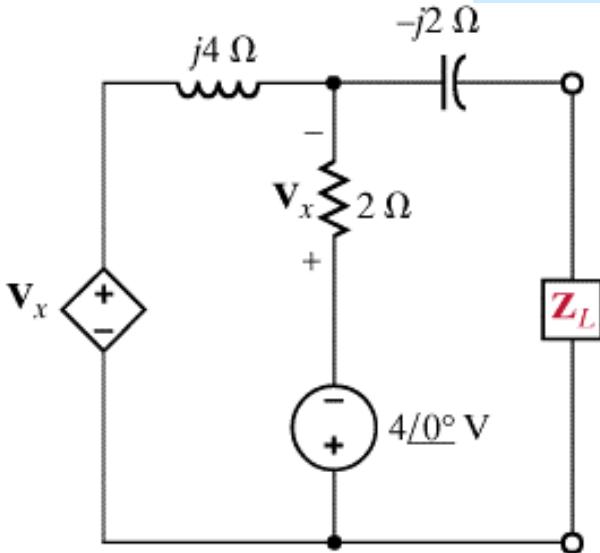
## LEARNING EXAMPLE

Find  $Z_L$  for maximum average power transfer.

Compute the maximum average power supplied to the load




$$\therefore Z_L^{opt} = Z_{TH}^*$$

$$P_L^{\max} = \frac{1}{2} \left( \frac{|V_{oc}|^2}{4R_{TH}} \right)$$

Circuit with dependent sources!

$$Z_{TH} = \frac{V_{oc}}{I_{sc}}$$

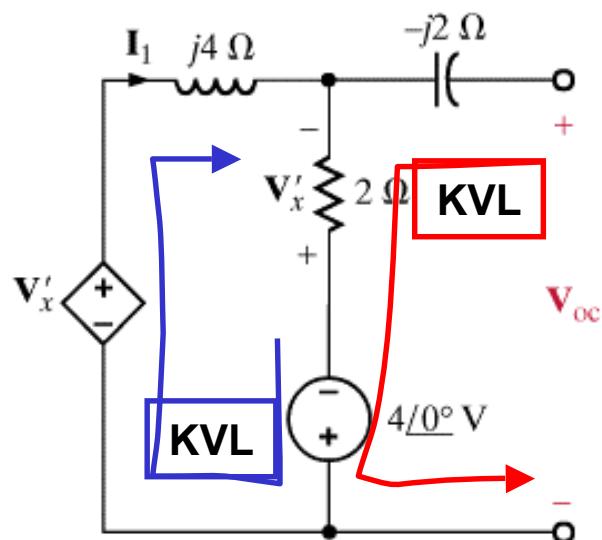

$$4\angle 0^\circ = -V'_x + (2 + j4)I_1$$

$$V'_x = -2I_1$$

$$4\angle 0^\circ = (4 + j4)I_1 = (4\sqrt{2}\angle 45^\circ)I_1$$



$$I_1 = \frac{4\angle 0^\circ}{4\sqrt{2}\angle 45^\circ} = 0.707\angle -45^\circ (A)$$

$$V_{oc} = 2I_1 - 4\angle 0^\circ = 1 - j1 - 4 = -3 - j1 = \sqrt{10}\angle -161.5^\circ$$

Next: the short circuit current ...

## LEARNING EXAMPLE (continued)...

### Original circuit

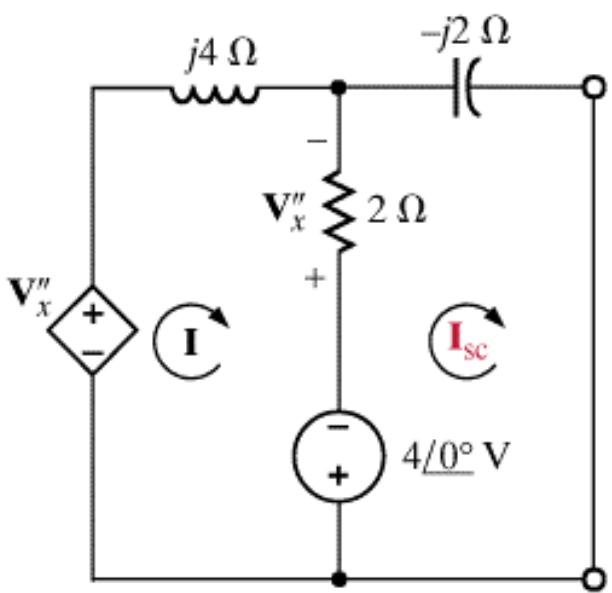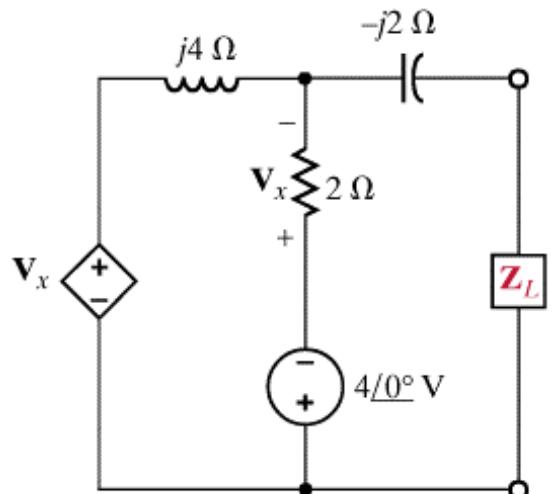

LOOP EQUATIONS FOR SHORT CIRCUIT CURRENT

$$-V_x'' + j4I + 2(I - I_{SC}) - 4\angle 0^\circ = 0$$

$$4\angle 0^\circ + 2(I_{SC} - I) - j2I_{SC} = 0$$

CONTROLLING VARIABLE

$$V_x'' = 2(I_{SC} - I)$$

Substitute and rearrange

$$(4 + j4)I - 4I_{SC} = 4$$

$$-2I + (2 - j2)I_{SC} = -4 \Rightarrow I = (1 - j1)I_{SC} + 2$$

$$4(1 + j)[(1 - j)I_{SC} + 2] - 4I_{SC} = 4$$

$$I_{SC} = -1 - j2(A) = \sqrt{5}\angle -116.57^\circ$$

$$V_{OC} = 2I_1 - 4\angle 0^\circ = 1 - j1 - 4 = -3 - j1 = \sqrt{10}\angle -161.57^\circ$$



$$Z_{TH} = \sqrt{2}\angle -45^\circ = 1 - j1 \Omega \Rightarrow Z_L^{opt} = 1 + j1 \Omega$$

$$P_L^{\max} = \frac{1}{2} \times \frac{(\sqrt{10})^2}{4} = 1.25(W)$$

$$\therefore Z_L^{opt} = Z_{TH}^*$$

$$P_L^{\max} = \frac{1}{2} \left( \frac{|V_{OC}|^2}{4R_{TH}} \right)$$

## LEARNING EXTENSION

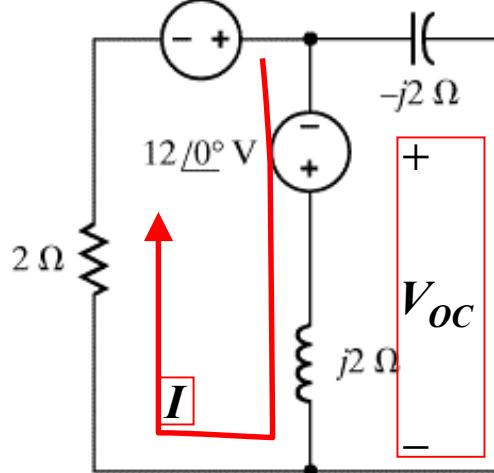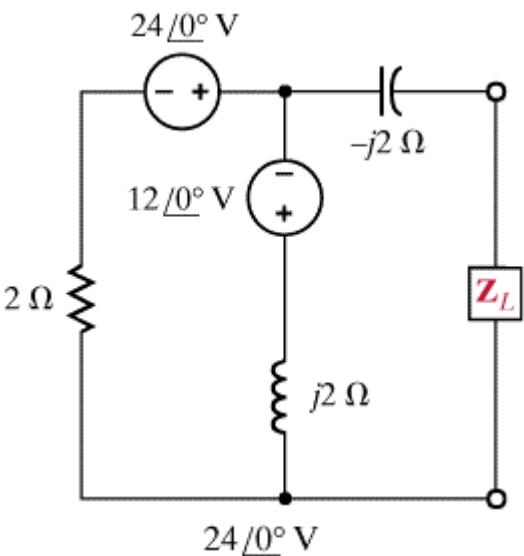


$$36\angle 0^\circ = (2 + j2)I$$

$$I = \frac{36(2 - j2)}{8} = 9(1 - j) = 12.73\angle -45^\circ$$

Find  $Z_L$  for maximum average power transfer.

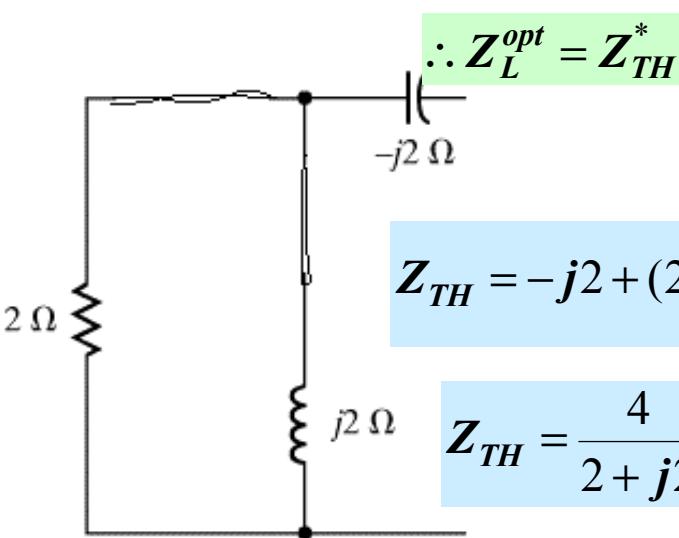Compute the maximum average power supplied to the load



$$\begin{aligned}V_{oc} &= -12\angle 0^\circ + j2I \\&= -12 + j2 \times 9(1 - j) \\&= 6 + j18\end{aligned}$$

$$V_{oc} = 18.974\angle 71.57^\circ(V)$$

$$|V_{oc}|^2 = 6^2 + 18^2 = 360$$

$$\therefore Z_L^{opt} = Z_{TH}^*$$

$$P_L^{\max} = \frac{1}{2} \left( \frac{|V_{oc}|^2}{4R_{TH}} \right)$$

$$Z_{TH} = -j2 + (2 \parallel j2) = -j2 + \frac{4j}{2 + j2} \Omega$$

$$Z_{TH} = \frac{4}{2 + j2} = \frac{8 - j8}{8} = 1 - j(\Omega)$$


$$Z_L^{opt} = 1 + j(\Omega)$$

$$P_L^{\max} = \frac{1}{2} \times \frac{360}{4} = 45(W)$$
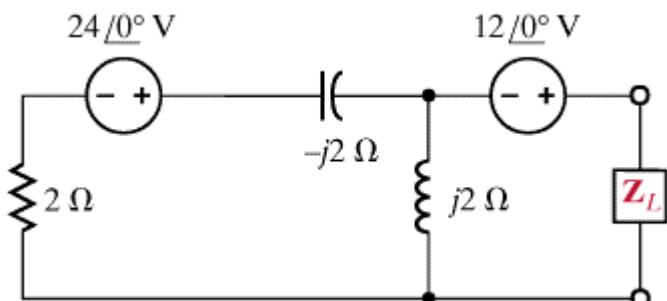
## LEARNING EXTENSION


Find  $Z_L$  for maximum average power transfer.

Compute the maximum average power supplied to the load



$$\therefore Z_L^{opt} = Z_{TH}^*$$

$$P_L^{\max} = \frac{1}{2} \left( \frac{|V_{oc}|^2}{4R_{TH}} \right)$$

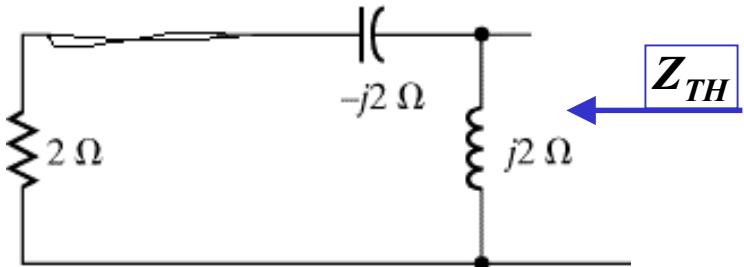


$$Z_{TH} = j2 \parallel (2 - j2) = \frac{j2(2 - j2)}{2 + j2 - j2}$$

$$Z_{TH} = 2 + j2(\Omega)$$

$$Z_L^{opt} = 2 - j2(\Omega)$$
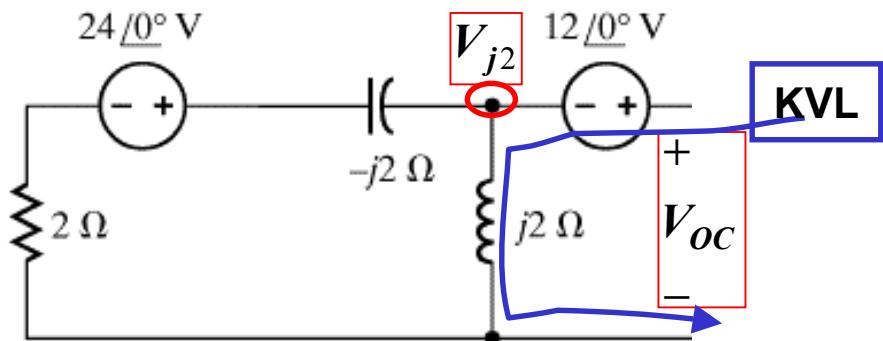
$$P_L^{\max} = \frac{1}{2} \times \frac{720}{4 \times 2} = 45(W)$$




$$V_{j2} = \frac{j2}{j2 - j2 + 2} 24\angle0^\circ = 24\angle90^\circ$$

$$V_{oc} = 12\angle0^\circ + 24\angle90^\circ = 12 + j24(V)$$

$$|V_{oc}|^2 = 12^2 + 24^2 = 720$$

# EFFECTIVE OR RMS VALUES

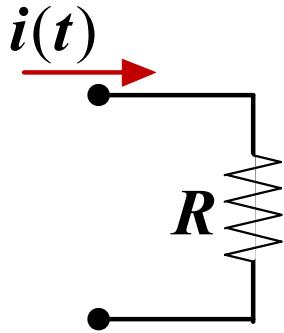

Instantaneous power

$$p(t) = i^2(t)R$$

If the current is sinusoidal the average power is known to be

$$P_{av} = \frac{1}{2} I_M^2 R$$

$$\therefore I_{eff}^2 = \frac{1}{2} I_M^2$$

For a sinusoidal signal

$x(t) = X_M \cos(\omega t + \theta)$   
the effective value is

$$X_{eff} = \frac{X_M}{\sqrt{2}}$$

The effective value is the equivalent DC value that supplies the same average power

If current is periodic with period  $T$

$$P_{av} = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt = R \left( \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt \right)$$

If current is DC ( $i(t) = I_{dc}$ ) then

$$P_{dc} = RI_{dc}^2$$

$$I_{eff}^2 = \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt$$

$$I_{eff} : P_{av} = P_{dc}$$

$$\text{For sinusoidal case } P_{av} = \frac{1}{2} V_M I_M \cos(\theta_v - \theta_i)$$


$$P_{av} = V_{eff} I_{eff} \cos(\theta_v - \theta_i)$$

effective  $\approx$  rms (root mean square)

Definition is valid for ANY periodic signal with period T

## LEARNING EXAMPLE
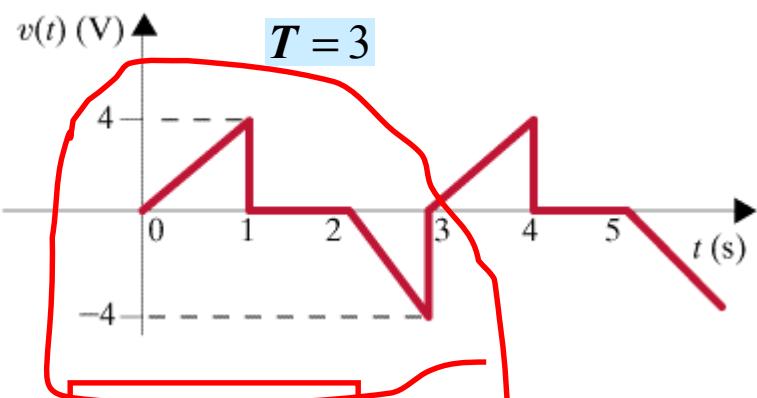
### Compute the rms value of the voltage waveform



$$X_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} x^2(t) dt}$$

$$v(t) = \begin{cases} 4t & 0 < t \leq 1 \\ 0 & 1 < t \leq 2 \\ -4(t-2) & 2 < t \leq 3 \end{cases}$$

The two integrals have the same value


$$\int_0^T v^2(t) dt = \int_0^1 (4t)^2 dt + \int_2^3 (4(t-2))^2 dt$$

$$\int_0^3 v^2(t) dt = 2 \times \left[ \frac{16}{3} t^3 \right]_0^1 = \frac{32}{3}$$

$$V_{rms} = \sqrt{\frac{1}{3} \times \frac{32}{3}} = 1.89(V)$$

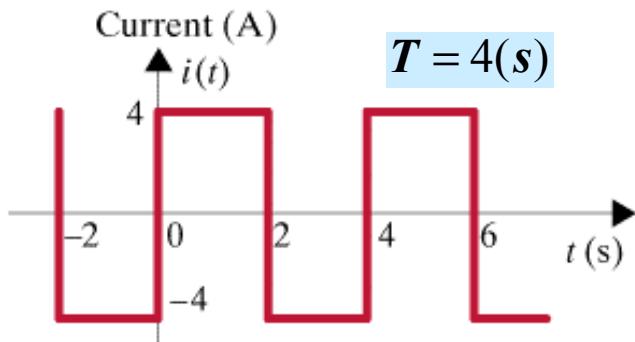
## LEARNING EXAMPLE

Compute the rms value of the voltage waveform and use it to determine the average power supplied to the resistor




$$i^2(t) = 16; \quad 0 \leq t < 4$$

$$I_{rms} = 4(A)$$

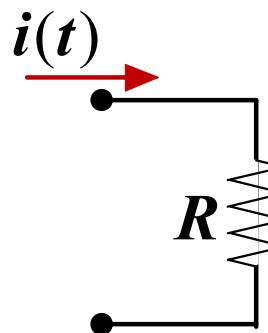

$$X_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} x^2(t) dt}$$

$$P_{av} = RI_{rms}^2 = 32(W)$$

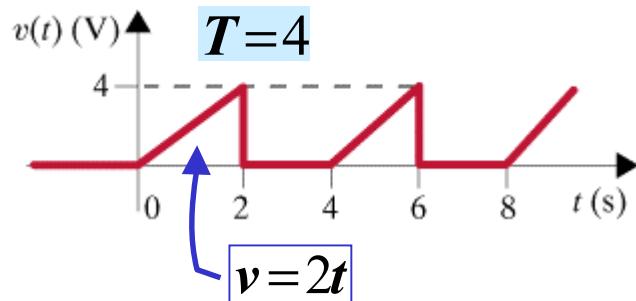


$$X_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} x^2(t) dt}$$


$$V_{rms} = \sqrt{\frac{1}{4} \int_0^2 (2t)^2 dt} = \sqrt{\left[ \frac{1}{3} t^3 \right]_0^2} = \sqrt{\frac{8}{3}} (V) = 1.633V$$
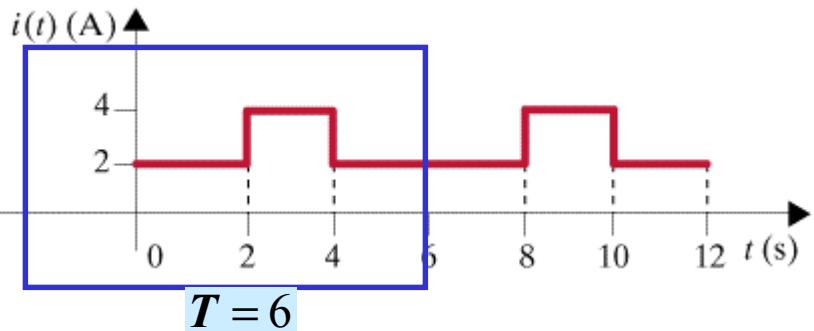
## LEARNING EXTENSION

Compute the rms value for the current waveforms and use them to determine average power supplied to the resistor



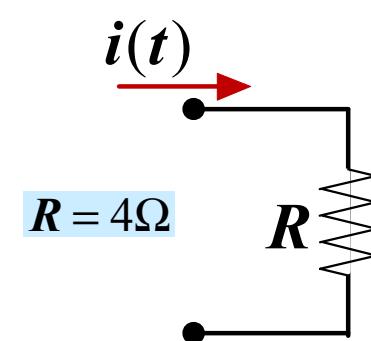
$$I_{rms}^2 = \frac{1}{6} \left[ \int_0^2 4 dt + \int_2^4 16 dt + \int_4^6 4 dt \right] = \frac{8+32+8}{6} = 8$$



$$X_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} x^2(t) dt}$$


$$P_{av} = I_{rms}^2 R$$

$$P = 8 \times 4 = 32(W)$$

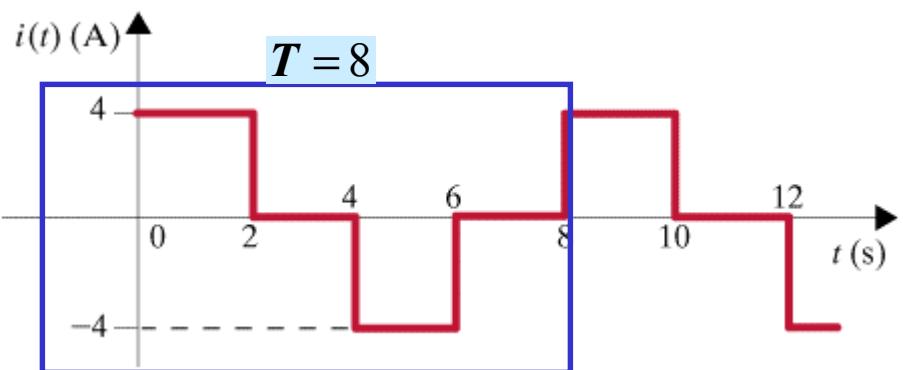


$$I_{rms}^2 = \frac{1}{8} \left[ \int_0^2 16 dt + \int_4^6 16 dt \right] = 8$$

# THE POWER FACTOR

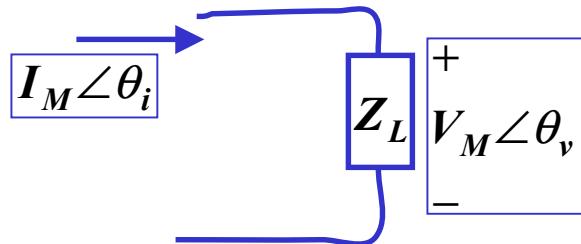

$$V = ZI \Rightarrow \angle V = \angle Z + \angle I$$

$$\theta_v = \theta_z + \theta_i$$

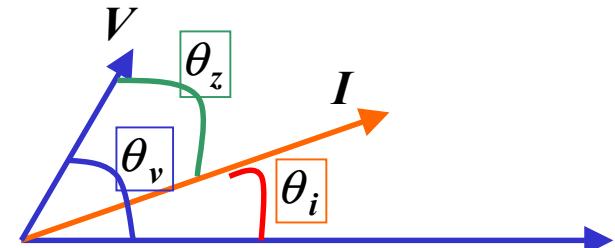


$$P = \frac{1}{2} V_M I_M \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$P_{\text{apparent}} = V_{rms} I_{rms}$$

$$pf = \frac{P}{P_{\text{apparent}}} = \cos(\theta_v - \theta_i) = \cos \theta_z$$


$$P = V_{rms} \times I_{rms} \times pf$$

$pf$	$\theta_z$	
0	-90°	pure capacitive
$0 < pf < 1$	$-90^\circ < \theta_z < 0^\circ$	leading or capacitive
1	0°	resistive
$0 < pf < 1$	$0^\circ < \theta_z < 90^\circ$	lagging or inductive
0	90°	pure inductive

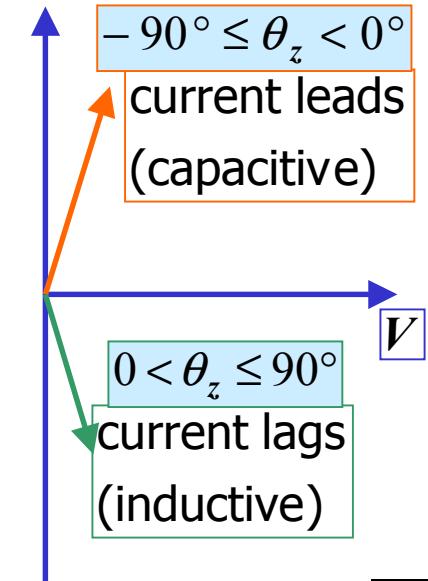
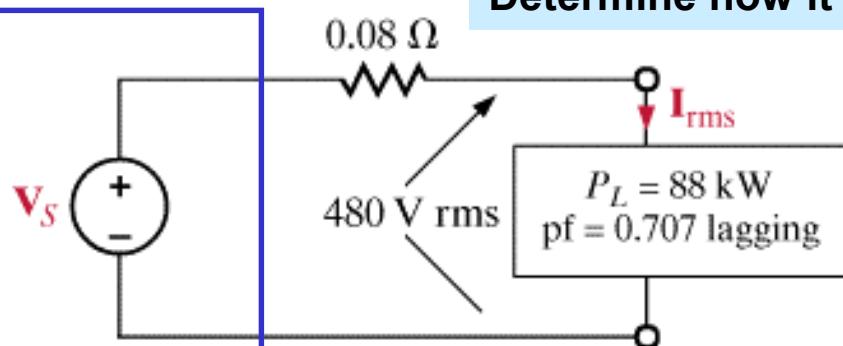
## LEARNING EXAMPLE

Find the power supplied by the power company.  
Determine how it changes if the power factor is changed to 0.9



**Power company**

$$I_{\text{rms}} = \frac{88 \times 10^3 (\text{W})}{480 \times 0.707} = 259.3 (\text{A}) \text{ rms}$$

$$P_{\text{losses}} = I_{\text{rms}}^2 R = 259.3^2 \times 0.08 = 5.378 \text{ kW}$$

$$P_S = P_{\text{losses}} + 88,000 (\text{W}) = 93.378 (\text{kW})$$

If  $\text{pf}=0.9$

$$I_{\text{rms}} = \frac{88,000}{480 \times 0.9} = 203.7 (\text{A}) \text{ rms}$$

$$P_{\text{losses}} = I_{\text{rms}}^2 R = 3.32 \text{ kW}$$

Losses can be reduced by 2kW!

Examine also the generated voltage

$$P = V_{\text{rms}} \times I_{\text{rms}} \times \text{pf}$$

$$\Rightarrow \cos \theta_z = 0.707 \Rightarrow \theta_z = -45^\circ$$

Current lags the voltage



$$\begin{aligned} V_{S_{\text{rms}}} &= 0.08 I_{\text{rms}} + V_L \\ &= 0.08 \times 259.3 \angle -45^\circ + 480 \end{aligned}$$

$$\begin{aligned} V_{S_{\text{rms}}} &= 0.08 \times (183.4 - j183.4) + 480 \\ &= 494.7 - j14.7 = 495 \angle -1.7^\circ (\text{V}) \end{aligned}$$

If  $\text{pf}=0.9$

$$I_{\text{rms}} = 203.7 \angle -25.8^\circ$$

$$V_S = 14.47 - j7.09 + 480 = 494 \angle -0.82^\circ$$

## LEARNING EXTENSION

$$P_L = 100kW, V_L = 480(V)rms, pf = 0.707$$

$$R_{line} = 0.1\Omega$$

$$P = V_{rms} \times I_{rms} \times pf$$

Determine the power savings if the power factor can be increased to 0.94

$$I_{rms} = \frac{P}{V_{rms} \times pf}$$

$$P_{losses} = I_{rms}^2 R_{line} = \frac{P^2 R_{line}}{V_{rms}^2} \times \frac{1}{pf^2}$$


$$P_{losses}(pf = 0.707) = \frac{10^{10} \times 0.1}{480^2} \times \frac{1}{0.707^2} (W)$$

$$= 2 \times 4.34kW$$

$$P_{losses}(pf = 0.94) = \frac{10^{10} \times 0.1}{480^2} \times \frac{1}{0.94^2} (W)$$

$$= 1.13 \times 4.34kW$$
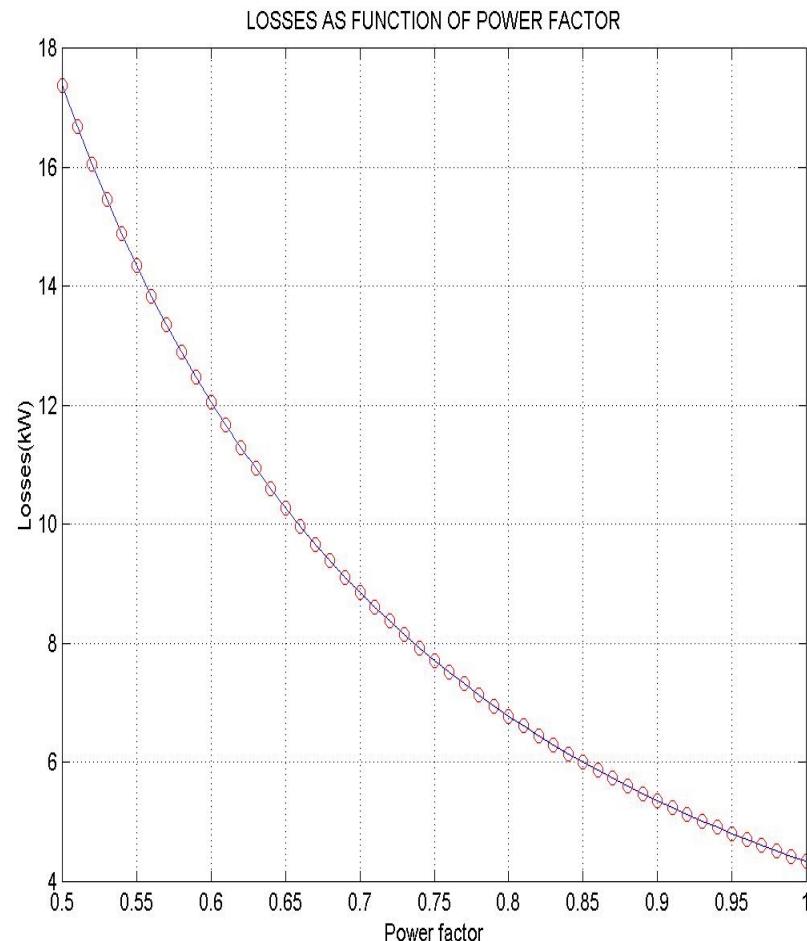
$$P_{saved} = 0.87 \times 4.34kW = 3.77kW$$




## Definition of Complex Power

$$S = V_{rms} I_{rms}^*$$
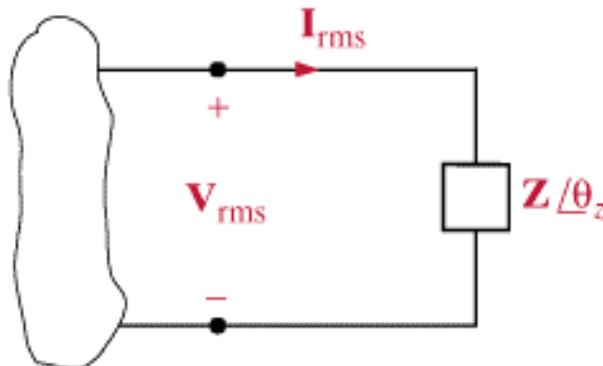
# COMPLEX POWER

The units of apparent and reactive power are Volt-Ampere



$$S = V_{rms} \angle \theta_v^\circ \times [I_{rms} \angle \theta_i^\circ]^*$$

$$S = V_{rms} I_{rms} \angle \theta_v - \theta_i$$



$$S = V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

**P**

**Active Power**

**Q**


**Reactive Power**

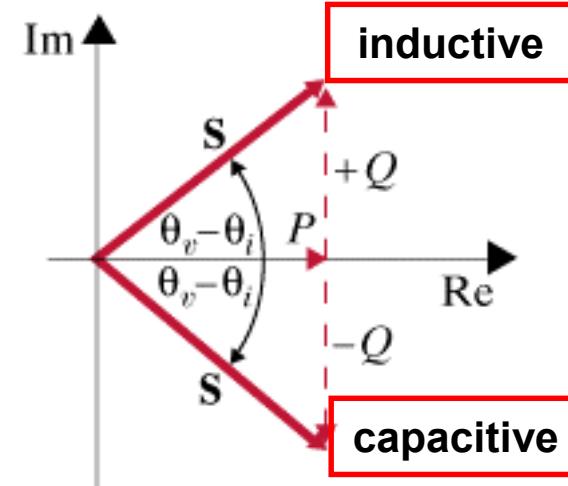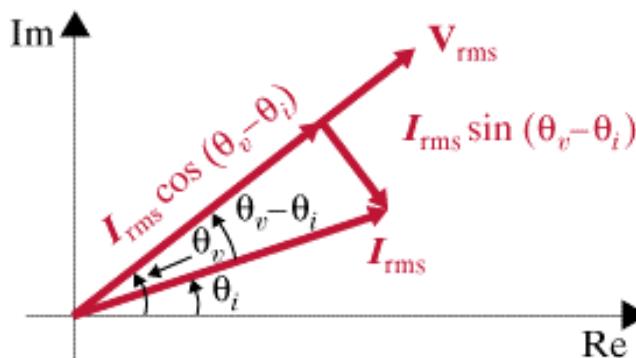

**Another useful form**

$$V_{rms} = Z I_{rms} \Rightarrow S = (Z I_{rms}) I_{rms}^* = Z |I_{rms}|^2$$

$$Z = R + jX \Rightarrow \begin{cases} P = R |I_{rms}|^2 \\ Q = X |I_{rms}|^2 \end{cases}$$

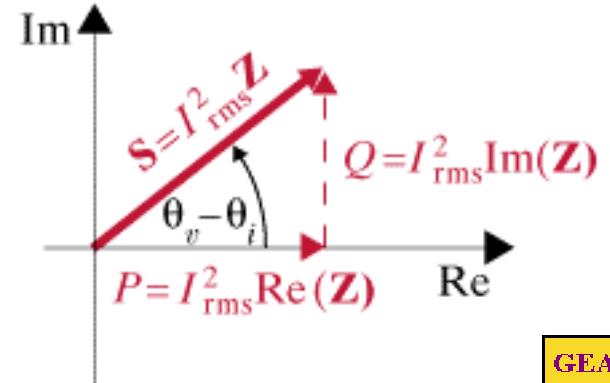


## LEARNING EXAMPLE

Given :

$$P_L = 20kW, pf = 0.8 \text{ lagging}, V_L = 220\angle 0^\circ \text{ rms}, Z_L = 0.09 + j0.3\Omega, f = 60\text{Hz}$$

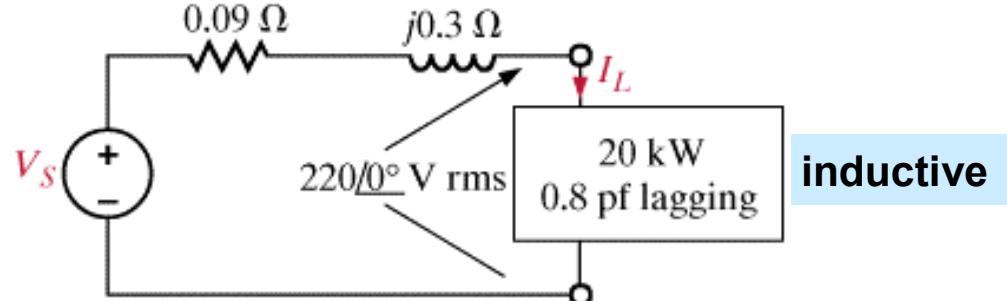Determine the voltage and power factor at the input to the line



$$P = \text{Re}\{S\} = |S| \cos(\theta_v - \theta_i) = |S| \times pf$$

$$\therefore |S_L| = \frac{P}{pf} = 25kVA$$

$$Q^2 = |S_L|^2 - P^2 \Rightarrow Q = 15kVA \quad S_L = 20 + j15(kVA) = 25\angle 36.87^\circ$$


$$S_L = V_L I_L^*$$

$$\Rightarrow I_L = \left[ \frac{S_L}{V_L} \right]^* = \left[ \frac{25,000\angle 36.87^\circ}{220\angle 0^\circ} \right]^* = 113.64\angle -36.86^\circ (A)$$


$$I_L = \left[ \frac{20,000 + j15,000}{220} \right]^* = 90.91 - j68.18(A)$$

$$V_s = (0.09 + j0.3)I_L + 220\angle 0^\circ$$
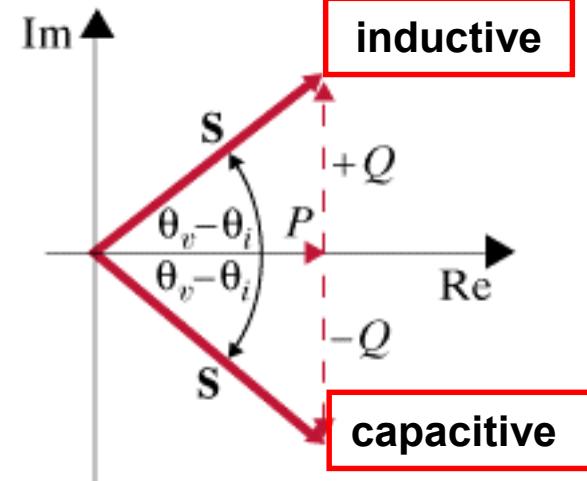
$$V_s = (0.09 + j0.3)(90.91 - j68.18) + 220(V)$$


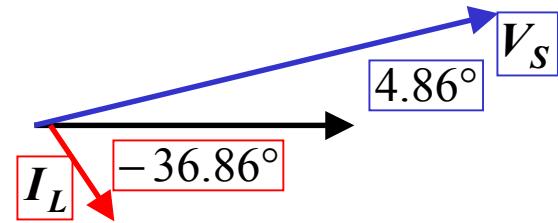
$$V_s = 248.63 + j21.14 = 249.53\angle 4.86^\circ$$




$$pf_{\text{source}} = \cos(41.72^\circ) = 0.746$$

lagging

GEAUX
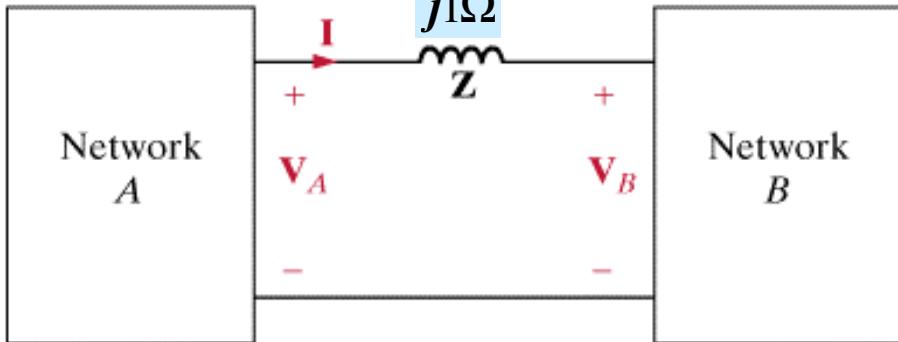
## LEARNING EXAMPLE

Compute the average power flow between networks  
Determine which is the source



$$V_A = 120 \angle 30^\circ (V) rms$$

$$V_B = 120 \angle 0^\circ (V) rms$$

$$I = \frac{V_A - V_B}{Z} = \frac{120 \angle 30^\circ - 120 \angle 0^\circ}{j1}$$

$$I = \frac{(103.92 + j60) - 120}{j} = 60 + j16.08 (A) rms$$

$$I = 62.12 \angle 15^\circ (A) rms$$

$$S_A = V_A(-I)^* = 120 \angle 30^\circ \times 62.12 \angle -195^\circ = 7,454 \angle -165^\circ VA_{rms}$$

$$P_A = 7,454 \cos(165^\circ) = -7,200 (W)$$

$$S_B = V_B(I)^* = 120 \angle 0^\circ \times 62.12 \angle -15^\circ = 7,454 \angle -15^\circ VA_{rms}$$


$$P_B = 7,454 \cos(-15^\circ) = 7,200 (W)$$

Passive sign convention.  
Power received by A

A supplies 7.2kW average power to B
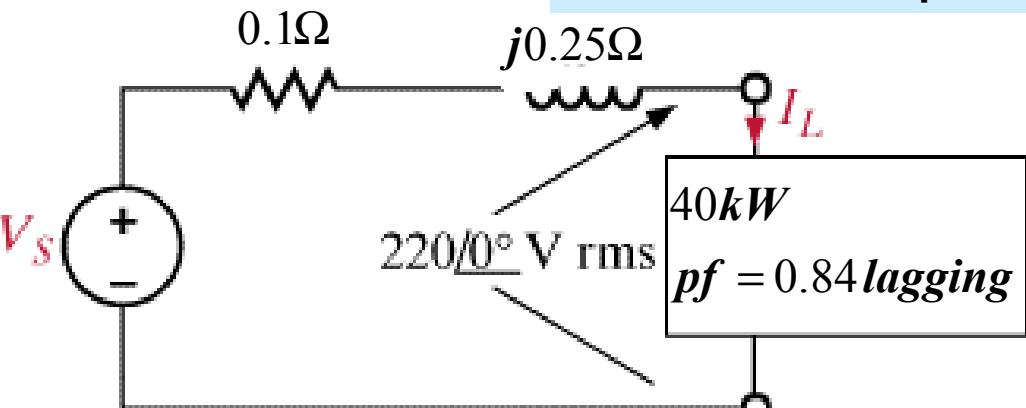
## LEARNING EXTENSION

Determine real and reactive power losses and real and reactive power supplied



$$P = \text{Re}\{S\} = |S| \cos(\theta_v - \theta_i) = |S| \times pf$$

$$|S_L| = \frac{P}{pf} = \frac{40}{0.84} = 47.62 \text{ kVA}$$



$$|Q_L| = \sqrt{|S_L|^2 - P^2} = 25,839 (\text{VA})$$

$$S = VI^* \Rightarrow |I_L| = \frac{|S_L|}{|V_L|} = 216.45 (\text{A})_{\text{rms}}$$

$$pf = \cos(\theta_v - \theta_i) \Rightarrow \theta_v - \theta_i = 32.86^\circ$$

$$S_{\text{losses}} = (Z_{\text{line}} I_L) I_L^* = Z_{\text{line}} |I_L|^2$$

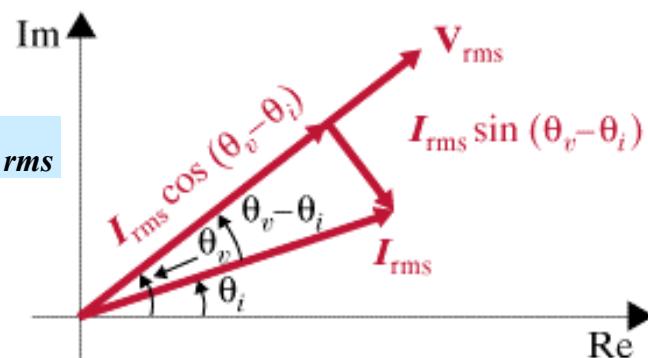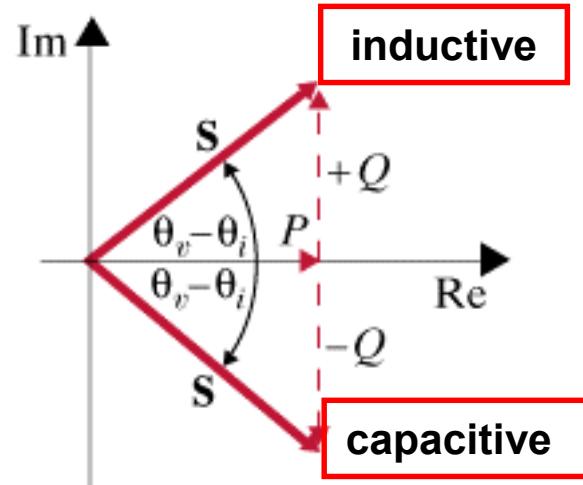
$$S_{\text{losses}} = (0.1 + j0.25)(216.45)^2 = 4,685 + j11,713 \text{ VA}$$


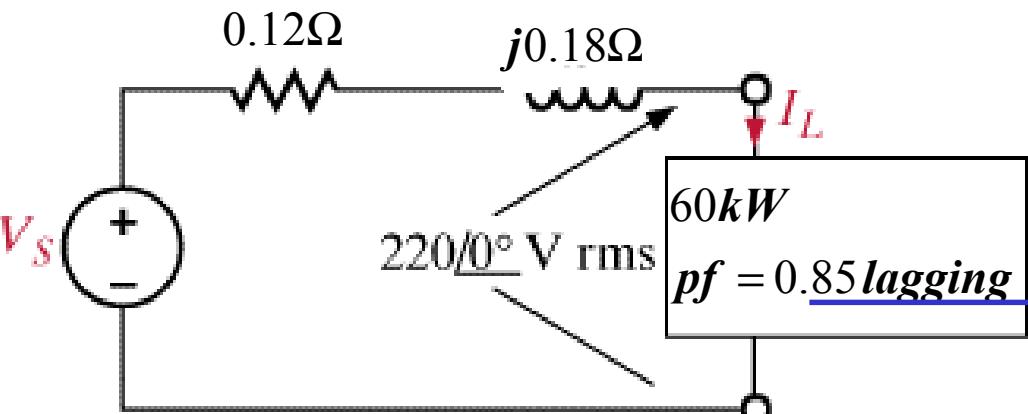
## Balance of power

$$S_{\text{supplied}} = S_{\text{losses}} + S_{\text{load}}$$

$$= 4.685 + j11.713 + 40 + j25.839 = 44.685 + j37.552 \text{ kVA}$$



$$P = \operatorname{Re}\{S\} = |S| \cos(\theta_v - \theta_i) = |V_L| \times |I_L| \times \text{pf}$$

$$S_L = V_L I_L^*$$

$$|I_L| = \frac{P}{|V_L| \times \text{pf}} = 320.86(A)_{\text{rms}}$$



$$\theta_v - \theta_i = \cos^{-1}(\text{pf}) \Rightarrow \theta_v - \theta_i = 31.79^\circ$$

$$I_L = 320.86 \angle -31.79^\circ(A)_{\text{rms}} = 272.72 - j169.03(A)_{\text{rms}}$$

$$V_S = Z_{\text{line}} I_L + V_L = (0.12 + j0.18)(272.72 - j169.03) + 220$$

$$V_S = 283.15 + j28.81(V)_{\text{rms}} = 284.61 \angle 5.81^\circ(V)_{\text{rms}}$$

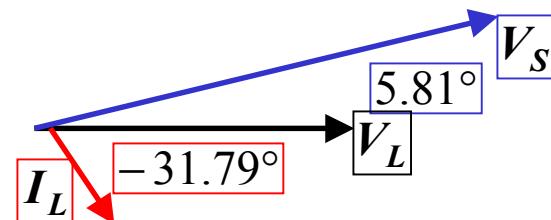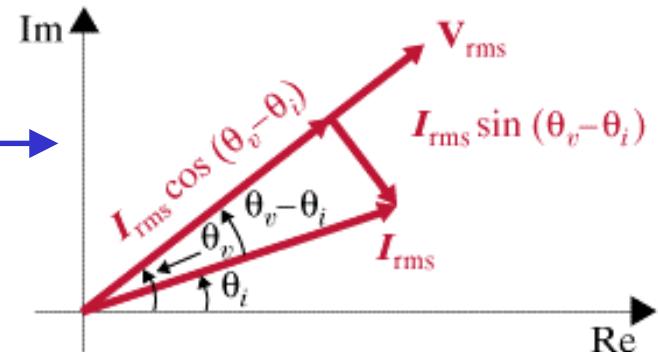The phasor diagram helps in visualizing the relationship between voltage and current




$$\text{pf}_{\text{source}} = \cos(37.6^\circ) = 0.792$$


lagging
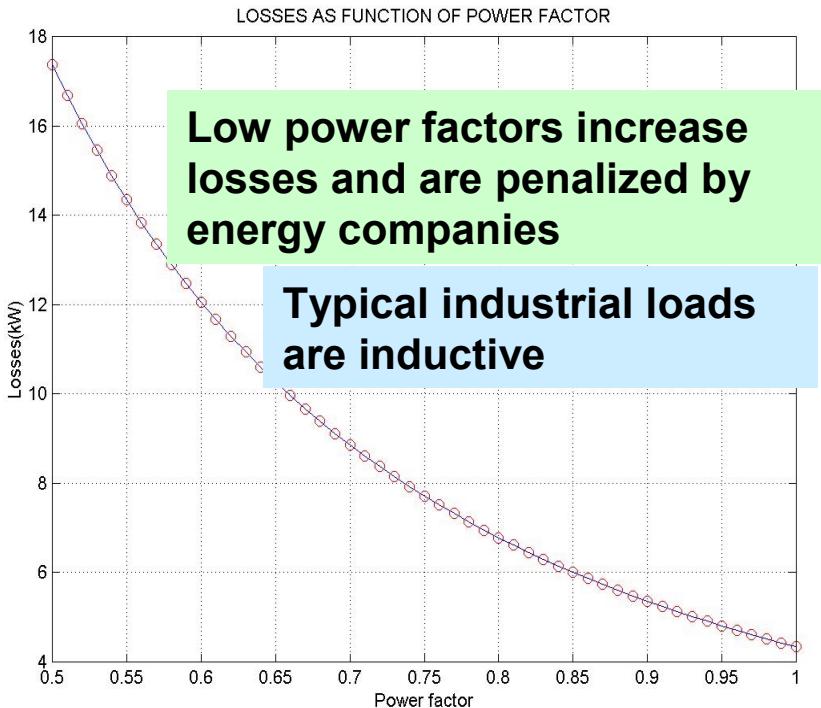
# POWER FACTOR CORRECTION

$$V_L = \frac{1}{j\omega C} I_{\text{capacitor}}$$



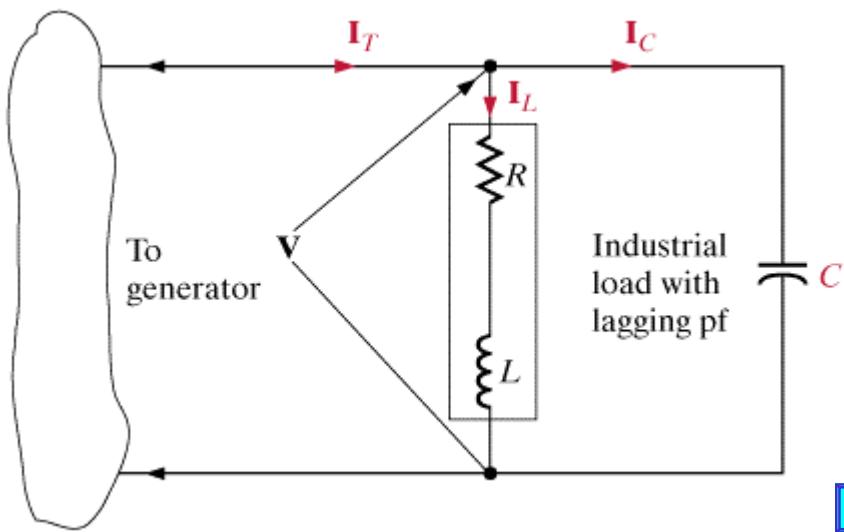Simple approach to power factor correction



Without capacitor :

$$S_{\text{old}} = P_{\text{old}} + jQ_{\text{old}} = |S_{\text{old}}| \angle \theta_{\text{old}}$$

$$pf_{\text{old}} = \cos(\theta_{\text{old}})$$

With capacitor

$$S_{\text{new}} = S_{\text{old}} + S_{\text{capacitor}}$$

$$= P_{\text{old}} + jQ_{\text{old}} - jQ_{\text{capacitor}}$$


$$= |S_{\text{new}}| \angle \theta_{\text{new}}$$

$$pf_{\text{new}} = \cos(\theta_{\text{new}})$$

$$\begin{aligned} Q_{\text{capacitor}} &= |V_L \parallel I_{\text{capacitor}}| \\ &= |V_L|^2 \omega C \end{aligned}$$

$$\tan \theta_{\text{new}} = \frac{Q_{\text{old}} - Q_{\text{capacitor}}}{P_{\text{old}}}$$

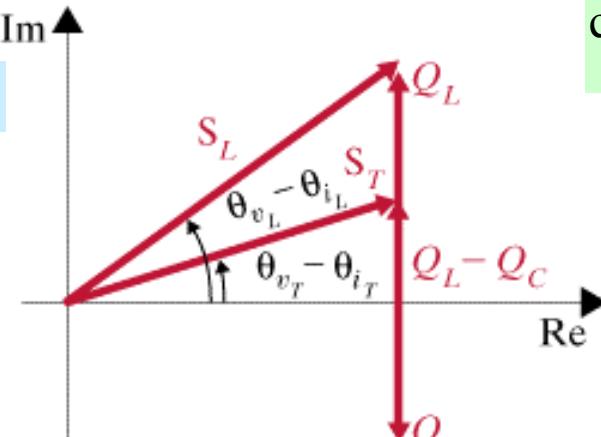
$$\cos \theta = \frac{1}{\sqrt{1 + \tan^2 \theta}}$$


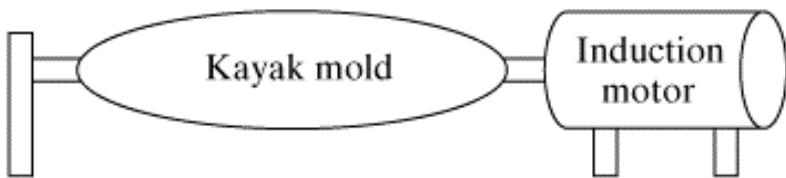
## LEARNING EXAMPLE

$$f = 60 \text{ Hz.}$$

Determine the capacitor required to increase the power factor to 0.95 lagging



**Roto-molding  
process**

$$50kW, V_L = 220\angle 0^\circ \text{ rms}$$

$$pf = 0.8 \text{ lagging}$$

$$P = \text{Re}\{S\} = |S| \cos(\theta_v - \theta_i) = |S| \times pf$$

$$|S_{old}| = \frac{P}{pf} = \frac{50}{0.8} = 62.5 \text{ kVA}$$

$$|Q_{old}| = \sqrt{|S_{old}|^2 - P^2} = 37.5 \text{ (kVA)}.$$

$$\cos \theta_{new} = 0.95 \Rightarrow \tan \theta_{new} = \frac{\sqrt{1 - pf_{new}^2}}{pf_{new}} = 0.329 = \frac{Q_{new}}{P} \Rightarrow Q_{new} = 0.329 \times P = 16.43 \text{ kVA}$$

$$\therefore Q_{capacitor} = Q_{old} - Q_{new} = 37.5 - 16.43 = 21.07 \text{ kVA}$$

$$Q_{capacitor} = |V_L| |I_{capacitor}|$$

$$= |V_L|^2 \omega C$$

$$\therefore C = \frac{Q_{capacitor}}{\omega |V_L|^2} = \frac{21.07 \times 10^3}{(220)^2 \times (2\pi \times 60)} = 0.001156(F) = 1156 \mu F$$

## LEARNING EXTENSION

Determine the capacitor necessary to increase the power factor to 0.94

$$P_L = 100kW, V_L = 480(V)_{rms}, pf = 0.707$$

$$R_{line} = 0.1\Omega, f = 60Hz$$

$$P = \text{Re}\{S\} = |S| \cos(\theta_v - \theta_i) = |S| \times pf$$

$$|S_{old}| = \frac{P}{pf} = \frac{100}{0.707} = 141.44kVA \quad |Q_{old}| = \sqrt{|S_{old}|^2 - P^2} = 100.02(kVA).$$

$$\cos \theta_{new} = 0.94 \Rightarrow \tan \theta_{new} = \frac{\sqrt{1 - pf_{new}^2}}{pf_{new}} = 0.363 \quad = \frac{Q_{new}}{P} \Rightarrow Q_{new} = 0.363 \times P = 36.3kVA$$


$$\therefore Q_{capacitor} = Q_{old} - Q_{new} = 100.02 - 36.3 = 63.72kVA$$

$$Q_{capacitor} = |V_L \parallel I_{capacitor}| \\ = |V_L|^2 \omega C$$

$$\therefore C = \frac{Q_{capacitor}}{\omega |V_L|^2} = \frac{63.72 \times 10^3}{(480)^2 \times (2\pi \times 60)} = 0.000733(F) = 733\mu F$$
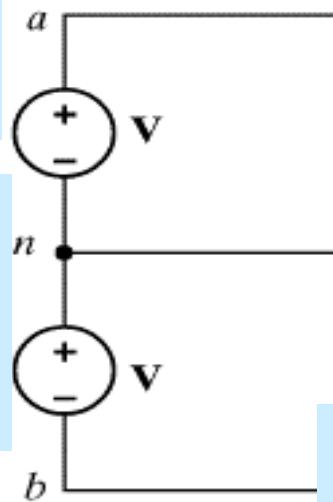
# SINGLE-PHASE THREE-WIRE CIRCUITS


Power circuit normally used for residential supply



Line-to-line used to supply major appliances (AC, dryer). Line-to-neutral for lights and small appliances

General balanced case




An exercise in symmetry

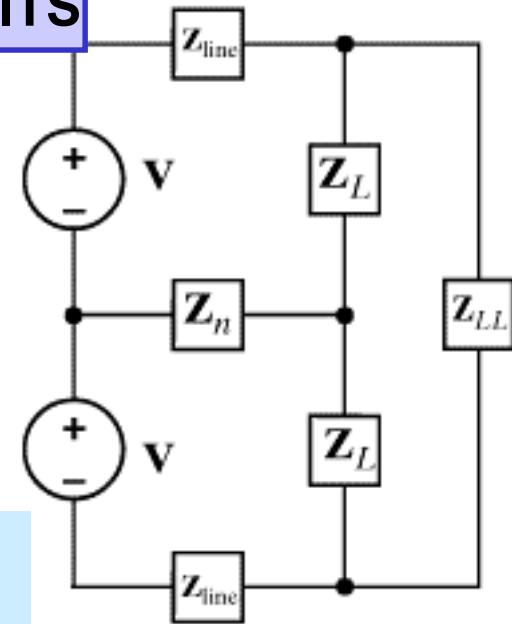

General case by source superposition

Basic circuit.

Neutral current is zero

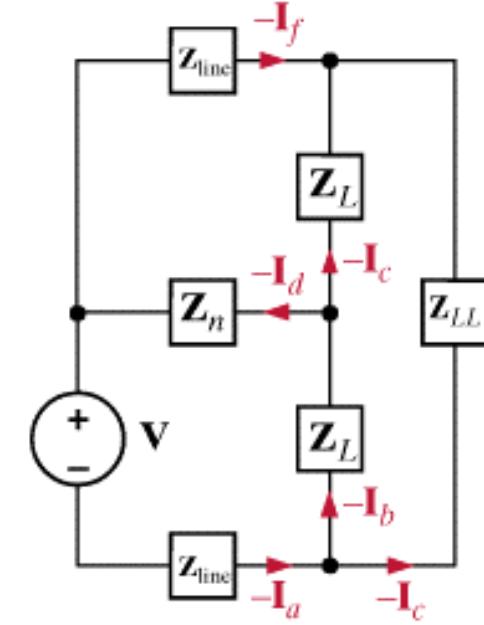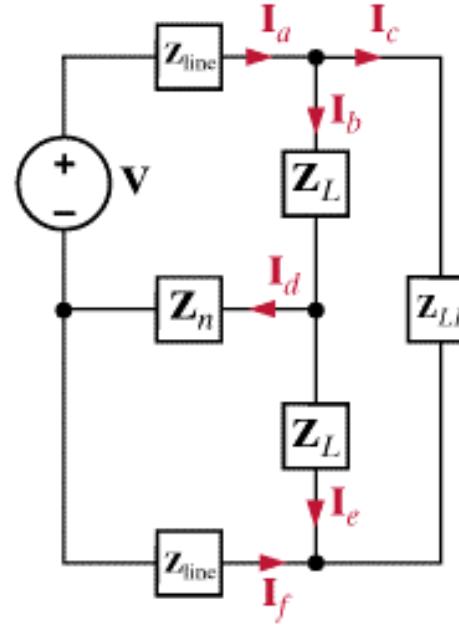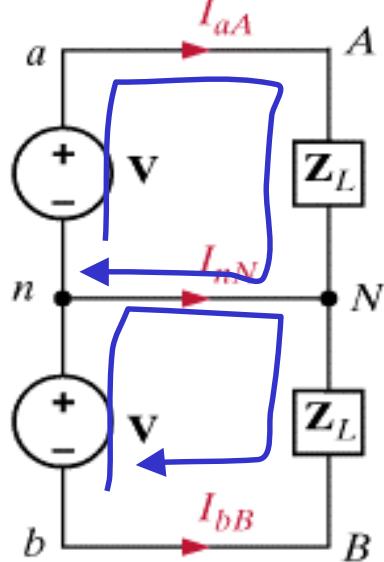


Neutral current is zero

## LEARNING EXAMPLE

Determine energy use over a 24-hour period and the cost if the rate is \$0.08/kWh

Assume all resistive

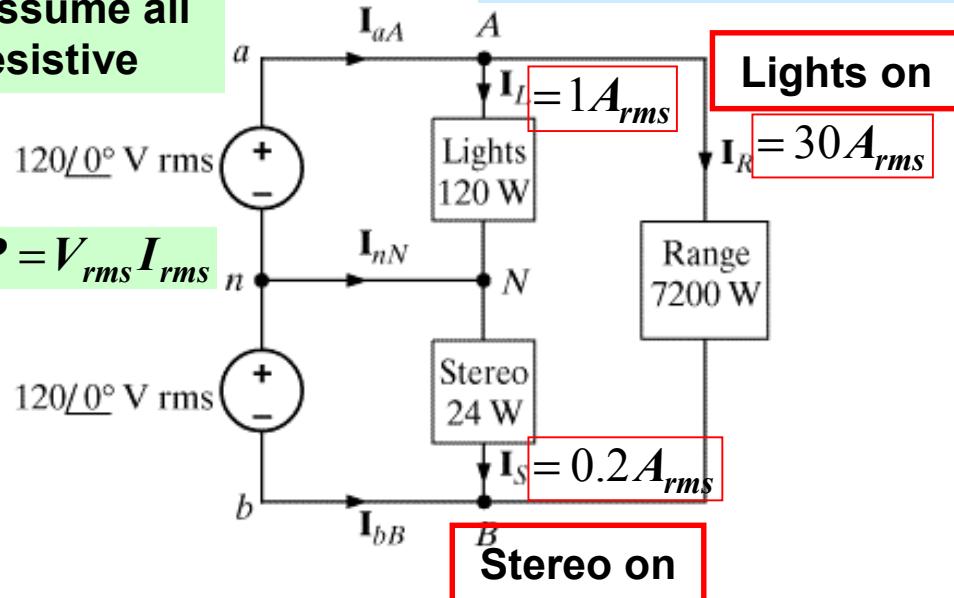

$$\text{Energy} = \int p(t)dt = P_{average} \times \text{Time}$$


$$E_{lights} = 0.12kW \times 8\text{Hr} + 0.12kW \times 7\text{Hr} = 1.8kWh$$

$$E_{range} = 7.2kW \times (2+1+1)\text{Hr} = 28.8kWh$$

$$E_{stereo} = 0.024kW \times (5+3)\text{Hr} = 0.192kWh$$

$$E_{daily} = 30.792kWh$$

$$\text{Cost} = \$2.46/\text{day}$$

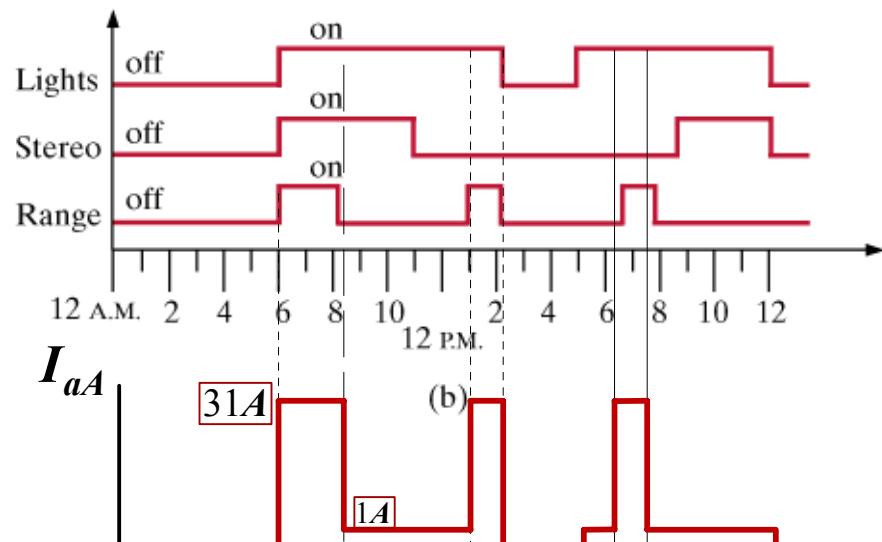

KCL

$$I_{aA} = I_L + I_R$$

$$I_{bB} = -I_S - I_R$$

$$I_{nN} = I_S - I_L$$


Outline of verification

$$E_{\text{supplied}} = \int p_{\text{supplied}} = V_{rms} \int I_{rms} dt$$
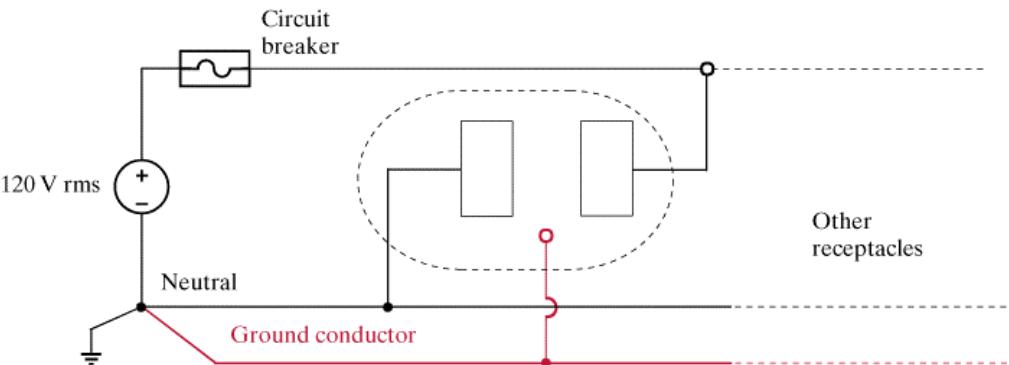
# SAFETY CONSIDERATIONS


Average effect of 60Hz current from hand to hand and passing the heart

Required voltage depends on contact, person and other factors




Typical residential circuit with ground and neutral

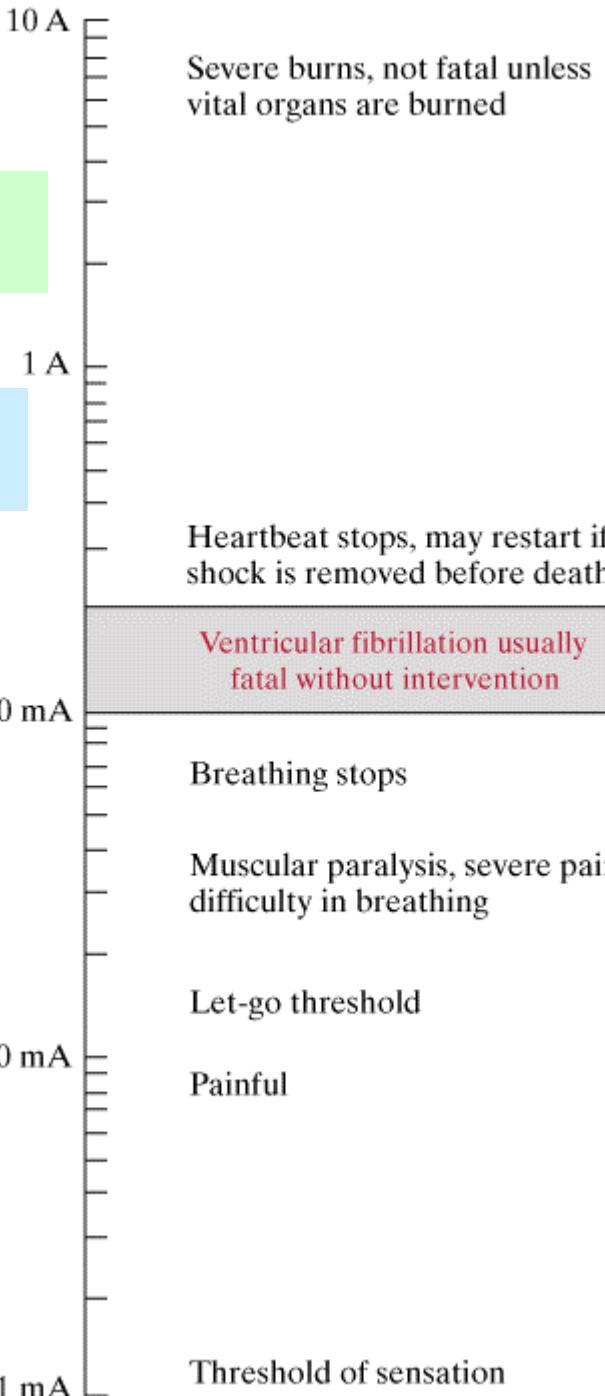Ground conductor is not needed for normal operation



## LEARNING EXAMPLE


### Increased safety due to grounding

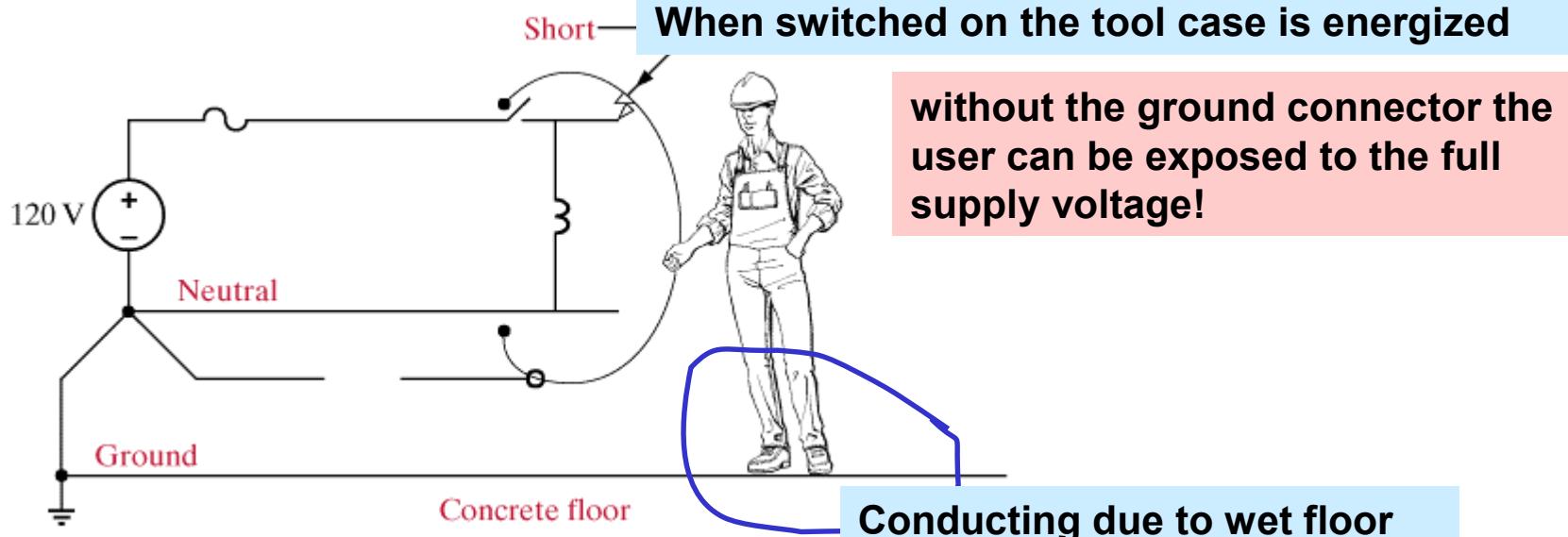

If case is grounded then the supply is shorted and the fuse acts to open the circuit

More detailed numbers in a related case study

## LEARNING EXAMPLE

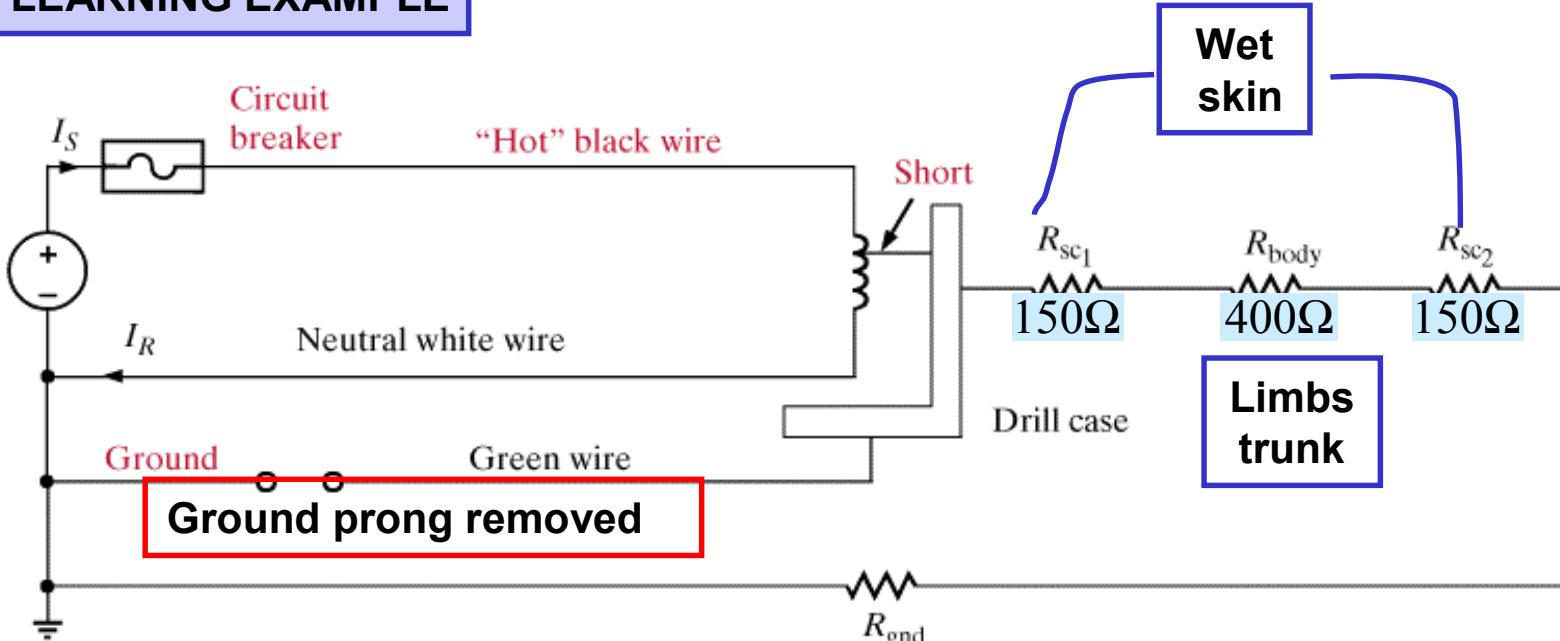


$R(\text{dry skin})$	15kOhm
$R(\text{wet skin})$	150Ohm
$R(\text{limb})$	100Ohm
$R(\text{trunk})$	200Ohm

Suggested resistances  
for human body

$$I_{body} = \frac{120}{701} = 171mA$$

Can cause ventricular fibrillation

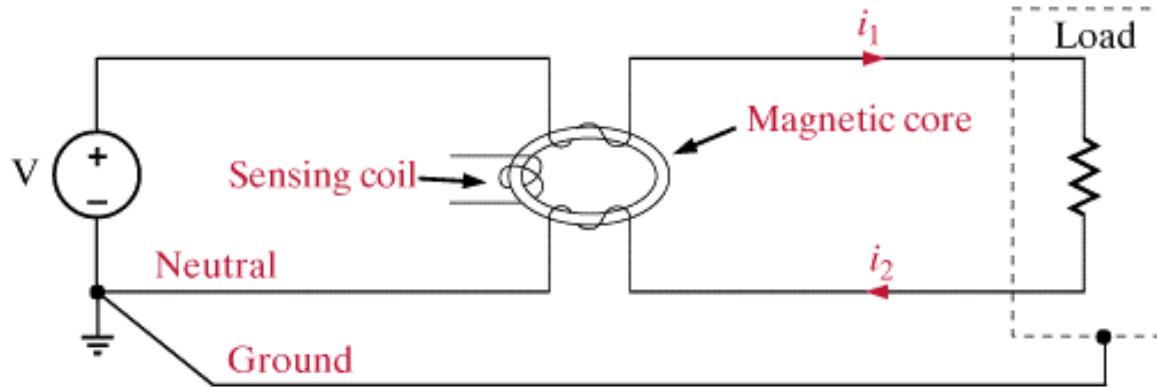

In normal operating mode the two currents induce canceling magnetic fluxes



No voltage is induced in the sensing coil

If  $i_1$  and  $i_2$  become different (e.g., due to a fault)  
then there is a voltage induced in the sensing coil

## LEARNING EXAMPLE



### A ground fault scenario

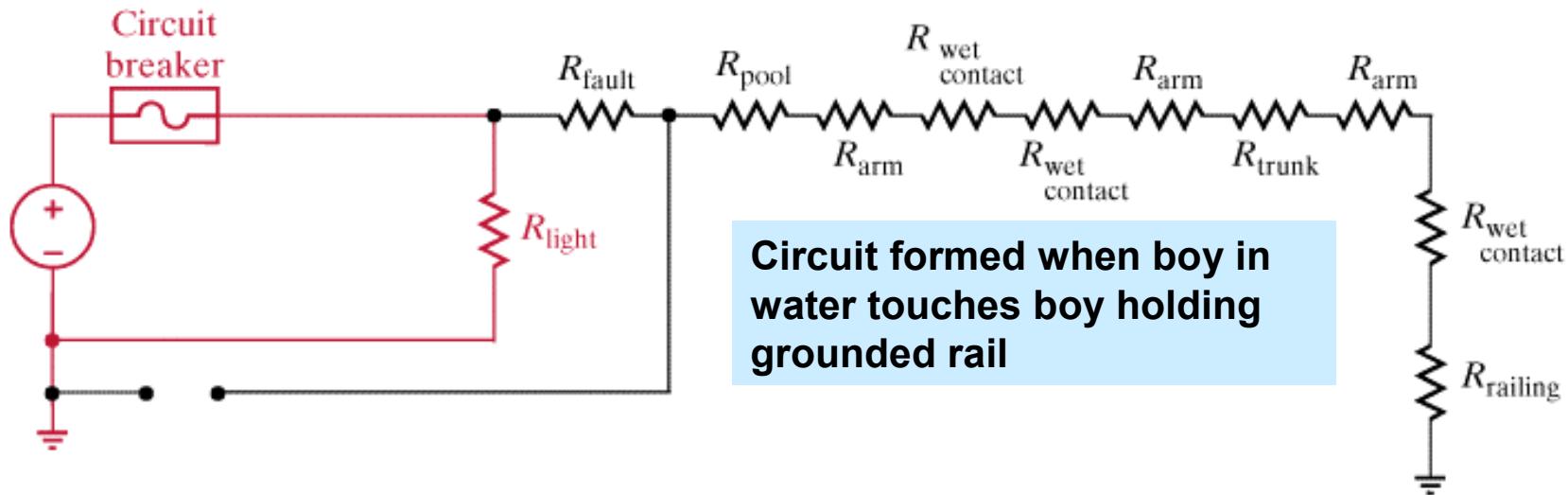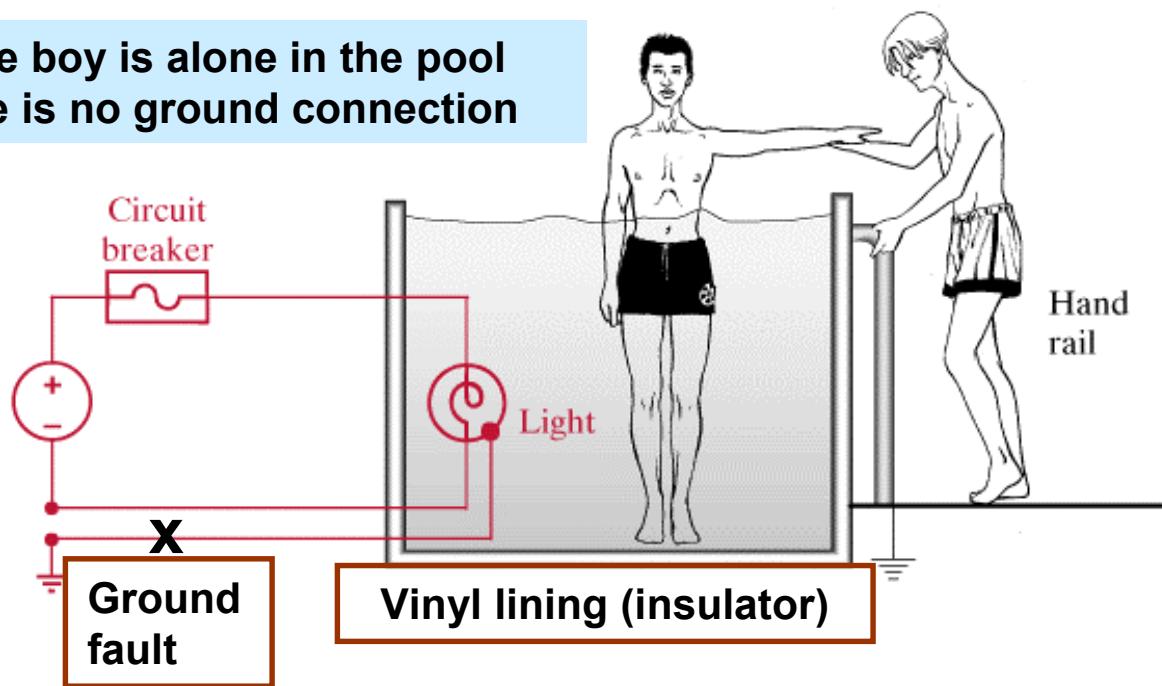**While boy is alone in the pool there is no ground connection**



## LEARNING EXAMPLE

### Accidental grounding

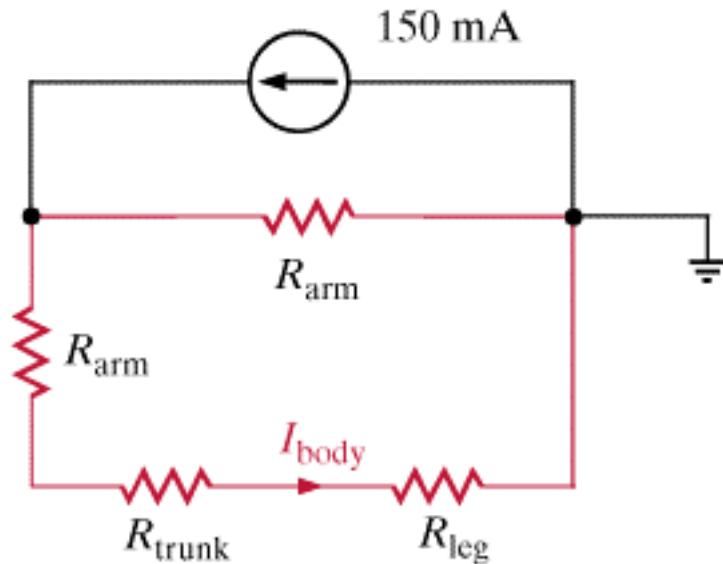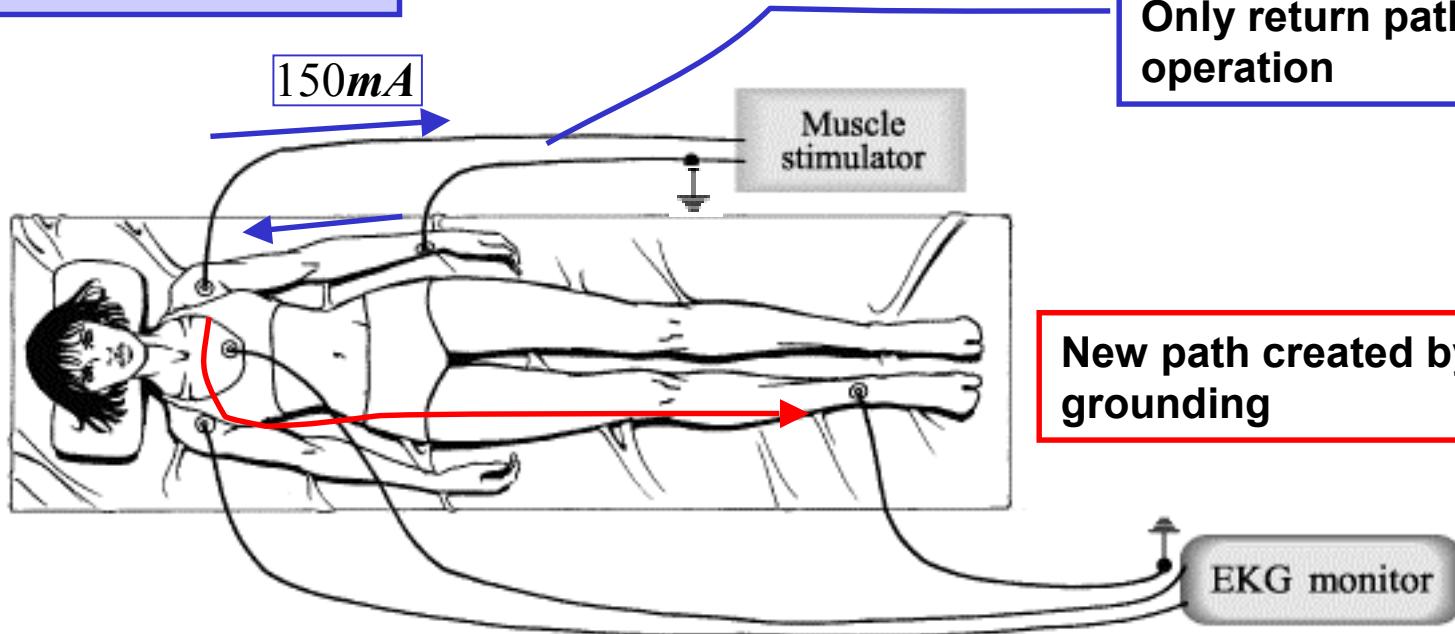


Using suggested values of resistance the secondary path causes a dangerous current to flow through the body

## LEARNING EXAMPLE
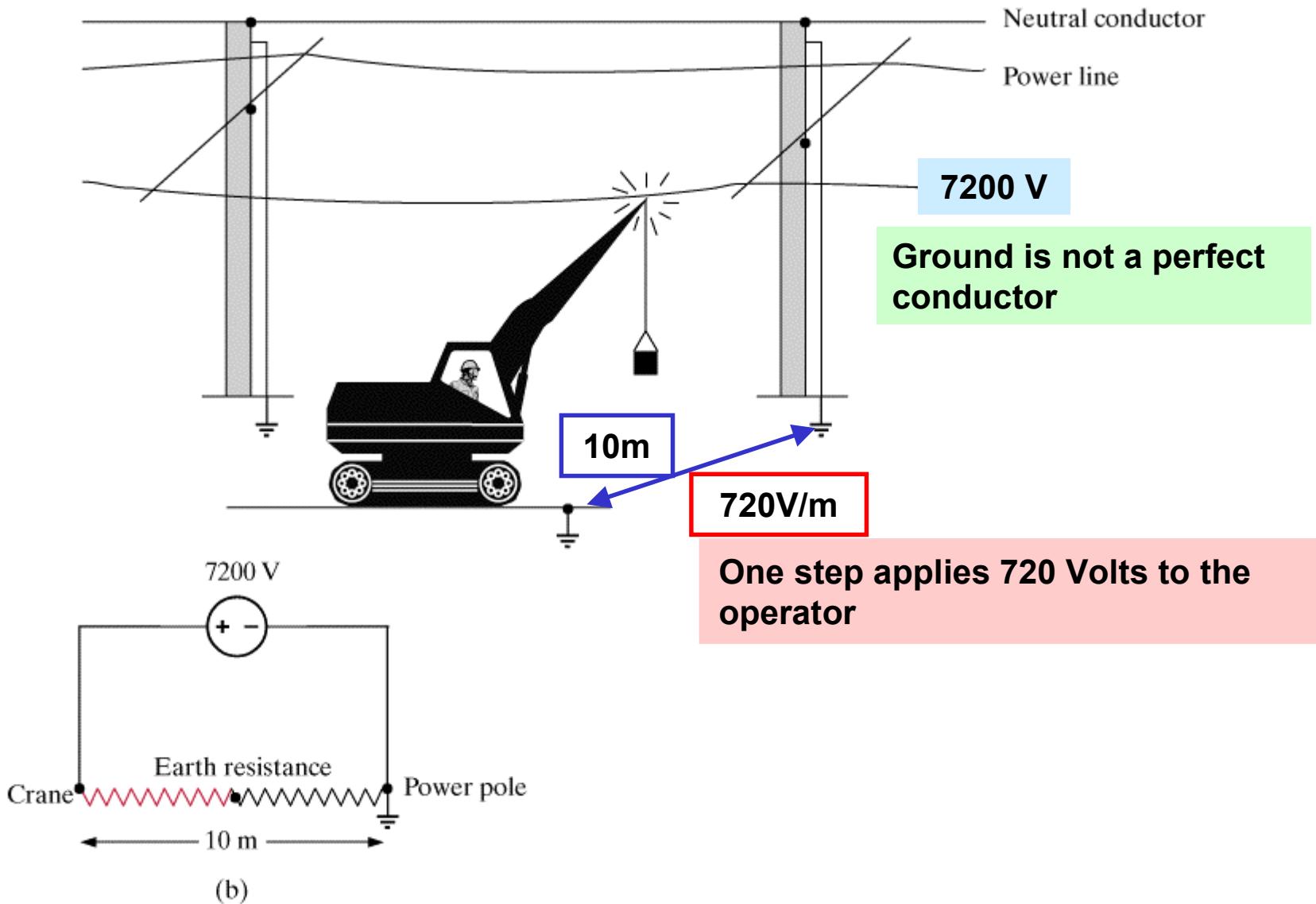
### A grounding accident

After the boom touches the live line the operator jumps down and starts walking towards the pole



## LEARNING EXAMPLE

A 7200V power line falls on the car and makes contact with it

7200V

Tires are insulators

Car body is good conductor

Wet Road

Option 1.  
Driver opens door and steps down

Option 2:  
Driver stays inside the car

$$I_{\text{body}} = \frac{7200}{R_{\text{dry skin}} + 2R_{\text{limb}} + R_{\text{trunk}}}$$

R(dry skin)	15kOhm
R(wet skin)	150Ohm
R(limb)	100Ohm
R(trunk)	200Ohm


$$I_{\text{body}} = 0$$

$I \approx 460mA$  Very dangerous!

Suggested resistances  
for human body

## LEARNING EXAMPLE

### Find the maximum cord length

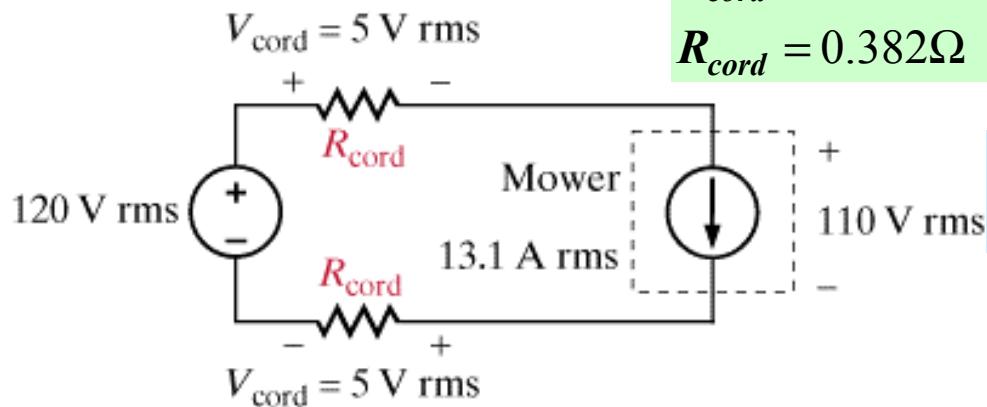

$$R_{cord} \times 13.1A = 5V$$

$$R_{cord} = 0.382\Omega$$

Minimum voltage for proper operation

CASE 1: 16-gauge wire

$$4 \frac{m\Omega}{ft}$$

$$L = \frac{R_{cord}}{4 \frac{m\Omega}{ft}} = 95.5 ft$$

CASE 2: 14-gauge wire


$$2.5 \frac{m\Omega}{ft}$$

$$L = \frac{R_{cord}}{2.5 \frac{m\Omega}{ft}} = 152.8 ft$$


Working with RMS values the problem is formally the same as a DC problem

## LEARNING EXAMPLE


### Light dimming when AC starts

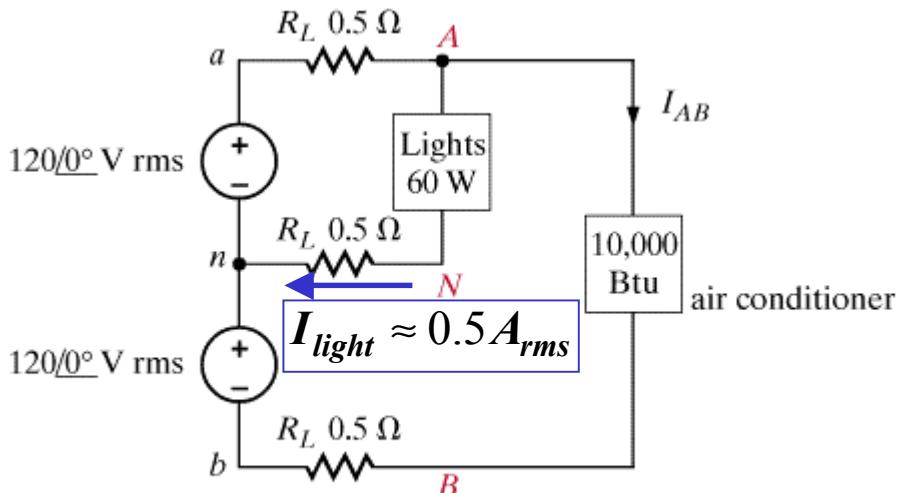


Typical single-phase 3-wire installation

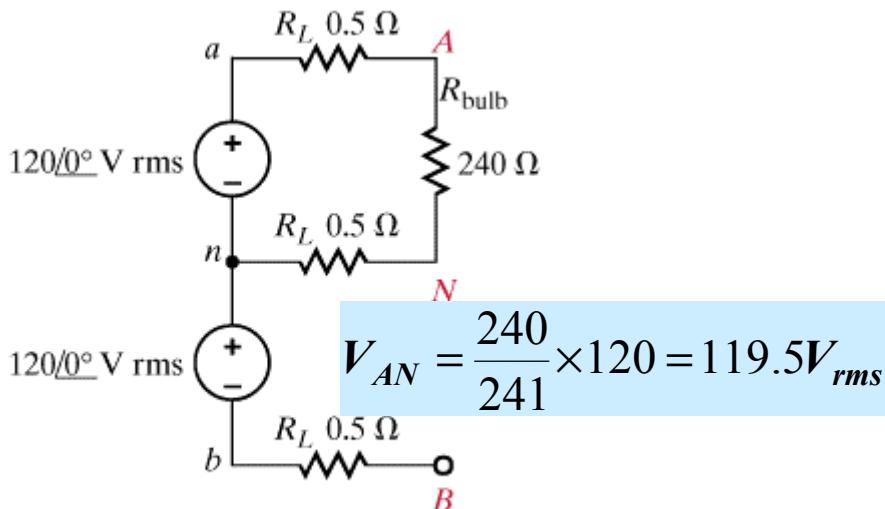

AC off

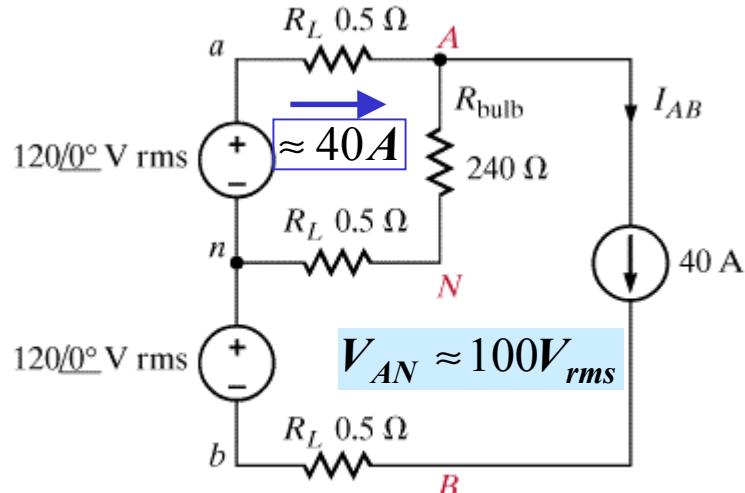


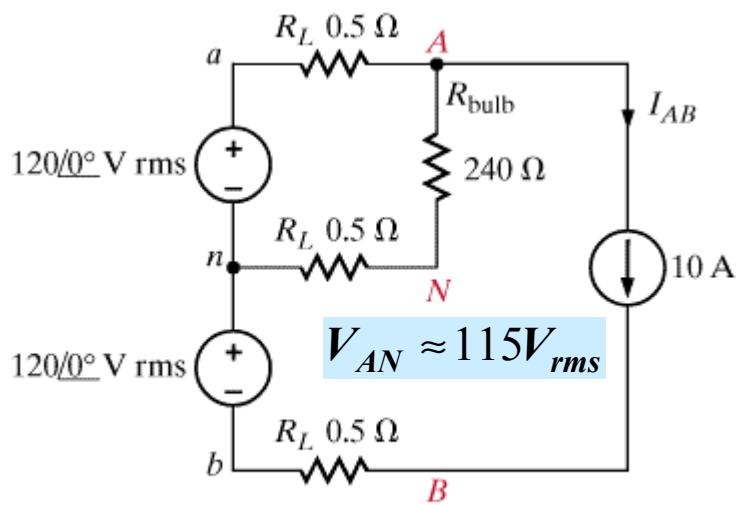Circuit at start of AC unit. Current demand is very high



AC in normal operation
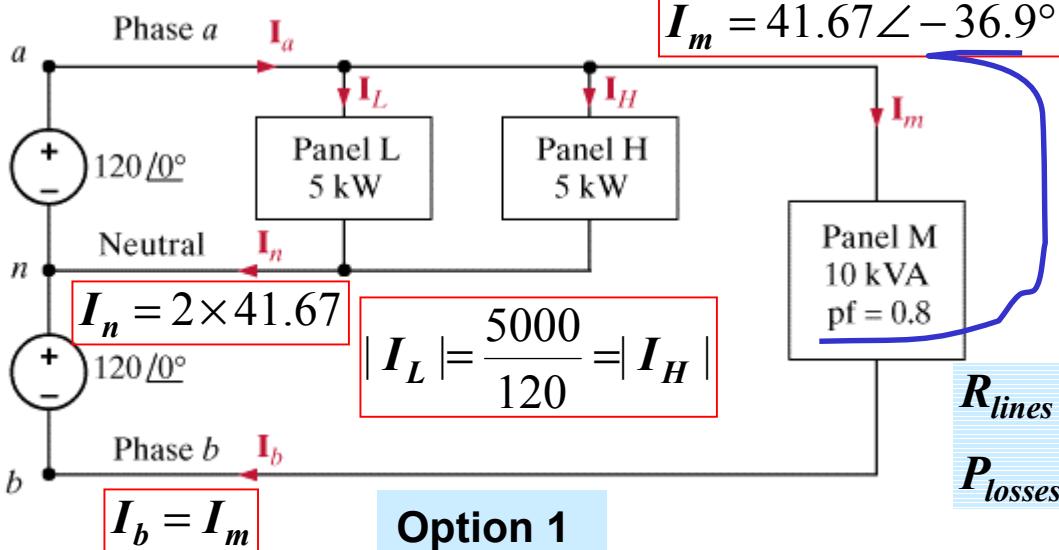
$$I_a = 41.67 \angle 0^\circ + 41.67 \angle 0^\circ + 41.67 \angle -36.9^\circ = 119.4 \angle -12.1^\circ (A)$$




$$\begin{aligned} S_A &= 120 \angle 0^\circ \times [119.4 \angle -12.1^\circ]^* \\ &= 14.38 \angle 12.1^\circ kVA = 14 + j3 kVA \end{aligned}$$

$$\begin{aligned} S_B &= 120 \angle 0^\circ \times [41.67 \angle -36.9^\circ]^* \\ &= 5 \angle 36.9^\circ kVA = 4 + j3 kVA \end{aligned}$$

$$R_{\text{lines}} = 0.05 \Omega$$

$$P_{\text{losses}} = 0.05 \times (|I_a|^2 + |I_b|^2 + |I_n|^2) = 1.147 kW$$
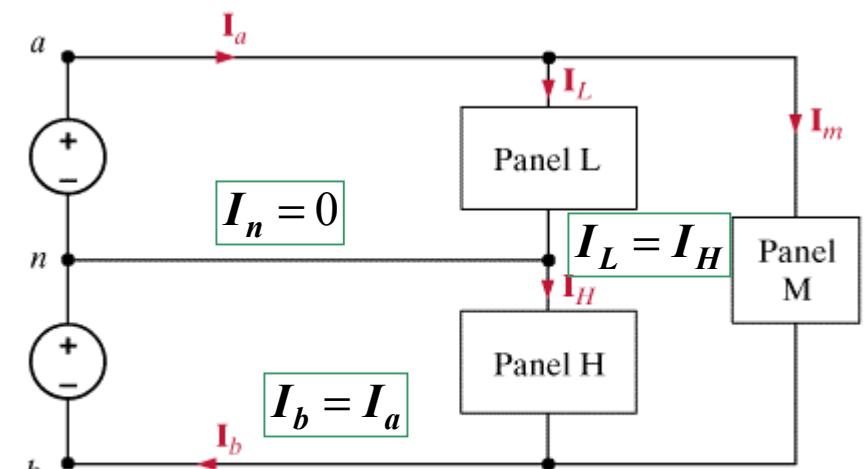
$$I_a = 41.67 \angle 0^\circ + 41.67 \angle -369^\circ = 79.07 \angle -18.4^\circ (A)$$



$$\begin{aligned} S_A &= S_B = 120 \angle 0^\circ \times [79.07 \angle 18.4^\circ]^* \\ &= 9.5 \angle 18.4^\circ kVA = 9 + j3 kVA \end{aligned}$$

$$R_{\text{lines}} = 0.05 \Omega$$

$$P_{\text{losses}} = 0.05 \times (|I_a|^2 + |I_b|^2) = 0.625 kW$$

$$P_{\text{saved}} = 0.522 kW$$

$$\$/\text{year} = 366(@0.08\$/kWh)$$

Steady-state  
Power Analysis

