

CIRCUITS WITH DEPENDENT SOURCES

A CONVENTION ABOUT DEPENDENT SOURCES.
UNLESS OTHERWISE SPECIFIED THE CURRENT AND VOLTAGE VARIABLES ARE ASSUMED IN SI UNITS OF *Amps* AND *Volts*

DEPENDENT VARIABLE

$$V_D = \alpha I_X$$

CONTROLLING VARIABLE

FOR THIS EXAMPLE THE MULTIPLIER MUST HAVE UNITS OF OHM

OTHER DEPENDENT SOURCES

$$V_D = \beta V_X \quad (\beta \text{ scalar})$$

$$I_D = \gamma \mathcal{W}_X \quad (\gamma \text{ Siemens})$$

$$I_D = \beta I_X \quad (\beta \text{ scalar})$$


AN ALTERNATIVE DESCRIPTION

$$V_D = \alpha I_X, \quad \alpha = 2 \left[\frac{V}{mA} \right] \quad \text{UNITS ARE EXPLICIT}$$

ASSUMES CURRENT IN mA

GENERAL STRATEGY

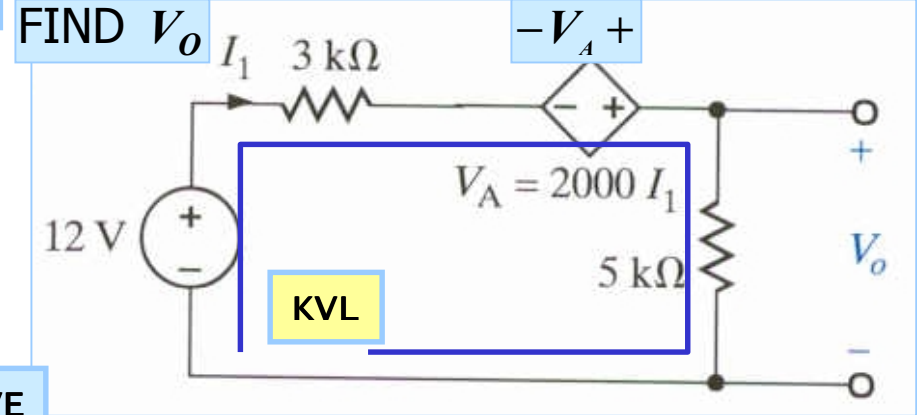TREAT DEPENDENT SOURCES AS REGULAR SOURCES AND ADD ONE MORE EQUATION FOR THE CONTROLLING VARIABLE



A PLAN:

SINGLE LOOP CIRCUIT.

USE KVL TO DETERMINE CURRENT

$$\text{KVL: } -12 + 3k * I_1 - V_A + 5k * I_1 = 0$$

ONE EQUATION, TWO UNKNOWN. CONTROLLING VARIABLE PROVIDES EXTRA EQUATION

$$V_A = 2k * I_1$$

REPLACE AND SOLVE FOR THE CURRENT


$$I_1 = 2mA$$

USE OHM'S LAW

$$V_o = 5k * I_1 = 10V$$





FIND V_o

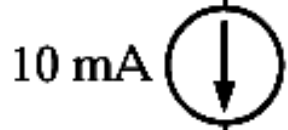

2 k

4 k

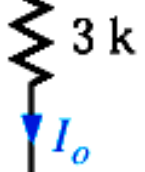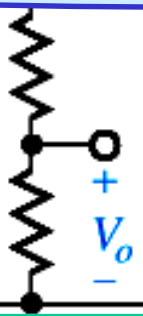

$4I_o$

V_s



KCL TO THIS NODE. THE DEPENDENT SOURCE IS JUST ANOTHER SOURCE

A PLAN:

IF V_s IS KNOWN V_o CAN BE DETERMINED USING VOLTAGE DIVIDER.
TO FIND V_s WE HAVE A SINGLE NODE-PAIR CIRCUIT

10×10^{-3}

$$10 \times 10^{-3} + \frac{V_s}{2k + 4k} + \frac{V_s}{3k} - 4I_o = 0$$

THE EQUATION FOR THE CONTROLLING VARIABLE PROVIDES THE ADDITIONAL EQUATION

$$I_o = \frac{V_s}{3k}$$

ALGEBRAICALLY, THERE ARE TWO UNKNOWNS AND JUST ONE EQUATION

SUBSTITUTION OF I_o YIELDS


$$\frac{V_s}{6k} + \frac{V_s}{3k} - \frac{4V_s}{3k} = 0 \quad */6k \Rightarrow 5V_s = 60$$

VOLTAGE DIVIDER

$$V_o = \frac{4k}{4k + 2k} V_s = \frac{2}{3} (12)V$$

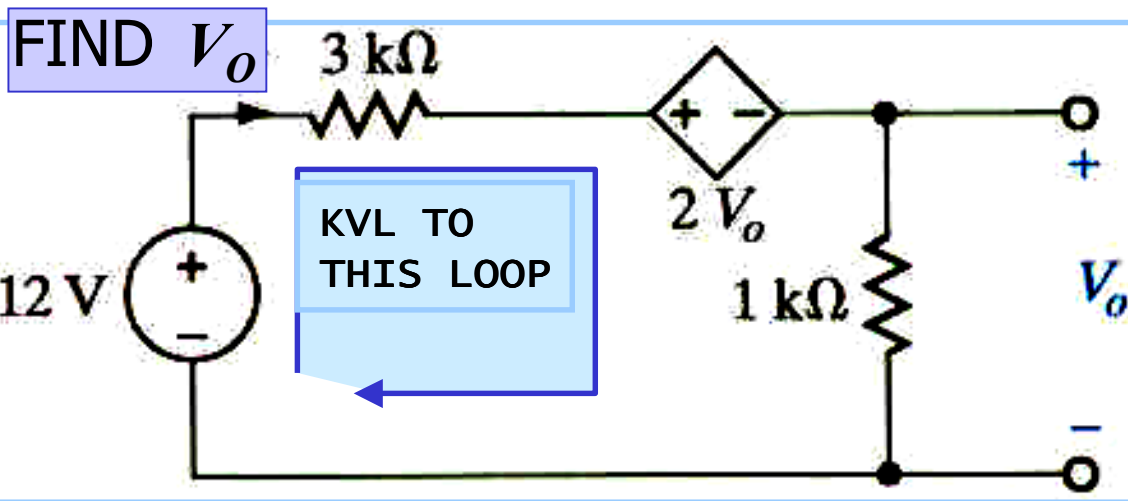NOTICE THE CLEVER WAY OF WRITING mA TO HAVE VOLTS IN ALL NUMERATORS AND THE SAME UNITS IN DENOMINATOR





A PLAN:
 ONE LOOP PROBLEM.
 FIND THE CURRENT
 THEN USE OHM'S LAW.

THE DEPENDENT SOURCE IS ONE MORE VOLTAGE SOURCE

$$-12 + 3kI + 2V_o + 1kI = 0$$

THE EQUATION FOR THE CONTROLLING VARIABLE PROVIDES THE ADDITIONAL EQUATION

$$V_o = 1kI$$

REPLACE AND SOLVE FOR CURRENT I


$$I = 2 \text{ mA}$$

... AND FINALLY

$$V_o = 1kI = 2 \text{ V}$$



FIND $G = \frac{v_o(t)}{v_i(t)}$

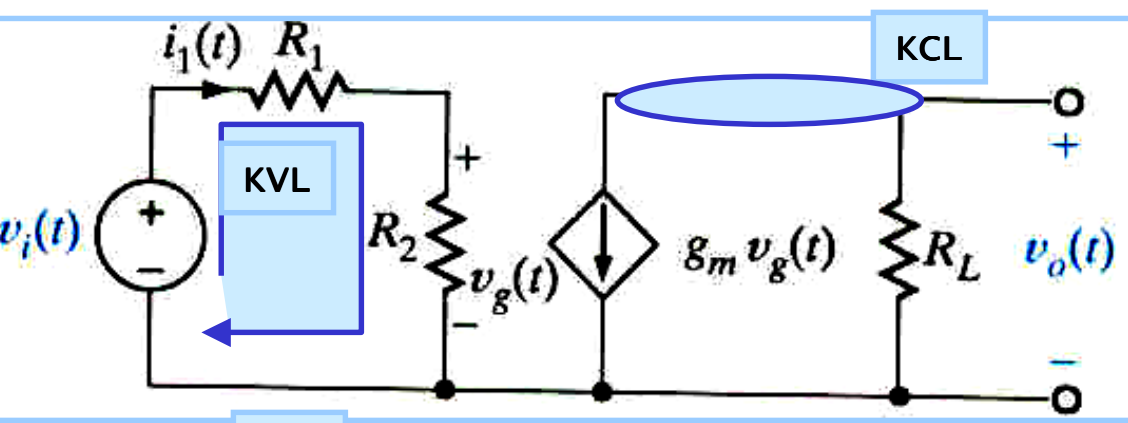

A PLAN:
 ONE LOOP ON THE LEFT - KVL
 ONE NODE-PAIR ON RIGHT - KCL

KVL

$$v_i(t) = i_1(t)(R_1 + R_2)$$

$$v_g(t) = i_1(t)R_2 \quad v_g(t) = \frac{R_2}{R_1 + R_2} v_i(t)$$

KCL

ALSO A VOLTAGE DIVIDER

$$g_m v_g(t) + \frac{v_o(t)}{R_L} = 0 \quad v_o(t) = -g_m v_g(t) R_L$$

$$v_o(t) = \frac{-g_m R_L R_2}{R_1 + R_2} v_i(t) \quad \frac{v_o(t)}{v_i(t)} = -\frac{g_m R_L R_2}{R_1 + R_2}$$

