

13.48 In the network in Fig. P13.48, the switch opens at $t = 0$. Use Laplace transforms to find $v_o(t)$ for $t > 0$.

CS


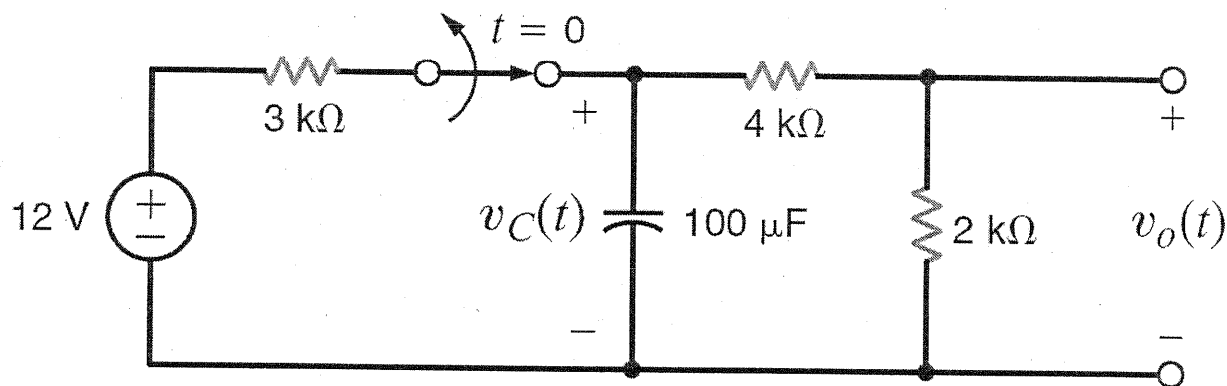


Figure P13.48

SOLUTION:

$t = 0^-$
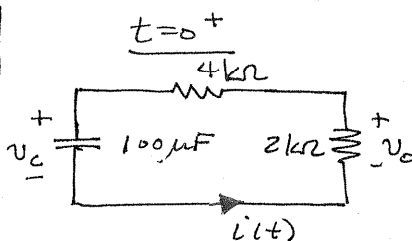
$$V_C(0^-) = \frac{12(6000)}{6000 + 3000} = 8V$$



$$6000 i(t) + 10^{-4} \int i(t) dt = 0 \quad \text{or} \quad 10^{-4} \frac{dv_C}{dt} + \frac{v_C(t)}{6000} = 0$$

$$0.6 [sV_C(s) - v_C(0^-)] + V_C(s) = 0 \Rightarrow V_C(s) [0.6s + 1] = 4.8$$

$$\text{But } \frac{V_o(s)}{V_C(s)} = \frac{2000}{2000 + 4000} = \frac{1}{3} \Rightarrow V_o(s) = \frac{V_C(s)}{3}$$

$$3V_o(s) [0.6s + 1] = 4.8 \Rightarrow V_o(s) [s + 1.67] = 2.67$$

$$V_o(s) = \frac{2.67}{s + 1.67}$$

$$v_o(t) = 2.67 e^{-1.67t} u(t)$$