

14.35 Find $v_o(t)$, for $t > 0$, in the network in Fig. P14.35.

CS


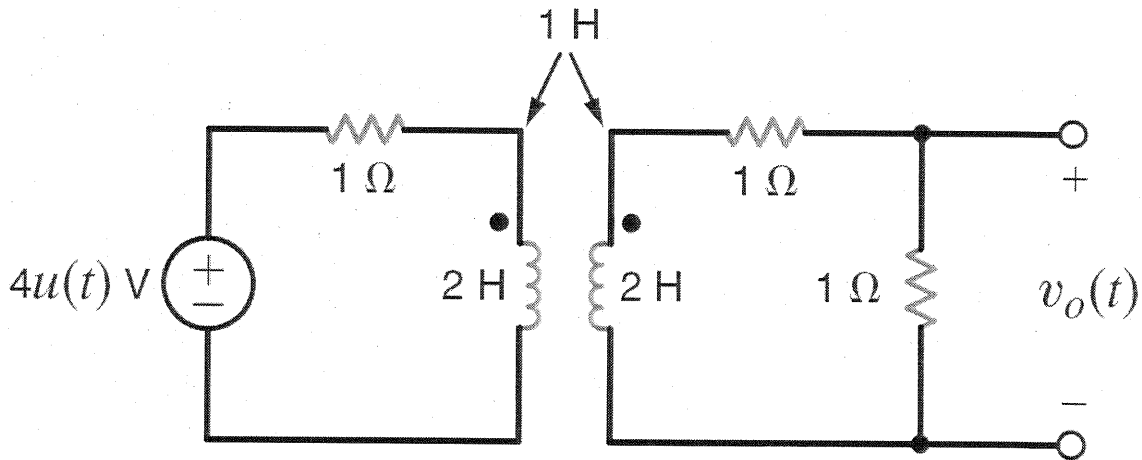


Figure P14.35

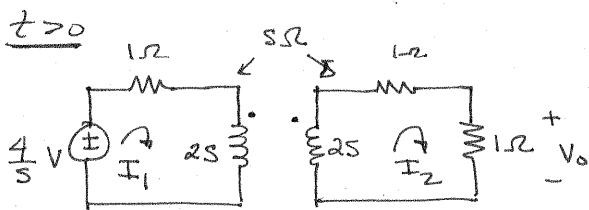SOLUTION: $t=0^-$: no excitation \rightarrow initial conditions



$$\frac{4}{s} = I_1(2s+1) - sI_2$$

$$0 = -sI_1 + I_2(2s+2)$$

$$\text{or, } I_1 = I_2(2s+2)/s$$

$$\text{yields, } I_2 = \frac{4/3}{s^2 + 2s + 2/3}$$

$$V_o = (1)I_2 = \frac{4/3}{(s+0.42)(s+1.58)}$$

$$V_o = \frac{1.15}{s+0.42} - \frac{1.15}{s+1.58}$$

$$v_o(t) = 1.15 [e^{-0.42t} - e^{-1.58t}] u(t) \text{ V}$$