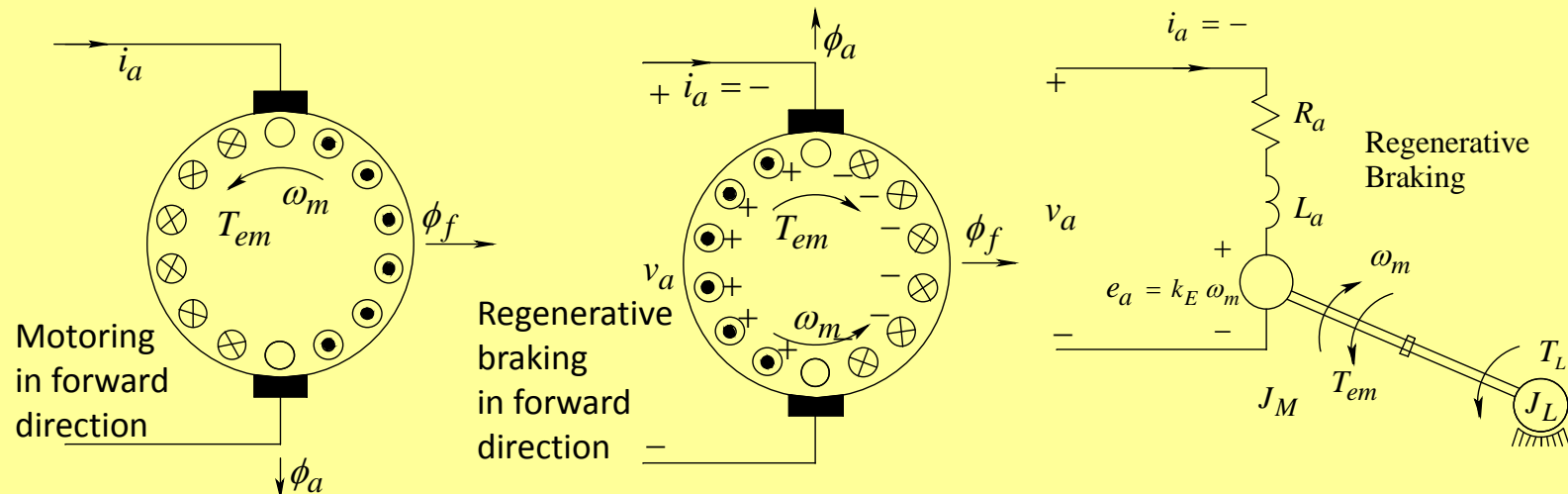


# DC Motor Drives


- Operating Modes
- Four-Quadrant Operation
- Flux-Weakening
- Power-Processor Unit (PPU)
- Electronically-Commutated Motor Drives

# Operating Modes




- Regenerative Braking: Feeding energy back while braking
  - ◆ current and torque direction reversed
  - ◆ same polarity of induced emf
  
- Operation in reverse direction: polarity of applied voltage reversed
  - ◆ Motoring  $i_a < 0$
  - ◆ Regenerative braking  $i_a > 0$

# Four Quadrant Operation

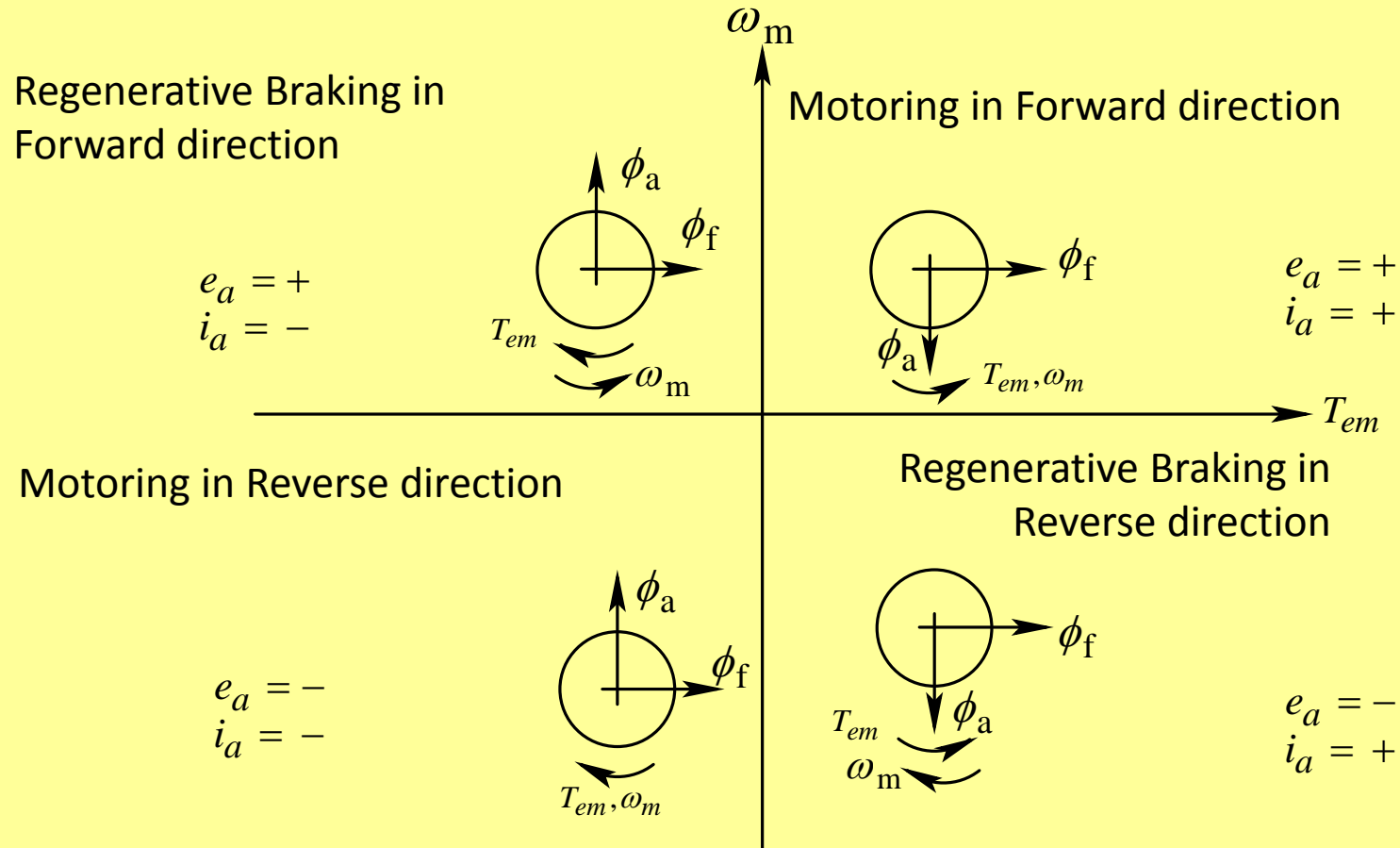

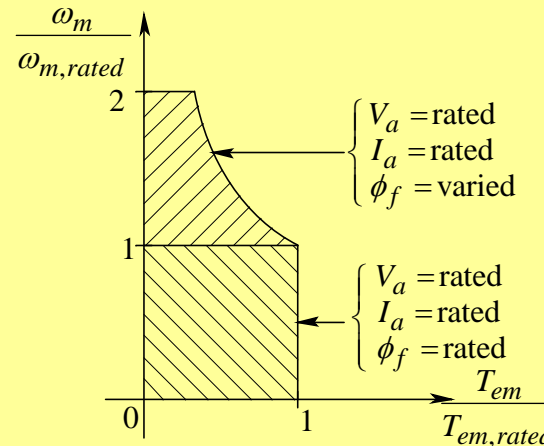
# Flux-weakening in wound field machines to Allow Overspeed Operation



- Below rated speed,  $k_T$  maximum to ensure maximum torque/Ampere thereby minimizing resistive losses
- Above rated speed,  $B_f$  reduced to keep  $V_a$  at its rated value.
- $B_f$  reduced by reducing  $I_f$
- $k_T$  and  $k_E$  changed;  $k_T = k_t B_f$ ;  $k_E = k_e B_f$ ;  $k_t = k_e$
- Since  $I_a$  is limited to its rated value maximum,  $T_{em}$  reduces


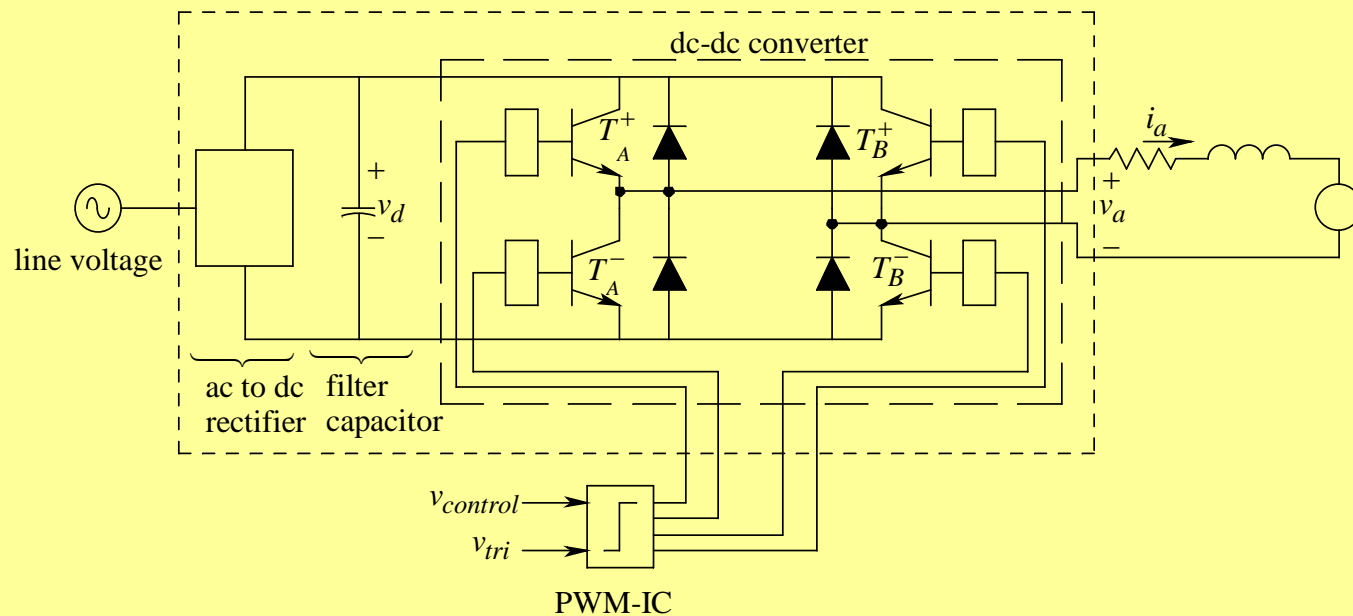
# Power Processing Unit for DC Drives

- Draw power from utility - power quality problems
  - Ideally power flow should be reversible
- Provide nearly dc voltage and current to the dc motor





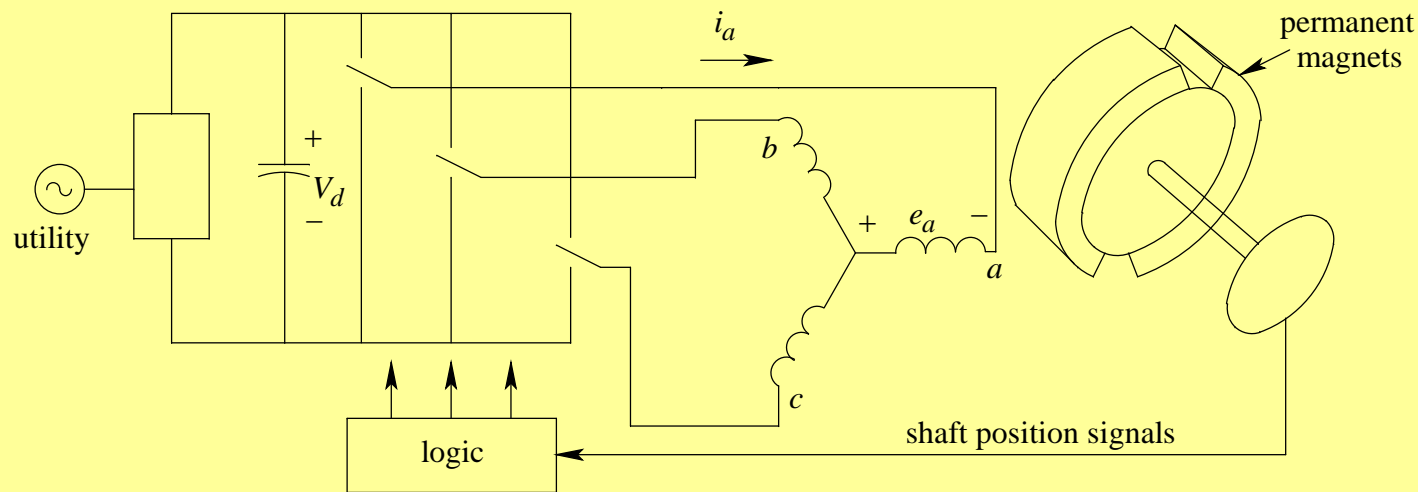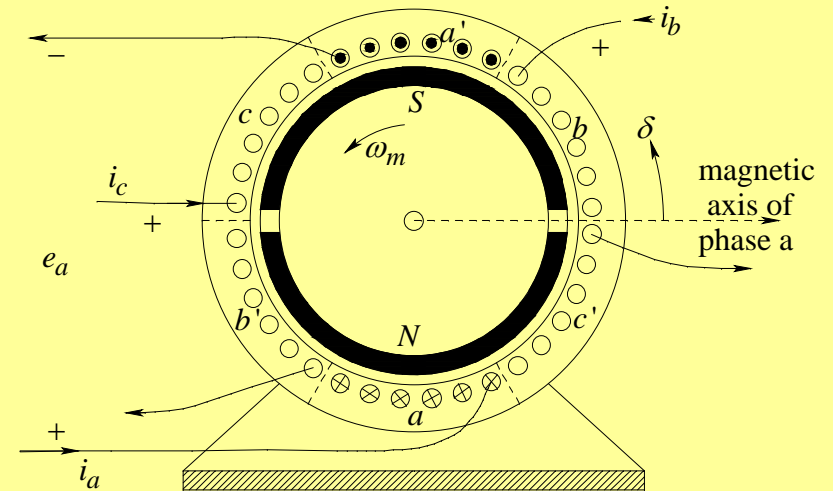
# Electronically Commutated Motor Drives (Trapezoidal waveform brush-less dc)

- “Inside out” machines
- Electronically commutated armature
- At any instant, only two sets of windings carry currents. As the rotor turns, different pairs of windings are chosen.



# Rotating Field & Stationary Conductors

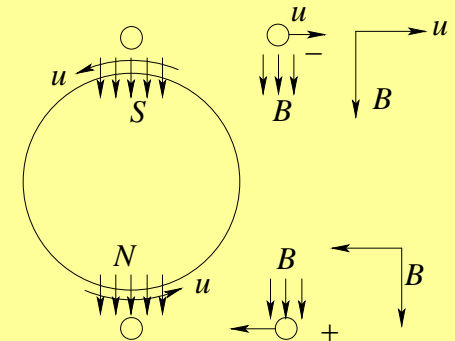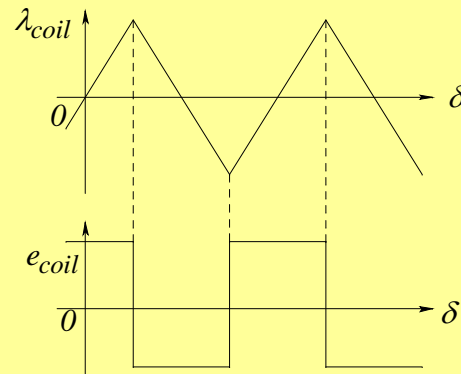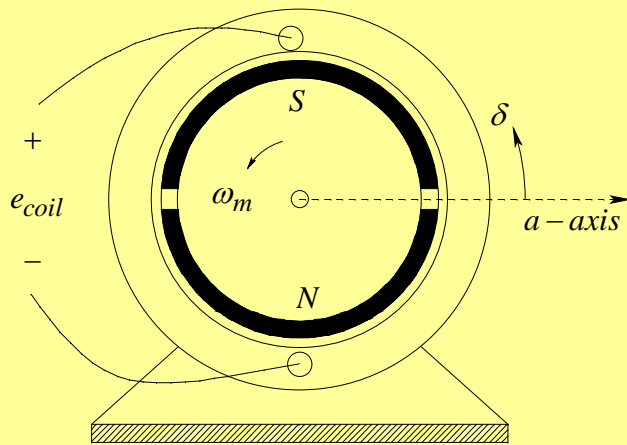

- Flux linkage of a single turn coil

$$\lambda_{coil} = (\pi r l) B_f \left( \delta / (\pi / 2) \right) \quad (-\pi / 2 \leq \delta \leq \pi / 2)$$

- emf induced


$$\text{total induced emf} = 2 N_s B_f l r \omega_m$$

(when all turns are under common pole)

- Polarity determined by assuming field to be stationary and and the conductor moving in opposite direction

$$e_{coil} = \frac{d\lambda}{dt} = \frac{d\lambda}{d\delta} \frac{d\delta}{dt} = \frac{\pi r l B_f \omega_m}{\pi / 2} = 2 \underbrace{B_f l r \omega_m}_{e_{cond}}$$


# Induced emf

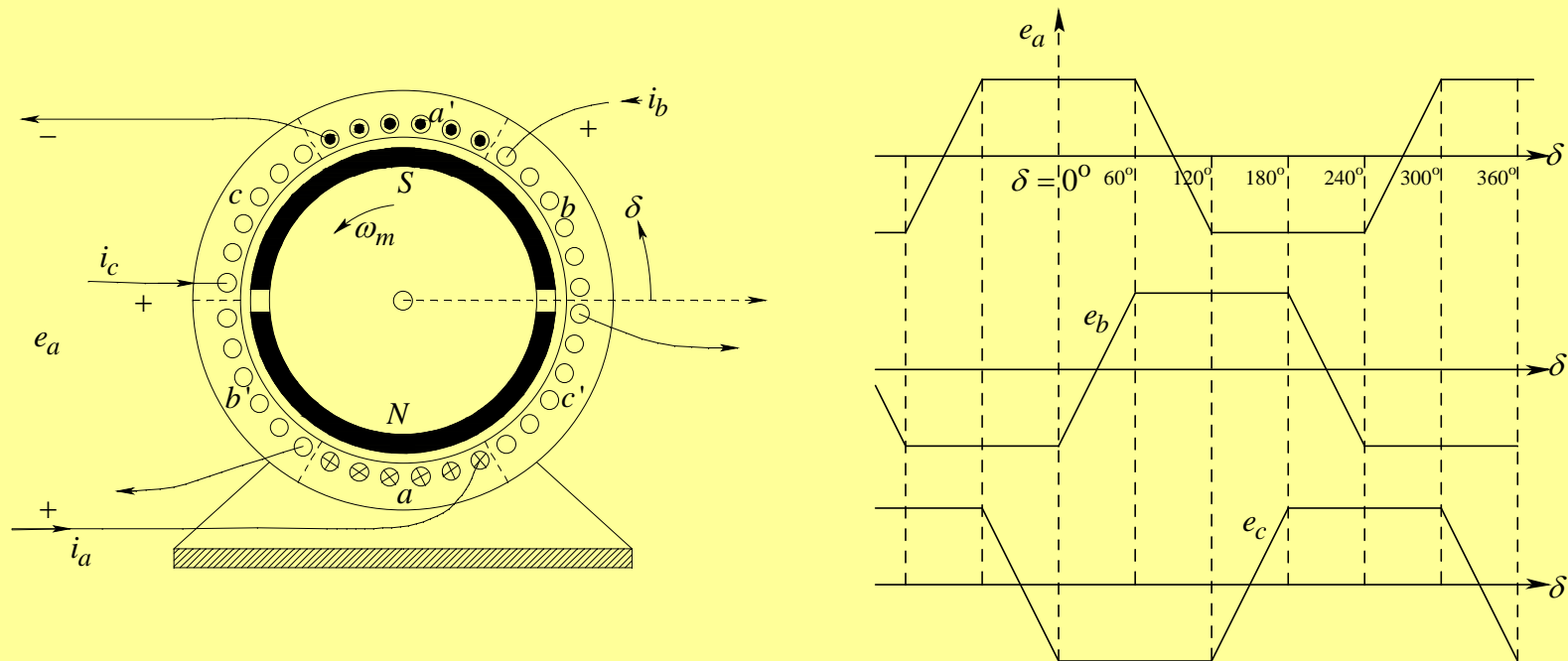

- In flat regions all turns are under same pole
- In sloped regions some turns are under  $N$  pole while others are under  $S$  pole



# Torque Production

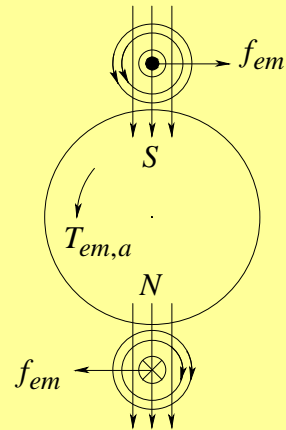


□ Force on conductors  $f = Bli$



torque on rotor CCW

□ Excite two phases simultaneously
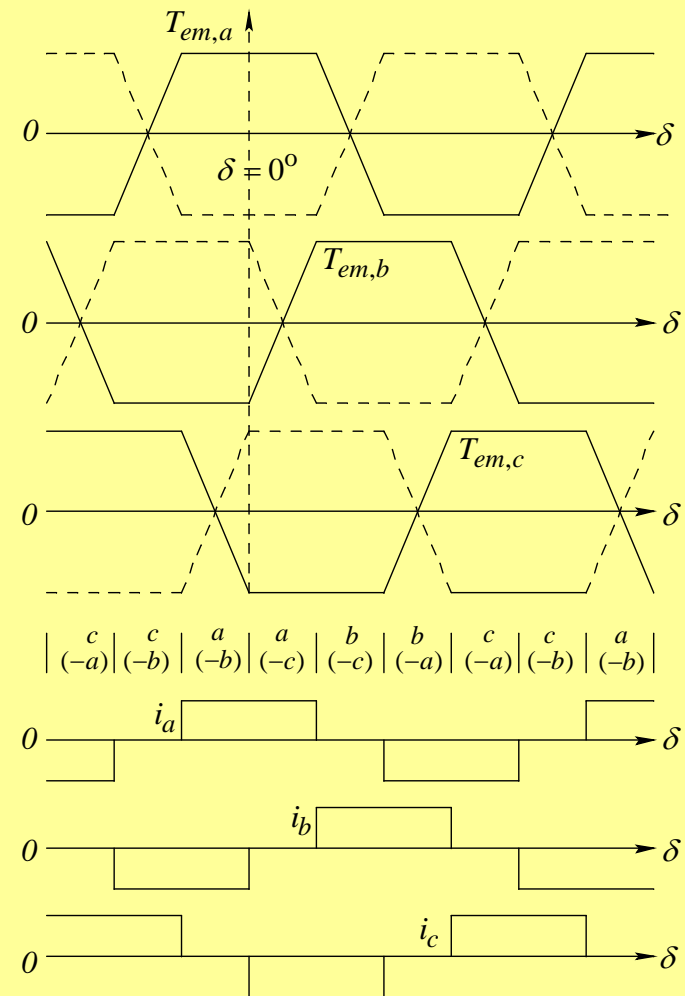
$$\text{Total } T_{em} = 2 \times (2N_s B_f l r) I = k_T I$$




## □ Equivalent circuit

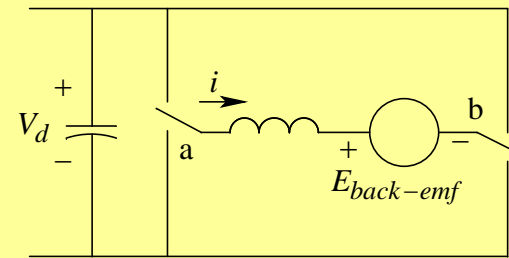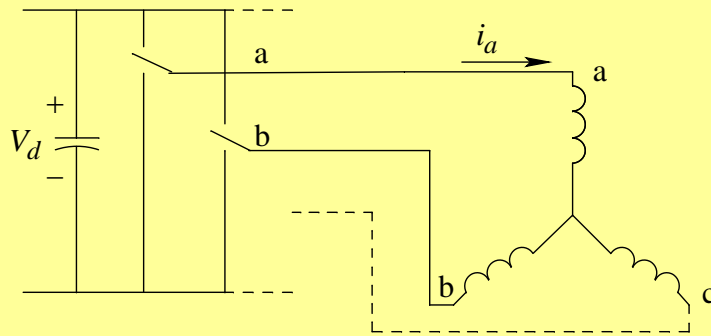

Phase-to-phase back induced emf

$$e_{back-emf} = 2e_{ph} = 2 \times (2N_s B_f l r) \omega_m = k_E \omega_m \quad k_E = k_T$$

## □ Hysteresis current control

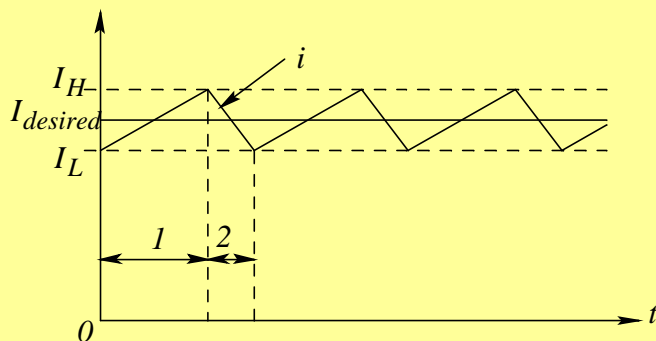

Position 1: Pole  $a$  high, Pole  $b$  low  
 Position 2: Pole  $a$  low, Pole  $b$  high  
 After  $60^\circ$  rotor rotation, a new pair of poles ( $a, c$ ) are used

# Summary

## DC Motor Drives

- Operating Modes
- Four-Quadrant Operation
- Flux-Weakening
- Power-Processor Unit (PPU)
- Electronically-Commutated Motor Drives