


Basic Understanding of Power Processing in Electric Drives

- Role of PPU's
 - Switching Power-Pole as the Building Block
 - PWM Control
 - Average Model

Power Processing Unit (PPU)


- Efficient conversion of power from line frequency AC to appropriate form required by the motor

Sub-blocks of PPU

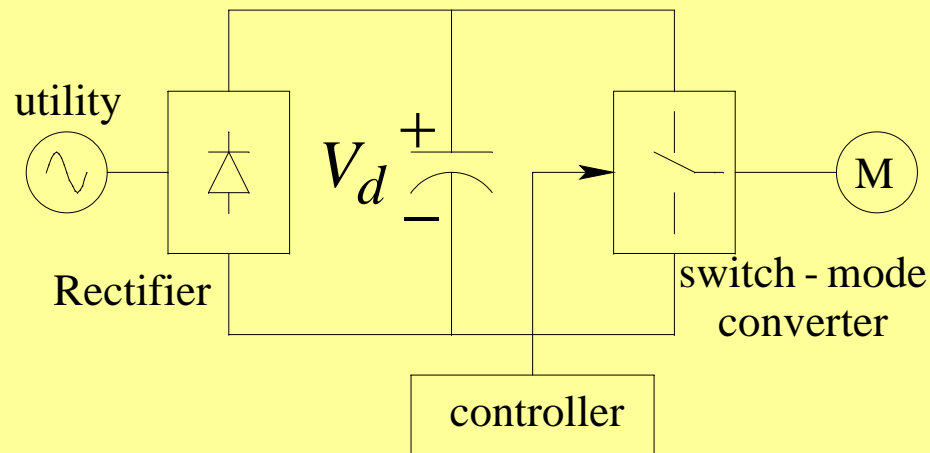


- Rectifier: Line frequency AC to DC
- Switch-Mode Converter: DC to the form required by motor

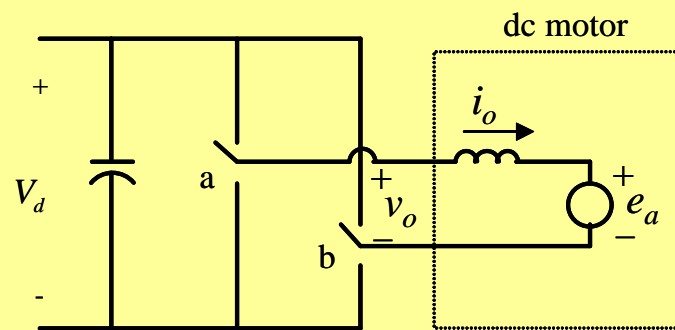Switch-Mode Converters for dc- and ac-motor drives



(a)

For DC Drives

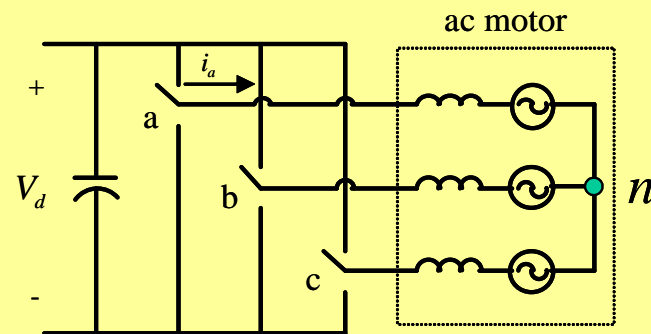


(b)

For AC Drives

Analysis of Switch-Mode Converters

□ Pole as a Building Block

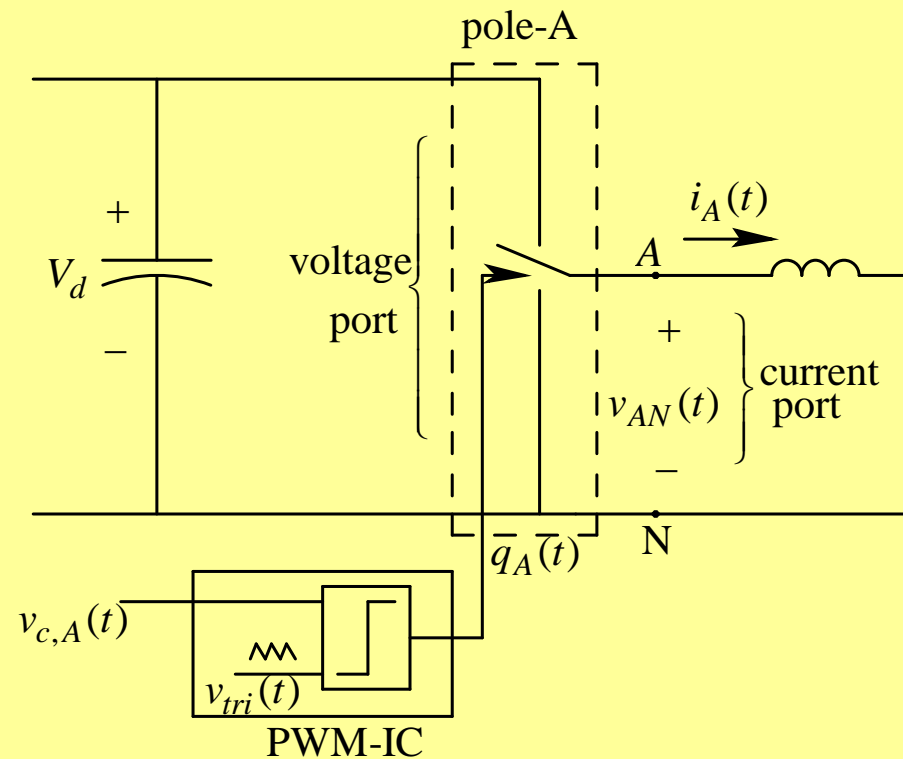


- V_d uncontrolled
- $v_{c,A}$: control voltage depicting desired output voltage
- Switch modulated to produce desired average voltage \bar{v}_{AN}

Pulse Width Modulation (PWM)

if $v_{c,A}(t) > v_{tri}(t) \Rightarrow q_A(t) = 1 \Rightarrow$ switch "up" $\Rightarrow v_{AN}(t) = V_d$

if $v_{c,A}(t) < v_{tri}(t) \Rightarrow q_A(t) = 0 \Rightarrow$ switch "down" $\Rightarrow v_{AN}(t) = 0$

$$v_{AN}(t) = q_A(t)V_d$$

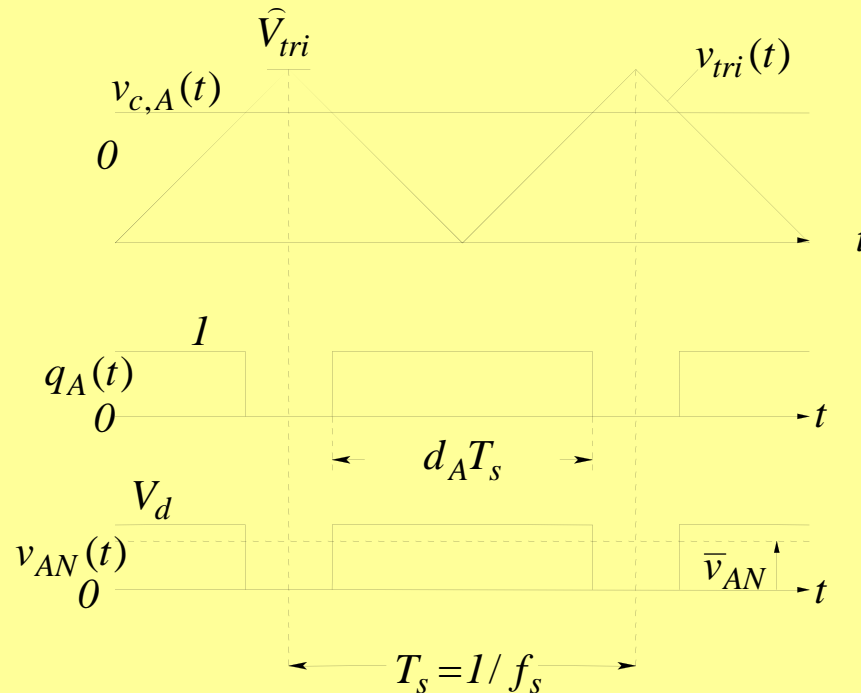

Average Representation of a Pole Output Voltage

Average output voltage over one switching cycle


$$\bar{v}_{AN} = \frac{1}{T_s} \int_0^{T_s} v_{AN}(t) dt = d_A V_d$$

Duty ratio $d_A = \frac{v_{c,A}}{\hat{V}_{tri}}$

$$\bar{v}_{AN} = \underbrace{\frac{V_d}{\hat{V}_{tri}}}_{k_{pole}} v_{c,A}$$

Pole gain


$$k_{pole} = \frac{V_d}{\hat{V}_{tri}}$$

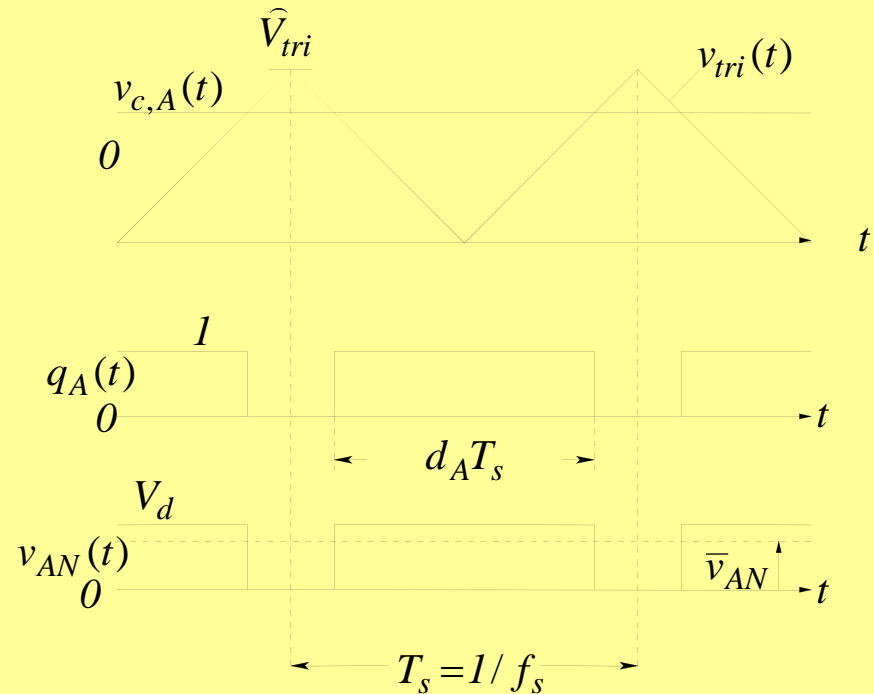


Average Representation of a Pole Input and Output Currents

- Assuming ripple in $i_A(t)$ to be negligible, i.e. $i_A(t) = \bar{i}_A(t)$
average values of input and the output currents can be related as,

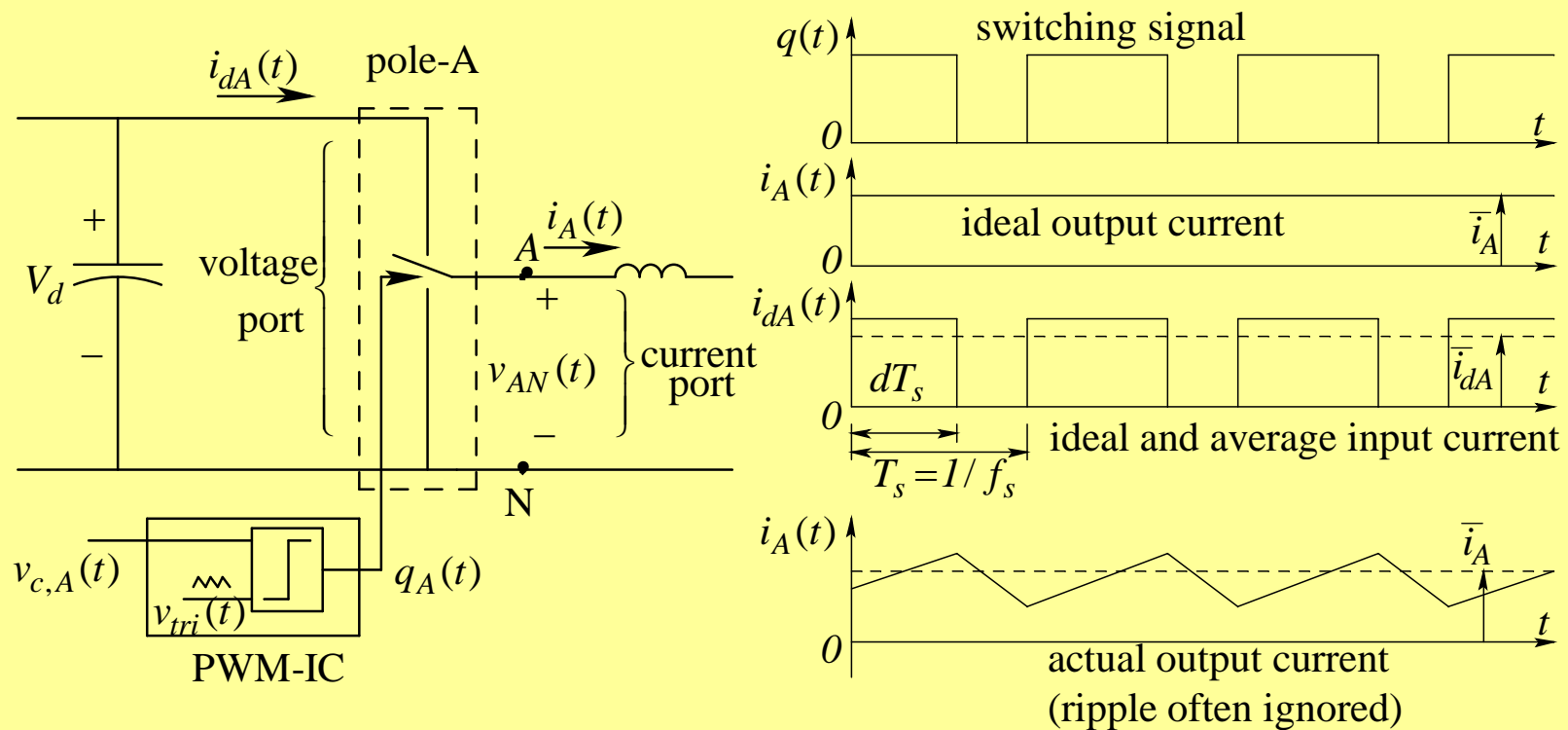
$$\bar{i}_{dA}(t) = d_A(t) \bar{i}_A(t)$$



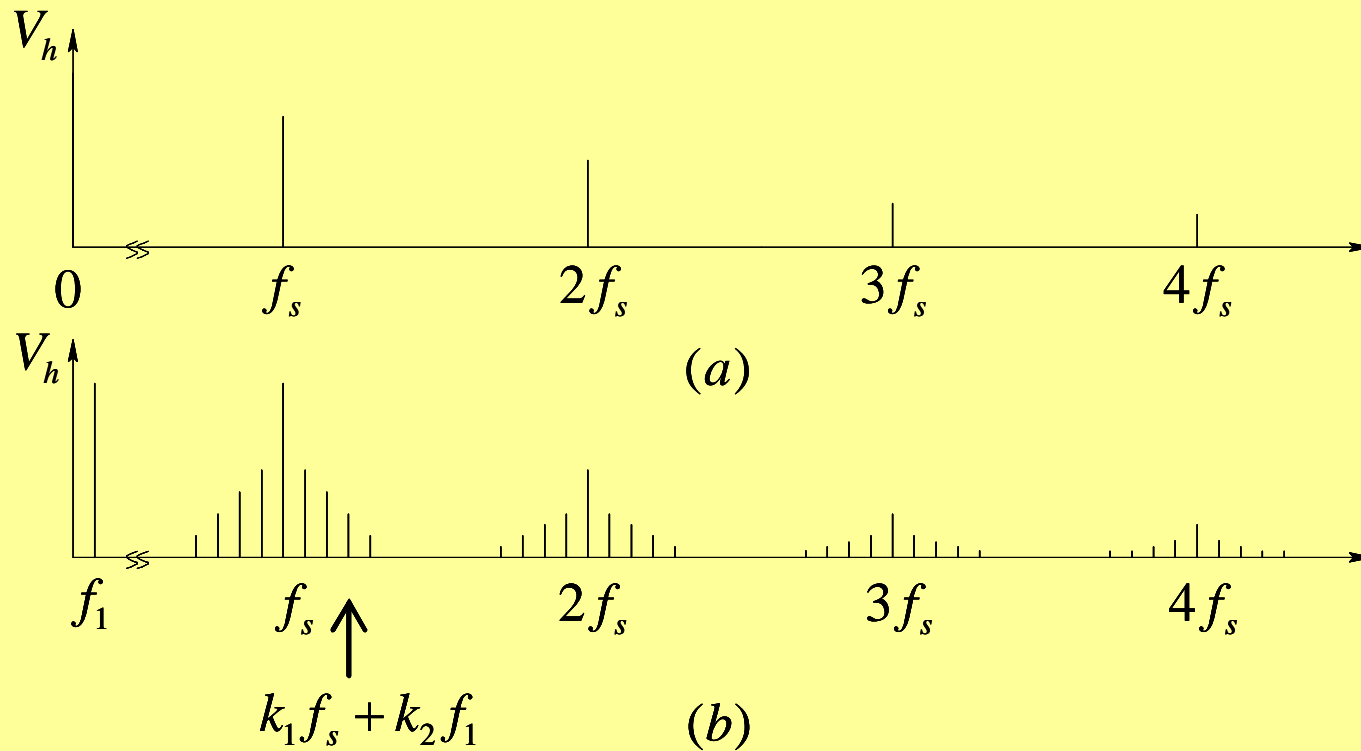Harmonics in the voltage across the Current-Port



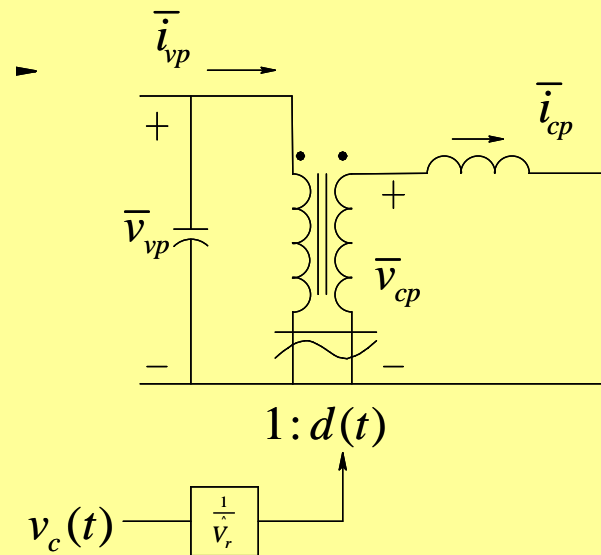
Average Representation of a Pole as An Ideal Transformer




- Transformer turns-ratio is adjustable via Pulse Width Modulation
- This Transformer can pass AC and DC currents but only unipolar voltages

Pole as a Two-Quadrant Converter

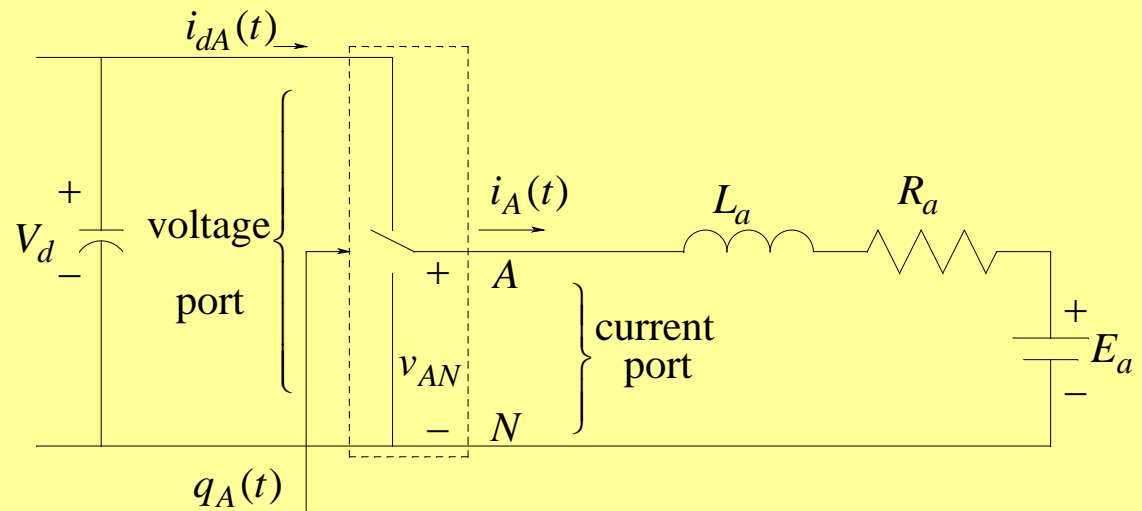- v_{AN} always positive
- i_A can reverse
 - ◆ $i_A > 0$ if $\bar{v}_{AN} > E_a$
power $V_d \rightarrow E_a$
Buck Mode
 - ◆ $i_A < 0$ if $v_{AN} < E_a$
power $E_a \rightarrow V_d$
Boost Mode



Calculation of Ripple Current

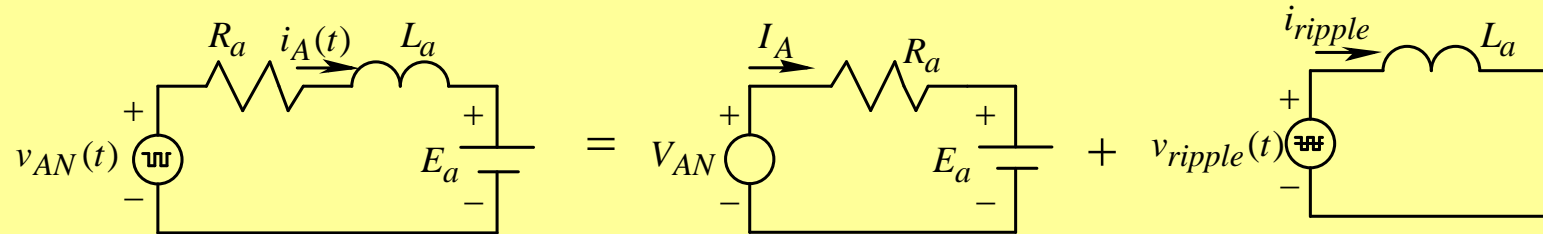


$$i_A(t) = I_A + i_{ripple}(t)$$

$$v_{AN}(t) = V_{AN} + v_{ripple}(t)$$



$$I_A = \frac{V_{AN} - E_a}{R_a}$$

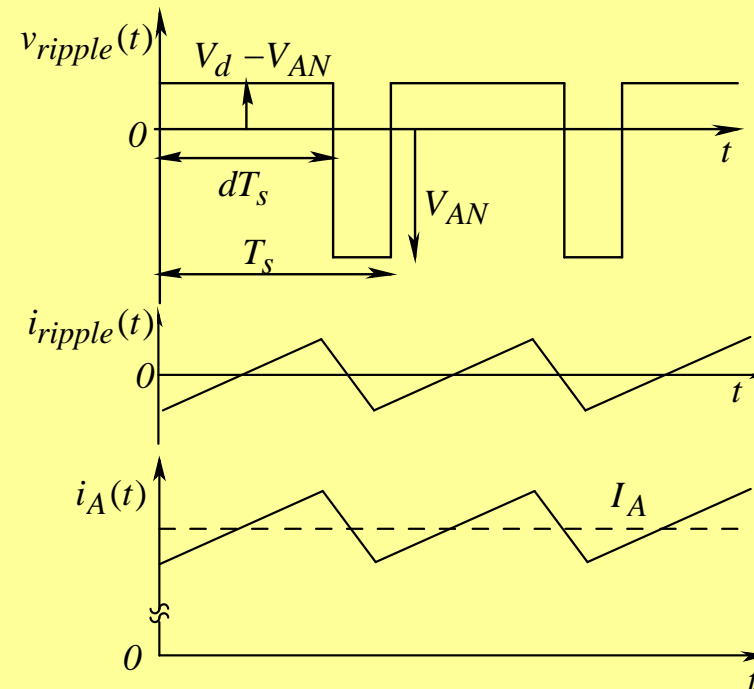$i_{ripple}(t)$ = sawtooth with zero DC average



$$\Delta i_A = \frac{\text{volt-seconds}}{L_a} = \frac{(V_d - V_{AN})dT_s}{L_a}, \text{ or } \frac{V_{AN}(1-d)T_s}{L_a}$$

Implementation of Bi-Positional Switches

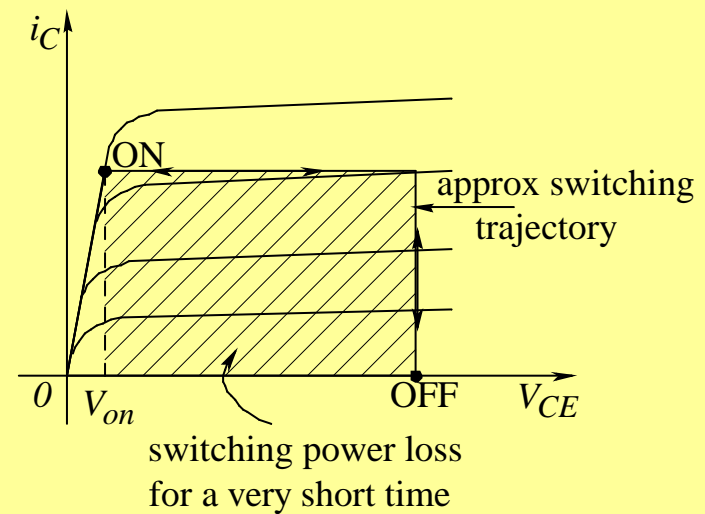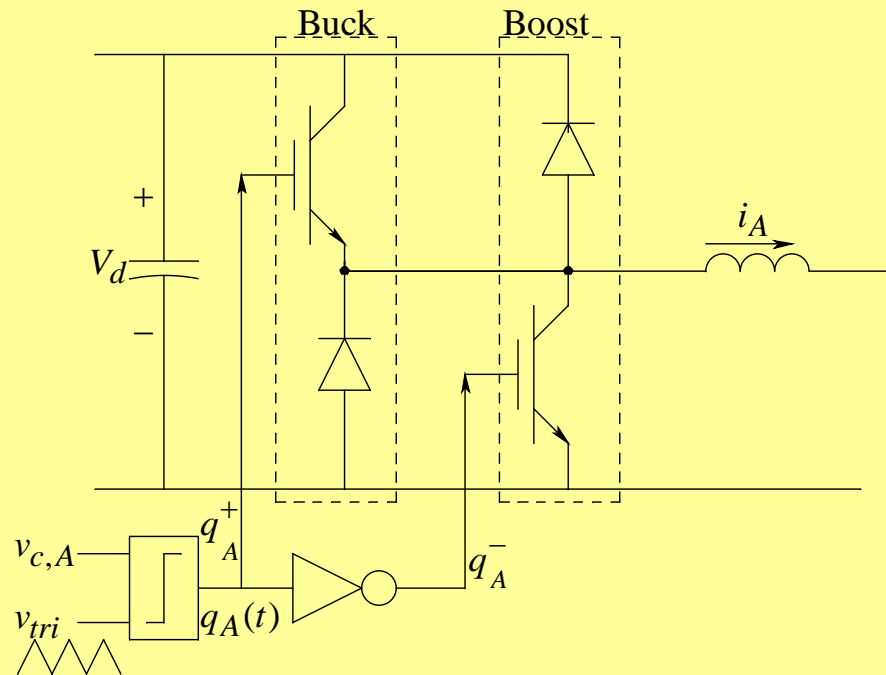

- Switching frequency 6kHz to 50kHz
- Switching power loss: kept low by fast switching devices
- Conduction loss: kept low by having switches fully ON or fully OFF

Summary

Basic Understanding of Power Processing in Electric Drives

- Role of PPU's
 - Switching Power-Pole as the Building Block
 - PWM Control
 - Average Model