

# First Course on Power Systems

## Module 6: High-Voltage DC (HVDC) Transmission Systems

By  
Ned Mohan  
Professor of ECE  
University of Minnesota


**Reference Textbook:**  
**First Course on Power Systems by Ned Mohan,**  
**[www.mnpere.com](http://www.mnpere.com)**

# Module 6: HVDC Transmission Systems

<b>Chapter 7</b>	<b>HIGH VOLTAGE DC (HVDC) TRANSMISSION SYSTEMS</b>	<b>7-1</b>
7-1	INTRODUCTION	7-1
7-2	POWER SEMICONDUCTOR DEVICES AND THEIR CAPABILITIES	7-1
7-3	HVDC TRANSMISSION SYSTEMS	7-2
7-4	CURRENT-LINK HVDC SYSTEMS	7-3
7-5	VOLTAGE-LINK HVDC SYSTEMS	7-13
	REFERENCES	7-18
	PROBLEMS	7-18
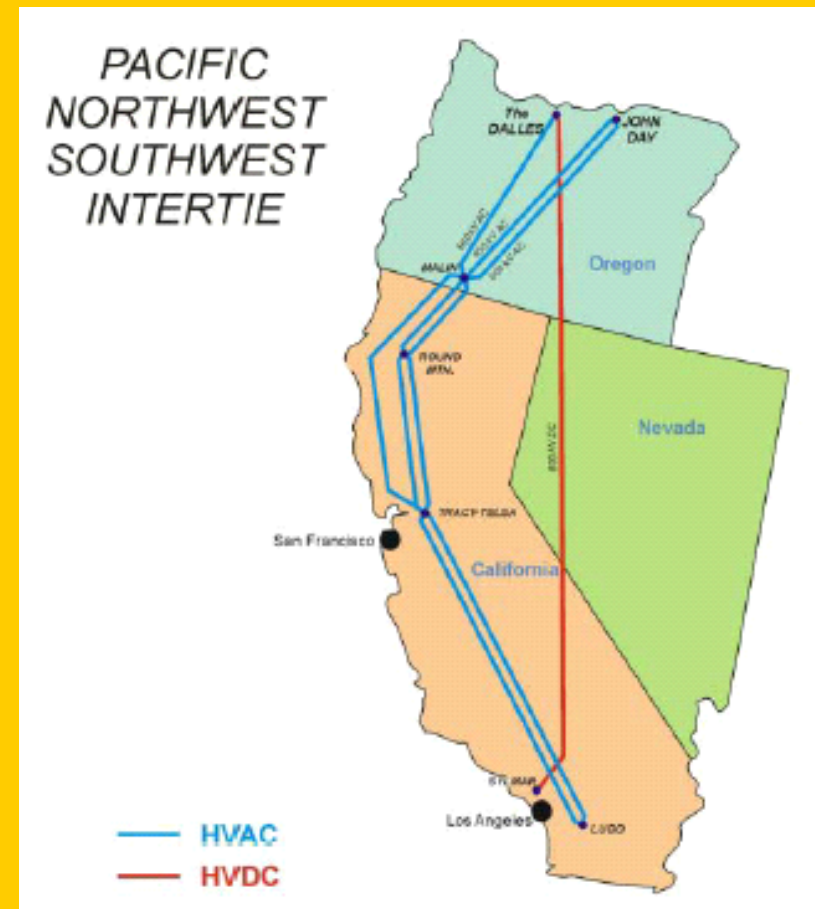
# Benefits of HVDC Systems

- Lower Cost at higher power and longer distances
- Lower Losses
- Stability
- Suited for Underwater Transmission



# Symbols and Capabilities of Power Semiconductor Devices


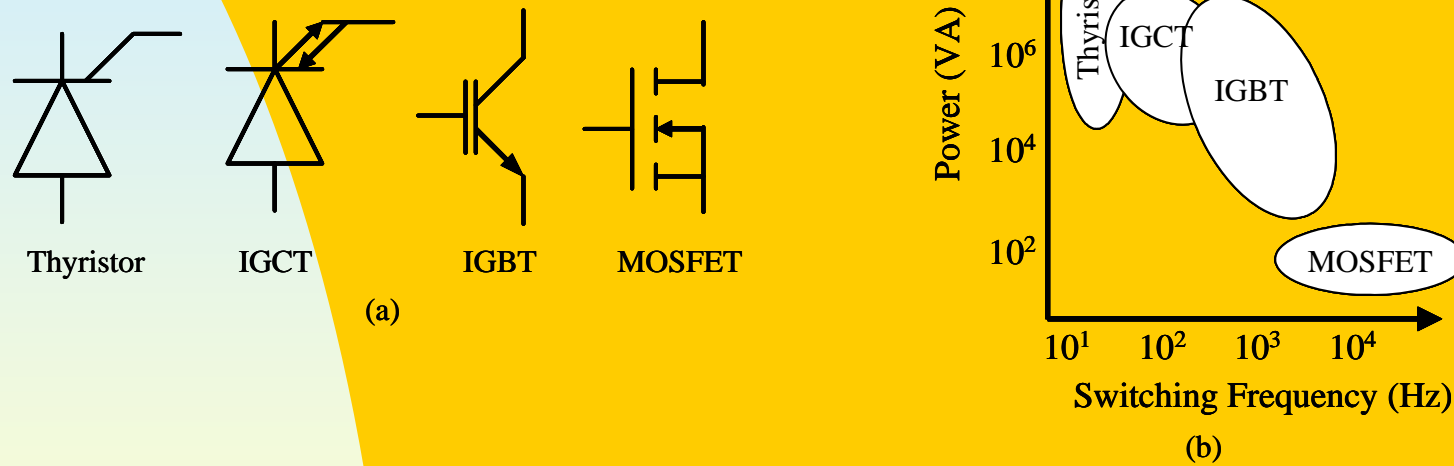


Fig. 7-1 Power semiconductor devices.
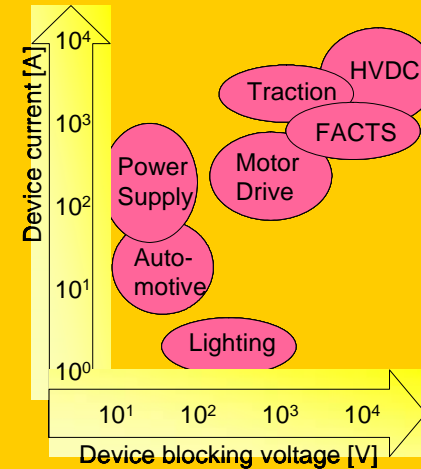
# Power Semiconductor Devices and Applications



(a)



(b)

Figure 7-2 Power semiconductor devices: (a) ratings (source: Siemens), (b) various applications (source: ABB).

# HVDC System

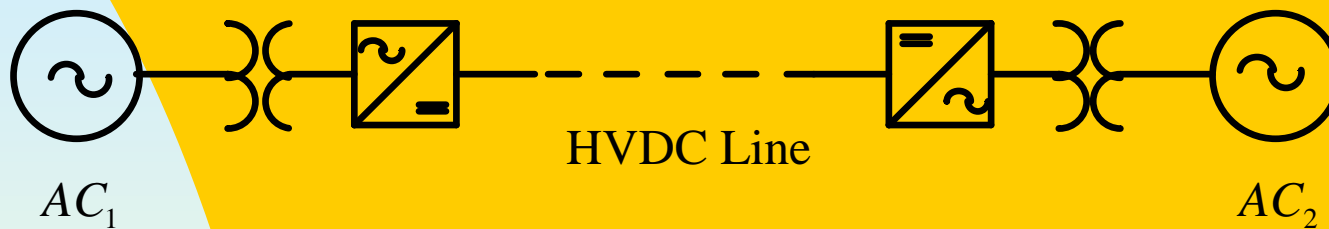


Fig. 7-3 HVDC system – one-line diagram.

# HVDC Systems: Voltage-Link and Current-Link

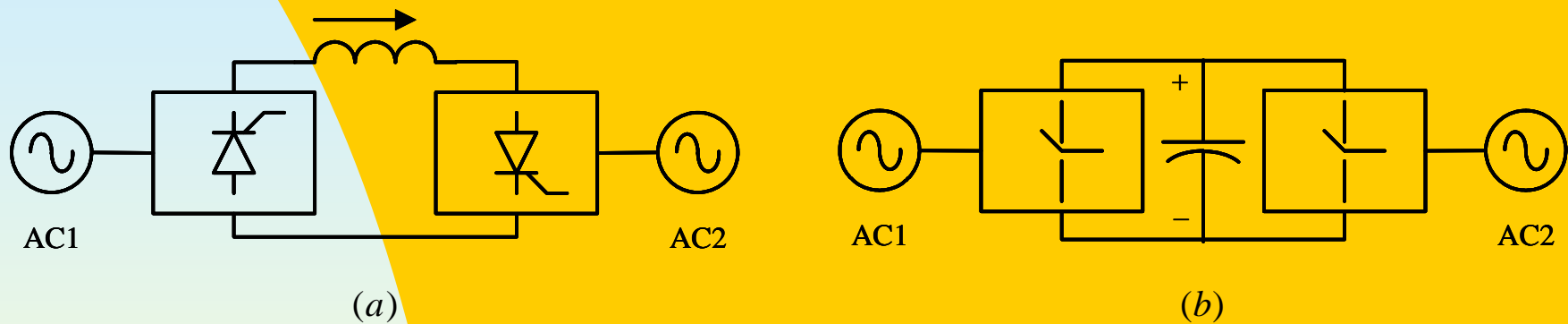


Fig. 7-4 HVDC systems: (a) Current-Link, and (b) Voltage-Link.

# HVDC Projects in North America

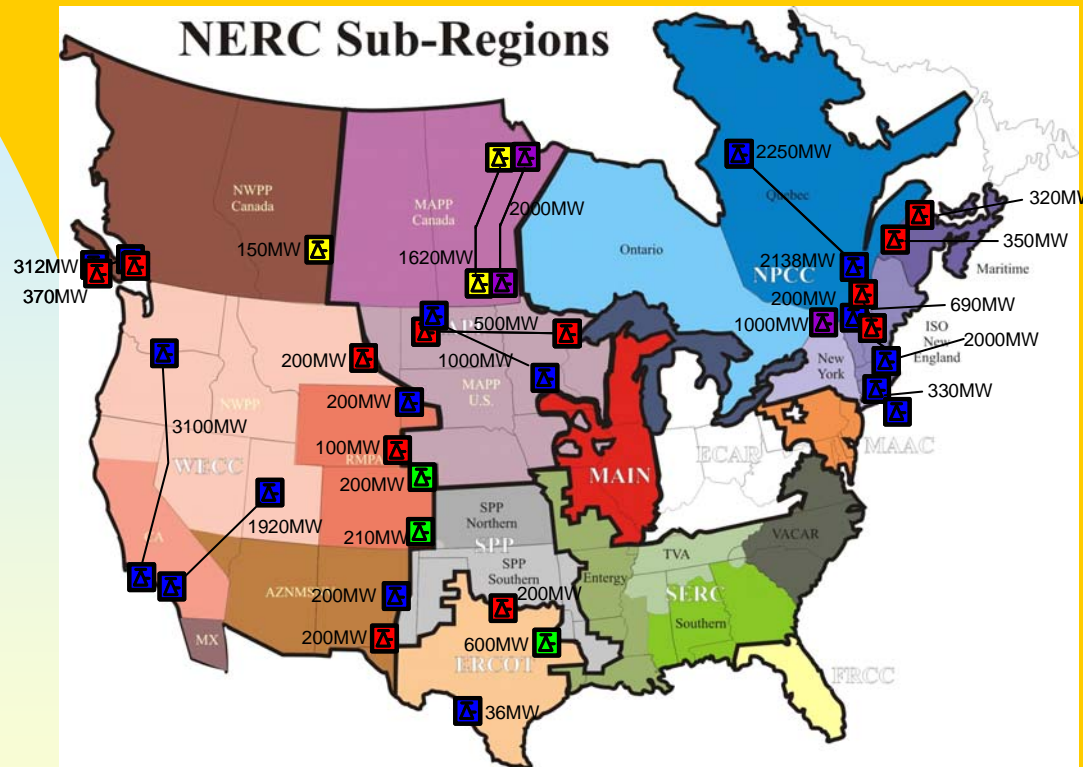


Fig. 7-5 HVDC projects, mostly current-link systems, in North America [source: ABB]



# Current-Link HVDC System



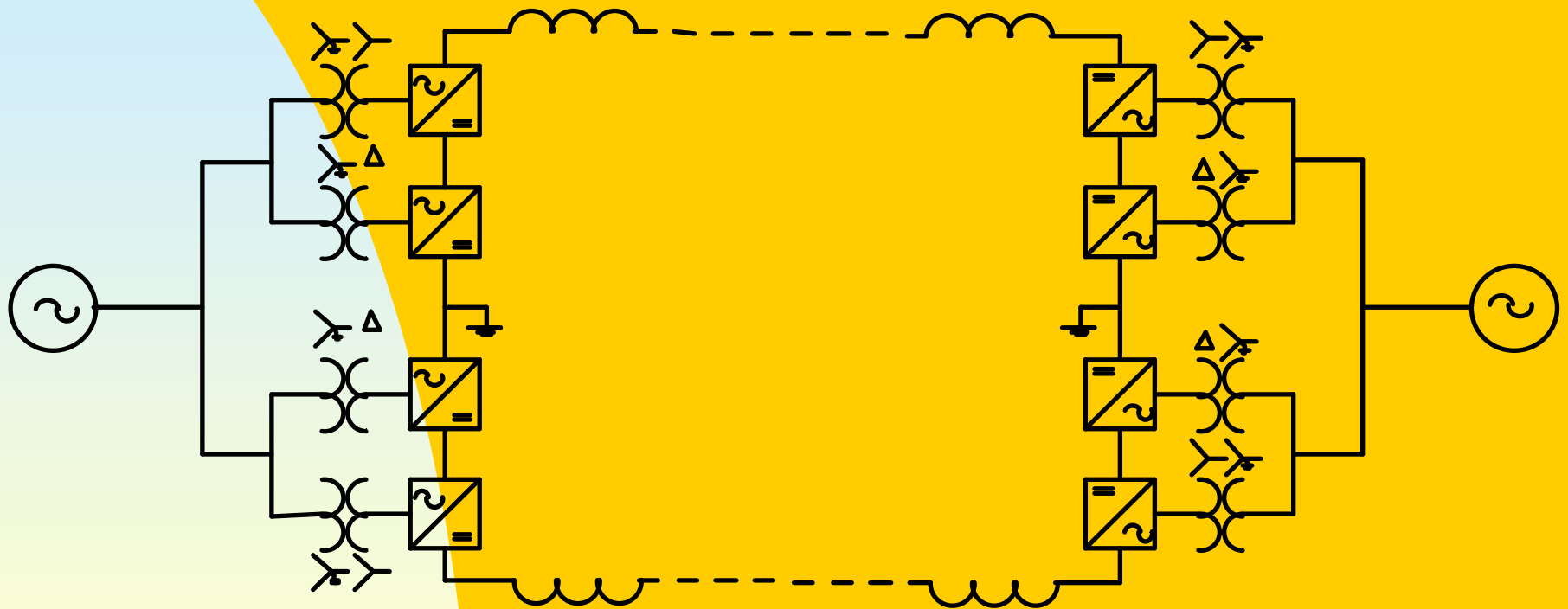


Fig. 7-6 Block diagram of a current-link HVDC system.

# Diodes


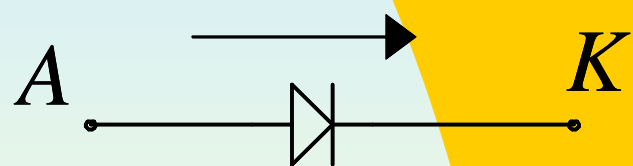


(a)


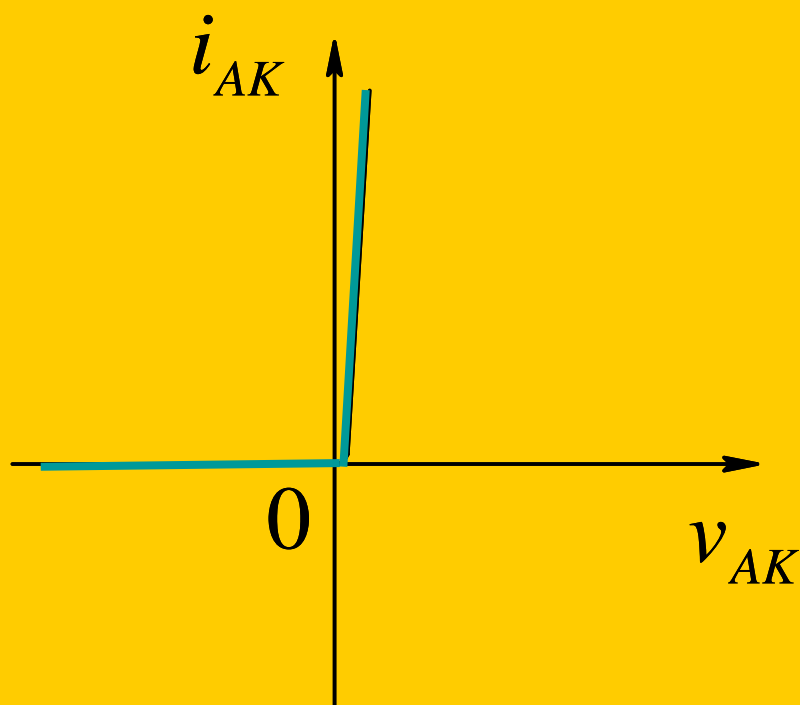


(b)

# Thyristors

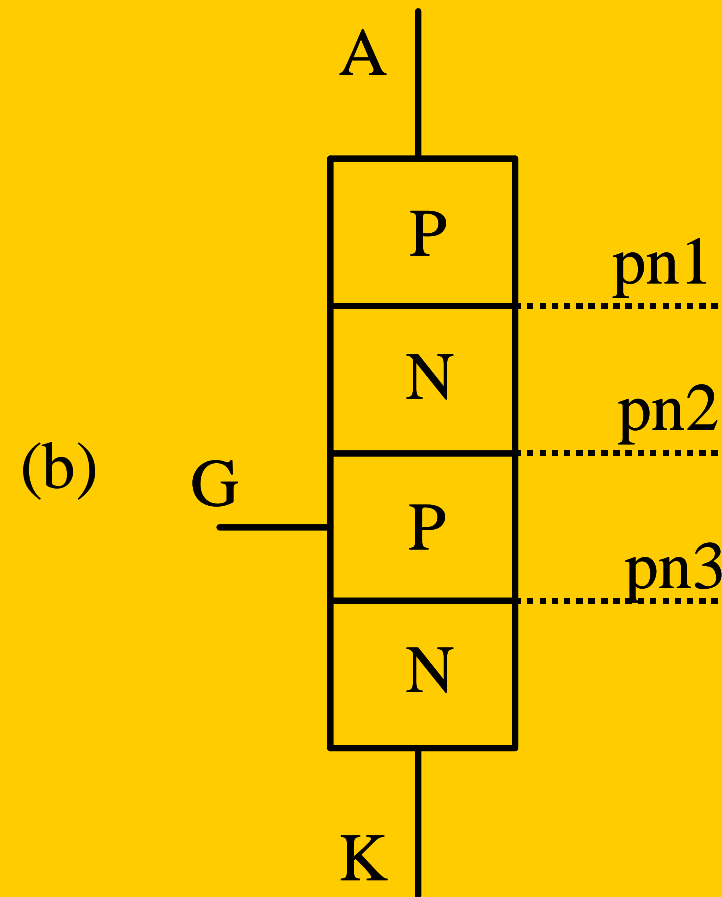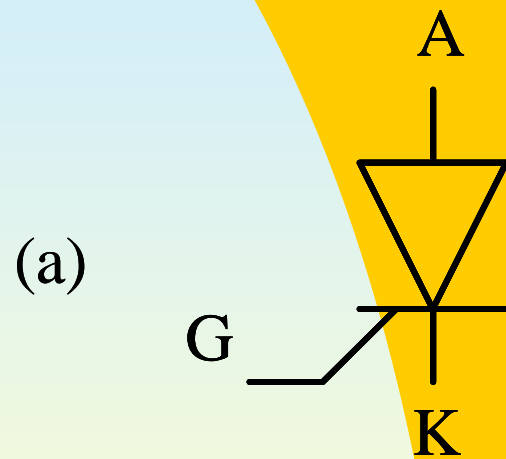

# A Primitive Resistive Circuit

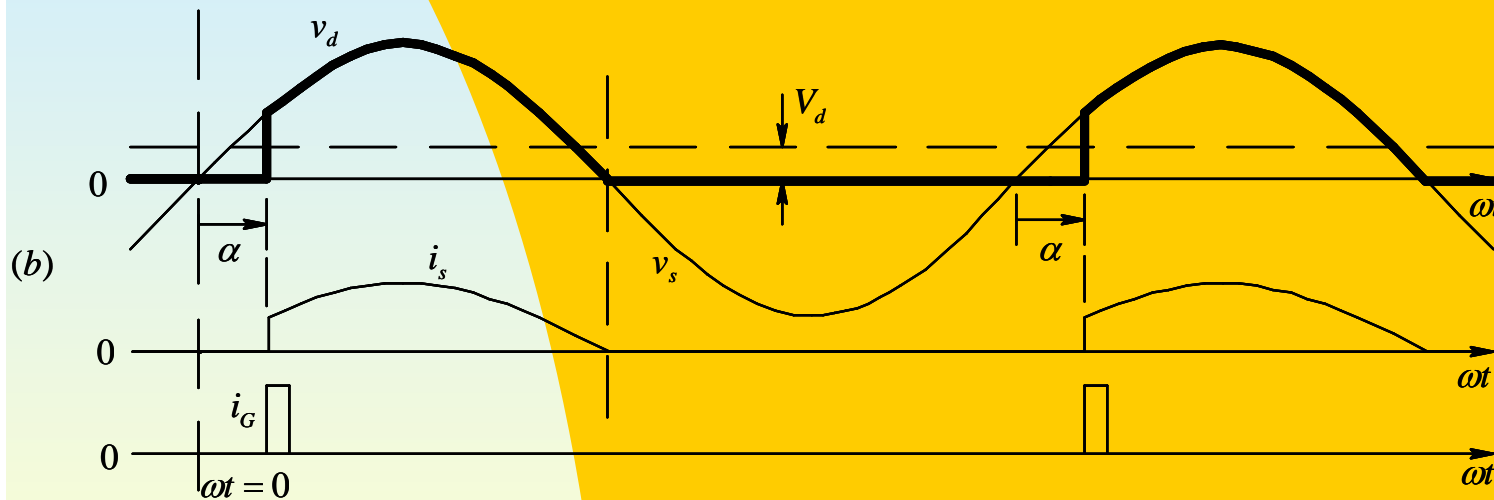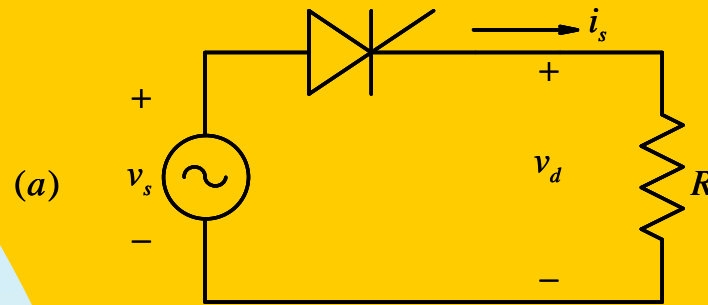

$$V_d = \frac{1}{2\pi} \int_{\alpha}^{\pi} \hat{V}_s \sin \omega t \cdot d(\omega t) = \frac{\hat{V}_s}{2\pi} (1 + \cos \alpha)$$

# With Series Inductance:

