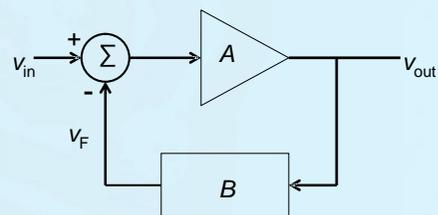


Chapter 32

Oscillators

Basics of Feedback

- Block diagram of feedback amplifier
- Forward gain, A
- Feedback, B
- Summing junction, Σ
- Useful for oscillators



Basics of Feedback

- Op-amps
 - Inverting & non-inverting
 - Negative feedback 180° out of phase w/input
 - High input impedance
 - Low output impedance
 - Wide bandwidth
 - Stable operation

3

Basics of Feedback

- Oscillators
 - Positive feedback
 - In-phase with input
 - Unstable

4

Basics of Feedback


- Block diagram analysis

$$v_e = v_{in} - v_f$$

$$v_{out} = A(v_{in} - v_f)$$

$$v_f = Bv_{out}$$

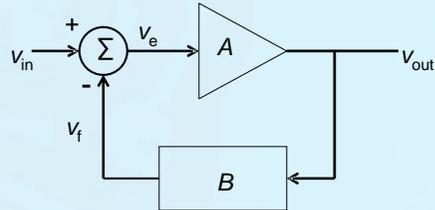
$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + AB}$$



5

Basics of Feedback

- Inverting amplifier

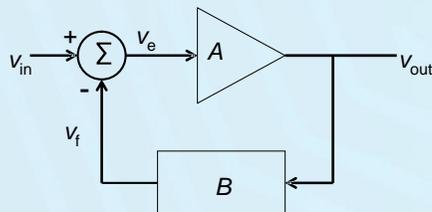

$$v_e = -v_{in} - v_f$$

$$v_{out} = A(-v_{in} - v_f)$$

$$v_f = Bv_{out}$$

$$\frac{v_{out}}{v_{in}} = -\frac{A}{1 + AB}$$

$$\frac{v_{out}}{v_{in}} = -\frac{1}{\frac{1}{A} + B} \approx \frac{1}{B}$$

$$B = \frac{R_1}{R_F}$$

6

Relaxation Oscillator

- Square wave generator
- Composed of
 - Schmitt trigger comparator
 - Positive feedback
 - RC circuit to determine period

7

Relaxation Oscillator

- Schmitt Trigger
 - R_1 and R_2 form a voltage divider
 - Portion of output applied at + input
 - Hysteresis: output dependent on input and previous value of input

8


Relaxation Oscillator

- Schmitt Trigger
 - Hysteresis: upper and lower trip points
 - Can use a voltage follower for adjustable trip points

9

Relaxation Oscillator


- Schmitt trigger

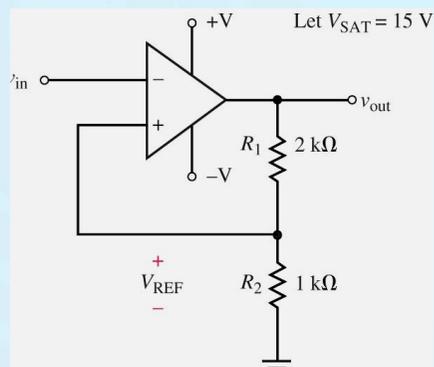

10

Relaxation Oscillator

- Schmitt Trigger Relaxation Oscillator

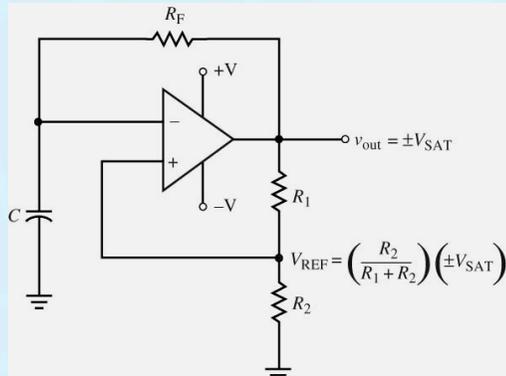

11

Relaxation Oscillator

- R_1 and R_2 voltage divider

$$V_{REF} = \frac{R_2}{R_1 + R_2} (\pm V_{SAT})$$

- Capacitor charges through R_F
- $V_C < +V_{SAT}$ then C charges toward $+V_{SAT}$
- $V_C > -V_{SAT}$ then C charges toward $-V_{SAT}$

12

Relaxation Oscillator

- Schmitt Trigger Relaxation Oscillator Equations

$$\tau = R_F C$$

$$v_C(t) = (V_F - V_O) \left(1 - e^{-\frac{t}{RC}}\right)$$

$$T = 2R_F C \ln \left(1 + \frac{2R_2}{R_1}\right)$$

13

Wien Bridge Oscillator

- For a sinusoidal oscillator output
 - Closed loop gain ≥ 1
 - Phase shift between input and output = 0° at frequency of oscillation
- With these conditions a circuit
 - Oscillates with no external input
- Positive feedback = regenerative feedback

14


Wien Bridge Oscillator

- Regenerative oscillator
 - Initial input is small noise voltage
 - Builds to steady state oscillation
- Wien Bridge oscillator
 - Positive feedback, RC network branch
 - Resistor branch establish amplifier gain

15

Wien Bridge Oscillator

- Circuit

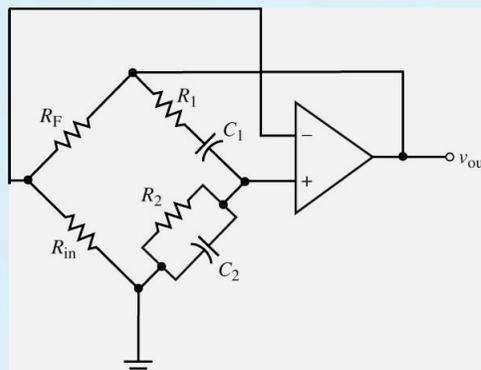

16

Wien Bridge Oscillator

- Equations

$$f_0 = \frac{1}{2\pi\sqrt{R_1R_2C_1C_2}} = \text{Output frequency}$$

$$B = \frac{R_2C_1}{R_1C_1 + R_2C_2 + R_2C_1}$$


if $R_1 = R_2$ and $C_1 = C_2$ then

$$f_0 = \frac{1}{2\pi RC} \text{ and } B = \frac{1}{3}$$

17

Wien Bridge Oscillator

- Another form of Wien Bridge

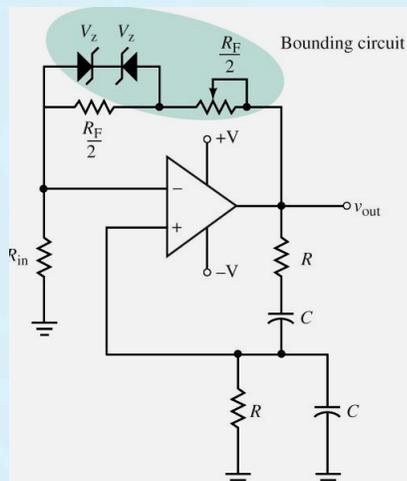

18

Wien Bridge Oscillator

- For a closed-loop gain, $AB = 1$
 - Op-amp gain ≥ 3
- Improved circuit
 - Separate R_F into 1 variable and 1 fixed resistor
 - Variable: minimize distortion
 - Zener Diodes: limit range of output voltage

19

Phase-Shift Oscillator

- Three-section R - C network
 - $\approx 60^\circ$ per section
 - Negative FB = 180°
 - $180^\circ + (60^\circ + 60^\circ + 60^\circ) = 360^\circ =$
Positive FB


$$f_0 = \frac{1}{2\pi\sqrt{6}RC} \text{ Output frequency}$$

$$A = 29 \text{ Required voltage gain}$$

20

Phase-Shift Oscillator

- Circuit

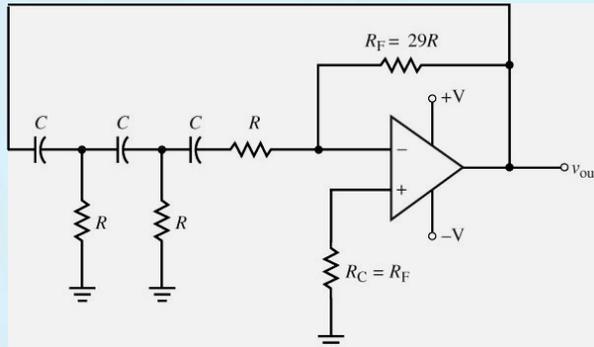

21

LC Oscillators

- LC circuits can produce oscillations
- Used for
 - Test and measurement circuits
 - RF circuits

22

LC Oscillators

- Named after pioneer engineers
 - Colpitts
 - Hartley
 - Clapp
 - Armstrong


23

LC Oscillators

- Colpitts oscillator
 - f_s = series resonance
 - f_p = parallel resonance
 - L - C network \rightarrow 180° phase shift at f_p

24

LC Oscillators

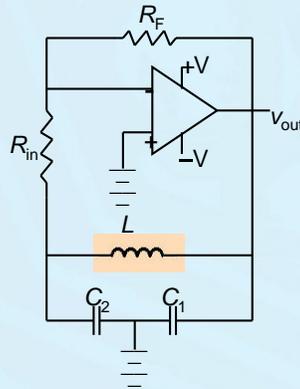

25

LC Oscillators

- Equations

$$\text{Impedance: } Z(s) = \frac{1 + s^2 LC_2}{s(C_1 + C_2) \left(1 + \frac{s^2 LC_1 C_2}{C_1 + C_2} \right)}$$

$$\text{Oscillator frequency: } f_0 = \frac{1}{2\pi \sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$

26

LC Oscillators


- Hartley oscillator
 - Similar to Colpitts
 - L and C 's interchanged
 - Also have f_s and f_p

27

LC Oscillators

$$Z(s) = \frac{sL_1(1 + s^2L_2C)}{1 + s^2(L_1 + L_2)C}$$
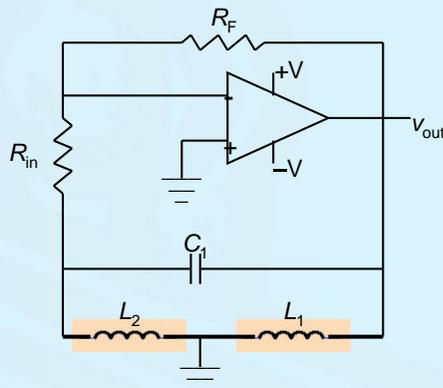
$$f_0 = \frac{1}{2\pi\sqrt{(L_1 + L_2)C}}$$



28


Crystal Oscillators

- Quartz crystals
- Mechanical device
- Higher frequencies (>1 MHz)
- Stability
- Accuracy
- Reliability
- Piezoelectric effect

29

Crystal Oscillators

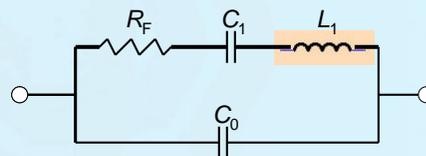
- Electrical model
 - Both have parallel and series resonance
- Symbol
 - Quartz crystal
 - metal plates



30


Crystal Oscillators

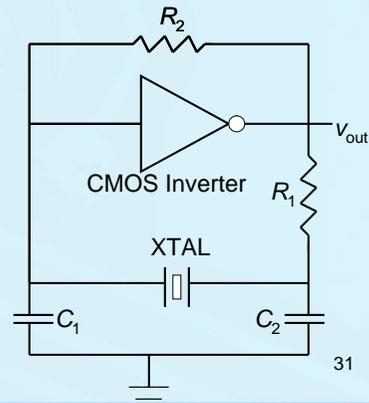- Impedance varies with frequency
- Square wave crystal oscillator circuit
- Choose C_1 and C_2
 - Oscillation frequency between f_s and f_p



555 Timer

- IC
 - Internal circuit

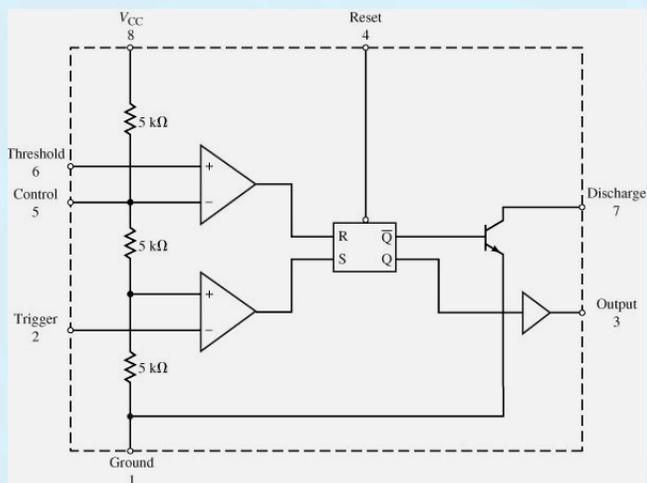

555 Timer

- Usage
 - Monostable timing
 - Astable mode = relaxation oscillator
 - Trigger voltage
 - Control voltage
 - Threshold voltage
 - R-S flip-flop

33

555 Timer


- Relaxation oscillator

$$T_1 = \ln(2) * (R_B C)$$

$$T_2 = \ln(2) * (R_A + R_B) C$$


$$T = \ln(2) * (R_A + 2R_B) C$$

$$f = \frac{1}{T}$$

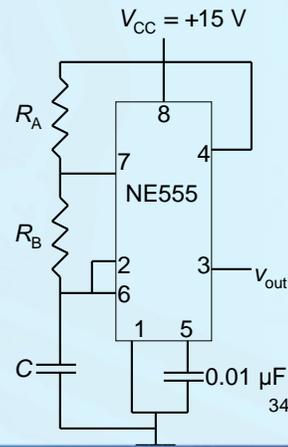


555 Timer

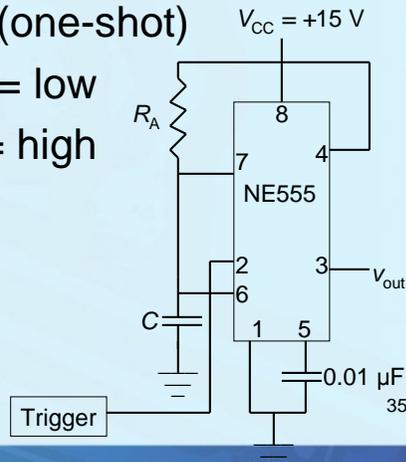- Monostable Circuit (one-shot)
- Trigger high $\rightarrow v_{out} = \text{low}$
- Trigger low $\rightarrow v_{out} = \text{high}$



Voltage Controlled Oscillator- VCO

$$\Delta f_{out} \propto \Delta V_{in}$$

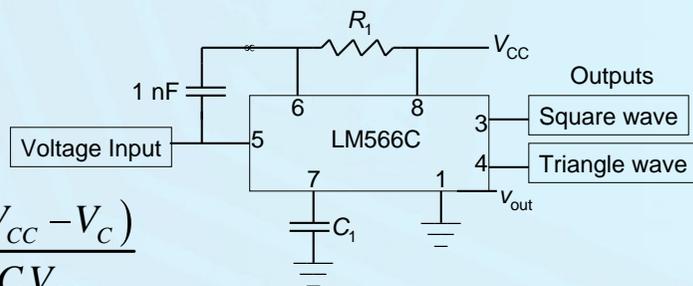

$$f_o = \frac{2.4(V_{CC} - V_C)}{R_1 C_1 V_{CC}}$$

36

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.