

Series/Parallel Circuit Simplification: Kirchoff, Thevenin & Norton

Session 1d of Basic Electricity
A Fairfield University E-Course
Powered by LearnLinc

Basic Electricity

Two Parts

- Electron Flow and Resistance
 - 5 on-line sessions
 - Lab
- Inductance and Capacitance
 - 5 on-line sessions
 - Lab

Mastery Test, Part 1

Basic Electricity (Continued)

- **Text:** “Electricity One-Seven,” Harry Mileaf, Prentice-Hall, 1996, ISBN 0-13-889585-6 (Covers several Modules and more)
- **References:**
 - “Digital Mini Test: Principles of Electricity Lessons One and Two,” SNET Home Study Coordinator, (203) 771-5400
 - [Electronics Tutorial](#) (Thanks to Alex Pounds at alex_tb@hotmail.com)
 - [Electronics Tutorial](#) (Thanks to Mark Sokos at sokos@desupernet.net)

Section 1:

Electron Flow and Resistance

- **OBJECTIVES:** This section introduces five basic electrical concepts as well as the underlying atomic structure of electrical materials.
 - Conductance(G),
 - Resistance (R),
 - Current (I),
 - Power (P), and
 - Electromotive force (E) or voltage (V).

Section 1 Schedule:


Session a – 03/04 <i>03/06 & 03/08 were Math Tutorials</i>	Atoms, Charge and Current Conductivity (G), Electric Fields and Electromotive Force (EMF)	Text 1.1 – 1.39 Text 1.40 – 1.68
Session b – 03/11	Resistance (R), Conductance (G), Ohms Law (Ω) & Power (Watts)	Text 2.1 – 2.52
Session c – 03/13 (lab - 03/16, sat.)	Resistors in Series and Parallel and Working with Equations	Text 2.53 – 2.98
Session d – 03/18	Series / Parallel Simplification Kirchoff, Thevenin & Norton	2.99 – 2.115 2.116 – 2.133
Session e – 03/20	Review: The Water Model	1.42, 1.63, 2.5, 2.129 Sokos

Session 1c Review

- Resistors in series add
 - $R_{\text{total}} = R_1 + R_2 + R_3$
- Resistors in parallel add as reciprocals
 - $1/R_{\text{total}} = 1/R_1 + 1/R_2 + 1/R_3$
- Equations
 - The same operation on both sides of the equal sign leaves the equation valid.
 - You can add or subtract valid equations and get another valid equation.


Series-Parallel Circuits

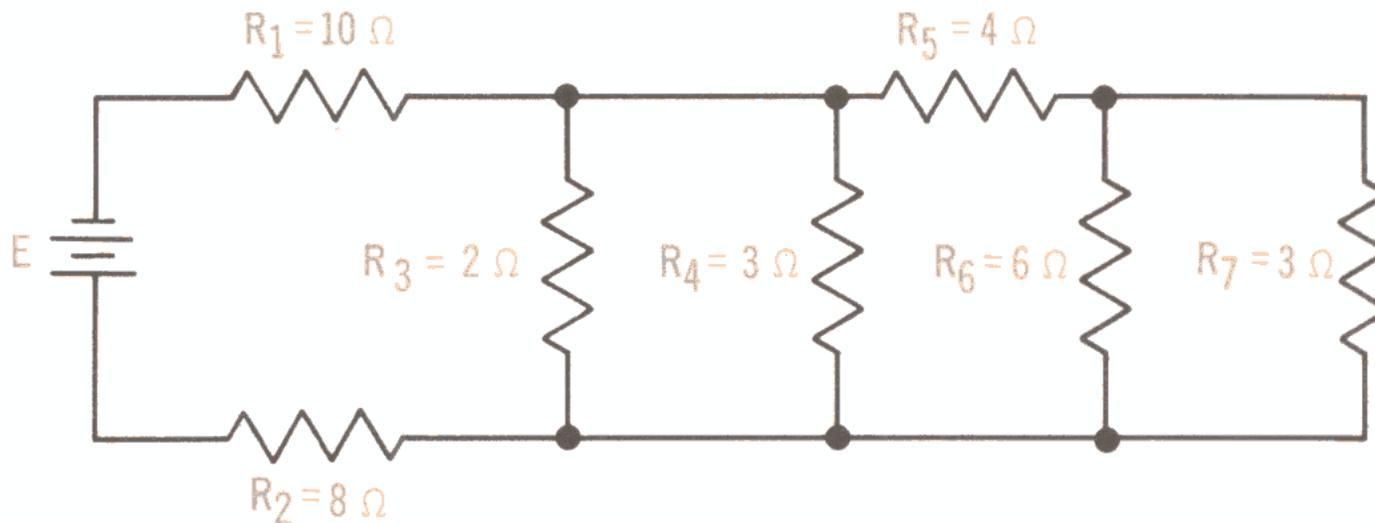- A mixture of series and parallel circuit elements
- A sequence of small steps will find an “equivalent” circuit.




S-P Step 1

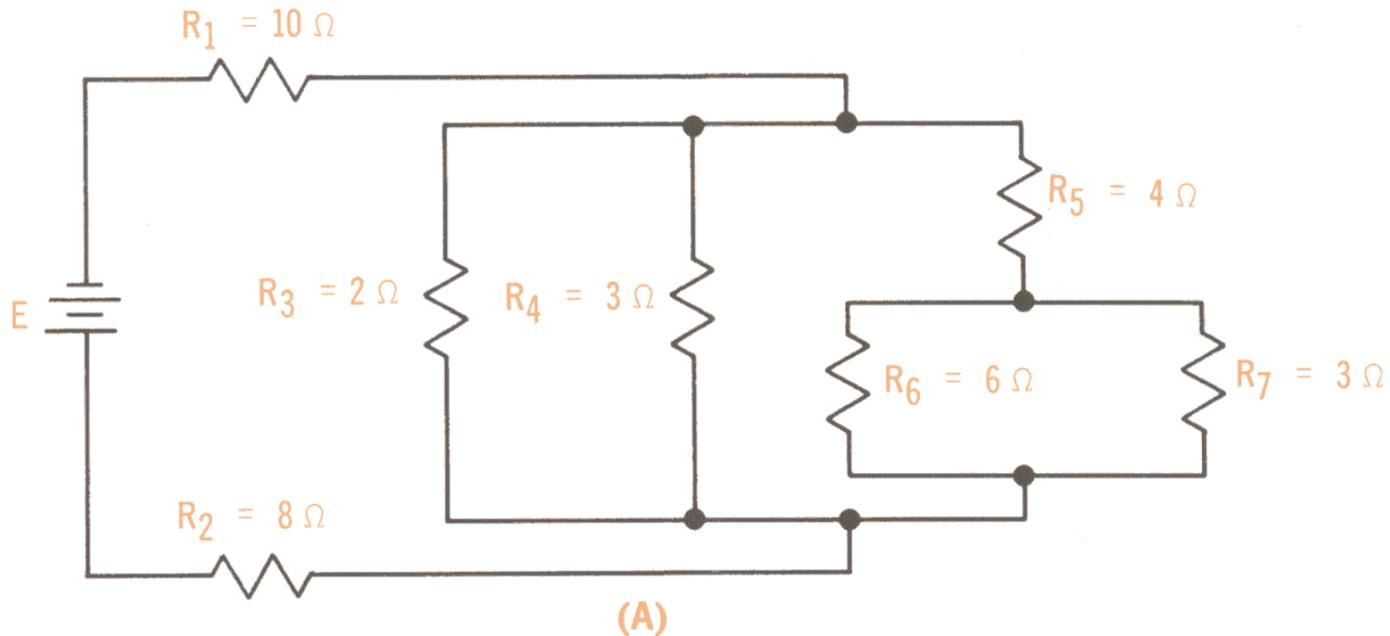- Redraw the circuit to show series and parallel elements clearly.




S-P Step 2

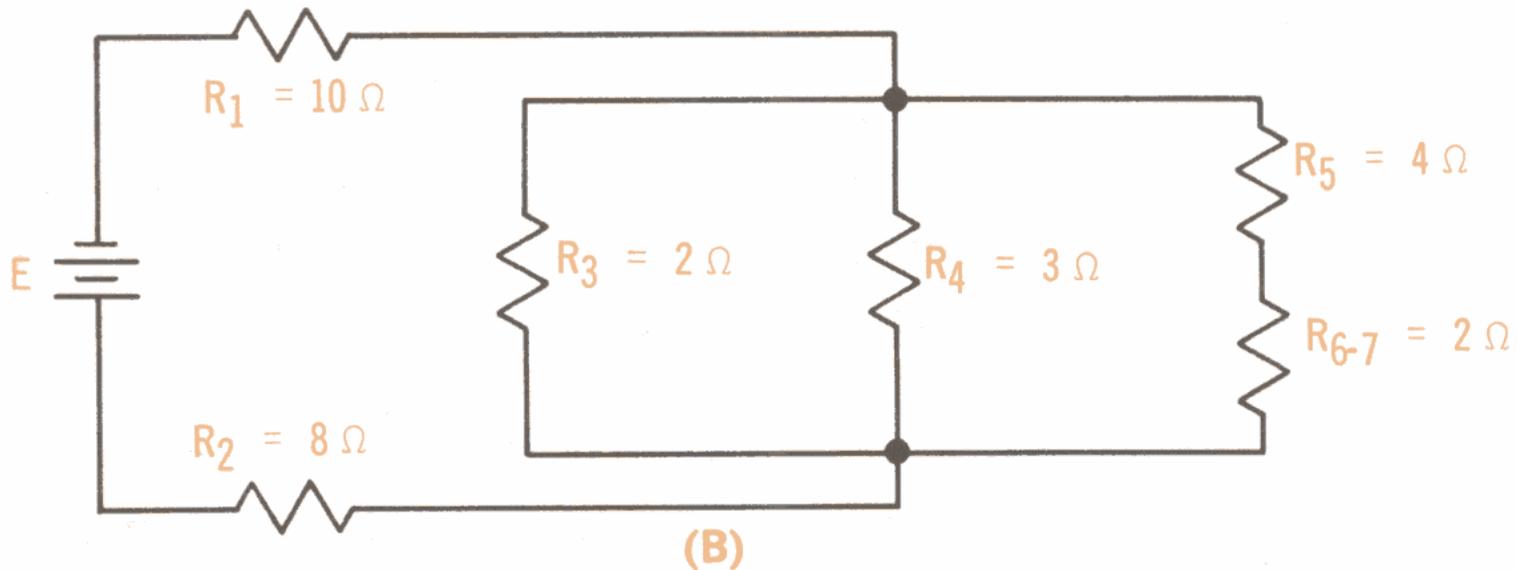- Combine some elements to simplify the circuit
 - Here R_6 and R_7 (parallel) are replaced with their equivalent resistance (2 Ohms)




S-P Step 3

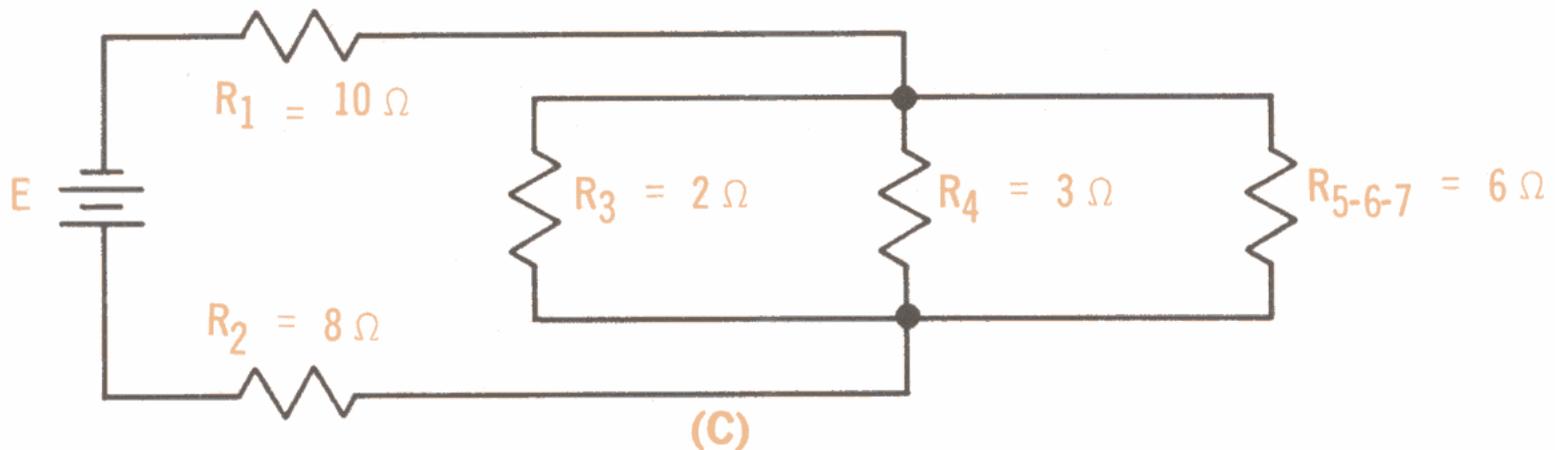- Now we can add R_5 and R_{6-7} (series) to further simplify the circuit
- Now we have three resistors in parallel




S-P Step 4

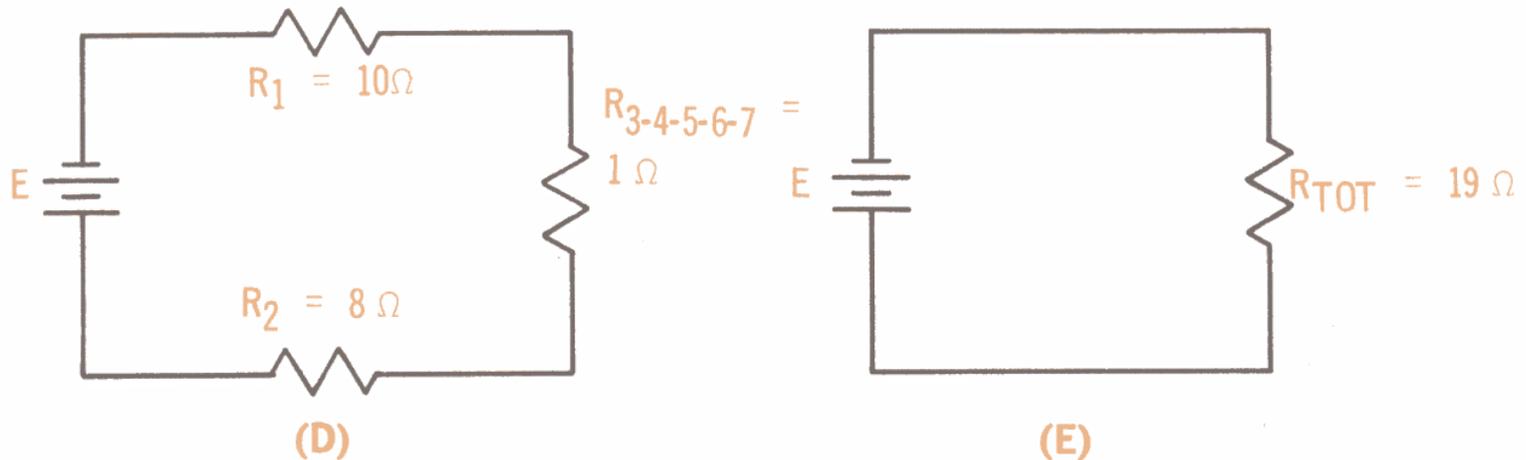- Replacing R_3 , R_3 and R_{5-6-7} (parallel) with their equivalent resistance (1 Ohm) yields a simple series circuit which simplifies by adding and we're done.




S-P: Example 1

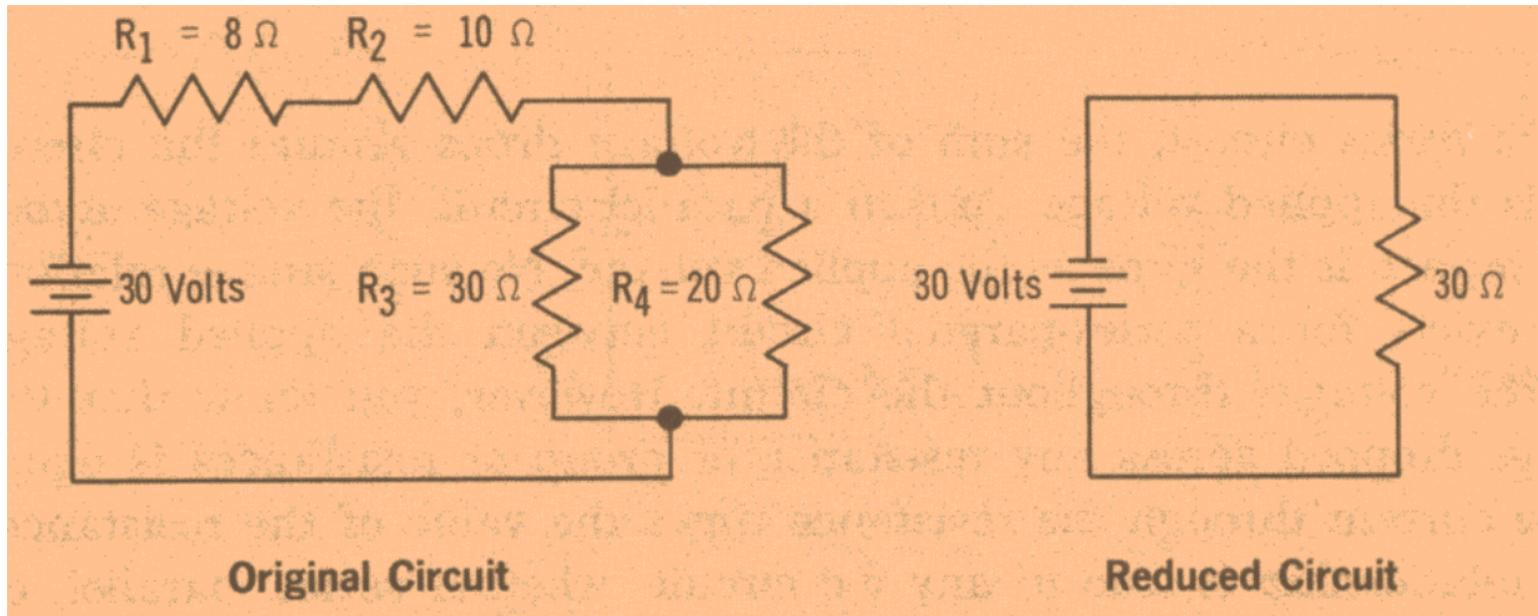- $1/30 + 1/20 = 5/60 = 1/12$
- $8 + 10 + 12 = 30$ Ohms
- $I_{\text{total}} = 30 \text{ volts} / 30 \text{ ohms} = 1 \text{ amp}$




S-P: Example 2

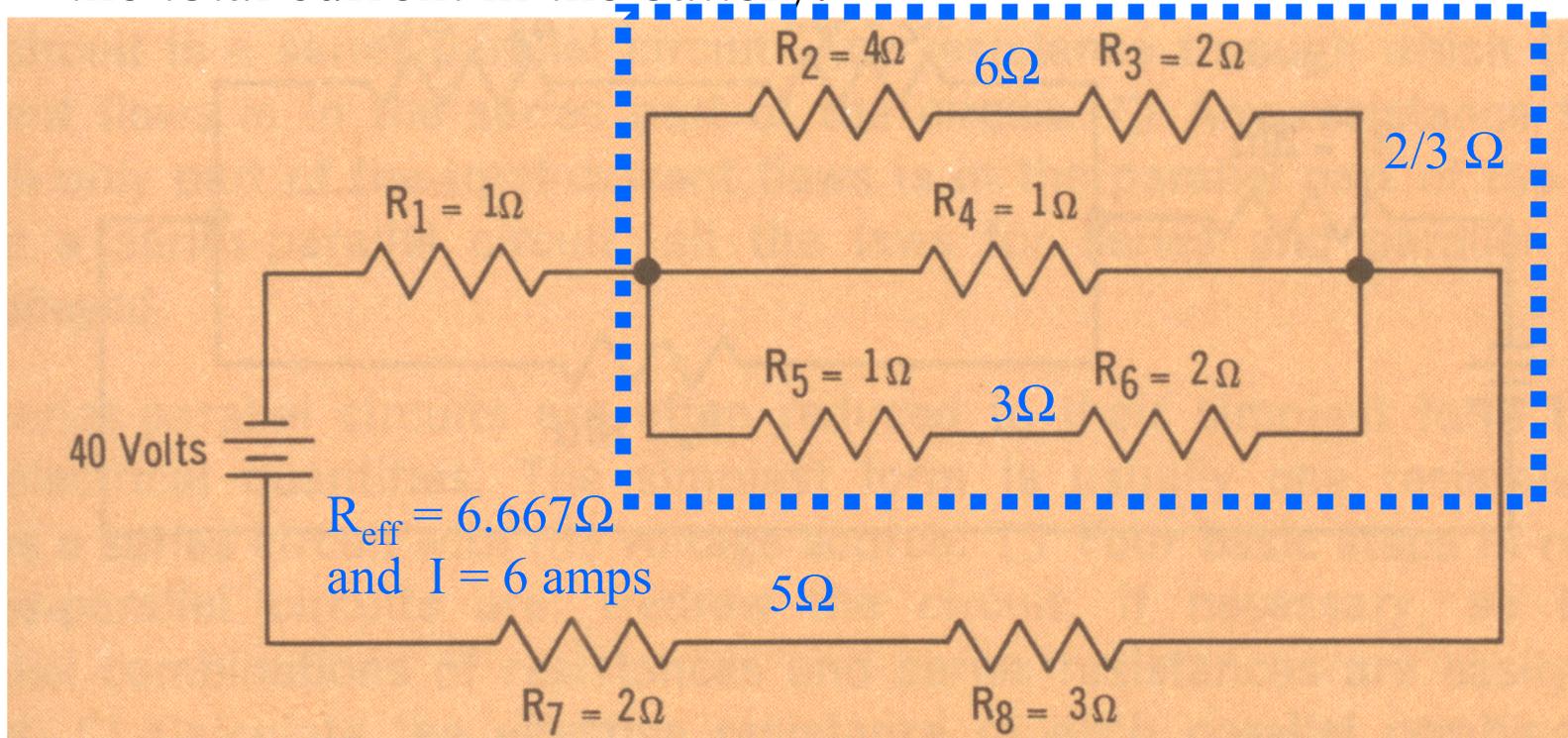- Find the equivalent resistance and use Ohm's law to get the total current in the battery.




S-P Example 3

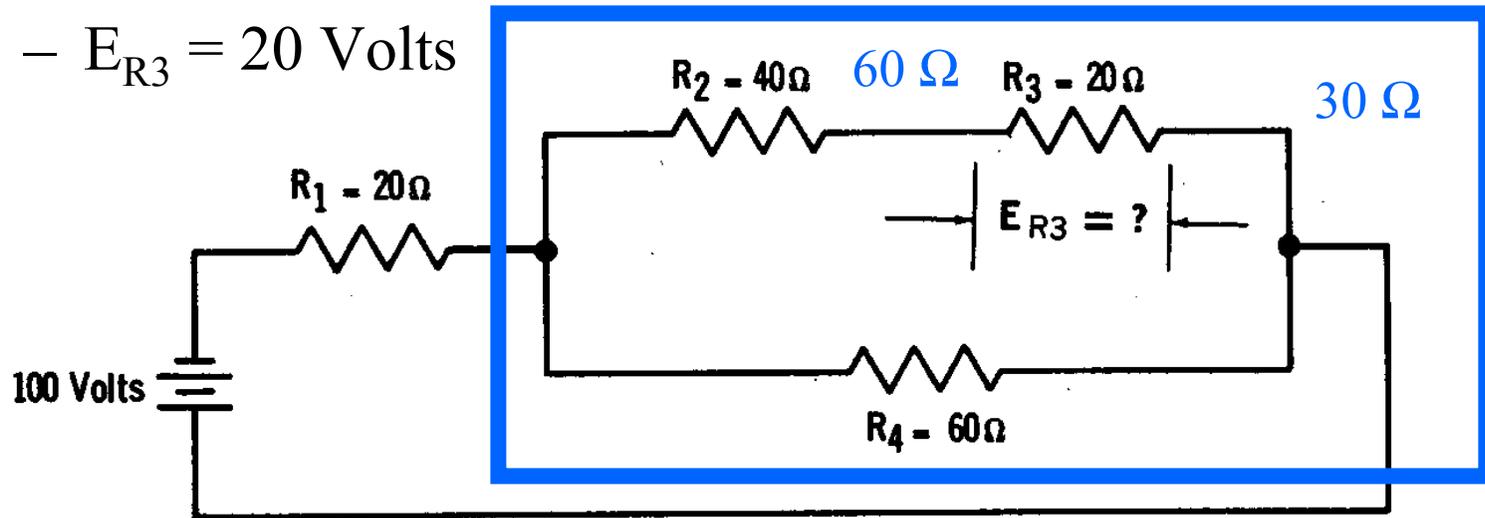- Small steps to find E_{R3}
 - $R_{eq} = 50 \text{ Ohms}$, $I_{total} = 2 \text{ Amps}$
 - $I_{R3} = 1 \text{ Amp}$ ($1/2 I_{total}$)
 - $E_{R3} = 20 \text{ Volts}$




Voltage Divider

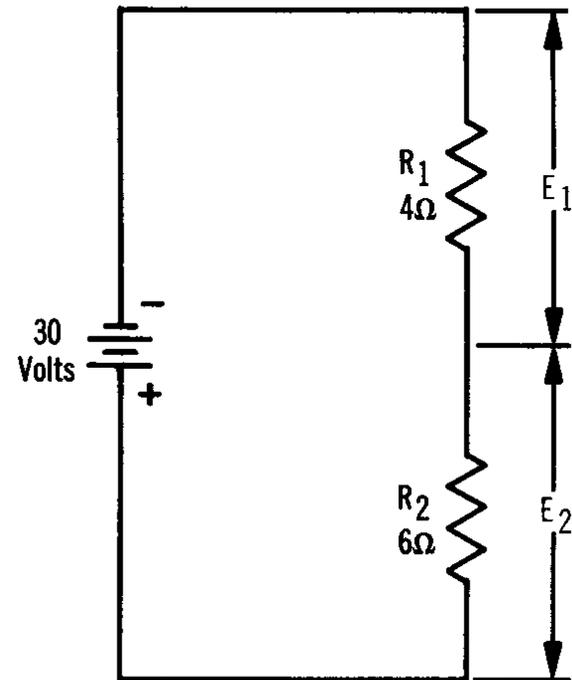- Since the total current flows through both resistors, the bigger resistor has the larger share of the total voltage.
- $E_2 = E_{in} * R_2 / R_{total}$



Current Divider

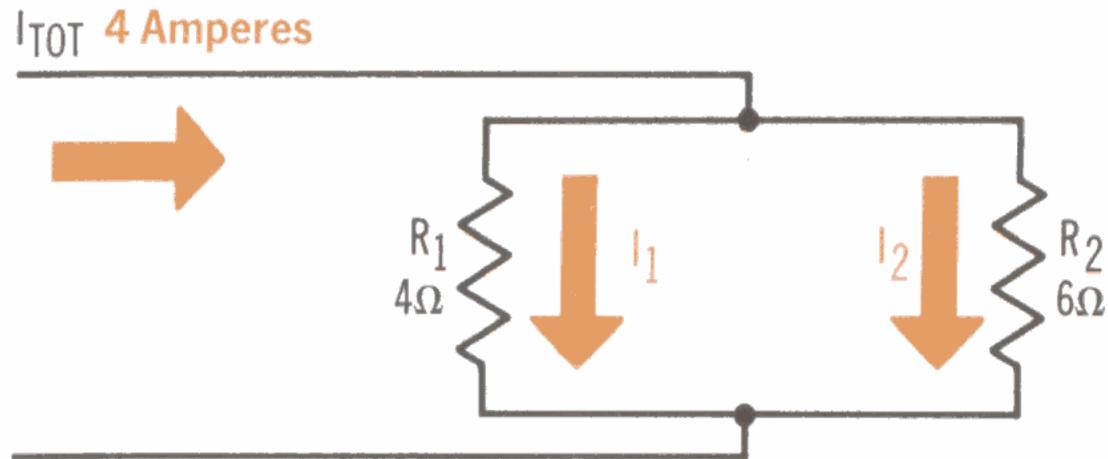
- The smaller resistor gets the larger share of the current.
 - $I_1 = I_{\text{total}} * 1/R_1 / (1/R_1 + 1/R_2)$ or
 - $I_1 = I_{\text{total}} * R_2 / R_{\text{total}}$



Kirchoff's Voltage Law


- The sum of all the voltages around a “loop” is zero
- Be careful to take signs into account
- Starting at the top left corner and going clockwise:

$$20 * I - 75 + 10 * I + 60 = 0$$

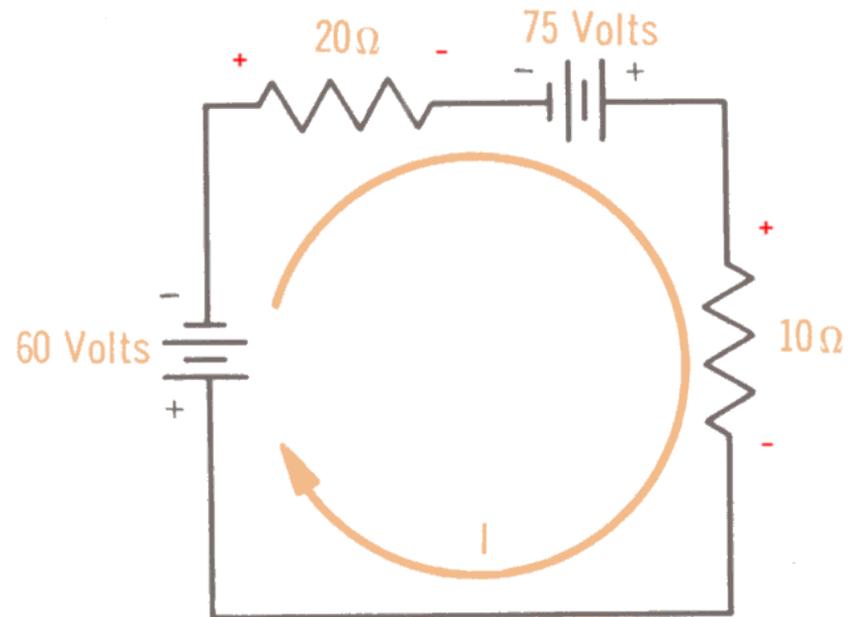


Kirchoff's Current Law

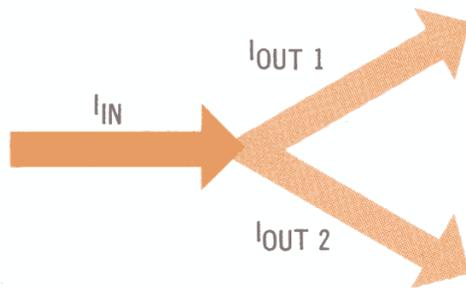- The sum of all currents into a node equals zero.
- Again watch out for signs (direction of current flow)




$$I_{IN} = I_{OUT 1} + I_{OUT 2}$$

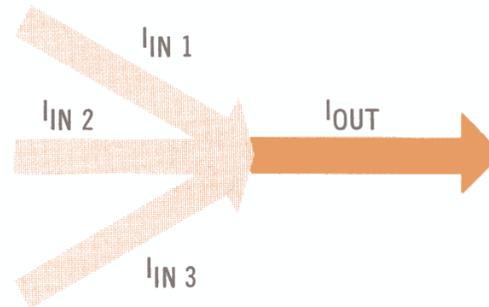

$$I_{IN 1} + I_{IN 2} + I_{IN 3} = I_{OUT}$$


Using Kirchoff

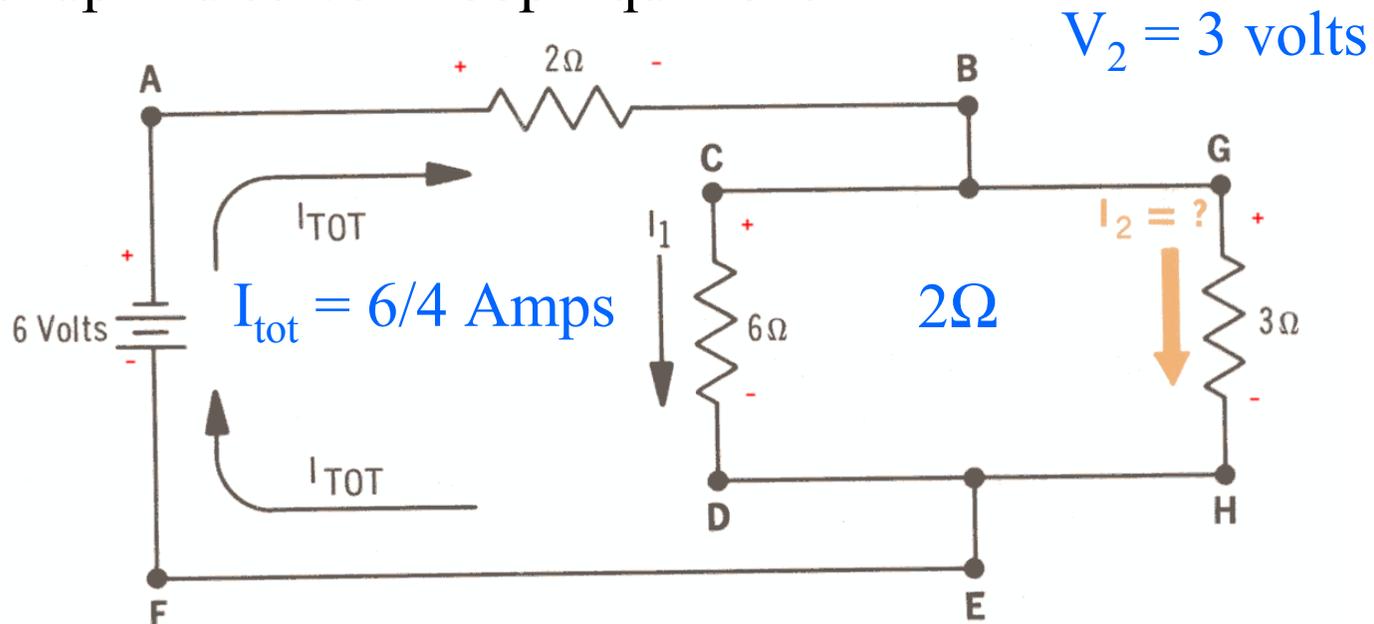- Use voltage divider or,
- Kirchoff's Voltage Law and a current divider, or
- Set up and solve "Loop Equations"






Superposition

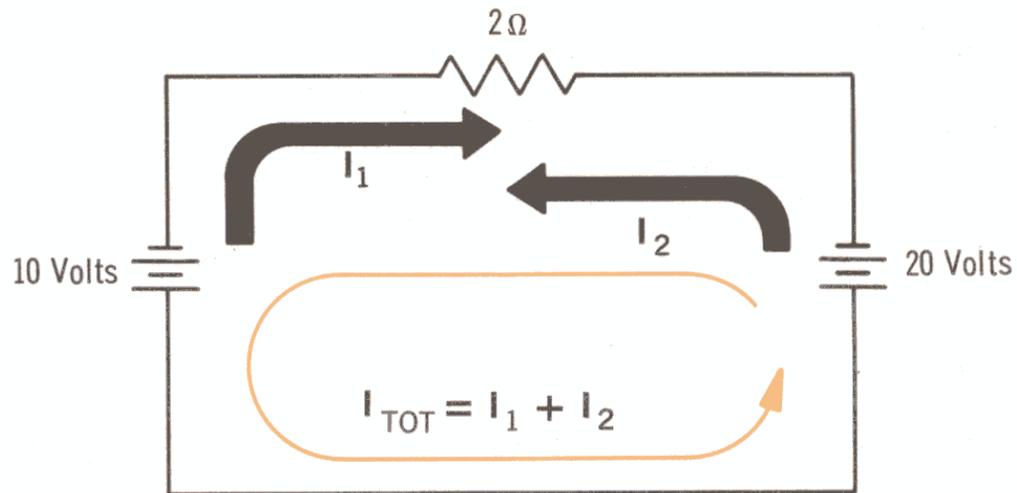- Linear systems (R, L and C circuits are linear)
 - You can deal separately with each power source and then add the resulting currents to get the total result



Thevenin Equivalent Circuits

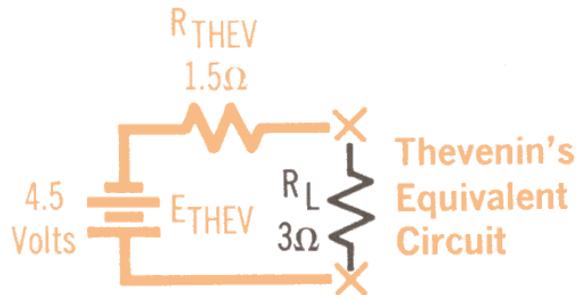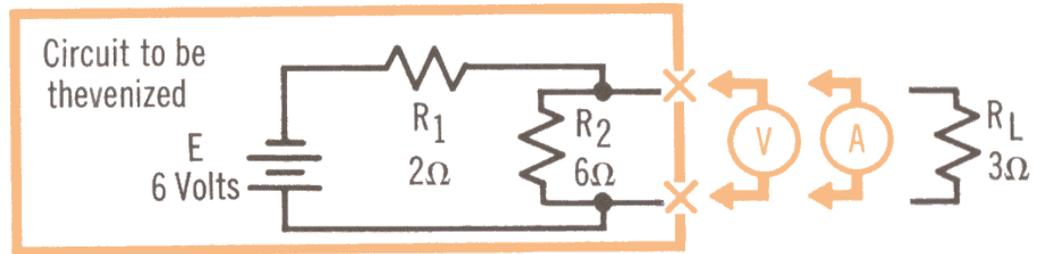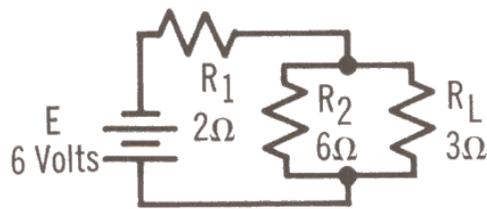


$$\text{Voltmeter reading} = E \left(\frac{R_2}{R_1 + R_2} \right) = 4.5 \text{ Volts} = E_{\text{THEV}}$$

$$\text{Ammeter reading} = E/R_1 = 6/2 = 3 \text{ Amperes} = I_{\text{THEV}}$$

$$E_{\text{THEV}}/I_{\text{THEV}} = 4.5/3 = 1.5 = R_{\text{THEV}}$$


$$I_L = \frac{E_{\text{THEV}}}{R_{\text{THEV}} + R_L} = \frac{4.5}{1.5 + 3} = 1 \text{ Ampere}$$

Thevenin (Continued)

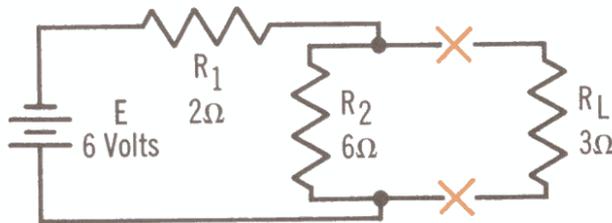


E_{THEV} is the voltage drop across R_2
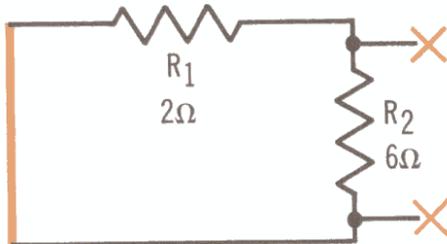
$$E_{THEV} = E \left(\frac{R_2}{R_1 + R_2} \right) = 6 (6/8) = 4.5 \text{ Volts}$$



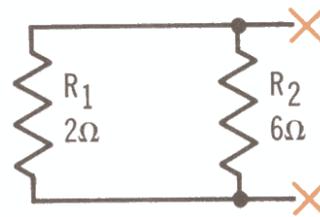
When the source voltage is shorted, this circuit becomes



this circuit




and reduces to R_{THEV}

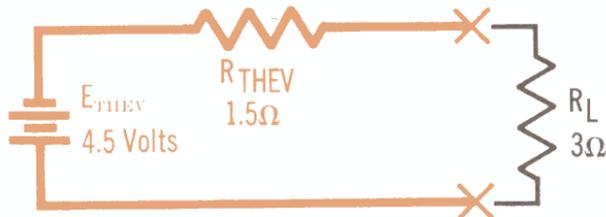


E_{THEV} and R_{THEV} are connected in series with R_L to produce Thevenin's equivalent circuit

Norton Equivalent Circuits

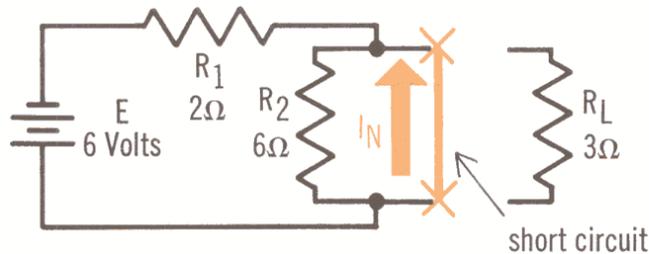

I_{NORTON} is the current through a short across the output terminals
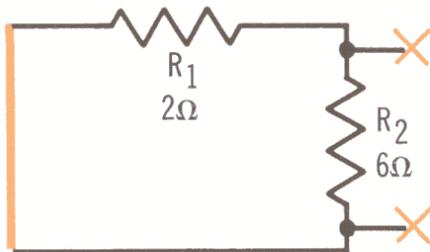
$$I_N = E/R_1 = 6/2 = 3 \text{ Amperes}$$



When the voltage source is shorted, this circuit becomes



this circuit



and reduces to R_{NORTON}



The constant current source, I_N feeds R_N and R_L in parallel to produce Norton's equivalent circuit

Next Class

- Module Review: “Electron Flow and Resistance”
 - Conductance(G),
 - Resistance (R),
 - Current (I),
 - Power (P),
 - Electromotive force (E) or voltage (V), and
 - DC Circuit Analysis.
- Quiz (via email to see how we’re doing)