

Multiplexers and Demultiplexers

Part 8d of
“Electronics and Telecommunications”
A Fairfield University E-Course
Powered by LearnLinc

Module: Digital Electronics

(in two parts)

- Text: “[Digital Logic Tutorial](#),” [Ken Bigelow](#),
<http://www.play-hookey.com/digital/>
- References:
 - “[Electronics Tutorial](#)”, part 10 (Thanks to Alex Pounds)
http://doctord.dyndns.org:8000/courses/Topics/Electronics/Alex_Pounds/Index.htm
- Contents:
 - 7 – Digital Electronics 1
 - 5 on-line sessions plus one lab and a quiz
 - 8 – Digital Electronics 2
 - 5 on-line sessions plus one lab and a quiz
- Mastery Test part 4 follows this Module

Section 7: Digital Electronics 1

- Logic gates and Boolean algebra
- Truth Tables
- Binary numbers
- Memory
- Flip-Flops

Section 8: Digital Electronics 2


- Clocks and Counters
- Shift Registers
- Decoders
- Multiplexers & Demultiplexers
- Sampling
- **MT4**

Section 8 Schedule


Session 8a	04/02	Clocks and Counters	“Hookey”: “Counter” pages Alex Pounds: Part 27
Session 8b	04/09	Shift Registers	“Hookey”: “Register” pages
Session 8c	04/14	Decoders	“Hookey”: Decoders and Demultiplexers
Session 8d	04/16	Multiplexers and Demultiplexers	“Hookey”: Multiplexers, Decoders and Demultiplexers
Session 8e	04/21	Sampling (A/D & D/A)	Notes
Session 8f (Quiz 8 due 04/27)	04/23	Review for Quiz 7	
Session 8g	04/28	Quiz Results	
Session 8h (Lab - 05/03, Sat.)	04/30	MT4 Q&A	
MT4 (Sat, Cheshire)	05/10		
MT4 Results	05/12		

Decoder Review

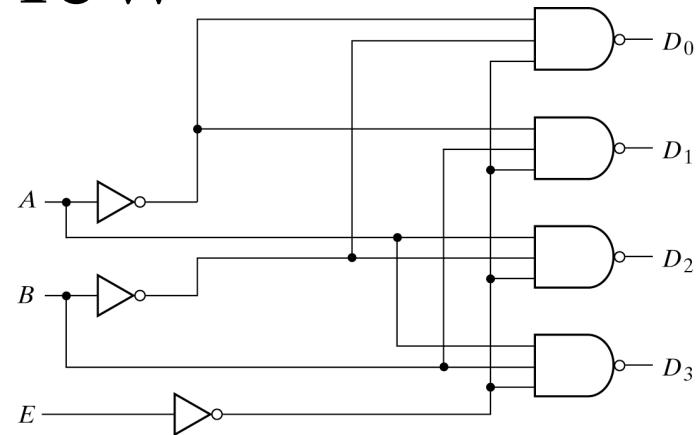- A small number of input bits; treated as a binary number
- A larger set of output bits (up to 2^n)
- The output bit values are “decoded” from the combination of the input bits
- Examples:
 - 1 of N decoding
 - Line Decoder
 - Address Decoder
 - Seven segment display decoder
 - BCD to Decimal line decoder




BIN/7SEG	
x3 (MSB)	a
x2	b
x1	c
x0	d
8	e
4	f
2	g
1	g

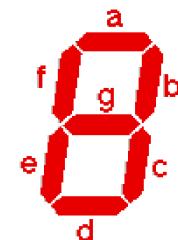

Multiplexers and Demultiplexers

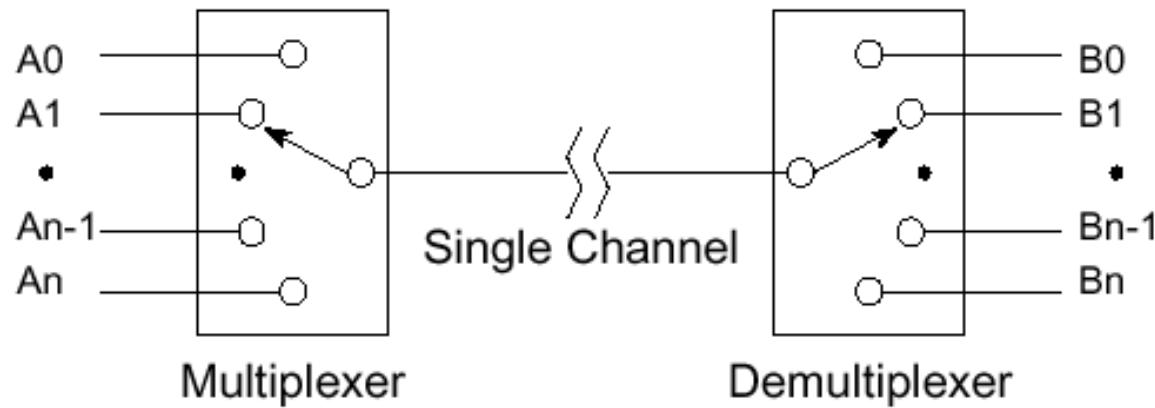
4.4 Multiplexer

- Multilexer - A ***data selector*** that selects one of many inputs to appear on a single output line
- Demultiplexer - A ***data distributor*** that takes a single input line and routes it to one of several output lines




A 4 to 1 Multiplexer

Multiplexer - 4-to-1

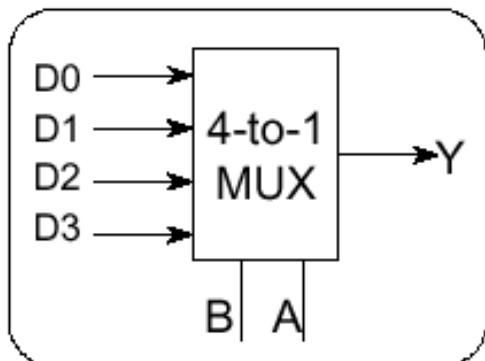

B	A	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3
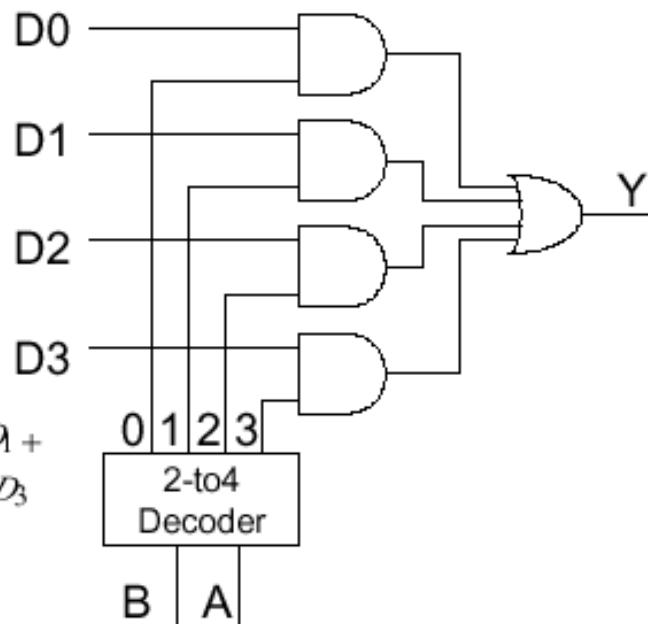
$$Y = \sum_{i=0}^3 m_i D_i$$
$$Y = (BA)D_0 + (\bar{B}\bar{A})D_1 + (\bar{B}A)D_2 + (B\bar{A})D_3$$




National Central University

www.ee.ncu.edu.tw/~ccsu


Introduction to Digital Systems

Chapter 4 P.26

2-to-1 Line Multiplexer

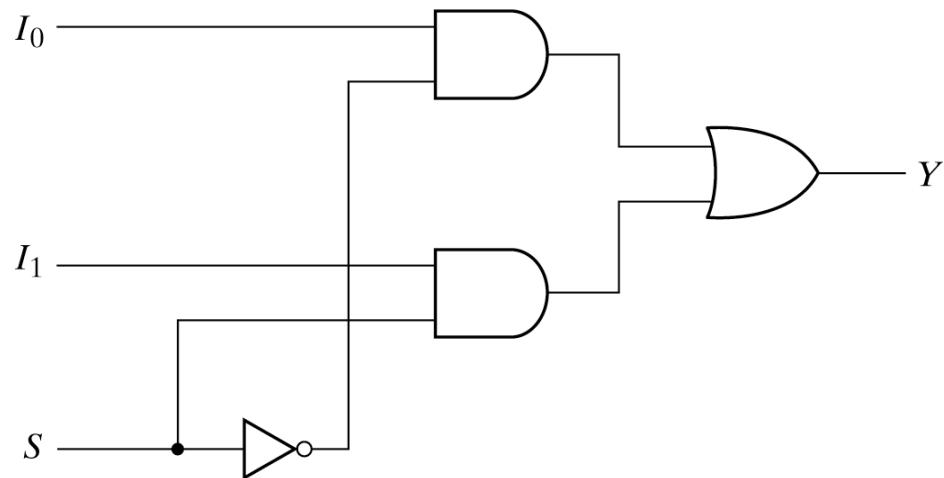


(a) Logic diagram

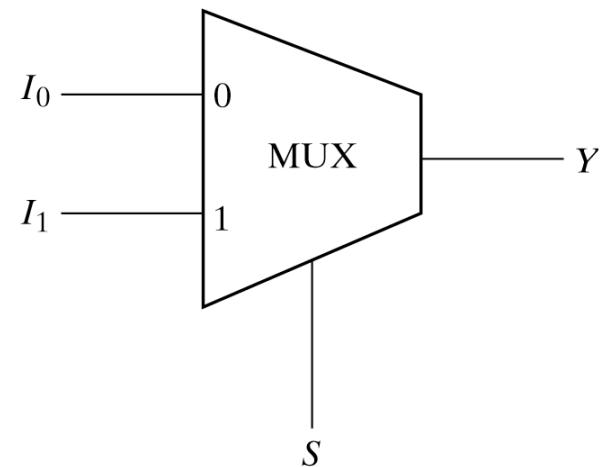

(b) Block diagram


Fig. 4-24 2-to-1-Line Multiplexer

2-to-1 Line Multiplexer * 4 Bits

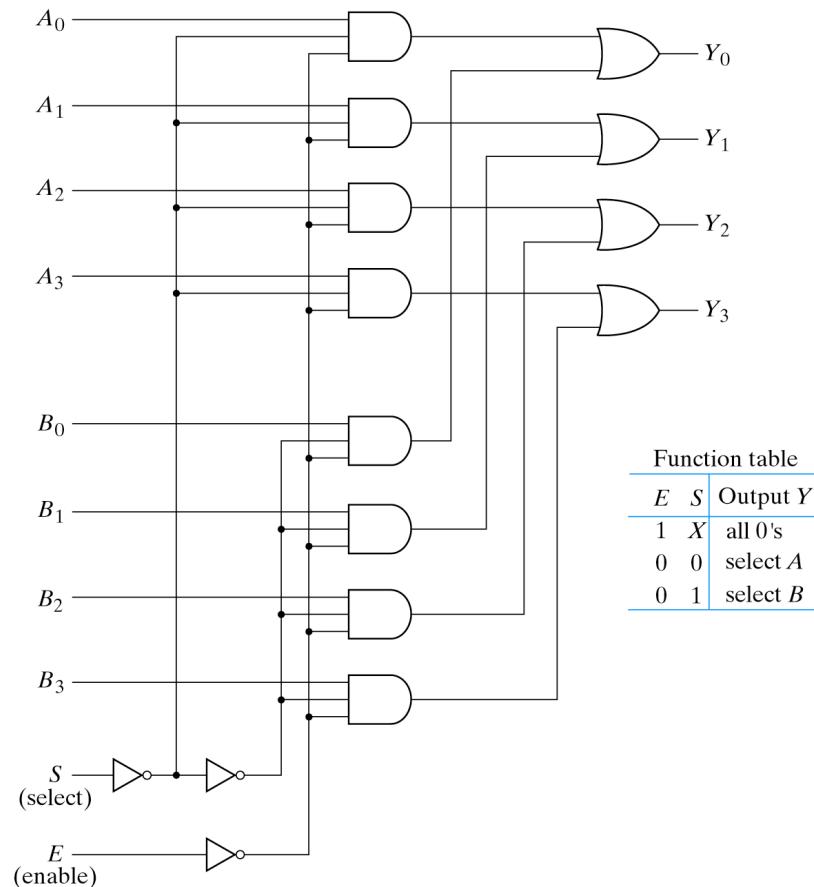


Demultiplexer

Demultiplexer

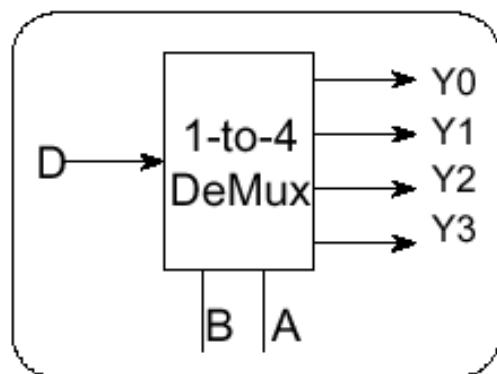

B	A	Y0	Y1	Y1	Y1
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

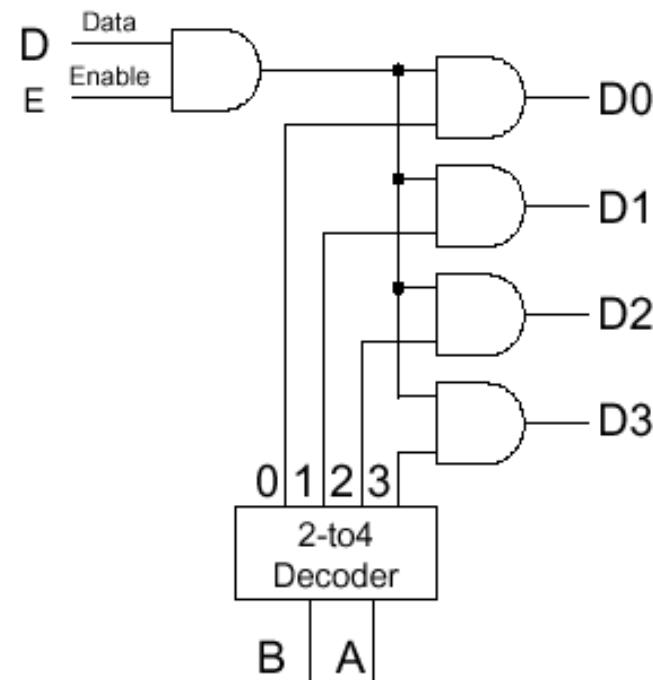


National Central University

www.ee.ncu.edu.tw/~ccsu

Introduction to Digital Systems

Chapter 4 P.34

74151 Multiplexer IC

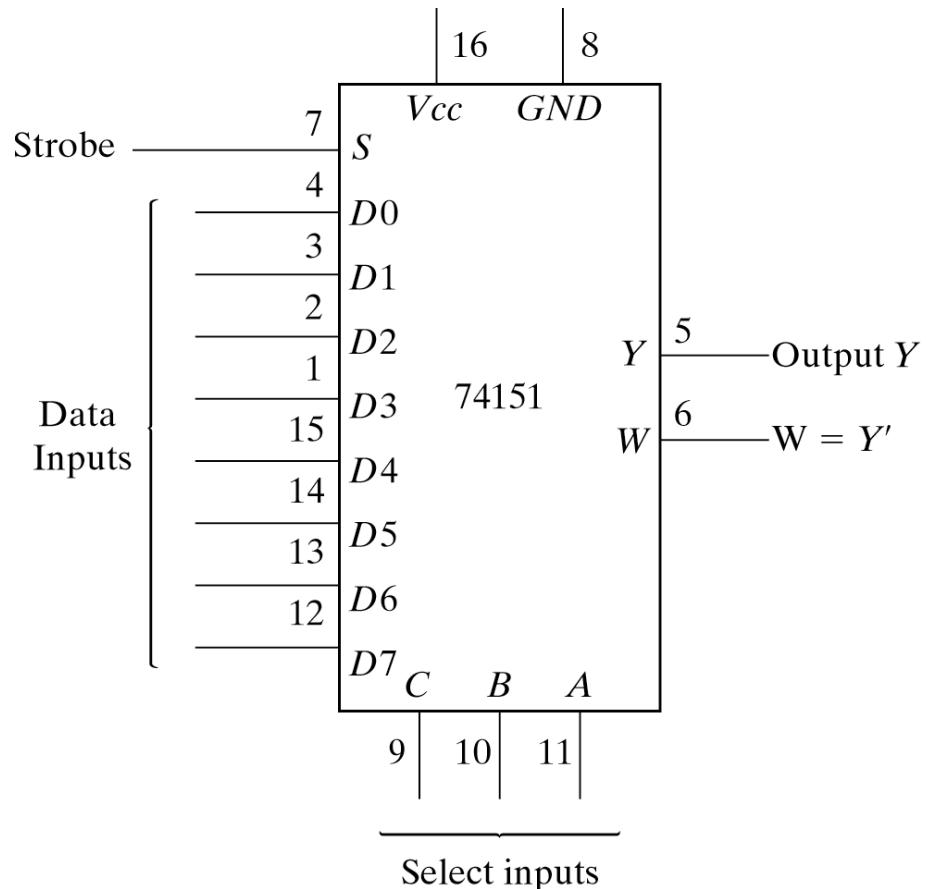

Strobe <i>S</i>	Select			Output <i>Y</i>
	<i>C</i>	<i>B</i>	<i>A</i>	
1	<i>X</i>	<i>X</i>	<i>X</i>	0
0	0	0	0	D_0
0	0	0	1	D_1
0	0	1	0	D_2
0	0	1	1	D_3
0	1	0	0	D_4
0	1	0	1	D_5
0	1	1	0	D_6
0	1	1	1	D_7

Fig. 11-9 IC Type 74151 8×1 Multiplexer

Simulation

- We'll again go to www.play-hookey.com/digital to see Multiplexers and Demultiplexers in action

Section 8 Schedule

Session 8a	04/02	Clocks and Counters	“Hookey”: “Counter” pages Alex Pounds: Part 27
Session 8b	04/09	Shift Registers	“Hookey”: “Register” pages
Session 8c	04/14	Decoders	“Hookey”: Decoders and Demultiplexers
Session 8d	04/16	Multiplexers and Demultiplexers	“Hookey”: Multiplexers, Decoders and Demultiplexers
Session 8e	04/21	Sampling (A/D & D/A)	Notes
Session 8f (Quiz 8 due 04/27)	04/23	Review for Quiz 7	
Session 8g	04/28	Quiz Results	
Session 8h (Lab - 05/03, Sat.)	04/30	MT4 Q&A	
MT4 (Sat, Cheshire)	05/10		
MT4 Results	05/12		